

# Take this GIANT CIRCUIT LIBRARY FOR ONLY \$14<sup>95</sup>

when you join the  
*Electronics Engineers' Book Club*®

Hundreds of circuit ideas  
alphabetically arranged—from  
Alarm circuits to Zero  
crossing detector circuits!


*"...includes schematics for the latest electronics circuits  
from industry leaders..."* —Popular Electronics

Turn to this comprehensive circuit library for  
hundreds of project ideas...and concise pinout  
diagrams and schematics. In each volume you'll  
find more than 700 electronic and integrated  
circuits and 100+ circuit categories right at your  
fingertips to give you ideas you can use on the job  
or at your workbench.

## THE ENCYCLOPEDIA OF ELECTRONIC CIRCUITS

Volumes 1-4

by Rudolf F. Graf

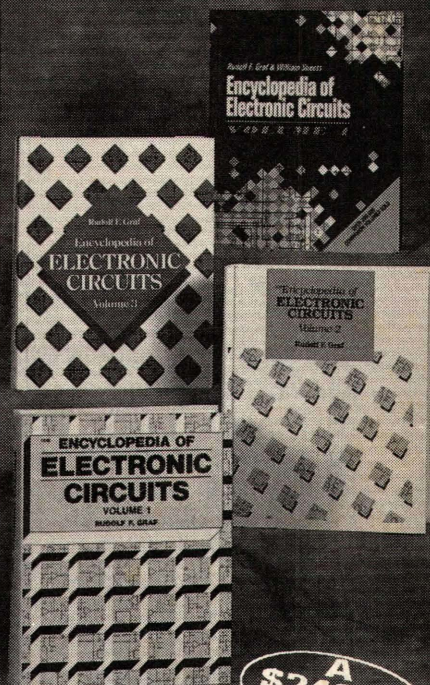

A  
\$240.00  
Value

3,088 total pages  
4,490 total illustrations

If coupon is missing, write to: **Electronics Engineers' Book Club,**  
A Division of The McGraw-Hill Companies, P.O. Box 549, Blacklick, OH 43004-9918

### As a member of the Electronics Engineers' Book Club...you'll enjoy re-

ceiving Club bulletins every 3-4 weeks  
containing exciting offers on the latest  
books in the field at savings of up to  
50% off the regular publishers' prices.  
If you want the Main selection, do  
nothing and it will be shipped auto-  
matically. If you want another book, or  
book at all, simply return the reply  
to us by the date specified. You'll  
have at least 10 days to decide. If you  
give a book you don't want due  
to every of the bulletin, you can  
return it at our expense. And you'll be  
able to order 5 BOOKS through the  
club. Your only obligation  
is to order books during the  
period in which you may  
cancel at any time.  
©1996 EEBC

### **ELECTRONICS ENGINEERS'** BOOK CLUB®

A Division of The McGraw-Hill Companies,  
P.O. Box 549, Blacklick, OH 43004-9918

**YES!** Please send me *The Encyclopedia of Electronic Circuits—Vols. 1-4*  
(5861488), billing me just \$14.95 plus shipping/handling & sales tax. Enroll me as  
a member of the **Electronics Engineers' Book Club** according to the terms  
outlined in this ad. If not satisfied, I may return the books within 10 days for a full  
refund and have my membership cancelled.

Name \_\_\_\_\_

Address/Apt. # \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_ Phone \_\_\_\_\_

Valid for new members only, subject to acceptance by EEBC. Canada must remit in U.S. funds drawn on U.S. banks.  
Applicants outside the U.S. and Canada will receive special ordering instructions. A shipping/handling charge & sales  
tax will be added to all orders.

RPIF1196



# CONTENTS


NOVEMBER 1996

## ON THE COVER

### 33 BUILD THIS AUTOMATIC PARTS TRAY

The trend these days in industry is toward more and more automation. For example, in electronics, robotics is used to pick and place surface-mount components on printed-circuit boards with unerring accuracy. While such a level of automation is beyond the reach of almost any hobbyist, it is possible to bring some of its benefits to nearly any workbench. This month, we present the first part of a system that will, under computer control, greatly simplify the task of assembling PC boards. It is an automatic parts tray that brings to hand the next part to be mounted on the board. Coupled with a computer display that shows the location of that part on the board, project building may never be easier. Best of all, it is inexpensive to build and use.

— James J. Barbarello

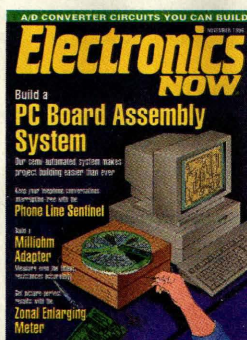


## BUILD THIS

- 40 MILLIOHM ADAPTER**  
Use it to accurately measure even the smallest resistance.  
— Skip Campisi

- 43 ZONAL ENLARGING METER**  
It is easier to use and gives better results than standard darkroom equipment.  
— Michael A. Covington



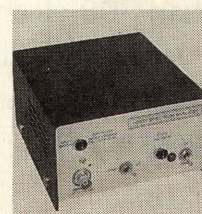- 50 HOBBY SPECTRUM ANALYZER**  
We put the finishing touches on this under-\$100 unit.  
— Bob Kopski



- 53 PHONE LINE SENTINEL**  
Put an end to phone-call interruptions.  
— Mordechai Saad

As a service to readers, ELECTRONICS NOW publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, ELECTRONICS NOW disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry in ELECTRONICS NOW may relate to or be covered by U.S. patents, ELECTRONICS NOW disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

ELECTRONICS NOW, (ISSN 1067-9294) November 1996. Published monthly by Gernsback Publications, Inc., 500 Bi-County Boulevard, Farmingdale, NY 11735. Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Canada Post IPM Agreement No. 334103, authorized at Mississauga, Canada. One-year subscription rate U.S.A. and possessions \$19.97, Canada \$27.79 (includes G.S.T. Canadian Goods and Services Tax, Registration No. R125166280), all other countries \$28.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S. bank. Single copies \$3.50. © 1996 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to ELECTRONICS NOW, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-address envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should the publisher disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.




TECHNOLOGY

55 USING THE 7107

The versatile 7107 A/D converter and display driver is a virtual voltmeter on a chip, but it can be used to do much more than just measure voltage, as you will see in this compendium of circuits that you can build and use.

— Carl J. Bergquist

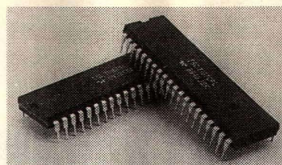

DEPARTMENTS

6 VIDEO NEWS

What's new in this fast-changing industry. — David Lachenbruch

18 EQUIPMENT REPORTS

DynaPulse PC-based blood-pressure monitor.

61 TECH MUSINGS

Understanding digital filters, using your time profitably, and more — Don Lancaster

68 SERVICING

Troubleshooting VCR tape-path alignment. — Robert Epperson

70 LASER EXPERIMENTS



Generating laser-light patterns. — Carl J. Bergquist

74 AUDIO UPDATE

Microphone basics. — Larry Klein

77 COMPUTER CONNECTIONS

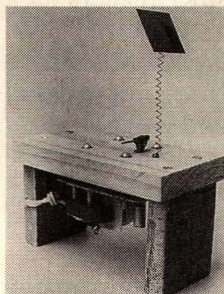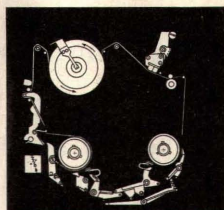IP addressing and HTML coding. — Jeff Holtzman



AND MORE

4 EDITORIAL

8 WHAT'S NEWS

11 LETTERS

14 Q&A

22 NEW PRODUCTS

25 NEW LITERATURE

136 ADVERTISING INDEX

136 ADVERTISING SALES OFFICE

# Electronics NOW®

Hugo Gernsback (1884-1967) founder

LARRY STECKLER, EHF, CET,  
Editor-in-chief and publisher

EDITORIAL DEPARTMENT

CARL LARON, editor  
JOSEPH J. SUDA, associate technical editor  
JULIAN S. MARTIN, associate editor  
TERI SCADUTO, assistant editor  
MICHAEL A. COVINGTON, N4TMI contributing editor  
JEFFREY K. HOLTZMAN, computer editor  
LARRY KLEIN, audio editor  
DAVID LACHENBRUCH, contributing editor  
DON LANCASTER, contributing editor  
EVELYN ROSE, editorial assistant

ART DEPARTMENT

ANDRE DUZANT, art director  
RUSSELL C. TRUELSON, illustrator

PRODUCTION DEPARTMENT

RUBY M. YEE, production director  
KATHRYN R. CAMPBELL, production assistant  
KEN COREN, desktop production director  
LISA BAYNON, desktop production

CIRCULATION DEPARTMENT

JACQUELINE P. CHEESEBORO, circulation director  
THERESA LOMBARDO, circulation assistant

REPRINT DEPARTMENT

MICHELE TORRILLO, reprint bookstore

Typography by Mates Graphics  
Cover design by David Loewy

Electronics Now is indexed in *Applied Science & Technology Index*, and *Readers Guide to Periodical Literature*, *Academic Abstracts*, and *Magazine Article Summaries*.  
Microfilm & Microfiche editions are available. Contact reprint bookstore for details.

Advertising Sales Offices listed on page 136.

Electronics Now Executive and Administrative Offices  
1-516-293-3000.  
Customer Service:  
1-800-999-7139.  
7:00 AM - 6:00 PM M-F MST



Audit Bureau  
of Circulations  
Member



Buy One Get One  
**50%**  
off!



Explore the Caribbean  
on a 6 or 13 day  
sailing adventure.

Call your travel agent or  
**1-800-327-2601**  
<http://www.windjammer.com>



**Windjammer**  
**Barefoot Cruises**

P.O. Box 190120, Dept. 5569  
Miami Beach, FL 33139-0120

June - mid Dec. sailings only. Restrictions apply.

**ATTENTION!**  
**ELECTRONICS**  
**TECHNICIANS**

**EARN YOUR**  
**B.S.E.E.**  
**DEGREE**



**THROUGH HOME STUDY**

Our Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete the program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through our Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the engineering level. Advance rapidly! Many finish in 12 months or less! Students and graduates in all 50 states and throughout the world! Established Over 50 Years! Write or call for free Descriptive Literature. (601) 371-1351

**COOK'S INSTITUTE**  
OF ELECTRONICS ENGINEERING



4251 CYPRESS DRIVE  
JACKSON, MISSISSIPPI 39212

CIRCLE 58 ON FREE INFORMATION CARD

# EDITORIAL

## Introducing [www.gernsback.com](http://www.gernsback.com)

In my first editorial (September 1996), I mentioned that we were making our long awaited move onto the Internet. Well, that move is now largely complete and everyone here is extremely excited about it.

Our Web site, [www.gernsback.com](http://www.gernsback.com), hosts the home pages of both **Electronics Now** and our sister magazine, **Popular Electronics**. But there is also much more. By the time you read this, our FTP site will be up and running. There you will find all of the current and past story-related files for both titles.

Also in the works is a searchable article index. Need to find out if or when we covered a specific topic? Just go to our site and you'll have your answer with just a few keystrokes. The system is undergoing testing now, and we hope to have it operational by early next year.



Also on the way are discussion forums. If you are looking for somewhere to discuss the pros and cons of a particular project, article, or issue, it's the place to go. You'll also be able to interact with other readers on just about any electronics-related topic.

Our Web site is also where you'll find late-breaking updates for our stories and projects. We, of course, publish significant corrections and updates as soon as we become aware of them. However, due to publishing schedules, it can sometimes take months for them to appear in print. Now, that information will be available to you almost as soon as we have it.

There's also information on our two most current issues, subscription information with online ordering, back-issue ordering, links to our editorial and other staff members, links to our advertisers, and much more. Check it out and let us know what you think. You can contact me at [claron@gernsback.com](mailto:claron@gernsback.com).

Carl Laron  
*Editor*



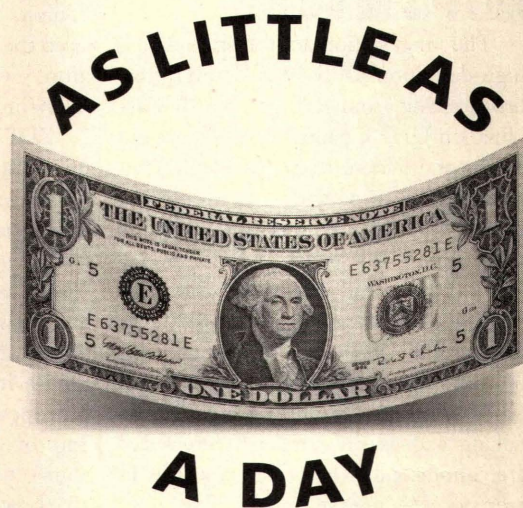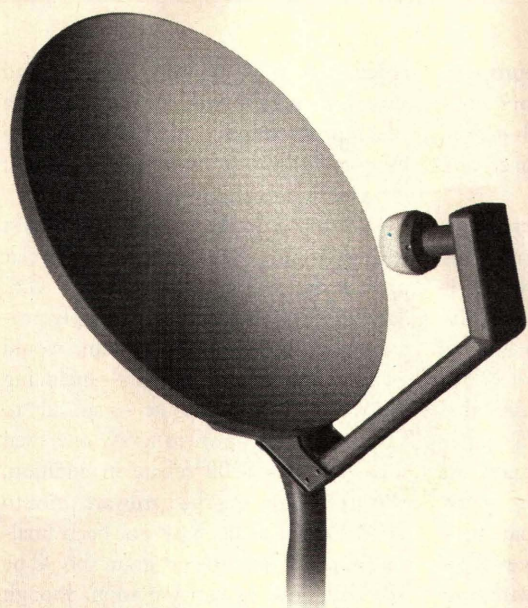

If this satellite deal won't get you off the couch, check your pulse.

**B**een thinking about satellite TV? Come to RadioShack. Now for as little as a dollar a day, you can own an RCA®-brand DSS system with programming. Up to 200 channels on USSB® and DIRECTV®. Or subscribe to PRIMESTAR®, with equipment and programming, also for as little as a buck a day. You can have up to 95 channels with no equipment to buy. If access to tons of movies, pay-per-view, music and sports with digital picture and sound gets your heart racing, come on in. For a store near you, call **1-800-THE SHACK**™.

RCA-brand system and programming sold separately. PRIMESTAR system and programming included in monthly payments. Price and equipment may vary. Installation cost not included. Some restrictions apply. Broadcast networks are only available to customers in those limited areas not served by local affiliates. Blackout and other restrictions may apply.



**RadioShack**™

You've got questions.  
We've got answers.®





# VIDEO NEWS

WHAT'S NEW IN THE FAST-CHANGING VIDEO INDUSTRY

BY DAVID LACHENBRUCH

## HDTV is on the Air

The first station to transmit digital high-definition TV is WRAL-HD, now broadcasting from Raleigh, North Carolina, on UHF Channel 23 under an experimental license from the FCC. That sister station of WRAL-TV mainly has been transmitting numbers for field measurements, but is sending full-bandwidth HDTV at its full authorized power of 100 kHz. The station plans to start transmitting actual video programs in the near future, using tapes provided by PBS and CBS. The station's executives have been talking with receiver manufacturers and are confident that HDTV sets will be in area stores by next spring.

Two more HDTV stations were due shortly at our deadline. The industry's model high-definition station, being financed by the Electronic Industries Association (EIA) and the Maximum Service Television trade association, was scheduled to take to the air soon at NBC's WRC-TV in Washington, D.C. Washington-based WETA, a PBS affiliate, is also building an HDTV counterpart, due on the air this year. The first HDTV receivers are expected to sell for more than \$2000.

## Olympics in HDTV

At one time, the U.S. electronics and broadcasting community had planned to use the 1996 Summer Olympics in Atlanta as a showcase for American technology by broadcasting the games in HDTV. American HDTV slipped a cog as it wasn't quite ready. But the Olympics—390 hours of it—went on the air in HDTV anyway. It just wasn't American HDTV.

The Europeans and the Japanese collaborated to record 24 hours of Olympic competition daily in high definition.

Backed by a grant from the European Union, Germany's ZDF network covered the games in 1250-line high definition, while Japan's NHK used its 1125-line equipment.

ZDF's coverage was converted to 1125 lines and sent, along with NHK's coverage, by satellite to Japan, where it was broadcast using Japan's analog Hi-Vision system from satellite to homes. ZDF's coverage, along with the NHK signal, was also converted to a PALplus signal for transmission to Europe, where it was broadcast to virtually all European countries. PALplus is an improved-definition system that permits specially equipped widescreen TVs to show widescreen pictures with full definition, while other sets display the same widescreen image as a letterbox picture. The additional information required to bring the letterbox picture to 625-line quality is encoded digitally in the black area above and below the widescreen picture.

## DBS Prices Falling

Prices of direct-to-home satellite equipment are falling rapidly, thanks to competition and subsidies by programmers. While the first digital satellite receivers for the DSS system—introduced under the RCA brand, using an 18-inch antenna—sold for \$600 and up, some prices are now as low as \$199. But there's a catch. The programming for these systems is available by subscription only. Obviously, those who install the equipment have to have programs. So the program providers increasingly are helping to subsidize equipment prices.

The first major move in that direction came from EchoStar, which was in a good position to undertake such a project because it sells both the programming and the hardware. It stunned its

competitors by offering a receiver and antenna for \$199 with the purchase of a year's programming at \$300. The promotion was so effective in test areas that it was offered nationwide last summer.

Not to be outdone, DSS, the biggest selling system, was planning a similar promotion. In it, DirecTV and U.S. Satellite Broadcasting, which supply programming for the DSS system, would give the equipment suppliers—including RCA, Sony, and Panasonic—a subsidy to bring the price down to \$399, and then send buyers a \$200 rebate in addition, effectively reducing the hardware price to \$199. While details have not been finalized at press time, the program should be in effect now, or starting soon, though perhaps in a somewhat different form.

The situation is reminiscent of what happened in the cellular-phone industry, where service providers are subsidizing phone instrument prices. The DBS competition hasn't yet gotten to the point where the receiver is free—but stay tuned.

## WebTV Becomes Contagious

There is absolutely no evidence that combining the 1990's fad of Web browsing with the television fad begun in the 1950's is a workable idea, but profit-starved TV manufacturers and Silicon Valley entrepreneurs are joining forces to test the idea in a large-scale way.

Probably the most persuasive force in that direction is WebTV Network, which has signed Sony and Philips (Magnavox) to supply set-top boxes to let consumers surf the Internet on their large-screen TVs from their easy chairs. The box provides on-line access and e-mail service to TV users, and has a slot for smart-card financial transactions.



The box will cost somewhere between \$200 and \$400.

The box is connected to a phone jack and the TV's audio and video terminals. It contains a 33.6-kilobyte-per-second modem and a 64-bit Orion MIPS RISC microprocessor. WebTV features its own Internet guide and simple menus for navigation, along with parental-control software. Wireless and wired keyboards will be available as e-mail accessories, although mail can be authored using an on-screen depiction of a keyboard as well. Sony and Magnavox are expected to have the boxes in stores before year-end.

Other TV manufacturers are using different approaches. As reported here, Zenith is fielding a Net-browsing TV, but prefers the built-in approach to the separate set-top box. RCA's parent, Thomson Consumer Electronics, has been demonstrating prototypes of its "Genius Home Theater," which combines Internet access, e-mail, CD-ROM changer, and other computer features with a high-end 35-inch TV set. Thomson says that it might offer a simplified Web-browsing TV or attachment as well.



RCA'S "GENIUS THEATER" PROTOTYPE is one of a host of new PC/TVs.

Another TV manufacturer, Curtis Mathes, plans to introduce a combination computer and TV set. Computer manufacturer Gateway 2000 is already selling such a combination. Dubbed Destination, it includes a 31-inch TV set and an electronic program guide.

Actually, Toshiba probably foreshadowed the so-called "marriage" of PC and TV in 1994 with its "TIMM" (for Toshiba Integrated Multimedia Monitor), a 20-inch monitor and TV set designed for use both as a TV and a high-quality audio and video monitor for PCs. Unfortunately, it didn't sell particularly well.

EN

# Wavetek. The Way Value Is Measured.

For the best values in digital multimeters everyone is turning to the Wavetek XT Series. Each of these full-function DMMs measures voltage, current, resistance, and also a set of additional electrical or electronic properties you work with every day. Inductance. Capacitance. Frequency.

Temperature. There is an XT Series DMM right for you.

With oversized character displays, these DMMs are as easy to read as they are to use. All have fully-fused current inputs and input warning beepers to protect you and the meter. Each comes with safety test

leads and are approved to IEC1010-1 safety standards.

Our commitment to reliability and high-quality is backed by the industry's only "No Hassle" warranty program. If your XT Series meter requires warranty service, your local dealer replaces it immediately. Call today for full details and the names of your local Wavetek distributors. You'll find that when it comes to Wavetek performance and price, nothing else measures up.

Wavetek Corporation  
9145 Balboa Avenue, San Diego, CA 92123  
(800) 854 2708

**WAVETEK**



## 27XT

A unique combination of DMM and component checking in a single meter:

- Inductance
- Capacitance
- Logic
- Frequency

Accessories include current clamps, RF & HV probes, temperature converters, holders, boots and carrying cases.

## 23XT

Electronic and electrical test functions for general duty and HVACIR.

- VAC Safety Tester™
- Temperature
- Capacitance
- Logic

## 25XT

A full C-meter in a DMM, and more! Ideal for AN, cell-phone & antenna matching, component inspection.

- Full Capacitance 0.1pF to 20mF
- Capacitance
- Zeroing & Test Slots

## 28XT

A thermometer + DMM for HVACIR, building or plant maintenance.

- Temperature
- Capacitance
- Frequency
- Max-Hold

## 85XT

A precision True RMS reading DMM, ideal for equipment like copiers.

- 4 1/2 digit
- 0.05% Accuracy
- True-RMS
- Frequency
- Duty Cycle

## LCR55

Full-function LCR, extra test features for "best-buy" in a component checker.

- Inductance
- Capacitance
- Resistance
- Transistor
- Dual Diode



CIRCLE 98 ON FREE INFORMATION CARD





# WHAT'S NEWS

A REVIEW OF THE LATEST HAPPENINGS IN ELECTRONICS


## Measuring Individual Carbon Nanotubes

Researchers at NEC Corporation (Japan) and NEC Research Institute (Princeton, NJ) have succeeded in measuring electrical conductivity in individual carbon nanotubes. Using an evaluation method developed by scientists at NEC and Micrion Europe, they discovered that each nanotube has unique electronic properties, including both metallic and non-metallic behavior, and that the differences between nanotubes are far greater than expected. The results confirm that, at this scale, geometry and electronic properties are closely linked.

By attaching four 80-nanometer tungsten leads directly to individual nanotubes, and using a focused ion beam (FIB) system, the NEC scientists were able to achieve a more accurate and informative evaluation of the nanotubes' properties. It was learned that the current carrying capacity of nanotubes is extremely high, the temperature dependence of the conductivity greatly differs between nanotubes, different segments of a single nanotube do not always have the same temperature profile, and nanotubes have significant variation in resistivities.

The interest in carbon nanotubes has been stimulated by theoretical predictions that their electronic properties would be strongly modulated by small structural variations. In particular, the diameter and helicity of carbon atoms in the nanotube shell are believed to determine whether the nanotube is metallic or a semiconductor. Prior to the NEC method of measuring individual nanotubes, however, experimental evidence had been mainly linked to bulk measurements.

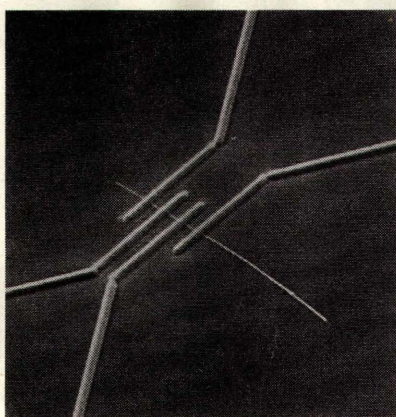"This work opens up for the first time full electrical measurements on carbon nanotubes," said Dr. William Gear, president of NEC Research Institute. "These tubes may be able to function as



NEC RESEARCHERS MEASURE the electrical conductivity of individual carbon nanotubes by attaching four 80-nanometer-wide tungsten leads to each nanotube.

wires with a diameter about one hundredth the line-width used in current 16-megabit memory chips. Early results suggest that nanotubes can be fabricated with a very wide range of electrical properties.

## Solar Success Story

Engineers from Sandia National Laboratories (Albuquerque, NM) played a key role in the development of Solar Two, a large pilot solar power plant that is capable of producing 10 megawatts of electricity—enough to supply power to 10,000 homes. The project was sponsored by the Solar Two Consortium, a group of ten organizations led by Southern California Edison Company, and the Department of Energy (DOE). At a June 5 dedication ceremony, presided over by DOE Secretary Hazel O'Leary, Solar Two was officially connected to the utility grid in Southern California.

Solar Two is unique in its use of molten salt to capture and store the sun's heat. The solar plant uses large, sun-tracking mirrors to concentrate sunlight on a receiver that sits atop a tower. The concentrated sunlight heats the molten

salt as it flows through the receiver. The hot liquefied salt is then piped away, stored, and used when needed to produce steam to drive a turbine/generator that produces electricity.

Solar Two's predecessor, Solar One, was a direct-steam solar generator that operated from 1982 to 1986. Solar One generated steam directly from water in its receiver, and was plagued by low energy-storage efficiency and interrupted operation from passing clouds. Solar Two, in contrast, can operate smoothly through intermittent clouds and continue generating electricity long into the night.

Sandia conducted large-scale experiments on the components needed in a molten-salt system at its Central Receiver Test Facility in Albuquerque. "Sandia played a key role in providing assistance by transferring molten-salt technology to the project, by leading the Technical Advisory Committee which oversaw all technical aspects of the project, and by supporting the design, construction, and startup of the plant through the outstanding efforts of its staff," said Gary Burch, director of the DOE's Thermal and Biomass Power Division.

## IC Expo/96

Co-sponsored by Wescon, EE Times, Electronic Buyer's News, and OEM Magazine, IC Expo/96 is scheduled to take place as part of Wescon/96 on October 22–26, 1996, at the Anaheim Convention Center in Anaheim, California. The Wescon International Electronics Conference and Exhibition is a major OEM event for electronics, computer, and communications professionals.

The IC Expo/96 show-within-a-show, an extensive semiconductor trade exhibition, will celebrate the 25th anniversary of the microprocessor—and the 45th anniversary of Wescon—with a series of

*continued on page 12*





# LETTERS

SEND YOUR COMMENTS TO THE EDITORS OF ELECTRONICS NOW MAGAZINE

## L/C Meter Correction

In my article, "Build This Self-Calibrating L/C Meter" (*Electronics Now*, June 1996), I inadvertently submitted the incorrect schematic diagram. The schematic published was for an experimental unit that used a different display module and thus had different pinouts on the CPU-to-display interface. The PCB layout is correct, so any units built using a printed circuit board should be okay. This proves the saying, "To err is human, to really foul things up use a computer."

A copy of the correct schematic can be obtained by requesting it and sending a self-addressed, stamped envelope to the address below. The correct schematic is also available as *lcmsch.gif* on the Electronics Now BBS (516-293-2283).

NEIL HECKT

*Almost All Digital Electronics*  
1412 Elm Street SE  
Auburn, WA 98092

## New Product Correction

Thank you for mentioning HC Protek's D-980 digital Multimeter in the July "New Products" column. Unfortunately, two errors appeared. First, the DC accuracy specification was cited as 5%. The actual specification is 0.5%.

Our Web site URL was also incorrect. The correct URL is <http://www.techexpo.com/WWW/hcprotek>.

ROY TAFFARO

*HC Protek Applications Engineer*  
Northvale, NJ

## Non-Stereo Compressor

I would like to share my thoughts about the article, "Build a Stereo Compressor" (*Electronics Now*, August 1996). Although the two-channel compressor project will prove to be a fine addition to someone's audio-processing needs (Analog Devices makes great, innovative ICs), it is not a stereo compressor.

For the unit to operate in the stereo mode, both rectifier log converters from channels one and two would need to be summed into a single control voltage that would then feed directly to the VCAs of both channels in a strapped configuration, thereby preserving correct stereo imaging. By that I mean that any high-level peak appearing in only one channel will cause an equal amount of gain reduction in both channels, keeping the left/right balance correct.

Any two-channel processor, when connected to a stereo signal (*i.e.*, complete mix), would process the left and right channels independently. If a sudden loud signal appeared in only one channel, such as a lead instrument that was panned hard left or right within a total stereo mix, only that channel's VCA would respond, causing the overall level in that channel to decrease. That decrease in level to only one channel will cause image shifting. All mono information (bass drum, bass guitar, etc.) would sound off-center from the original mix.

As a two-channel compressor, I'm sure the unit will be a wonderful addition to an effects rack. As for stereo compressing a final mix, say from CD or DAT to a cassette format—no way!

RON TOZIER

*Newton, KS*

## Laser Article Brought Into Focus

In reading the August installment of "Laser Experiments," I found what I

Write To:

Letters,  
Electronics Now Magazine,  
500 Bi-County Blvd.,  
Farmingdale, NY 11735

Due to the volume of mail we receive, not all letters can be answered personally. All letters are subject to editing for clarity and length.

believe to be several serious errors. First of all, a diffraction grating does not consist of thousands of very small parallel prisms per millimeter, as suggested. In actuality, a diffraction grating consists of many closely spaced parallel lines scored onto an aluminized plastic or polished glass surface. Those lines break up light into its component frequencies by the physical process of diffraction (the interference produced when light encounters an obstacle), as their name implies. Each scratch serves as a source of scattered light. Prisms operate through the entirely different process of refraction—the selective bending of different light wavelengths as they pass from one media (such as air) to another (such as glass). If gratings really operated as microscopic prisms as suggested, then they would have to be called refraction gratings!

Another type of grating consists of many parallel apertures or obstacles that ideally present a pass-block squarewave type pattern to the incident wave front. Yet another type (there are many), called a "blazed" grating, consists of grooves cut onto a glass surface whose serrated edges do resemble an array of prisms but which still operates by diffraction. Consult any standard physics or optics text for more details.

Another statement in the article suggested that the focusing of "light" is somehow more crisp and pronounced than that obtainable by other forms of electromagnetic energy such as "radio or sound." The big error here is that sound is *not* a form of electromagnetic energy. In addition, there is no fundamental difference between radio waves and visible light. They are both EM waves that differ only in their frequency. Radio waves are routinely focused by parabolic antennas and the like.

A further misconception was that placing black tapes around a bent glass rod would act as a shield to keep light from escaping out the sides. In reality,



the process called "Total Internal Reflection" is what keeps light trapped within the rod or optical fiber. To operate, the incident light rays must enter the rod at an angle less than some critical angle determined by the material of the rod or fiber and the surrounding medium. If the incident angle exceeds that value, or if the rod/fiber is bent too sharply, then light can indeed leave through the sides. However, black tape will not redirect the light back into the pipe or cause Total Internal Reflection to occur, as implied.

Several times in the article, the author mentioned that lasers are coherent and monochromatic, but still contain all the other colors in the visible spectrum (albeit in small quantities). Thus, the article continued, colored light can be produced by passing laser light through a prism or a frosted plastic sheet. While it is true that no laser is perfectly monochromatic (the frequency spectrum is predominantly distributed over a band known as the line width), its bandwidth is extraordinarily narrow. For a common He-Ne laser, the line width is roughly 1500 MHz, which might seem large compared to radio frequencies but is less than 1/1000 of

one percent of the visible light spectrum. Technically, all frequencies in that narrow band are of different "colors." But to suggest that a full-color spectrum can be obtained through refraction of laser light is nonsense. Lasers are called monochromatic or quasi-monochromatic for good reason. Any colors thus perceived are due to interactions with ambient sunlight or non-monochromatic room illumination.

The use of the word "sub-reflection" to describe the speckling effect produced by shining laser light off a diffuse surface is non-informative. The speckles are caused by a stationary interference pattern set up in the space in front of the surface. Due to the long coherence length of the laser light, individual reflections from the rough surface combine together coherently at each point in space with a random but stationary (non-changing) phase to create the speckles. When viewed in sunlight, the speckles might take on various colors.

While lenses are extremely important in optical science, the rules that govern the focusing of laser light (Gaussian beams) are not quite the same as those for non-coherent light. This

difference had disastrous consequences for some early designers of optical systems using lasers, who used the standard rules of geometrical optics and couldn't figure out why their systems failed to work! The interested reader can find a wealth of information on these topics in the many available books on lasers, optics, laser electronics, holography, and other related fields.

JAY RABKIN

Pasadena, CA

## Audio System Integration Update

In "Audio Update" (*Electronics Now*, August 1996), Franklin Miller stated that it is optimum to match microphone impedance to the input impedance of the mixer. That is wrong. If the impedances are matched, the level will drop 6 dB and the signal-to-noise ratio will drop 3 dB. For condenser microphones with a built-in amplifier, there will be a bass roll-off and added distortion.

Instead, the input impedance should be at least ten times the source impedance. That mismatch is called a "bridging load."

DAVID HADAWAY

Rindge, NH

EN

## WHAT'S NEWS

*continued from page 8*

industry events. Hundreds of exhibits will display many of today's most advanced microelectronics products and technologies by leading semiconductor manufacturers. Industry and editorial advisers have structured the event to meet the needs of technology professionals from the communications, computer, and high-end VLSI components industries, who need to know the latest in microprocessors, microcontrollers, memories, ASICs, and communications ICs.

The Applications Conference on Communications and Computer Technologies will provide extensive solutions-oriented presentations in a series of several one- and two-hour sessions. New and emerging technologies will be featured in multiple sessions throughout the conference.

Information about Wescon/96 and IC Expo/96 is available by phone (800-877-2668), fax (310-641-5117), e-mail (m.pothoff@ieee.org), and Web site (<http://www.wescon.com>).

## Scholarship Donation

The Consumer Electronics Manufacturers Association (CEMA) announced that DeVry Institute has contributed \$60,000 in scholarships to the winners of the Electronics Products Servicing Competition, held June 27 at the 1996 Skills Championships in Kansas City, Missouri.

Throughout the year, students compete in local, regional, and state competitions sponsored by the Vocational Industrial Clubs of America (VICA). The competitions culminate in VICA's annual Skills USA Championships, which pit state title winners against each other. CEMA sponsors the electronic skills portion of the championships.

DeVry awarded scholarships to both the secondary and post-secondary winners of the electronics competition. Both scholarships, valued up to \$30,000, will cover full tuition to any of the DeVry Institutes in the United States. As a private, degree-granting higher-education system, DeVry, with 13 campuses throughout the United States and Canada, offers

bachelor's degree programs in electronics-engineering technology, computer-information systems, business operations, accounting, and telecommunications management, as well as an associate's degree program for electronics technicians.

"Consumer electronics manufacturers rely heavily on qualified technologists and technicians for the installation, servicing, and maintenance of their products," said Don Hatten, vice president, CEMA Product Services. "The generous DeVry scholarships will provide our two winners with a valuable education and an opportunity for promising careers once they graduate."

CEMA, through its Product Services Department, supports vocational education programs that offer training for those entering the servicing profession. CEMA also provides in-depth preparatory training for students seeking engineering degrees.

Information on CEMA is available via EIA/CEMA's World Wide Web Site at <http://www.eia.org/cema>. Information on DeVry programs can be accessed at <http://www.devry.com>.

EN



# SEC Sun Equipment Corporation

3121-A Glen Royal Rd., Raleigh, NC 27612

## Test Equipment for Cost-Minded People

**LODESTAR** Lodestar Electronics Corp. Since 1979  
 One Year Warranty. 15 Day Money Back Guarantee. OEM welcome.  
 School purchase order accepted. Bids accepted. VISA, DISCOVER  
 SALES REP./DISTRIBUTORS/OEM WANTED. MASTER, & AMER.  
 1-800-870-1955/(919)870-1955 24-hr Fax:(919)870-5720

### DC POWER SUPPLY

**PS-303 \$159.00**  
 0-30VDC, 0-3A; 0.02%+2mV line regulation; 0.02%+3mV load regulation; 1mVrms noise & ripple; Short circuit/overload protection; constant current/voltage(CC/CV).  
**PS-303D \$314.95** dual output, tracking  
**PS-305 \$219.95**, 0-30VDC, 0-5A.  
**PS-305D \$399.95**, dual, tracking.  
**8110 \$289.95** 0-60VDC, 0-3A.  
**8112 \$399.95** 0-60VDC, 0-5A.  
**8108(8109) \$549.95(\$699.95)** 0-60VDC, 0-3A(5A), dual, independent tracking. Low ripple.  
**8102(8103) \$399.95(\$489.95)** dual 0-30VDC/0-3A(5A), fixed 5VDC/3A, independent tracking operation, constant voltage and current. Slave/Master, Serial/Parallel connection.  
**PS-1610S(8107) \$289.00(\$399.95)** 0-16VDC(0-30VDC), 0-10A.  
**PS-2243(2245) \$139.00(\$159.00)** 0-12/0-24VDC, 3A(5A).  
**8200(8201) \$179.95(\$239.95)** 0-30VDC(digital meter), 0-3A(5A).  
**8210(8211) \$199.95(\$259.95)** two digital meters.  
**8202(8203) \$499.95(\$549.95)** 3 outputs, digital display, dual 0-30VDC/0-3A(5A), a fixed 5VDC/3A, independent tracking operation, constant voltage and current.

### AM/FM SWEEMAR SCOPE

**SM-6225B/C \$199.95**  
 Freq Range: (AM)490KHz, (FM) 10-11.4MHz. Accuracy:  $\pm 0.1\%$   
 Marker: (AM)455KHz,  $\pm 5$ KHz,  $\pm 10$ KHz, (FM)10.7MHz,  $\pm 7.5$ KHz,  $\pm 150$ KHz.

**STEREO SCOPE OS-7505B \$369.00** trigger, 0-10MHz.

**ALIGNMENT SCOPE OS-7001A \$369.00** 0-200KHz.

### AM/FM STD SIGNAL GEN.

**SG-4110A \$179.00**  
 Freq: 100KHz-110MHz  
 Display: 6-digit LED  
 Accuracy:  $\pm (5 \times 10^{-5} \pm 1 \text{ count})$   
 Resolution: 100Hz (100-34.99MHz); 1KHz (35MHz-110MHz).  
 Output: -19dBu, -99dBu, 1dB steps. Impedance: 50  $\Omega$  VSWR 1.2.

### NTSC TV COLOR BAR PAT. GEN.

**CPG-1366A \$159.95**  
 VHF NTSC;  
 Freq: 45.75, 175.25, 187.25 MHz.  
 RF Output: 10mV.  
 Impedance: 75  $\Omega$ ;  
 Video Output: BNC, 1Vp-p

### SWR/RF POWER METER

**310 \$89.95**  
 Freq Range: 1.8-150MHz.  
 RF Power: 0-4W/20W/200W  
 SWR Measure: 1.0 -  $\infty$ , 4W min.  
 Accuracy: 5%-10%; SO-239 plugs.  
 Insertion Loss: 0.3dB.  
 Input/Output Imp: 50  $\Omega$ .  
**320 \$89.95**, 130-520MHz.  
**330 \$119.95**, 1.8-520MHz.  
**SWR-3P \$26.95** 1.7-150MHz.  
 RF Power: 0.5-10W, 0.5W-100W.  
**SWR-2P \$22.95**, 1.7-30MHz, RF Power: 0.5-10W.  
**mW RF Power Meter 340 \$219.00**, 1.8-500MHz, 20mW ~ 2W.

### MICROPROCESSOR/CONTROLLER TRAINER

Now, you can learn and apply Computer control on your PC with our low-cost trainers and lead yourself to the advanced 80386, 80486, etc. Learn ASSEMBLY, C, and BASIC languages programming and debugging, and Microprocessor based system hardware design and troubleshooting. Experiment guide and example programs are included in each trainer. These trainers are widely adopted by technical colleges.  
**8088 Trainer \$699.00** BGC-8088, teach yourself 8088 assembly language programming.  
**Features:** Assembly language coding, assembler, disassembler, single step and multi-breakpoint program debugger, display and rewrite registers, download/upload programs from/to external systems, I/O drivers, 56-key large size keyboard, LCD display, RS-232, UART, printer interface, two expansion slots,  $\pm 5$ V,  $\pm 12$ V switching power supply, 20 I/O applications available, e.g. servo & stepping motors, dot matrix display, D/A, A/D, sensors, ...  
**8051/8052 Embedded Microcontroller \$979.00** BGC-8052, teach yourself Intel 8051/8052 Microcontroller controls. 8051/8052 is one of the most popular Microcontroller used in today's appliance controls and is compatible with the new powerful MCS 251.  
**8051/52 In-Circuit Emulator, APEX-IE** assembly language programming and debugging.  
**CIC-100 \$549.00** I/O control applications, learn Assembly, C, and BASIC programming languages, 800-pin solderless breadboard for circuit design and test, I/O drivers for controlling relay, step motor, LED, speaker, sensor, etc.. Application control modules available.

### RF SIGNAL GENERATOR

**SG-4160B \$124.95**  
 100KHz-150MHz up to 450MHz on 3rd harmonics, 6 ranges; AM modulation. RF Output: 100mVrms to 3-5MHz. Modulation: Int. 1KHz AM, Ext. 50Hz-20KHz AM.  
 Audio Output: 1KHz, 1Vrms.  
**SG-4162AD \$229.95**, with Freq. Counter 1Hz-150MHz, 6 digits, for internal & external signals. Specification see SG-4160B above.

### AUDIO GENERATOR

**AG-2601A \$124.95**  
 10Hz-1MHz, 5 ranges;  
 Output Level: sine wave 0-8Vrms, square 10Vp-p.  
 Output Impedance: 600  $\Omega$ hm.  
 Distortion:  $< 0.05\%$  500Hz-50KHz,  $< 0.5\%$  50KHz-500KHz.  
**AG-2603AD \$229.95**, with Freq. Counter 1Hz-150MHz, 6 digits, for internal & external signals. Specification see AG-2601A above.

### FUNCTION GENERATOR

**FG-2100A \$169.95**  
 0.2Hz-2MHz in 7 ranges; Sine, Square, Triangle, Pulse & Ramp  
 Output: 5mVp-p-20Vp-p, 1% distortion.  
 VCF: 0-10V control freq. to 1000:1.  
**FG-2102AD \$229.95** generates signals same as FG-2100; 4-digit counter display, TTL & CMOS outputs, 30ppm  $\pm 1$  count accuracy.  
**FG-2020B \$159.00** 0.5Hz-500KHz; Sine, Square, Triangle.  
**(FG)2103 \$329.95**, Digital sweep generator, 0.5Hz-5MHz in 7 ranges. Operating Mode: sweep, AM, gated burst, VCG.  
 Freq. Counter: Int. 0.5Hz-5MHz; Ext. 5Hz-10MHz.

### FM STEREO MODULATOR

**AG-2011A \$549.00**  
 RF SECTION:  
 Carrier: 98MHz  $\pm 2$ MHz;  
 Output: 10mV, 1mV & 0.1mV  
 COMPOSITE SIGNALS:  
 Pilot: 19KHz  $\pm 2$ Hz, 0.8Vrms  
 INT. MODULATION: 400KHz;  
 1KHz  $\pm 1\%$ , 1Vrms, distortion  $< 5\%$  L-R Separation:  $> 50$ dB.  
 EXT. MODULATION: Freq: 50Hz-15KHz  
 L-R Separation:  $> 45$ dB 100Hz-3KHz;  $> 35$ dB 50Hz-15KHz.

### AC MILLIVOLT METER

**MV-3100A \$159.95** wide band  
 5Hz-1MHz; 3 scales, mV, dB & dBm;  
 300  $\mu$ V-100V in 12 ranges, 10  $\mu$ V resolution; -70-40dB in 12 ranges, 0dB=1Vrms, 0dBm=0.775V;  $\pm 3\%$  accuracy; Input impedance 10M $\Omega$ ;  
 Noise  $< 2\%$ . **MV-3201B \$309.95** dual channels, simultaneous measurement.

### OSCILLOSCOPE OS-7305B \$249.00

DC-7MHz.  
 Vertical: 10mV/Div; Horizontal: 250mV/Div; 10Hz-100KHz in 4 ranges; 3" CRT; Internal and External Sync.; Input: 1M $\Omega$ /35pF.  
**OS-7010A \$369.00** DC-10MHz 5" CRT, 10mV/Cm-10V/Cm, 1M $\Omega$ .  
**OS-622B \$344.95** 20MHz/dual trace  
**OS-653 \$699.95** 50MHz, dual, delay sweep, ALT trigger, TV syn.  
**OS-6100B \$1329.95** 100MHz, 4ch, 8 traces, delay sweep, best buy

### GRID DIP METER

**DM-4061 \$89.95** 1.5-250MHz,  
 6 bands, 6 plug-in coils,  
 3rd harmonics, 6 ranges; AM modulation. 2 transistor, and 1 diode.  
 Modulation: = 2KHz Sinewave. Crystal Oscillator: 1-15MHz.  
 Wave absorption meter. Using 9VDC power supply.

### AUTO DISTORTION METER

**DM-3104A \$799.95**  
**MEASUREMENT:**  
 Range: 0.01%-30%,  
 0.1/0.3/1/3/10/30% full scale.  
 Freq.: 400Hz  $\pm 10\%$ ,  
 1000Hz  $\pm 10\%$  (HPF).  
 Input: 3mV-100V,  
 ratio measuring 20dB.  
 Auto. Switching Ranges: Fundamental Freq. = (fo)  $\pm 10\%$ ;  
 Fund. Rejection:  $> 80$ dB at (fo)  $\pm 5\%$ ;  $> 70$ dB at (fo)  $\pm 10\%$ .  
 Harmonic Accuracy:  $\pm 0.5$ dB, 1/8(fo)-20KHz.  
**DM-3204 \$1,599.00** dual channels.

### FREQUENCY COUNTER

**FC-5250C \$119.95**  
 Freq. Range: 10Hz-220MHz  
 (HF) 10Hz-20MHz,  
 (VHF) 10MHz-200MHz  
 Gate Time: 0.1 & 1sec.  
 Max. Input: 10Vp-p.  
 Input Sensitivity: 35mV 10Hz-200MHz. Display: 7-digit LEDs.  
 Input Imped.: (HF) 1M $\Omega$ hm, (VHF) 50 $\Omega$ hm.

**FC-5260A \$146.00**  
 10Hz-600MHz. 7-digit LEDs.

**FC-5270 \$149.95**  
 10Hz-1.2GHz. 8-digit LEDs.

**FC-5600B \$321.00**  
 10Hz-600MHz. 10-digit LEDs.

**(FC)5700 \$329.95** 10Hz ~ 1.3GHz. 10-digit LEDs.

### SIGNAL TRACER/INJECTOR

**SE-6100 \$134.95**  
**TRACER:** Gain Max. 60dB  
 Attenuation: 0/20/40/60dB  
 Input Imped.: 100K $\Omega$ hm  
 Output Imped.: 600 $\Omega$ hm;  
 Speaker: 8  $\Omega$ hm.  
**INJECTOR:** Freq.: 1KHz  
 Squarewave; Output Level: Continuously variable 0 - 4.5Vp-p.

### AUTO. CAPACITANCE METER

**CM3300A \$139.00** 10 ranges, 99.9pF ~ 99.9mF, fully automatic.  
 Resolution: 0.1pF lowest,  
 0.1% full scale.  
 Accuracy:  
 0.5% of full scale  $\pm 1$  digit to 99.9  $\mu$ F,  
 1% of full scale  $\pm 1$  digit to 99.9  $\mu$ F.  
 Display: 3 digit LED.  
 Unit indicator: pF, nF,  $\mu$ F, mF. Overrange indicator.

### WOW-FLUTTER METER

**WF-3103A \$699.95**  
 Freq. Range: 3KHz  $\pm 10\%$   
 JIS/CCIR; 3.15KHz  $\pm 10\%$  DIN.  
 Range: 0.03/1/3/3% full scale.  
 Accuracy:  $\pm 5\%$ .  
**WF-3105A \$799.95**, digital;  
 Function: LIN/WOW/Flutter/WT.D.  
 Freq Cntr: 10Hz-9.99MHz.  
 Indication: CCIR/DIN/JIS.

### NEW PRODUCTS

#### mW RF Power Meter 340 \$219.00

1.8-500MHz, RF power: 20mW/200mW/2W; Imp: 50  $\Omega$ ;  
 Accuracy:  $\pm 10\%$  full scale; N-type connector; SWR  $< 1.15$

#### Digital DC Power Supply 8300 (8301)

\$199.95 (259.95), 0-30V/3A(5A), CC/CV.

#### Electronic UHF Attenuator 085E

(087E) \$399.00, DC-950MHz, Imp: 50(75  $\Omega$ ), 1 dB step.

#### Computer Monitor Tester MT801

\$175.00 Test MDA, CGA, EGA, VGA, SVGA, 8514A monitors; Video Patterns: color bars, cross hatch, dots, color raster and windows; Two video connectors: digital

TTL 9-D & analog 15-HD; Power: 120VAC.

**MT810 \$129**: Hand held model, Power: 9VDC.

**EDS-8804 \$89.00** A/D and D/A converters.

**EDS-8805 \$239.00** Servo and stepper motors.

**EDS-8806 \$159.00** Basic I/O experiments.

**EDS-8807N-16 \$619.00** 16 Dot matrix LEDs.

**EDS-8807N-8 \$419.00** 8 Dot matrix LEDs.

**EDS-8808 \$269.00** Opto-coupler controls.

**EDS-8809-1 \$589.00** stepper motor control,

digital clock, speaker cntrl, dot-

matrix LED, matrix keyboard, sign-

lights, electric piano, stop watch, ...

24 experiments,

example programs included.

**20% Off, DC POWER SUPPLIES**

**DEMO UNITS: 8102** triple outputs, 0-30V/0-

3A, 5V/3A serial/parallel \$399.95 \$319.95.

**PS-303D** dual outputs, \$314.95 \$252.95.



# Q & A

READERS QUESTIONS, EDITORS ANSWERS

## Electronic Dog Whistle

**Q** I would like to build a transmitter that emits a sound that only dogs can hear. It needs to be able to transmit approximately 100 to 150 yards. — J.S., Duluth, GA.

**A** Try the circuit in Fig. 1; it's an audio oscillator that adjusts from about 6 kHz to 25 kHz. The speaker is a piezo-electric tweeter; ordinary speakers aren't very efficient at those frequencies.

To check the oscillator, set R2 to its maximum resistance; you'll hear a loud squeal. Then adjust R2 to put the frequency above the range of human hearing. Use a pushbutton switch and train the dog to recognize a distinctive series of ultrasonic beeps.

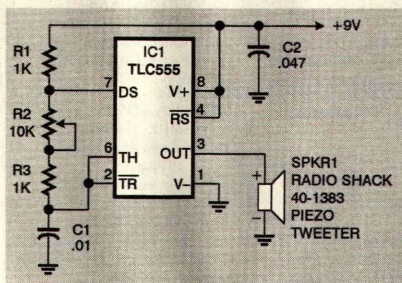


**FIG. 1**—THIS OSCILLATOR emits a tone that can be varied between 6 and 25 kHz. The higher frequencies can not be heard by most humans, although dogs can hear it just fine.

comparable to its weight in pounds.

Car batteries aren't rated in amp-hours because their total capacity isn't especially important; in fact they're designed never to be deeply discharged. What matters in a car battery is the total number of amps that it can deliver in cold weather ("cold cranking amps"), even though if you kept drawing current at that rate, the battery would go dead in just a couple of minutes.

## What's an Amp-Hour?

**Q** Can you please explain to me the meaning of amp-hours, and how they are figured in reference to a car battery? — B. M. Huntsville, TX.

**A** Certainly. The amount of energy you can get out of a battery depends on its voltage (which is fixed), the number of amps that the load draws, and the number of hours before the battery runs down. Multiply the amps by the hours and you get amp-hours.

For example, a battery that can supply 3 amps for 4 hours has a capacity of 12 amp-hours ( $3 \times 4 = 12$ ). The same battery could supply 1 amp for 12 hours, or 12 amps for 1 hour, or 2 amps for 6 hours, and so on.

To give you some realistic numbers, an alkaline D cell is good for about 10 amp-hours (which is actually quite impressive considering its small size). An alkaline 9-volt battery is only good for 0.4 amp-hour, but that's enough to power a 50-mA (0.05-amp) transistor radio for 8 hours. And here's a handy rule of thumb: The amp-hour capacity of a 12-volt lead-acid battery is roughly

## NiCd Charging

**Q** I have seen a number of NiCd charger circuits like the one in Fig. 2. Are the values shown appropriate to charge the battery in 6 to 7 hours. If there is a rule of thumb to follow, it would be appreciated. — P. S. M., Eaton, IN.

**A** The charging current for an NiCd battery depends on its capacity in amp-hours (see the previous question) and how quickly you want it charged.

The old standard is to charge for 12 to 14 hours at a current of C/10 amps, where C is the capacity in amp-hours. For example, a 1.2-AH battery gets a charging current of 0.12 amp.

To charge a battery in 6 or 7 hours, you'll want to use twice as much current, i.e., C/5. That's about as fast as you can go without using special circuits to monitor the battery voltage and/or temperature.

Since you asked for a rule of thumb, we'll do an approximate calculation; greater precision would gain us nothing because there is so much variation between NiCd batteries.

For good current regulation, the AC voltage should be at least twice that of the battery. The resistance depends on the voltage drop, but since the current is only flowing half the time, the resistance should be only half the value given by Ohm's Law.

Here's a concrete example. Suppose you're charging a 7.2-volt, 1200-mAH (1.2-AH) battery pack from a source of 18 volts AC, and you want to charge in 6 to 7 hours at C/5. First, find the average charging current:

$$I = C/5 = 1.2/5 = 0.24 \text{ ampere}$$

Next, the resistance, using  $R = E/I$  and then halving it:

$$R = 0.5 \times E/I = 0.5 \times (18 - 7.2)/0.24 = 22.5 \text{ ohms}$$

Finally, the resistor dissipation is found using  $P = I^2 R$  with the average charging current:

$$P = I^2 R = (0.24)^2 \times 22.5 = 1.3 \text{ watts}$$

So a 22-ohm, 2-watt resistor will do the job just fine. You'll find that batteries of different voltages (such as 7.2 and 9.6 V) can often be charged in the same charger as long as their amp-hour ratings are similar. Also, you can charge a higher-

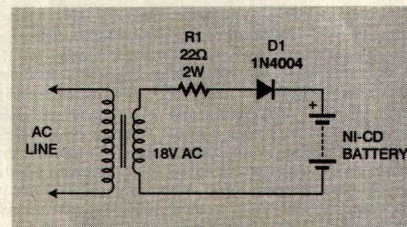


**FIG. 2**—WHILE THERE ARE many different NiCd-battery charger circuits, a simple resistor/diode combination like this one will do the job.



**DIGITAL is the Future**

**Introducing. . .**

**30% - 50% Savings!**

**Compare to Cable and Other 18" dishes**



**"The  
DISH™ is Small,  
The  
Programming  
BIG"**

Curious about those little dishes? Meet the newest arrival, the DISH™ Network System. This shining star, is small, attractive and the latest in technology, but what really sets it apart is the programming it delivers to your television screen. The DISH™ Network is full of the most popular programming at prices much lower than the competition. Call Skyvision now for more information.

Make digital your future...Today.

**Beat The Rush!  
Call the Digital Hotline Now!  
800-500-9264**



Call now for your FREE  
Skyvision 2000 Catalog of  
Home Entertainment Systems

**The Best Television Comes on a DISH™**

DISH Network is a service mark of EchoStar Comm. Corp.

**If you have one of these. . .**

**"Keep it Running Strong"  
With a Discount Buyer's Guide**

If you are the owner of a C/Ku-band Full View Satellite System, we know you'll want to keep it up and running strong. The Skyvision Discount Buyer's Guide will give you advice and products to get the job done right.

**You Will Find a Wide Selection of:**


- Complete Systems
- Advanced Upgrades
- Parts & Accessories
- Tune-Up Tools & Advice
- Technical Tips Galore
- Discount *Skypac*™ Programming

**For Your Free Issue Call Now**

**800-334-6455**

**Need a repair item Fast??**

**"We'll Get It Out Today"**

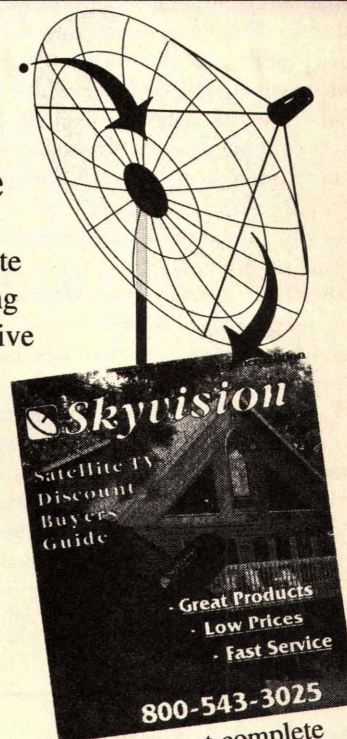

**800-543-3025**  
The most complete  
Big Dish Satellite  
Discount Buyer's Guide!  
Get your FREE copy now



amp-hour battery in a charger designed for batteries of lower capacity by prolonging the charging time.

Purists will no doubt note that we've ignored the diode voltage drop and the difference between RMS and average current. For all practical intents and purposes, they have no effect in this application.

## NiCd Zapping

**Q** *I have several non-functioning NiCd battery packs. I've found several battery zappers in Rudolf Graf's Encyclopedia of Electronic Circuits, but the circuits show widely varying zapping voltages and currents. How do I determine what voltage and current I need to use for this? — G. A. H., Santa Fe, NM.*

**A** Unfortunately, NiCd zapping is not an exact science. In fact, manufacturers don't recommend it at all, because it never leaves a battery as good as new. But we all know that it works and can often enable you to get several more weeks' or months' use out of an otherwise defunct battery.

The purpose of zapping is to clear an internal short circuit by burning away small crystalline structures that have formed inside a cell. There are many different techniques. One method is to charge a 1000- $\mu$ F capacitor to about 12 volts, then apply it briefly to the battery terminals. Another is to charge the battery briefly with heavy current (2 or 3 amps) while watching the terminal voltage; chances are it will come up to normal after half a minute or so. Make sure the current is indeed limited to 3 amps, since higher currents can make the battery explode.

All of those techniques are hit-or-miss, and the battery usually develops the same problem again in a short time. But there's no harm in trying. If possible, you should open up the battery pack to test and "zap" the individual cells. Be aware that some battery packs contain fuses that can be blown by the zapping process.

## Video In Dim Light

**Q** *I have a Sony 8mm camcorder and would like to be able to shoot video in low-light and extremely-low-light situations. Of course a video light will work up*

## HOW TO GET INFORMATION ABOUT ELECTRONICS

**Books:** Several good introductory electronics books are available at RadioShack, including one on building power supplies.

An excellent general electronics textbook is *The Art of Electronics*, by Paul Horowitz and Winfield Hill, available from the publisher (Cambridge University Press, Tel: 800-872-7423) or on special order through any bookstore. Its 1125 pages are full of information on how to build working circuits, with a minimum of mathematics.

Also indispensable is *The ARRL Handbook for Radio Amateurs*, comprising 1000 pages of theory, radio circuits, and ready-to-build projects, available from the American Radio Relay League, Newington, CT 06111, and from ham radio equipment dealers.

**Copies of past articles:** Copies of past articles in *Electronics Now* and *Popular Electronics* (post 1991 only) are available from Claggg, Inc., Reprint Department, P.O. Box 4099, Farmingdale, NY 11735 (Tel. 516-293-3751).

**Electronics Now** and many other magazines are indexed in the *Reader's Guide to Periodical Literature*, available at your public library. Copies of articles in other magazines can be obtained through your public library's interlibrary loan service; expect to pay about 30 cents a page.

**Service manuals:** Manuals for radios, TVs, VCRs, audio equipment, and some computers are available from Howard W. Sams & Co., Indianapolis, IN 46214 (Tel: 800-428-7267). The free Sams catalog also lists addresses of manufacturers and parts dealers. Even if an item isn't listed in the catalog, it pays to call Sams; they may have a schematic on file which they can copy for you.

Manuals for older test equipment and ham radio gear are available from Hi Manuals, PO Box 802, Council Bluffs, IA

51502, and Manuals Plus, Box 637, Spanaway, WA 98387.

**Replacement transistors, ICs, and other semiconductors:** Replacement components for a wide variety of popular devices is marketed by Philips ECG, NTE, and Thomson (SK) and are available through most parts dealers (including RadioShack on special order). The ECG, NTE, and SK lines contain a few hundred parts that substitute for many thousands of others; a directory (supplied as a large book and on diskette) tells you which one to use. NTE numbers usually match ECG; SK numbers are different.

Remember that the "2S" in a Japanese type number is usually omitted; therefore, a transistor marked D945 is actually a 2SD945.

**Hamfests (swap meets) and local organizations:** These can be located by writing to the American Radio Relay League (Newington, CT 06111; <http://www.arrl.org>). A hamfest is an excellent place to pick up used test equipment, older parts, and other items at bargain prices, as well as to meet your fellow electronics enthusiasts both amateur and professional.

**Internet:** On the Internet, electronics is discussed in Usenet newsgroups such as *sci.electronics.repair*, *sci.electronics.components*, *sci.electronics.design*, and *rec.radio.amateur.homebrew*. "For sale" messages are permitted only in *rec.radio.swap* and *misc.industry.electronics.marketplace*.

Many electronic-component manufacturers now have web pages; see the directory at <http://www.hitex.com/chipdir/>, or try addresses such as <http://www.ti.com> and <http://www.motorola.com> (substituting any company's name or abbreviation as appropriate). Many IC data sheets can be viewed online.

*to a certain distance, but what about objects farther away? Is there some kind of adapter that can be mounted on the camcorder to provide daytime range at night? — M. M., Denver, CO.*

**A** You're probably thinking about image-intensifier tubes, which are photoelectric devices that amplify a faint image. These are used in military night-vision binoculars and other instruments.


Image tubes and instruments that use them are available from STANO Components, Inc., PO Box 2048, Carson City, NV 89702 (Tel: 702-246-5281, Internet: <http://www.stano.night-vision.com>). You'll need a complete night vision scope with optics to form a viewable image, not just the tube alone; then you can aim the camcorder into the instrument instead of your eye.

*continued on page 28*



# CircuitMaker®

## The Virtual Electronics Lab™

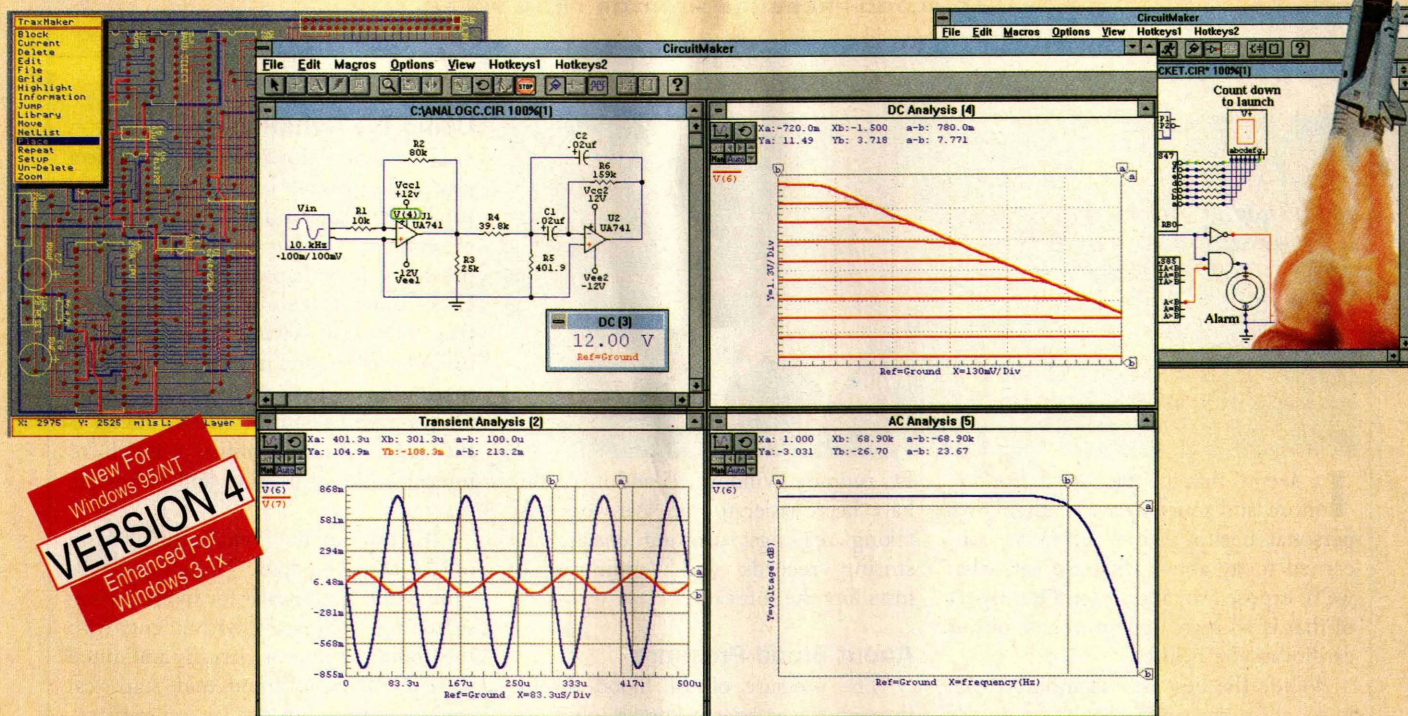

New For  
Windows 95/NT  
**VERSION 4**  
Enhanced For  
Windows 3.1x

### Professional Schematic Layout

CircuitMaker's schematic capabilities are unmatched and include many advanced editing features not found in similar programs. These powerful features minimize the time and task associated with drawing a schematic and insure a professional looking final product. Printout and export options are numerous and results are of the highest quality. But that's what people have come to expect from CircuitMaker.

### Unlimited, Indestructible Devices

CircuitMaker ships with over 1500 devices. That's more (at no additional cost) than any competing product. If you need a device that is not included, CircuitMaker provides industry standard SPICE import and a powerful macro capability. These indestructible devices accurately emulate actual devices and enable the user to try all those "what if" scenarios with no risk and at no additional cost.

### Accurate Simulation & Advanced Analysis

CircuitMaker features analog, digital and mixed-mode simulation. Obviously, simulation is of no value if the results are not accurate. CircuitMaker's simulation engine is based on Berkeley SPICE3, which is renowned for it's accuracy. That's why we can factually state that CircuitMaker provides it's user with the most accurate simulation available. Furthermore, CircuitMaker provides a wealth of analysis capabilities not found in other products in it's class. No other product offers this much simulation muscle at such a reasonable price.

### Printed Circuit Board Output

CircuitMaker's PCB output capability helps you complete your design cycle, by generating a netlist that can be imported into any compatible PCB program. This is not a costly "add-on module", it comes standard with every copy of CircuitMaker. MicroCode Engineering also offers TraxMaker, a professional level, PCB layout and autorouting program for just \$299. Used in conjunction with CircuitMaker, TraxMaker completes a powerful end-to-end circuit design system.

Full SPICE Compatibility  
Digital, Analog, and  
Mixed-Mode Simulation  
Advanced Schematic Features  
Schematic Capture  
SPICE Export/Import  
PCB Export  
Retail Price

| CircuitMaker                          | YES | YES | YES | YES | YES | YES | \$299 |
|---------------------------------------|-----|-----|-----|-----|-----|-----|-------|
| Electronics Workbench version 4       | YES | NO  | YES | NO  | NO  | NO  | \$299 |
| Electronics Workbench Engineer's Pack | YES | NO  | YES | NO  | YES | YES | \$599 |

**"CircuitMaker Shocks The Competition,  
With An Unbeatable Bottom-line"**

### Total Customer Satisfaction

At MicroCode Engineering we are committed to total customer satisfaction. When you purchase CircuitMaker you have the confidence of knowing that a trained staff of professionals is available to serve you after the sale. Our free unlimited customer service is second to none! Whether you have general or technical questions they will be answered promptly by a knowledgeable representative.

### FREE Functional Demo

A free functional demo is available on the Internet at <http://www.microcode.com>, on CompuServe (GO MICROCODE) and on America Online by doing a file search for CircuitMaker.

Call now to order or  
request additional information  
**800-419-4242**







# EQUIPMENT REPORTS

A PC-BASED BLOOD-PRESSURE MONITOR FROM PULSE METRIC.

*Monitoring and recording blood pressure is easy with the DynaPulse.*

CIRCLE 15 ON FREE INFORMATION CARD



It seems that people are becoming more and more aware of their own personal health. We're all more concerned today about what we eat, what we're exposed to, and so on. One aspect of that is an increased awareness of our cardiovascular health.

While the best way to monitor that is to make sure you visit your doctor regularly, in our hectic schedules, sometimes that gets put off longer than it should. To keep an eye on such things as pulse and blood pressure, some people have their own equipment. But even so, you have to be careful in taking measurements and then have to record the statistics.

The newest, easiest way to take and keep track of those measurements is to use Pulse Metric, Inc.'s (6190 Cornerstone Court East, Suite 103, San Diego, CA 92121; Tel: 619-546-9461, 800-927-8573) DynaPulse 200M, which is computer-controlled and keeps track of the records for you. The 200M monitor unit is housed in an attractive plastic enclosure that connects to a PC or Mac computer. You need DOS 3.3 or higher, Windows 3.0 or higher, or Macintosh System 6.0.7 or higher.

The kit comes with an inflatable, adult-sized cuff and inflation bulb that plugs into the side of the monitor. Different-sized arm cuffs—child-size and oversize—are optionally available. The monitor connects to the computer via a serial cable. Software then converts your computer screen into a cardiovascular laboratory. We tested DynaPulse on a

PC running Windows 95 and it couldn't have been easier to use. We were busy taking readings, printing charts, and storing records within minutes of installing the software.

## About Blood Pressure

The pressure of the blood flowing through the arteries is known, obviously enough, as blood pressure, which varies as the heart beats. When the heart pushes blood out from the heart, the pressure increases, and the *systolic* or maximum blood pressure is achieved. When the heart relaxes, the pressure in the artery decreases, and the *diastolic* or minimum pressure is reached. The average pressure throughout the pulse cycle is called the Mean Arterial Pressure (MAP). The units of measurement for blood pressure are millimeters (mm) of mercury, or Hg. Systolic blood pressure is given first followed by the diastolic blood pressure, or systolic/diastolic in mmHg. Normal blood pressure typically has a high from about 130 to 139 and a low from 85 to 89.

In healthy human beings, blood pressure can increase temporarily during stressful activities, including drinking coffee and smoking, but will return to normal when the activity ceases. However, when it stays high over a long period of time, a person is said to have high blood pressure, or *hypertension*.

Unfortunately, you have to actually measure your blood pressure to know if it's normal or high. There's no other way to know if a problem exists—until it is too late.

## Using the DynaPulse

The DynaPulse 200M is the perfect way to keep track of your blood pressure, your whole family's blood pressure, or even all of your customers' blood pressures if you happen to be a pharmacist or something similar. Note however, that we're only saying "keep track of" blood pressure, and nothing about interpreting it. Unless you are a doctor, you always have to consult one. A doctor is the only person qualified enough to interpret blood pressure and pulse-rate readings.

You can buy the DynaPulse 200M in one of three versions. The clinical version, \$499, is designed for hypertension screening in clinical environments with the ability to store a virtually unlimited patient database, trend and statistical analysis, histogram display, pulse-waveform analysis, and a physician's reference. The educational version, priced at \$295, is designed for teaching and comes complete with curriculum and lab material. A home version, which costs \$179, is simpler and can keep track of up to six people.

We found DynaPulse very easy to use. The software installed without a hitch, and we connected it to the COM1 port on a PC (software settings allow for operation on any available com port). There isn't even an on/off switch on the 200M, as software activates the unit when necessary. An inflatable cuff—just like your doctor's—wraps around your arm and secures with Velcro. A squeeze bulb with a relief valve inflates the cuff. But instead of having the output pressure tube connected to a mercury-filled instrument, it plugs into the DynaPulse monitor, which contains a semiconductor pressure sensor. The monitor, which is powered by four AAA batteries, converts the input pressure readings from the arm cuff into an RS-232 signal that your PC can understand.

When you use the DynaPulse, you can immediately begin measuring blood

*continued on page 73*



# GET HERE.


## LEARN A SKILL YOU ENJOY... ...THEN FIND A JOB THAT HAS A FUTURE.

**FREE**  
One Year Subscription  
of *Electronics Now*  
When You Enroll in Any  
CIE or World College  
Program!
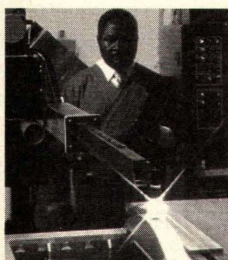
### Everyone has to start somewhere.


As 150,000 CIE graduates have discovered, independent study from The Cleveland Institute of Electronics can get you where you want to be. In a secure, financially rewarding, exciting career field of your choice.

Since 1934, CIE has been on the forefront of an ever expanding technological revolution.



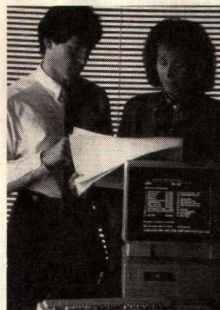
**Industrial Robotics**

ment. CIE's curriculum is unique from other independent-study schools in the respect that we not only provide hands-on training utilizing today's technology we also instill the knowledge and understanding of why technology works the way it does. This is the foundation upon which every CIE graduate can trace their success back to and in which CIE's reputation as a quality learning facility is based on.



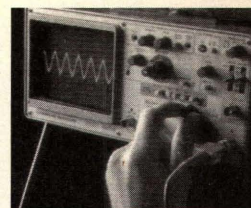**Project Engineer**


Independent study is not for everyone. But, if you have the desire, the basic intellect and the motivation to succeed, CIE can make it happen. Our learning program is patented and each lesson is designed for independent study while our instructors are available to assist you whenever you feel you need help. In fact, CIE's curriculum is so well respected many Fortune 1000 companies utilize it for their own employees.



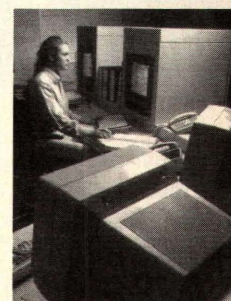**Telecommunications**

CIE offers personalized training to match your background with over ten career courses, an Associate Degree Program and a Bachelor Degree Program through our affiliation with World College. And every CIE graduate got started in a

successful career the same way you can...by sending for your free CIE course catalog and judging for yourself if CIE's for you.



**Computer Programming**

# START HERE...



**Electronics**

Back then it was radio and TV, today it's computer technology, programming and the electronics that make it all possible. Today and yesterday's similarities are

uncanny... Employers are looking for qualified applicants to hire and having a hard time finding them.

Students at CIE receive the training and the education needed to get hired and to succeed in challenging fields such as computer programming, robotics, broadcast engineering, and information systems manage-

**YES!** Please send me more information on:

- ☐ CIE's Associate Degree Program
- ☐ CIE's Computer Programming Course
- ☐ CIE's 12 Career Courses
- ☐ World College's Bachelor Degree Program

AE92

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Phone: \_\_\_\_\_

Check for G.I. Bill Details

☐ Active Duty ☐ Veteran

# CIE

*It's More Than Just Training...  
...It's an Education.*

1776 East 17th Street  
Cleveland, OH 44114  
(216) 781-9400 • 1-800-243-6446





# NEW PRODUCTS

USE THE FREE INFORMATION CARD FOR FAST RESPONSE

## Digital Real-Time Oscilloscopes

THE TDS 200 SERIES OF DIGITAL real-time (DRT) oscilloscopes from Tektronix cost about half the price of existing entry-level digital scopes and offer a combination of features that will

maintain full contrast at all sweep speeds and gain settings. Any signal that triggers the scope will be clearly visible on screen.

The TDS 200 series relies on Tektronix DRT oversampling technology to



CIRCLE 20 ON FREE INFORMATION CARD

overcome customers' objections to making the switch from analog to digital scopes. Designed for manufacturing, education, and service applications, the 60-MHz TDS 210 and the 100-MHz TDS 220 are priced competitively with similarly equipped analog scopes. They also offer superior measurement capability, analog-like controls and operating modes, and compact size—about one-fourth the size of other benchtop oscilloscopes.

One reason for that compact size is that both units in the TDS 200 series feature a bright, high-contrast, liquid-crystal display with a wide viewing angle. Unlike analog scope displays, the LCD main-

provide excellent waveform quality, update rate, and stability. Both models sample at 1 GS/s—at least ten times their bandwidth—which allows users to capture signal details invisible on analog scopes. Pre-programmed automatic measurements enable users to quickly quantify waveforms: period, frequency, cycle RMS, mean, and peak-to-peak. Other productivity features include automatic setups (similar to autoranging in a digital multimeter), stored reference waveforms, and stored front-panel setups that are not lost when the power is turned off.

The user interface looks and feels "analog," bringing back many of the

front-panel knobs that are familiar to analog-scope users. Routine functions such as gain, sweep speed, and vertical/horizontal positioning, are immediately accessible and respond like analog-scope controls. Automated digital functions are controlled by a simplified on-screen menu system, available in ten user-selectable languages.

The TDS 210 and TDS 220 carry suggested U.S. list prices of \$995 and \$1695, respectively.

**TEKTRONIX, INC.**

P.O. Box 500

Beaverton, OR 97077-0001

Tel: 1-800-479-4490, action code 317

## DSP Filter

MFJ Enterprises' MFJ-781 DSP filter will add "brick wall" DSP filtering to any TNC or multimode data controller, allowing you to copy signals buried in noise and QRM—signals you can't even hear. The device will improve all modes on any model TNC, and it will give you an array of 100 sharp *No\*Ring* linear-phase FIR filters. You can choose 20 filters to include on the front-panel switch for easy, one-knob selection.

The MFJ-781 plugs between your transceiver and multimode. It features input and output level controls and an accurate, easy-to-use input level indicator. Automatic gain control helps keep your audio level constant during signal fade. The on/off/bypass switch provides a true bypass.



CIRCLE 21 ON FREE INFORMATION CARD



Under severe QRM, the filter will greatly improve copy of packet, AMTOR, PACTOR, GTOR, Clover, RTTY, SSTV, WeFAX, Fax, CW, and just about any other digital mode. You can choose from 64 data filters with 16 mark/space pairs, four shifts, and four baud rates. Interference is 40-dB down, 60-Hz outsize passband. You also get 32 CW filters with eight CW tones (300-1000 Hz) and four bandwidths (50-500 Hz). Four customized filters are optimized for VHF packet, Clover, WeFAX, and SSTV.

The MFJ-781 DSP filter has a suggested retail price of \$129.95. For MFJ-1278B's, order the MFJ-780 plug-in DSP filter, priced at \$99.95.

#### **MFJ ENTERPRISES, INC.**

P. O. Box 494


Mississippi State, MS 39762

Tel: 601-323-5869 or 1-800-6477-TECH

Fax: 601-323-6551 or 1-800-647-1800
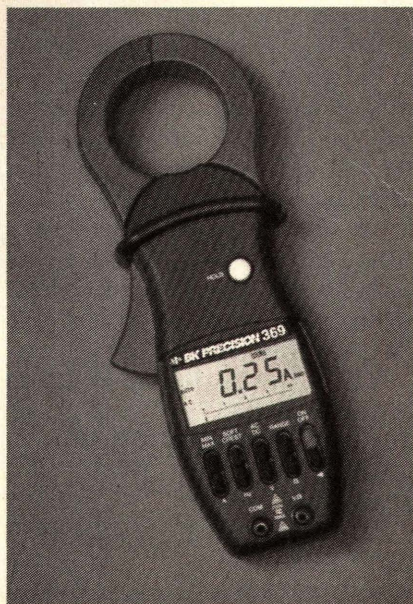
### **True-RMS Clamp Meter**

Electrical contractors, plant-maintenance engineers, electricians, and utility technicians will find B+K Precision's Model 369 multifunction clamp meter to be convenient and useful for measuring high electrical currents without direct electrical contact. The handheld instrument measures true-RMS AC current to 700 amps from 45 Hz to 1 kHz, and DC current to 700 amps with 2% accuracy. AC and



CIRCLE 22 ON FREE INFORMATION CARD

DC voltage can be measured to 750 volts with 1% accuracy, using test leads. The clamp can be used to measure resistance from 0.1 to 4000 ohms and frequency from 0.1 Hz to 10,000 Hz with 0.2% accuracy.

The Model 369 can also measure instantaneous AC amperes using its crest mode, which can log peak currents as high as 1000 amps. Data hold instantly freezes the displayed reading. Continuity check sounds a tone to verify an unbroken electrical path. Min-Max mode logs a running record of minimum, maximum, and average values.

The meter accepts conductors up to two inches in diameter. Its large, 4000-count LCD readout includes a 41-segment bar graph for peaking, nulling, and easy identification of varying signals.

The Model 369 clamp-on meter, complete with battery, clip-on carrying case, test leads, and manual, costs \$199.

#### **B+K PRECISION**

6470 West Cortland Street


Chicago, IL 60635

Tel: 1-800-462-9832

Fax: 312-794-9740
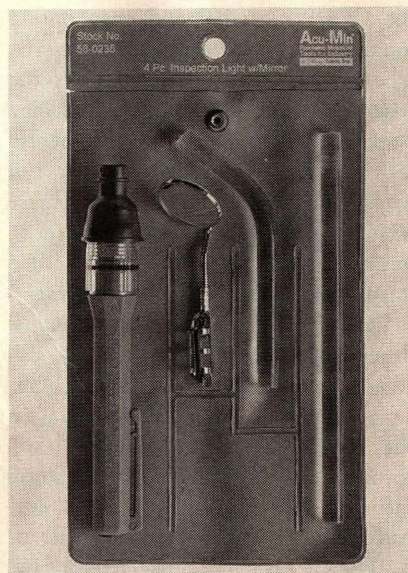
### **Four-Piece Inspection Light**

Specifically designed for the field technician, Moody's Acu-Min Inspection Light allows light to shine on hard-to-



CIRCLE 23 ON FREE INFORMATION CARD

reach areas. The set contains a flashlight, a straight conducting rod, a curved con-

ducting rod, and a mirror. The straight rod conducts the battery-powered xenon light down straight passages. The curved rod conducts light around corners to reach areas not normally visible. The small mirror fits snugly on both conducting rods to expand the user's field of view. The set comes packaged in a vinyl pouch.

The Acu-Min Inspection Light (stock #58-0235) costs \$42.95.

#### **MOODY TOOLS, INC.**

42-60 Crompton Avenue

East Greenwich, RI 02818-0230

Tel: 1-800-TOOL-INC

Fax: 401-885-4565

### **Memory Tester**

Aristo Computers' SIMCHECK II is a third-generation, state-of-the-art memory tester. With a fast 486 processor and sophisticated time-delay circuitry, the tester allows users to accurately test today's—and tomorrow's—large memory devices. The stand-alone, portable unit tests both 72-pin and 30-pin SIMM modules in sizes up to 4Gx40 with a 96-pin expansion slot for future add-on companion testers. The SIMCHECK II measures RAS and CAS access time at 1-ns resolution. It includes a generic interface for the Automatic Handler, parallel printer, and other devices. The fully automatic test program allows non-technical personnel to operate the tester with the push of a single button, yet



CIRCLE 24 ON FREE INFORMATION CARD

still allows engineers to set up complex custom tests.

The SIMCHECK II has a retail price of \$2495.

#### **ARISTO COMPUTERS INC.**

6700 SW 105th Avenue, Suite 300

Beaverton, WA 97008


Tel: 1-800-3ARISTO or 503-626-6333

Fax: 503-626-6492


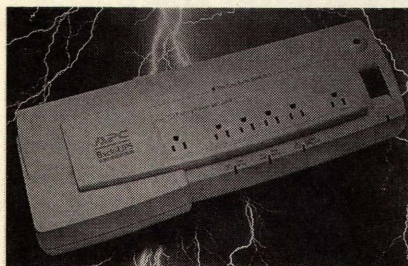
## Workstation Surge Protection

The Back-UPS Office from American Power Conversion is a multipath power device intended to combat hardware damage caused by surges and prevent data loss from brownouts and blackouts. The device offers multi-outlet surge protection, phone line protection for on-line users, network data-line protection for corporate workstations, and battery back-up for CPUs. Aimed at the small-office/home-office (SOHO) market, and backed by a \$25,000 equipment-protection guarantee, the device protects against all power problems on all power paths to a computer and peripherals including printers, scanners, external tape drives, and fax machines.



CIRCLE 25 ON FREE INFORMATION CARD

The Back-UPS Office offers six outlets, all with surge-suppression and EMI/RFI filtering, and three of them also provide battery power for data protection. The device provides 7 to 13 minutes of battery backup during a power disruption, allowing the user plenty of time to shut down the system in an orderly manner. Modem protection safeguards users' Internet access and prevents PC damage from surges and spikes entering through the "back door." An indicator lets the user know when a new battery is needed. A site-wiring fault indicator detects wiring problems in the building that could cause potential fire hazards. Unique "BlockSafe" outlet spacing allows transformer blocks to be used without sacrificing other outlets.

The Back-UPS Office surge protector costs \$179.

### AMERICAN POWER CONVERSION

P. O. Box 278  
132 Fairgrounds Road  
West Kingston, RI 02892  
Tel: 1-800-877-4080  
Fax: 401-789-3710

24 Web site: <http://www.apcc.com>

## 900-MHz Cordless Phone

Sanyo's Model CLT-986 900-MHz, digital spread-spectrum cordless telephone features a call-management caller-ID system, AC power-failure protection, and—for those who need still more freedom than that afforded by mere cordless phones—a "Speak Station" handset speakerphone for hands-free communication. The 900-MHz direct-sequence, spread-spectrum technology extends the transmission range and virtually eliminates interference. The digital technology also makes it difficult for eavesdroppers to tap into the signal.



CIRCLE 26 ON FREE INFORMATION CARD

AC power-failure protection allows the CLT-986 to be used even during interruptions in the supplied line power. The back-up battery pack, built into the base of the unit, uses four "AA" alkaline batteries. The speakerphone handset also provides two-way paging. Sanyo's call management system is intended for use with the Caller ID service provided by local phone companies. With a recorded log of up to 20 calls, the system maintains a list of caller names with bi-lingual prompts, call times, dates, and last call received, with area-code editing capability. A 16-digit, two-line LCD readout on the handset allows the user to scroll through recorded data. Other features include one-hour quick charge, dual keypad operation, and 20-number memory.

The CLT-986 cordless telephone has a suggested retail price of \$349.99.

### SANYO

21350 Lassen Street  
Chatsworth, CA 91311-2329


Tel: 818-998-7322

Fax: 818-701-4149
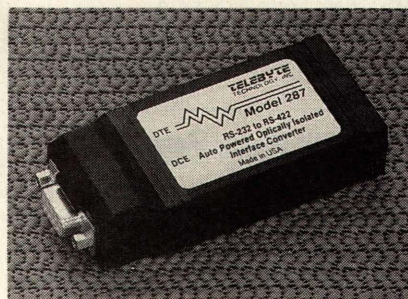
## Interface Converter

New safety standards such as IEC 8081-2 place limits on the shock hazards to which people are subjected when using electronic devices in a medical environment. Telebyte's Model 287 RS-232 to RS-422 opto-isolated interface converter satisfies those stringent requirements for computer systems.

The Model 287 does not require a separate AC or DC input because the power required is extracted from the PC's RS-232 interface. That power is further conditioned to develop an isolated power supply to operate the link side of the interface converter.



CIRCLE 27 ON FREE INFORMATION CARD

A DB9 female connector allows the converter to be directly attached to any PC communications port, and an RJ-12 modular connector creates the link interface. A DTE/DCE switch allows the user to reverse the transmit data and receive data signals to interface to a different type of port. Data is accommodated at rates up to 19.2 kilobytes per second. The transmit- and receive-data signals use the four inner pins of the RJ-12 connector, and the two outside pins are reserved for grounding a shield on the link cable, if one is used. The ground path includes a ground stud to which a 12-inch ground connection is attached. The Model 287 will withstand a 4-kilovolt discharge with the ground connection.

The Model 287 RS-232 to RS-422 converter costs \$155.

### TELEBYTE TECHNOLOGY, INC.

270 Pulaski Road  
Greenlawn, NY 11740

Tel: 516-423-3232 or 1-800-TELEBYT

Fax: 516-385-8184

E-mail: [sales@telebyteusa.com](mailto:sales@telebyteusa.com)

Web site: <http://telebyteusa.com>

EN






# NEW LITERATURE

USE THE FREE INFORMATION CARD FOR FAST RESPONSE
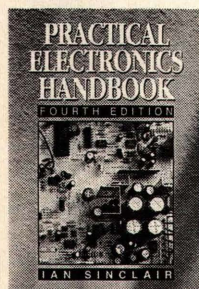
## Practical Electronics Handbook Fourth Edition

by Ian Sinclair  
Butterworth-Heinemann  
225 Wildwood Avenue, Unit B  
P. O. Box 4500  
Woburn, MA 01801  
Tel: 617-928-2500  
**\$32.95**



CIRCLE 337 ON FREE  
INFORMATION CARD

This comprehensive book provides a practical collection of circuits, rules of thumb, and design data for professional engineers, students, and electronics hobbyists. Enough background is included to make the book accessible to beginners and to facilitate the understanding and development of a range of basic circuits. For those with more electronics experience, the book can serve as a compact compendium of everyday information and a convenient reminder of electronic principles and circuits.

Topics covered include passive components, active discrete components, discrete-component circuits, linear ICs, digital ICs, microprocessors and microprocessor systems, transferring digital data, digital-to-analog conversions, computer aids in electronics, and hardware components. The fourth edition has been updated with new chapters and sections covering topics such as sensing components, connectors, and soldering.

## Switch Catalog #103

Switches Plus  
192 Pepe's Farm Road  
Milford, CT 06460  
Tel: 1-800-792-4757

Fax: 1-800-792-5877

Web site: <http://www.switchesplus.com/>  
**Free**




CIRCLE 338 ON FREE  
INFORMATION CARD

An all-metal, sealed, vandal-proof keypad leads off the new line of keypad devices included in this catalog. The brochure also features a wide variety of heavy-duty and signal-level pushbuttons, pilots, and selectors; emergency stop switches; snap-acting switches; joystick controls; pulse counters; and power supplies. All products feature UL and international approvals as well as ISO 9001 certification. The 56-page catalog contains ordering information, descriptions, illustrations, technical specifications, and prices.
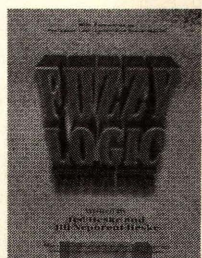
## Fuzzy Logic for Real World Design

by Ted Heske and Jill Neporent Heske  
Annabooks  
11838 Bernardo Plaza Court  
Suite 102A  
San Diego, CA 92128  
Tel: 619-673-0870 or 1-800-462-1042  
Fax: 619-673-1432  
**\$49.95, including disk**



CIRCLE 339 ON FREE  
INFORMATION CARD

This engineering guide is written for designers of embedded systems that make use of fuzzy logic. The book provides step-by-step instructions for designing fuzzy-logic systems, and its companion diskette includes a C-language fuzzy kernel, complete with

directions for cross-compiling it for a variety of Motorola and Intel microcontrollers. The diskette also contains all of the source code that is presented in the book.

The first three chapters present an overview of fuzzy-logic history, terminology, and theory of operation. Subsequent chapters discuss engineering fundamentals, embedded-systems considerations, and hardware/software partitioning. The book also discusses object-oriented fuzzy-logic design and C++ implementation. A fuzzy-logic primer ties it all together. Appendices include a list of fuzzy-logic development tools and suppliers, and instructions for cross-compiling the fuzzy kernel for a variety of Motorola microcontrollers.

## Multimedia DSO Teaching Aid

Metrix  
P.O. Box 332  
Brea, CA 92622-0332  
Tel: 714-992-1239  
**\$10**



CIRCLE 340 ON FREE  
INFORMATION CARD

The Metrix OX8020 CD-ROM is an interactive, multimedia demonstration of how to use a digital storage oscilloscope (DSO). Instruction is presented in French, English, German, and Spanish. Aimed at both teachers and students, the CD-ROM can be used for on-the-job or classroom instruction. Besides an introduction to the use of oscilloscopes to capture and store waveforms, the CD-ROM demonstrates how, after acquisition, data can be manipulated and displayed different ways, and how measurements can be output to plotters, computer files, and monitors.

Although it uses the Metrix OX8020



digital storage scope as a model, the disk can be used with a PC alone. Minimum system requirements are a 486 multimedia PC (with audio board), 8 megabytes of RAM, a video card, a CD-ROM drive, Windows 3.1, and at least 10 megabytes of free hard-drive space.

## The Corporate Intranet: Create and Manage an Internal Web for Your Organization

by Ryan Bernard

John Wiley & Sons, Inc.


605 Third Avenue

New York, NY 10158-0012

Tel: 1-800-225-5945

Web site: <http://www.wiley.com/compbooks/>

**\$29.95**

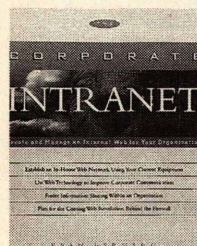

CIRCLE 341 ON FREE  
INFORMATION CARD

While many companies use the Internet to provide their outside customers with in-depth on-line information, relatively few take advantage of internal, or Intranet, Web sites. A corporate

Intranet site is an inexpensive yet powerful alternative to other forms of internal communications. It is a secure, interactive network that allows employees to instantly access, view, and contribute to live product-management documents, regardless of what kind of computer is being used.

This book shows Internet-savvy managers, marketers, and other communications specialists how they can dynamically distribute and share vital information across their organizations—even reaching foreign subsidiaries and home-offices. It presents a practical overview of everything needed to allow a computer network to support an Intranet system. After introducing basic Web tools and technology, the book helps various departments within a corporation budget to plan and promote the Intranet. It explains how to provide outside employees with secure access, and how to create “public” and “private” channels to interface the Intranet with the Internet. Case studies from Sun Microsystems, Chevron Petroleum,

Digital Equipment, and Nortel enhance the text.

## Easy Calculator Math for Electronics

by Larry R. Luchi

Limelight Books


Division of Tiare Publications

P. O. Box 493

Lake Geneva, WI 53147

Tel: 414-248-4845

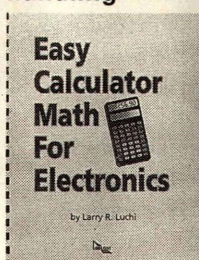**\$17.95 plus \$3 shipping and handling**



CIRCLE 342 ON FREE  
INFORMATION CARD

include Ohm's Law, phase angles, component values for resonance, transistor characteristics, and much more.

Each formula is carefully explained, with one or more step-by-step examples presented in an easy-view, easy-to-follow format. Explanations of terminology and theory are also included, along with diagrams to help readers understand the material.

This study guide helps readers make quick work of math problems involving electronics. It takes the reader through each required step in more than 30 formulas used in electronics; topics

## Coaxial Products Catalog #1995

Pasternack Electronics


P. O. Box 16759

Irvine, CA 92713

Tel: 714-261-1920

Fax: 714-261-7451

**Free**

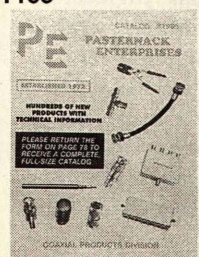

CIRCLE 343 ON FREE  
INFORMATION CARD

cable, adapters, cable-cutting and crimping tools, four types of attenuators, adapters, breakouts, coaxial switches,

patch cords, terminations, shorts, cable assemblies, directional couplers, power dividers, and twinax cables and connectors. The catalog includes photographs and pricing for single units as well as quantity discounts.

## Modern CMOS Circuits Manual

by R. M. Marston

Newnes

an imprint of Butterworth-Heinemann


225 Wildwood Avenue, Unit B

P. O. Box 4500

Woburn, MA 01801

Tel: 617-928-2500

**\$28.95**

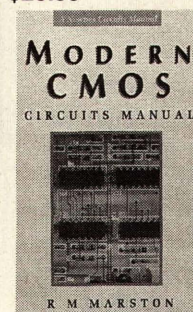

CIRCLE 344 ON FREE  
INFORMATION CARD

The first in a new series of circuit manuals from frequent **Electronics** Now contributor Ray Marston, this book examines operating principles and practical applications of modern medium-speed and fast CMOS digital ICs. The

informative, “how-to” text is accompanied by 470 carefully selected circuits, diagrams, graphs, and tables. Detailed descriptions of more than 120 modern CMOS ICs and their practical applications are included. Aimed at design engineers and technicians, the book's clear layout and easy-to-understand explanations also make it a good starting point for students and hobbyists.

Each chapter opens with an examination of the basic principles of the subject, followed by the presentation of circuits and useful data. The first chapter describes and explains digital-IC basics, CMOS and TTL principles, the various CMOS sub-families, and the basic rules of CMOS usage. Chapter 2 gives a practical introduction to CMOS fundamentals via the 4007UB IC, which can be used in both digital and linear applications. Subsequent chapters deal with modern logic circuitry, CMOS bilateral switches and data selectors, waveform-generator circuitry, clocked flip-flop and counter circuits, ICs, special counter/dividers, data latches, registers, comparators, code converters, and specialized ICs



# Catch Our New Waves



## Function Generator Breakthrough!

Introducing all new  
B+K Function  
Generators offering  
wider frequency  
bandwidths at new  
value pricing.  
Beats the competition  
big time!



### Product Features . .

- Proprietary integrated circuit doubles bandwidth for best performance and reliability.
- All the basic functions plus
  - Sine, Square and Triangle waves
  - TTL and CMOS outputs
  - Variable waveform symmetry
  - Variable DC offset.
- Made in the USA



\* Manufactured in USA from domestic and imported parts.

**For the name of your nearest B+K distributor  
Call 1-800-462-9832**

8am-5pm, CST, weekdays

| Bandwidth Counter | TTL | CMOS | SWP. | AM/FM | Price | Model |
|-------------------|-----|------|------|-------|-------|-------|
| 2MHz              | •   | •    |      |       | \$229 | 4010  |
| 5MHz              | •   | •    |      |       | \$284 | 4011  |
| 10MHz             | •   | •    | •    |       | \$369 | 4017  |
| 20MHz             | •   | •    | •    | •     | \$499 | 4040  |

Compare this price with  
those \$1,200 units! →



**BK PRECISION®**  
MAXTEC INTERNATIONAL CORP.

Domestic and International Sales  
6470 W. Cortland St., Chicago, IL 60635  
Tel: 312-889-1448 • Fax: 312-794-9740  
Canadian Sales: DCS Electronics, Ltd.  
Tel: 905-683-4500 • Fax: 905-683-8074



such as multiplexers and decoders. The final chapter presents a miscellaneous collection of CMOS circuits.

## Master Source-Book 1996 Edition 2

Industrial Computer Source

P. O. Box 910557

San Diego, CA 92191-0557


Tel: 1-800-523-2320

Fax: 619-677-0898

E-mail: [industrial.computer@industry.net](mailto:industrial.computer@industry.net)

Web site: <http://www.industry.net/ind-compsrc>

Free

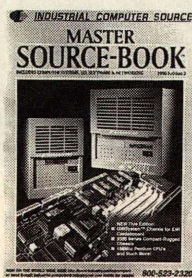

CIRCLE 345 ON FREE  
INFORMATION CARD

This 192-page catalog is filled with computer and network solutions, including software and complete integrated systems. Product categories include CPUs, chassis, rack enclosures, systems servers, embedded

controllers, drive controllers, multimedia cards, monitors, CD and tape backup systems, diagnostics and development boards and software, analog and digital I/O products, PC instrumentation, communications devices, software tools, and applications software. New product highlights include 166-MHz Pentium CPUs and the GIRSystem chassis for EMI containment. Photographs, descriptions, and prices are offered for each product, as well as dimensional outlines where applicable. The catalog also provides reference sections and product comparison charts.

## Error Coding Cookbook: Practical C/C++ Routines and Recipes for Error Detection and Correction

by C. Britton Rorabaugh


McGraw-Hill, Inc.

11 West 19th Street

New York, NY 10011

Tel: 1-800-2-MCGRAW

\$50, including disk

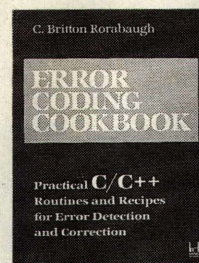

CIRCLE 346 ON FREE  
INFORMATION CARD

ions system. This book strives to simplify the complexities of error coding.

This non-theoretical guide clearly explains the error-coding process. It offers complete, step-by-step instructions on how to select the most appropriate code for your particular application, design the corresponding coders and decoders, and implement many of the most well-known and frequently used codes for error correction. The book's clear descriptions of each code are reinforced by worked-out examples and a brief review of only the necessary math. The accompanying disk provides access to ready-to-use C and C++ programs for generating hundreds of codes for error detection and correction. **EN**

## Q & A

continued from page 16

### PIC Information

**Q** I've designed an electronic product that I think could be greatly improved by using PIC microcontrollers. To redesign, I need information about microcontrollers. If you have any information that you can share with me, I would greatly appreciate it. — T. Z., Easton, PA.

**A** Go straight to the horse's mouth and get a set of PIC manuals (including the *Embedded Control Handbook*) from Microchip, Inc., 2355 West Chandler Boulevard, Chandler, AZ 85224 (Tel: 602-786-7200). Also take a look at their Web page, <http://www.microchip.com>, and Don Lancaster's web page, <http://www.tinaja.com>. Don Lancaster is our "Tech Musings" columnist, and he has written a lot about PICs.

Other than the manuals, there's no general book about PICs as far as we know. If you're entirely new to microcontrollers, you may want to start with the 8051 family simply because good textbooks are available. One of the best

is *The 8051 Microcontroller*, by Kenneth J. Ayala, published by West; any bookstore should be able to order that for you. If you go with an 8051-family controller, consider the Philips 87C750; it's cheap (under \$5) and a development kit that attaches to your PC is available from Philips for less than \$100.

### We've Been Surpassed

In the July installment of "Q&A" (see page 14), a reader asked how to light either a red or a green LED at the flip of a single SPST switch. We published a circuit with 3 resistors and a transistor. Several readers wrote in with simpler

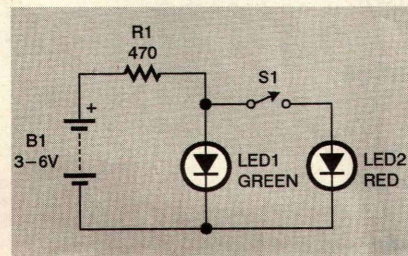


**FIG. 3**—THIS SIMPLER SOLUTION to the switch-operated LED problem takes advantage of the fact that red LEDs have a lower voltage drop than green ones.

solutions. Figure 3 shows the simplest, submitted by D. L. Bare of Kirby, Wyoming. Red LEDs have a lower voltage drop than green ones, so if you connect red and green LEDs in parallel, only the red one lights.

Mr. Bare points out that the voltage of an LED is directly related to the amount of energy in each photon—higher at shorter wavelengths of light. Thus infrared LEDs take the lowest voltage, and blue LEDs, the highest. The moral? Never connect LEDs in parallel—if there's even a slight difference in wavelength, the lower-wavelength LED will take all the current.

Thanks to everyone who wrote in!

### Writing to Q&A

As always, we welcome your questions. The most interesting ones are answered in print, usually within 9 months. Please be sure to include plenty of background information (we'll shorten your letter for publication). If you are asking about a circuit, please include a complete diagram. We regret that due to the volume of mail, we cannot give personal replies. **EN**



# The Four-Year Electronics Degree Program That Really Hits Home!

**Bring The Technology Home With A Bachelor Of Electronics Engineering Degree. No Hassles. No High Cost!**



*Now's the time to prepare for a profitable career.*

## **We've lowered the cost of higher education.**

It's true! You can earn a four-year Bachelor of Electronics Engineering Technology degree today ... and prepare yourself for a high-paying electronics career ... without quitting your job or ever leaving your home. Because World College, an affiliate of the Cleveland Institute of Electronics, offers you the total flexibility of independent study programs proven effective for people like you who truly want to succeed! World College independent study lessons help you build valuable skills

**Mail/Fax Today  
or Call  
1-800-696-7532**

step-by-step, and expert instructors are personally available to you with a toll-free call. What a way to earn an education!

## **A world of opportunity.**

Where is your career headed? With a four-year bachelor's degree from World College, you call the shots, choosing from incredible, high-paying opportunities in electronics, telecommunications, computer, electrical power, and many other growing fields.

World College gives you the skills, the knowledge, the power to take advantage of your best opportunity in electronics. And you can do it all at your own pace!

## **Without leaving home.**


World College continually works to provide its students with the most advanced education tools. From the latest equipment and reference books to breakthrough computer-simulated experiments, students are exposed to the latest technological advancements.

All the equipment, parts, and software you need are included in your affordable tuition, including more than 300 hands-on lab experiments you can complete in your home.
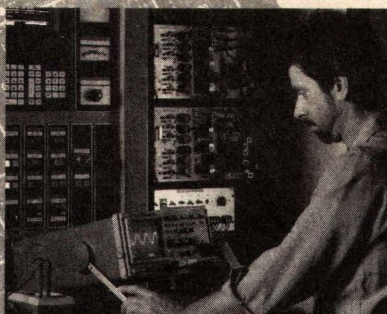
## **Choose your own pace.**

Earn your bachelor's degree on your time — and at your pace — because you pay tuition to World College only as you complete the upper-level semesters close to graduation. The faster you make it through, the less you pay. So you have an incentive to make your future happen quickly — yet the freedom to choose your own pace!

Send today for your FREE course catalog — and give yourself that future you've always wanted — with an electronics degree education from World College.



*Take charge of your future in electronics.*

## **Four Powerful Reasons To Connect With World College Today:**

- 1. Earn your four-year degree!**
- 2. Self-paced training!**
- 3. Independent study in your home!**
- 4. Expert instruction!**

## **Give Me The Power!**

Send me a FREE World College course catalog today!



(Please Print Neatly)

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State, Zip \_\_\_\_\_

Phone ( ) \_\_\_\_\_

Age \_\_\_\_\_

**For faster service, call  
1-800-696-7532,  
or call  
1-804-464-4600.**

**Or fax this coupon to  
1-804-464-3687.**



Lake Shores Plaza  
5193 Drive, Suite 113  
Virginia Beach, VA 23455-2500



Affiliated with  
Cleveland Institute of Electronics  
WAE38



# RETAILERS THAT SELL OUR MAGAZINE MONTHLY

## Alaska

Frigid North Co.  
1207 W. 36th Avenue  
Anchorage, AK 99503

## Arizona

Dalis Electronics  
2829 E. McDowell Road  
Phoenix, AZ 85008

## California

California Electronics  
221 N. Johnson Ave.  
El Cajon, CA 90202

Signal Electronics  
22307 Ocean Avenue  
Torrance, CA 90505

Ford Electronics  
8431 Commonwealth Avenue  
Buena Park, CA 90621

All Electronics  
14928 Oxnard Street  
Van Nuys, CA 91411

Gateway Electronics of CA  
9222 Chesapeake Drive  
San Diego, CA 92123

Mac's Electronics  
191 South "E" Street  
San Bernardino, CA 92401

Electronics Warehouse  
2691 Main Street  
Riverside, CA 92501

Orvac Electronics  
1645 E Orangethorpe Ave.  
Fullerton, CA 92631

Sav-On Electronics  
13225 Harbor Blvd.  
Garden Grove, CA 92643

Marvac Dow Electronics  
980 S. A Street  
Oxnard, CA 93030

Kandarian Electronics  
1101 19th Street  
Bakersfield, CA 93301

Whitcomm Electronics  
105 W. Dakota #106  
Clovis, CA 93612

Marvac Dow Electronics  
265-B Reservation Road  
Marina, CA 93933

Minuteman Electronics  
37111 Post St., Suite 1  
Fremont, CA 94536

HCS Electronics  
6819 S. Redwood Drive  
Cotati, CA 94931

Halted Specialties Co.  
3500 Ryder Street  
Santa Clara, CA 95051

Metro Electronics  
1831 J Street  
Sacramento, CA 95814

The Radio Place, Inc.  
5675-A Power Inn Road  
Sacramento, CA 95824

HSC Electronics  
4837 Amber Lane  
Sacramento, CA 95841

## Colorado

Gateway Electronics of CO  
2525 Federal Blvd.  
Denver, CO 80211

Centennial Electronics  
2324 E. Bijou  
Colorado Sps., CO 80909

## Connecticut

Signal Electronics Supply  
589 New Park Avenue  
W. Hartford, CT 06110

Cables & Connectors  
2198 Berlin Turnpike  
Newington, CT 06111

Electronic Service Prod.  
437 Washington Avenue  
North Haven, CT 06473

## Florida

Sanyca Electronics  
596 NW 99th Ct.  
Miami, FL 33172

## Georgia

Norman's Electronics, Inc.  
3653 Clairmont Road  
Chamblee, GA 30341

## Illinois

Tri State Elex  
200 W. Northwest Hwy.  
Mt. Prospect, IL 60056

## Maryland

Mark Elec. Supply Inc.  
5015 Herzel Place  
Beltsville, MD 20705

Amateur Radio Center  
1117 West 36th Street  
Baltimore, MD 21211

## Massachusetts

U-Do-It Electronics  
40 Franklin Street  
Needham, MA 02194

## Michigan

Purchase Radio Supply  
327 East Hoover Avenue  
Ann Arbor, MI 48104

Norwest Electronics  
33760 Plymouth Road  
Livonia, MI 48150

The Elec. Connection  
37387 Ford Road  
Westland, MI 48185

Elec. Parts Specialists  
711 Kelso Street  
Flint, MI 48506

## Minnesota

Acme Electronics  
224 Washington Avenue N.  
Minneapolis, MN 55401

## Missouri

Gateway Electronics Of MO  
8123-25 Page Blvd.  
St. Louis, MO 63130

William Elec & Ind Supply  
803 Davis Blvd.  
Sikeston, MO 63801

## New Jersey

Lashen Electronics Inc.  
21 Broadway  
Denville, NJ 07834

## New York

Sylvan Wellington Co.  
269 Canal Street  
New York, NY 10013

R&E Electronics  
4991 Rt. 209  
Accord, NY 12404

Unicorn Electronics  
Valley Plaza  
Johnson City, NY 13790

## Ohio

Philcap Electronic Suppliers  
275 E. Market Street  
Akron, OH 44308

## Oregon

Norvac Electronics  
7940 SW Nimbus Avenue  
Beaverton, OR 97005

## Pennsylvania

Business & Computer Bookstore  
213 N. Easton Road  
Willow Grove, PA 19090

## Texas

Mouser Electronics  
2401 Hwy. 287 N  
Mansfield, TX 76063

Electronic Parts Outlet  
17318 Highway 3  
Webster, TX 77598

## Washington


Amateur Radio Supply Co.  
5963 Corson Ave., Ste 140  
Seattle, WA 98108
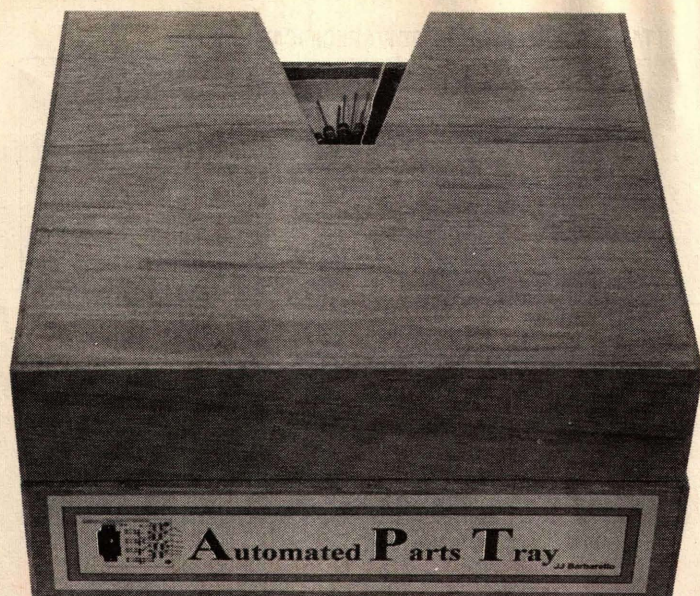
## Wyoming

Chris Supply  
2007 S. Douglas Hwy., Ste. C  
Gillette, WY 82716

If you'd like to sell our magazine in your store,  
please circle 210 on Free Information Card.





# BUILD THIS AUTOMATIC PARTS TRAY

*Learn how to use stepper motors, and build a great system that simplifies PC-board assembly in the process.*

JAMES J. BARBARELLO

**S**tepper motors are simultaneously exciting and intimidating for the hobbyist. There's something fascinating about a precision device with so many uses. That fascination dampens, however, when you consider the logistics of obtaining steppers, not to mention the hardware and software required to drive them. Wouldn't it be nice to see a complete project using parts obtainable in small quantities at low cost?

Well, this project does just that. Using a readily available 5-volt stepper motor and a handful of common parts, we'll create a computer-controlled device called the Automated Parts Tray (APT). Using a short and simple QBasic program, APT demonstrates the principles of optimizing PC-board assembly. APT uses a stepper-controlled rotating parts bin along with a graphical display of PC-board component locations to help ensure that the right parts are inserted in the right spots on the board in optimal order of assembly.

APT can handle boards up to  $6 \times 8$  inches. In addition, the project can be expanded easily to include closed-loop control. Further, it can even be used as the basis for a mini PC-board drilling system. (Those enhancements will be presented in future articles.) Best of all, you don't need a lot of money or special mechanical skills. All key parts are readily available from a single, well-established mail-order source, and parts cost about \$30.

**All about APT.** APT is a simplified adaptation of a semi-automatic electronics manufacturing system that has been in commercial use for years. The system is *semi*-automatic in that an operator must manually pick up and insert each part, but the actual part and its location are automatically determined and displayed.

In the commercial version, a series of trays are stacked vertically, like pies in a dessert display in a diner. Each tray contains several bins. The mechanism is such that all bins but one are covered. The cover can be visualized as a pie from which one slice has been removed. The area of the removed slice corresponds to the exposed bin. Each bin contains a specific part (a 10K resistor, a 2N2222 transistor, and so on).

The PC board being assembled mounts in a holder in front of the operator. To prepare for a part to be inserted, an X-Y table under the PC board moves a solid-state light source (a high-intensity LED or low-intensity laser) directly under a hole in the PC board where one lead of the part to be inserted will go. Then a parts tray rotates so the bin containing the correct part is exposed. The operator takes a part from the tray and inserts it into the position indicated by the lighted holes.

Our version contains one tray with twelve bins. However, the software can accommodate tray changes during parts insertion, thereby affording an unlimited number of bins. And instead of using a mechanically complicated X-Y table and solid-state light

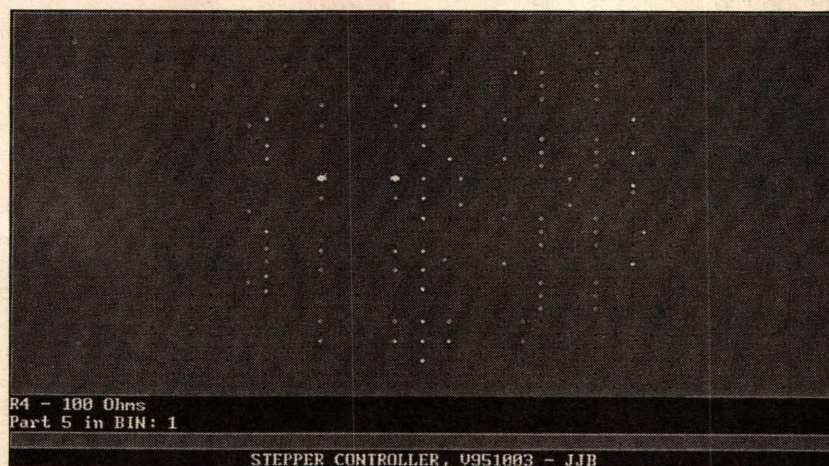


Fig. 1. The automated-parts-tray screen displays a grid overlaid with mounting holes for each component. The current component is highlighted.



source, our version displays a graphical replica of the PC board, all component holes, and a special representation of where the current part should be inserted. Figure 1 shows an example.

The mechanics of this project are quite simple, for two reasons. One is our use of an easily obtainable rotating "Lazy Susan" tray available anywhere kitchen products are sold. (We had good luck with a *Rubbermaid* brand tray.) Second is that we control tray movement using a direct-drive system, thereby eliminating the need for lead screws or gears. So let's get started.

**The Stepper and Drive Circuit.** The stepper motor is a two-phase, four-wire type. It consists of a permanent-magnet rotor and two field coils, as shown in Fig. 2. Table 1 lists the specifications for the selected motor. When the field coils are switched in the proper sequence, they attract the rotor, pull it to a precise position, and hold it there. By energizing coils A and B in the sequence shown in Table 2, the rotor will move precisely 7.5°, which amounts to 48 discrete steps through its rotation.

In Table 2, note that the four inner columns represent two things: The motor winding leads (A, A\*, B, B\*), and the PC parallel-port pin numbers that control those leads. Those numbers correspond to the pin numbers shown in the schematic (Fig. 3). Pin 2 represents the least-significant bit, and Pin 5 represents the most-significant bit. Column six of Table 2 shows the decimal value that should be written to the port to achieve the desired bit pattern for each step in the sequence.

As shown in Fig. 3, it doesn't take much in the way of electronics to drive a stepper. The circuit contains four identical functional blocks. The

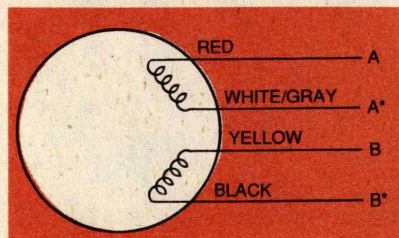


Fig. 2. A two-phase, four-wire stepper motor consists of a permanent-magnet rotor and two field coils.

TABLE 1—STEPPER MOTOR SPECIFICATIONS

| Item           | Description                                          |
|----------------|------------------------------------------------------|
| Motor          | Bipolar (2 phase) AIRPAX stepper motor (LB2773-M1)   |
| Size           | 2.25 (D) × 0.99 (H) inches                           |
| Weight         | 0.61 lb                                              |
| Electrical     | 5-volts DC, 800 mA, 6.25 ohms                        |
| Resolution     | 7.5 degrees/step                                     |
| Shaft          | 0.25 (D) × 0.75 (L) inches                           |
| Mounting Holes | Two 0.2-inch mounting holes, spaced 2.6-inches apart |
| Torque         | 100 g-cm (detent), 1080 g-cm (holding)               |

TABLE 2—MOTION CONTROL SEQUENCE

| STEP | A(5) | B*(4) | B(3) | A*(2) | Decimal |
|------|------|-------|------|-------|---------|
| 1    | 1    | 0     | 1    | 0     | 10      |
| 2    | 0    | 0     | 1    | 1     | 3       |
| 3    | 0    | 1     | 0    | 1     | 5       |
| 4    | 1    | 1     | 0    | 0     | 12      |

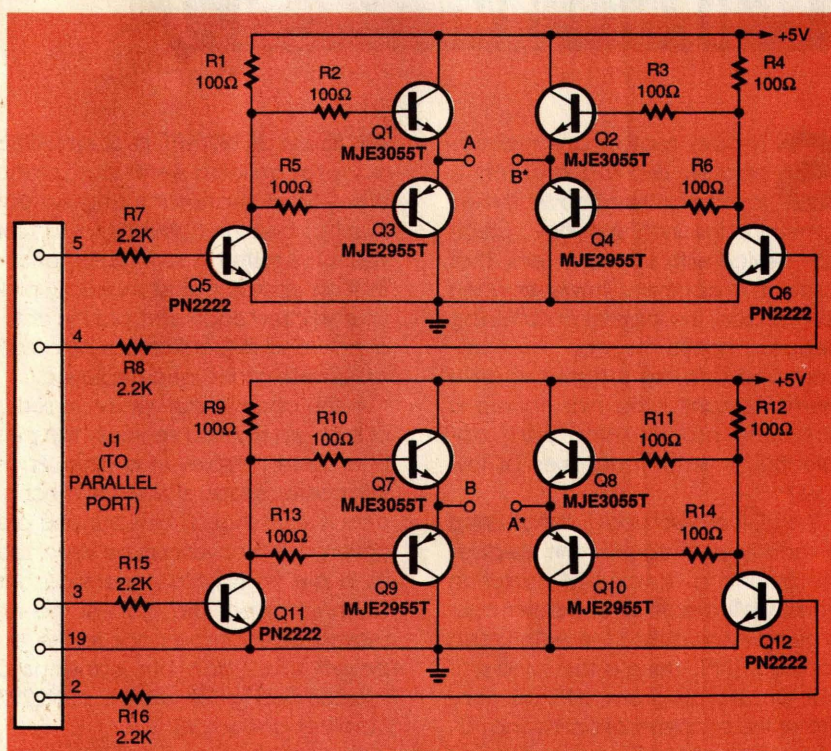


Fig. 3. The driver circuit allows a standard PC parallel port to alter the direction of current flow in both windings of the stepper motor according to the states of the four inputs.

purpose of each block is simply to provide a path from one end of a motor winding to either +5 volts or ground. By alternately switching the polarity of the voltage applied across the windings, we can cause motion to occur.

To see how that works, let's concentrate first on the block that controls the A lead. That block contains Q1, Q3, and Q5, along with the associated resistors. If pin 5 of J1 goes high, Q5 conducts, bringing its collector near ground. That in turn forward-biases

Q3, which brings its emitter near ground. Of course,  $V_{CE}$  of both Q5 and Q3 depends on the current being drawn by the load.

Now let's examine the block that controls the A\* lead, including Q8, Q10, and Q12, and the associated resistors. If pin 2 of J1 goes low, the collector of Q12 goes high. That in turn causes Q8 to conduct, and Q10 to remain off. So, with A low and A\* high, a current path has been established through Q8, coil A of the stepper motor, and Q3.




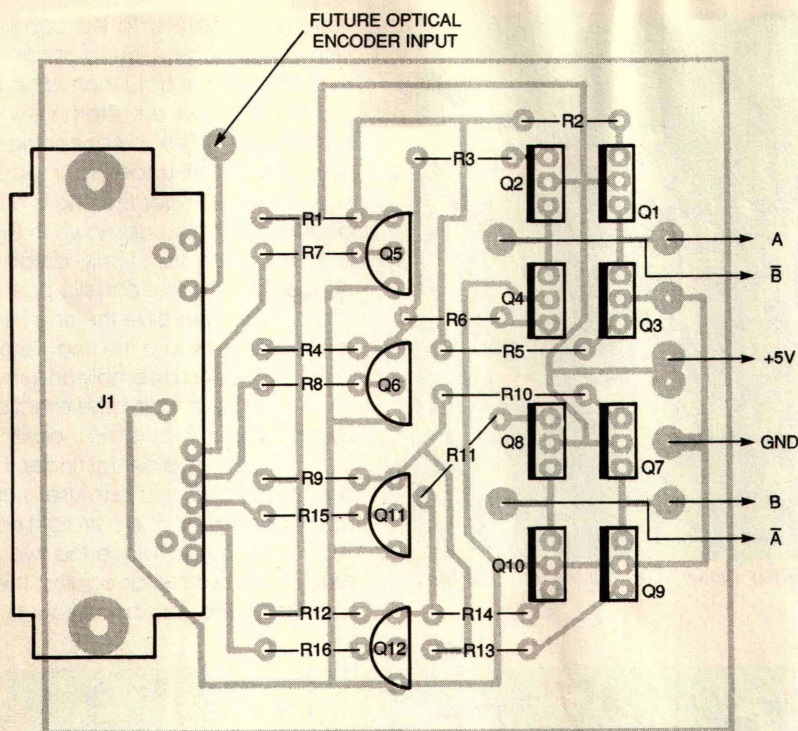


Fig. 4. Mount all components as shown here. A future installment will show how to use the optical encoder inputs.

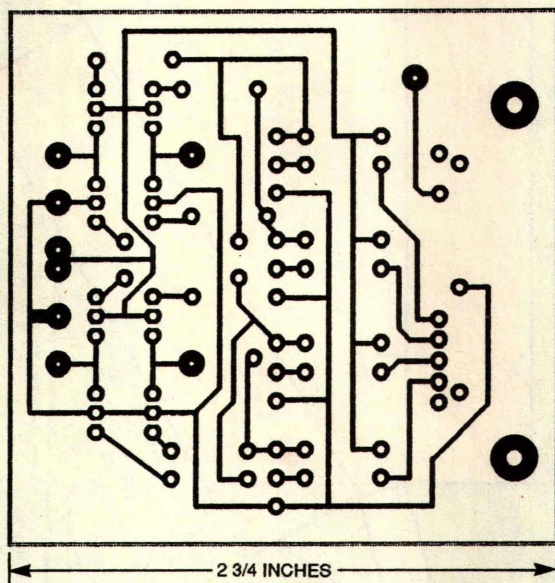

Use this foil-pattern when etching the PC board.

**Moving the Stepper.** By driving input pins 2-5 in the proper sequence, we can cause motion to occur. We've already seen the motion-control sequence in Table 2. The question now is how to deliver that sequence in a format acceptable to the motor. The code fragment in Listing 1 shows how. Note that we sequentially output the decimal values from column six of Table 2, with a delay of about 150 ms

after each. The delay is required to accommodate the mechanical inertia of the stepper motor. Without the delay, the control sequences would arrive from the PC so fast that the motor would simply sit there and chatter!

**Power Considerations.** Many stepper-motor control circuits use a current-limiting resistor to prevent exces-

#### LISTING 1— MOVING THE STEPPER

```
...
OUT 888, 10 : GOSUB DELAY
OUT 888, 3 : GOSUB DELAY
OUT 888, 5 : GOSUB DELAY
OUT 888, 12 : GOSUB DELAY
```

```
...
END
```

```
DELAY:
START! = TIMER
WHILE (TIMER-START!) < 0.15 : WEND
RETURN
```

sive current from causing the motor to overheat. In our circuit, the relatively large current demand of the motor causes a measurable voltage drop across the power-providing transistors (in the preceding example, Q3 and Q8). Each will have a  $V_{BE}$  drop approaching 1 volt. Therefore, the stepper motor coil sees a net of only about 3 volts. With a coil resistance of 6.25-ohms, the current provided is then  $3/6.25$ , or about 480 mA. That is well within the motor's dissipation capability, so no current-limiting resistor is required.

The tradeoff, of course, is that the motor provides less than maximum torque. That's acceptable in our application, but it might not be in others. You could increase torque by increasing the supply to six volts without modifying the circuit. You might be tempted to increase the supply to seven volts to offset the  $V_{BE}$  drops in the transistors and provide full power to the coils. That increase is not recommended, however, as you will exceed the motor's ability to dissipate heat, leading, naturally enough, to overheating.

We calculated current demand of each coil in this circuit configuration as about 400 mA. That implies that a 1-amp power supply should be sufficient. However, depending on the actual  $V_{BE}$  drops across the transistors, as well as variations in the motor coils, that value could increase to 1 amp or even more. To provide a margin of safety, we recommend use of a 1.5- or 2-amp power source.

There are many sources for new 5-volt, 1.5-2 amp power supplies. However, you can save a bundle by buying surplus. For example, some suppliers sell suitable power supplies for less than \$10. A potential draw-



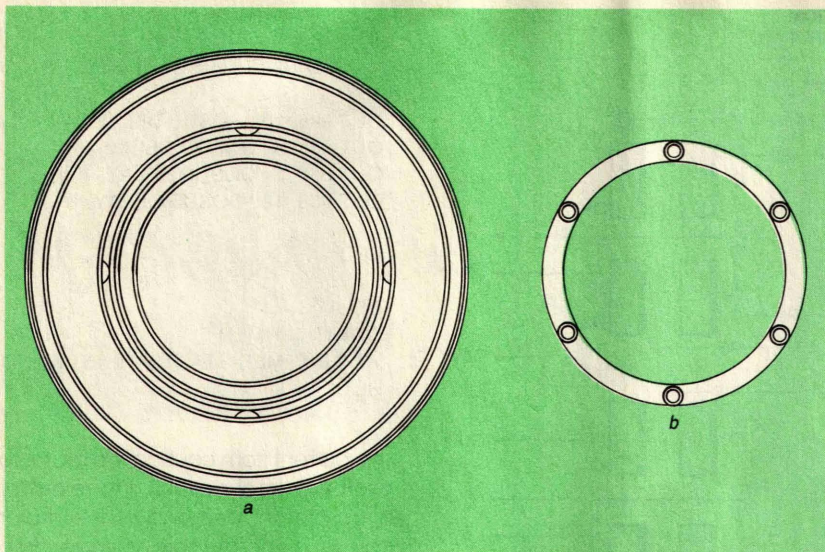


Fig. 5. The rotating tray—the complete assembly is shown in a, and the ball-bearing ring in b.

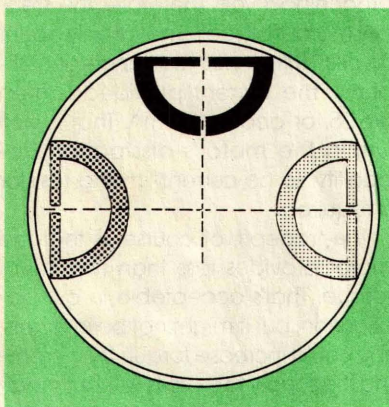


Fig. 6. Finding the center of the tray using a protractor and a straight edge; the point where the lines cross is the center of the circle.

back of that type of supply is that it may require a minimum load at all times. If that minimum isn't met, voltage may rise, for example, to about 5.3 volts. That presents no problem in our application.

**Construction.** Begin construction with the motor-control circuitry. A PC board layout accompanies this article; the parts-placement diagram appears in Fig. 4. Install the sixteen resistors first. Then install the eight TO-220 package transistors, ensuring both that you install the MJE3055s and MJE2955s in the right positions, and that they have the correct orientation. Next install the four TO-92 transistors (Q5, Q6, Q11, and Q12), again with the proper orientation. Now remove the connectors (if any) on the ends of the

various diameters; to be consistent with our prototype, try to obtain one that has about a 10-inch diameter. Figure 5-a shows a bottom view of a typical tray. It has a concentric ring that is press-fit under four equally spaced tabs. Under the ring is a ball-bearing assembly, as shown in Fig. 5-b. Holding the tray firmly, distort the concentric ring so it can slip past one of the tabs. Then slide the ring free of the tray and discard the ring. Remove the ball-bearing assembly and save it.

Now we have to find the exact center of the tray. That is most easily accomplished with a center finder. If you don't have one, you can use a clear plastic protractor and a straight edge. As shown in Fig. 6, place the two corners of the protractor against the inside lip of the tray and draw a line

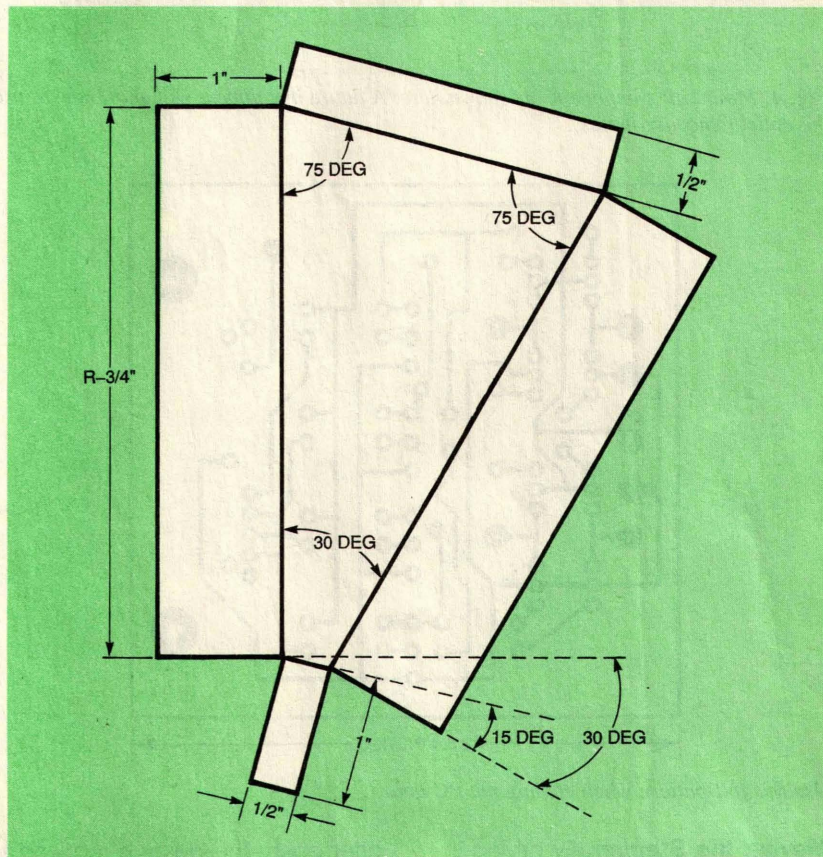


Fig. 7. Use this pattern to create the bins. The length of a side is given by the radius of the tray minus three-quarters of an inch. You'll need twelve of these.

stepper motor leads, and connect them to the appropriate points on the PC board. Attach the positive and negative power supply leads to the PC board.

Now let's look at the mechanics, starting with the tray. Trays come in

from the center marker on the straight portion of the protractor through the 90° indicator on the protractor's arc. Do the same thing at three or more locations on the tray. Where the lines cross is the exact center of the tray. (In geometric terms, each protractor



## PARTS LIST FOR THE AUTOMATIC PARTS TRAY

R1-R6, R9-R14—100-ohm, 1/4-watt resistor  
 R7, R8, R15, R16—2200-ohm, 1/4-watt resistor  
 Q1, Q2, Q7, Q8—MJE3055T NPN transistor, TO-220 case  
 Q3, Q4, Q9, Q10—MJE2955T PNP transistor, TO-220 case  
 Q5, Q6, Q11, Q12—PN2222 NPN transistor, TO-92 case  
 J1—DB-25 connector, female, PC-mount  
 5-volt DC, 6.25-ohm coil, bipolar stepper motor (Airpax LB82773-M1; JAMECO I17954 or equivalent); PC board; 5-volt/2-amp power supply (JAMECO I07326, I09276, or equivalent); 2.5-mm female power jack; 2.5-mm male power plug; Universal shaft coupler (JAMECO I06606 or equivalent) (2); Rubber coupler (JAMECO I06622 or equivalent); "Lazy Susan" tray (Rubbermaid or equivalent, 10-inch diameter); 1/4-20 × 1 1/2-inch machine bolt; 1/4-20 nut (2); 1 3/4 × 4-inch aluminum or plastic panel; #4 sheet metal screws (4); #6 or #8 sheet-metal screws (2); 24 × 36-inch piece of "Oaktag" or poster paper; 1/2-inch plywood; 1/4-inch Luan mahogany plywood; glue, nails, DB-25 extension cable, solder, wire, etc.

**Note:** The following are available from James J. Barbarello, 817 Tennent Road, Manalapan, NJ 07726: PC Board; APT-PC (\$12.00). Software including source and executable code for all software in the series, sample data files, and an enhanced version of the APT software (including the optical encoder application); APT-S (\$12.00). All prices include shipping. International orders add \$5.00 (U.S. funds only). NJ residents must add appropriate sales tax. The author will accept phone calls 6-8:00 PM EST., Monday through Friday **ONLY** (908-536-5499). The author will gladly answer written questions if accompanied by a self-addressed stamped envelope.

edge is a chord, and the line you draw is a perpendicular bisector of that cord. Perpendicular chord bisectors are, by definition, along a radius, and therefore cross the circle's center).

Drill a 1/4-inch diameter hole in the

## LISTING 2—STEPPER CONTROL PROGRAM

```

REM** STEPPERS.BAS (c) 1995, JJ Barbarello
REM** V951007
CLS : DEF SEG = 64: DEFINT A: add = 888
DIM a(4): a(1) = 5: a(2) = 3: a(3) = 10: a(4) = 12
abinold = 1: ainit = 12: OUT add, ainit
COLOR 15, 1: LOCATE 2, 1: PRINT SPACE$(79)
LOCATE 2, 26: PRINT "APT STEPPER CONTROLLER TESTER"
COLOR 7, 0: LOCATE 10, 20: PRINT "Position Tray At Bin 1, then press Enter"
waitforenter:
a$ = INPUT$(1)
IF a$ <> CHR$(13) THEN SOUND 800, 1: SOUND 500, 1: GOTO waitforenter
LOCATE 10, 20: PRINT SPACE$(40)
loop01:
LOCATE 10, 27: PRINT "TRAY CURRENTLY AT BIN:"; abinold
LOCATE 20, 10: PRINT SPACE$(60)
LOCATE 20, 23: LINE INPUT "Which Bin (1-12, Enter to end)... "; abin$
IF LEN(abin$) = 0 THEN END
abin = VAL(abin$): IF abin < 1 OR abin > 12 THEN BEEP: GOTO loop01
abin2 = abin: IF abin2 < abinold THEN abin2 = abin2 + 12
asteps = abin2 - abinold
SELECT CASE asteps
CASE 1 TO 6
lo = 1: hi = 4: steps = 1
CASE IS > 6
lo = 4: hi = 1: steps = -1: asteps = 12 - asteps
CASE IS < 0
lo = 4: hi = 1: steps = -1: asteps = -asteps
END SELECT
OUT add, ainit
bin = abinold
FOR i = 1 TO asteps
FOR j = lo TO hi STEP steps
OUT add, a(j)
IF i > 1 AND i < asteps THEN delay = .075 ELSE delay = .125
start! = TIMER
WHILE (TIMER - start!) < delay: WEND
NEXT j
bin = bin + steps
SELECT CASE bin
CASE IS = 0
bin = 12
CASE IS = 13
bin = 1
CASE ELSE
END SELECT
LOCATE 10, 27: PRINT "TRAY CURRENTLY AT BIN:"; bin; SPACE$(2)
SOUND 625, 1
NEXT i
IF steps = -1 THEN
OUT add, a(lo)
ainit = a(lo)
ELSE
ainit = a(hi)
END IF
start! = TIMER
WHILE (TIMER - start!) < 1: WEND
OUT add, 0
abinold = abin
GOTO loop01
END
  
```

center of the tray. Obtain a 1/4-20 machine screw at least 1 1/2-inch long, and two 1/4-20 machine nuts. Thread

one nut on the screw and insert the screw into the drilled hole from the top of the tray. Now thread the other



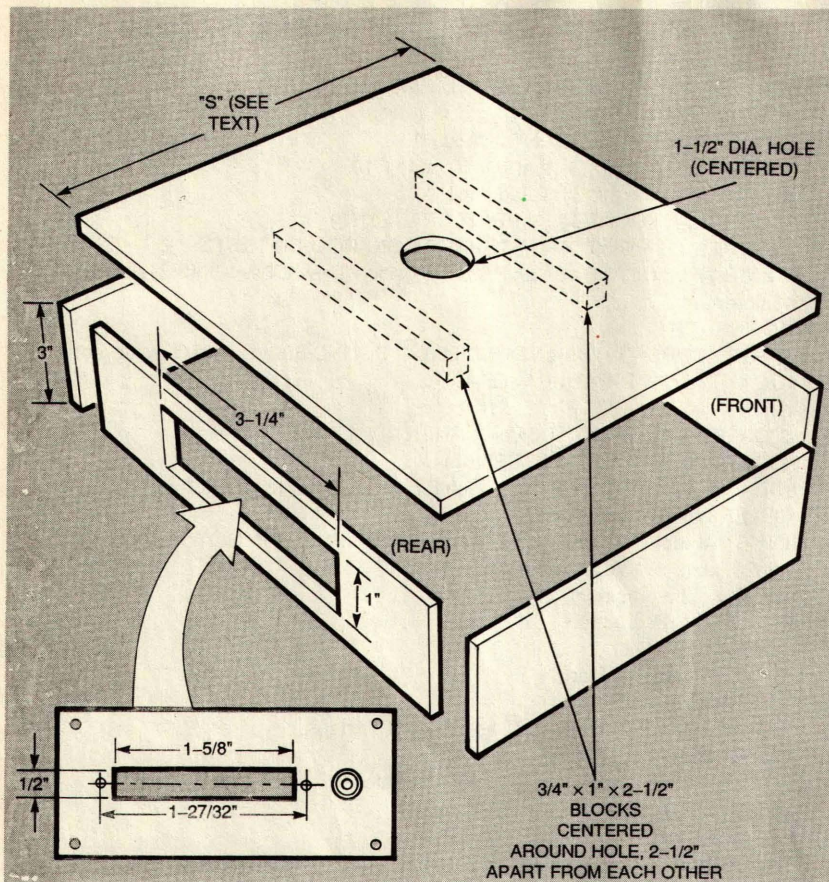


Fig. 8. One-half inch plywood serves well in building the case. The blocks on the underside hold the stepper motor, and the slot in the rear panel is for a mounting plate that connects power and the parallel port.

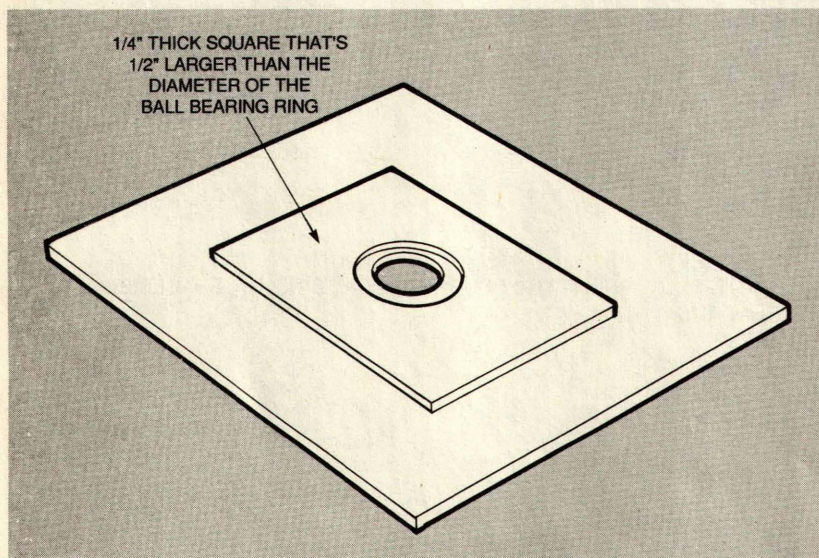


Fig. 9. The spacer provides clearance for the shaft-coupling mechanism.

nut onto the screw, locking it in place. Do not tighten the nuts at this point, as the protruding length of the screw will be adjusted later.

The next task is to make the twelve bins. Figure 7 shows a pattern for one

bin. Note that all dimensions are constants, except the length, which is defined as  $R - \frac{3}{4}$ -inch. Measure the inside diameter of the tray and divide by two to obtain the radius. For example, the author's prototype used a

10½-inch diameter tray, and  $10\frac{1}{2} \div 2 - \frac{3}{4} = 4.5$ -inches. You can make the bins from thin aluminum, wood, plastic, or other materials. An effective alternative is poster paper (commonly called "Oaktag" paper). It's easy to work with, has the thickness of about five normal sheets of paper, and is stiff enough to hold the required bends.

Using the length calculated for your tray, cut twelve blanks. Fold the four flaps upward, being careful to fold them straight and along the lines indicated on the pattern. Secure the tabs with transparent tape. When all twelve bins are complete, arrange them in a circle and secure them to one another where they meet with additional transparent tape. With careful assembly, the bins should fit snugly into the tray. However, an exact fit isn't necessary. The requirement is for twelve approximately equal bins in an assembly that won't rotate inside the inner lip of the tray.

**Building the Case.** Now we're ready to build the case. We used ½-inch plywood for our prototype. Form a square box with a closed top and an open bottom, as shown in Fig. 8. Side dimension S should be ½-inch larger than the outside diameter of the tray, plus twice the thickness of the material you're using for the case top cover. For example, with our 10½-inch tray and ½-inch plywood for the cover,  $S = 10.5 + 0.5 + 2 \times 0.5 = 12$  inches.

A good material for the box top is ¼-inch luan mahogany plywood. Draw a line through diagonal corners and mark the point where the lines cross. Draw a line through the center perpendicular to the sides. Draw two parallel lines on either side of that one, each ¼-inch from the first line. You should end up with two lines straddling the centerline of the top, and 2½-inches from each other.

Drill or otherwise form a 1½-inch hole at the center of the top. The actual diameter or shape is not critical, as long as the opening is at least 1 inch in diameter. Now prepare two  $\frac{3}{4} \times 1 \times 2\frac{1}{2}$ -inch blocks. Attach the two blocks to the underside of the top and along the two parallel lines drawn previously. Screw or glue the blocks in place.

Measure the diameter of the ball-bearing assembly (BBA) shown in Fig. 5-b. Add ½-inch to that amount, and



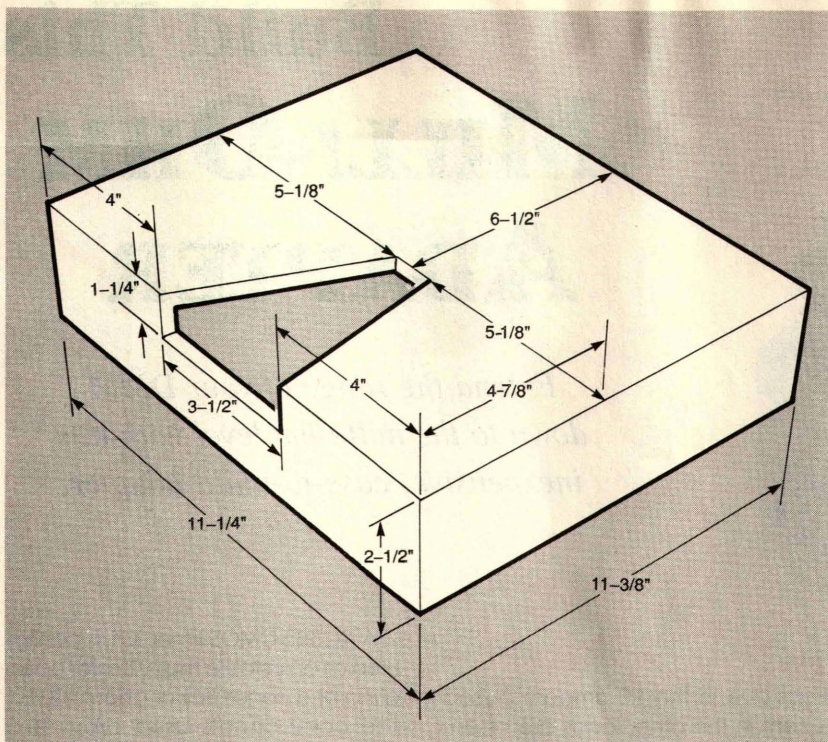


Fig. 10. The top cover is the same size as the base, and has a wedge-shaped cutout to allow access to the current bin.

call it L. Cut a piece of  $\frac{1}{4}$ -inch material into a square, with sides of length L, to form a spacer. Form a  $\frac{1}{2}$ -inch opening similar to that formed in the top and secure the spacer to the top of the case. Align the BBA to the spacer so it is concentric with the center hole, as shown in Fig. 9. After that's done, staple or otherwise attach the BBA to the spacer.

Create a centered rectangular opening  $1 \times 3\frac{1}{2}$  inches in the rear side as shown. Then make a cover of plastic or metal and mount J1 to the cover. Also mount a power connector, and attach the cover to the rear panel with #4 sheet metal screws.

Using the value of S calculated earlier, build a cover, as shown in Fig. 10. The height should be  $2\frac{1}{2}$  inches. Do not drill a center hole; instead, form a wedge-shaped cutout as shown in Fig. 10. Using a 30-60 triangle, draw two lines from the center to one end, forming a pie shaped wedge. Fatten the wedge by drawing lines parallel to the first two lines, but  $\frac{1}{4}$ -inch farther out. Extend the two lines down the front side and then connect them, forming a rectangle. Then, to trim the sharp edge of the wedge, draw a line  $\frac{3}{4}$ -inch from the center. Cut out the wedge.

**Final Assembly and Checkout.** To finish up we need to mount the stepper motor and connect its shaft to the  $\frac{1}{4}$ -20 bolt with a flexible coupling. Start by centering the tray on the case bottom. Hold it in place temporarily with masking tape. Position the motor against the blocks with the shaft of the motor facing the bolt. If the motor has a gear attached, remove and discard it. Adjust the bolt's depth as necessary so it and the shaft almost touch. Position the motor so the bolt and shaft are concentric, and mark the position of the two mounting holes. Attach the motor to the blocks with #6 or larger sheet-metal screws. Remove the masking tape.

Attach one shaft coupler to the motor shaft, and another to the bolt. Place a rubber coupler in one of the shaft couplers, and loosen the nuts holding the bolt. Mate the two couplers. Adjust the bolt depth so the tray floats  $\frac{1}{16}$  to  $\frac{1}{8}$ -inch above the BBA. The object is to minimize drag, but allow the bearings to come into use if the tray tips slightly from uneven weight distribution. Tighten the nuts to secure the bolt.

Attach the power connector and the DB-25 connector to the parallel port of your PC using an appropriate

cable. Mark the front flap of one of the bins as "1," and place numbered slips of paper in each bin, beginning with bin 1 and going counter-clockwise. Place the bin assembly in the tray so bin 1 is accessible through the wedge cutout in the top.

Type the test program shown in Listing 2 into QBASIC. Center bin 1 in the opening and run the program. As you select different bins, the tray should rotate to show the appropriate bin through the opening.

That's it for this installment. Next time, we'll present the general-purpose APT program, show how to create the ASC-II data file for a PC board, and use the program to populate the stepper controller's own PC board. We'll also show how to add an optical encoder that can provide position feedback for the stepper motor.  $\Omega$

## ANTIQUE RADIO CLASSIFIED Free Sample!


Antique Radio's  
Largest Circulation Monthly.  
Articles, Ads & Classifieds.



6-Month Trial: \$18.95. 1-Yr: \$36.95 (\$53.95-1st Class).  
A.R.C., P.O. Box 802-L17, Carlisle, MA 01741  
Phone: (508) 371-0512 VISA/MC Fax: (508) 371-7129

## Get your copy of the CRYSTAL SET HANDBOOK

THE CRYSTAL SET  
HANDBOOK

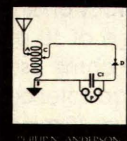

Go back to antiquity and build the radios that your grandfather built. Build the "Quaker Oats" type rig, wind coils that work and make it look like the 1920's! Only \$10.95 plus \$4.00 for shipping and handling. Clagg Inc., P.O. Box 4099, Farmingdale, NY 11735. USA Funds ONLY! USA and Canada—no foreign orders. Allow 6-8 weeks for delivery. MA01

## THE COLLECTED WORKS OF MOHAMMED ULLYES FIPS

#166—By Hugo Gernsback.

Here is a collection of 21 April Fools Articles, reprinted from the pages of the magazines they appeared in, as a 74-page,  $8\frac{1}{2} \times 11$ -inch book. The stories were written between 1933 and 1964. Some of the devices actually exist today. Others are just around the corner. All are fun and almost possible. Stories include the Cordless Radio Iron, The Visi-Talkie, Electronic Razor, 30-Day LP Record, Teleglasses and even Electronic Brain Servicing. Get your copy today. Ask for book #166 and include \$16.00 (includes shipping and handling) in the US and Canada, and order from CLAGG Inc., P.O. Box 4099, Farmingdale, NY 11735-0793. Payment in US funds by US bank check or International Money Order. Allow 6-8 weeks for delivery. MA05





# Build This MILLI-OHM ADAPTER

*Extend the range of your DMM down to the milliohm level with this inexpensive, easy-to-build adapter.*

SKIP CAMPISI

**H**ave you ever tried to measure accurately a low-value resistance, only to find that your test leads had a higher resistance than the device you were measuring? Even with a meter capable of *nulling out* the lead resistance, the null is never stable due to the hooks or clips used for the connections.

The Milliohm Adapter was specially designed to get around that problem and to do it with an accuracy of  $\pm 1\%$  for readings over a range of 10 milliohms (0.01 ohms) to 5.0 ohms. Used with a 4½-digit DVM, the adapter can resolve resistances as low as 10 micro-ohms, and be able to measure the resistance of a short length of hookup wire! Checking switch-contact resistance is a breeze with the adapter plugged into your DVM.

When measuring a resistance below 1.0 ohm, the leads of a resistor contribute significant error to the reading. Thus, a novel circuit approach was taken in designing the adapter. To generate an output-signal voltage high enough to be measured easily, a current of about 1.0 ampere is desirable. That current could easily fry some circuit components and damage the unit under test. However, by applying a low duty-cycle, 1.0-ampere pulse, no damage will occur. By using Kelvin voltage sensing probes right at the connections to the resistance, all of the other voltage

drops due to the 1.0-ampere pulsed current in the other leads are essentially eliminated.

**About the Circuit.** The schematic diagram (Fig. 1) for the adapter can be partitioned into four sections: power supply, oscillator, current source, and peak detector. The  $R_x$  (resistance to be measured) is connected between BP1 and BP2, and with the 1.0-ampere pulse applied to  $R_x$ , the resulting output transfer function appearing at J1 is 1.0 ohms-per-volt output to the DVM.

The power supply consists of IC2, a 78L12 voltage-regulator chip that provides regulated +12 volts to the circuit, and a 2N2222 transistor, Q2, which provides -0.7 volts to IC3 and a virtual power ground to the rest of the circuit. Transistor Q2 is used as a diode-connected transistor; that type produces only half of the ripple voltage that would appear if a standard rectifier were used. Battery B1 is user selectable and, although 18 volts is specified in the schematic diagram, it also can be any voltage source from 15-volts DC to 25-volts DC. For example, two series-connected 9-volt batteries will power the adapter quite nicely. Further, note that the prototype shown in the photos does away with B1 entirely; it uses a 117-volt AC power-pack adapter rated at 17.4-volts DC at 50 mA plugged into a jack on the instrument. Power switch S2 was not used on the prototype.

A TLC555 CMOS timer, IC1, is configured as an astable multivibrator operating at a frequency of about 100 Hz. The components used provide a duty-cycle of 99%; thus, a negative-going pulse of about 100  $\mu$ s results at the output, which in turn gates (switches) the current source on for 100  $\mu$ s at a duty-cycle of 1%. The resulting average current is 10 mA—safe for almost all circuits and circuit elements.

Light-emitting diodes LED1 and LED2 are standard red LEDs that have a forward voltage of about 1.75 volts each, and they are used as the voltage-reference diodes. As Q1 (a TIP125) has a forward voltage of about 1.5 volts, about 2.0 volts appears across R2 and R3, whose net resistance is 2.0 ohms; thus, a current pulse of 1.0 ampere is generated at Q1's collector. The current pulse is supplied via a capacitive-discharge type set-up, from C1 (100  $\mu$ F), which is recharged via R1 (33 ohms) during the 99% off state.

Adequate compensation for any temperature drift by Q1's two base-emitter junctions are provided by LED1 and LED2, and calibration is provided via CAL potentiometer R4, which adjusts the LEDs' forward voltage by varying the bias current. The prototype adapter uses a one-turn potentiometer for R4; you might wish to use a multi-turn trimmer instead. Also, you can trim fixed resistors R2 and R3 to adjust into R4's calibration range.

The TLC272 CMOS dual op-amp, IC3, is configured as a positive voltage-peak detector, which converts





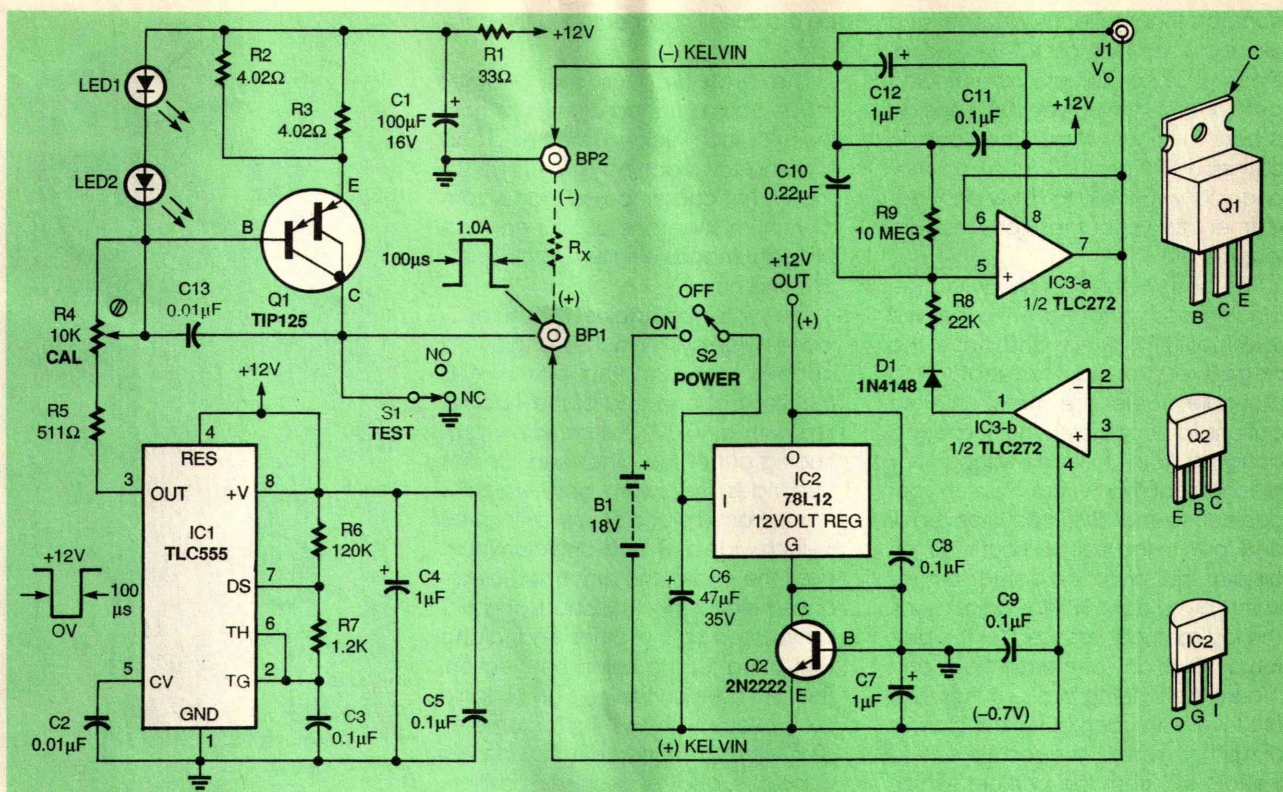


Fig. 1. Here's the schematic diagram for the Milliohm Adapter. The circuit can be separated into four sections: power supply, oscillator, current source, and peak detector.

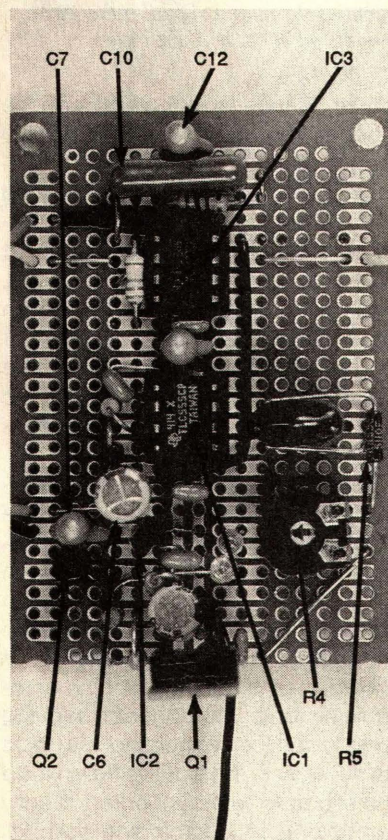

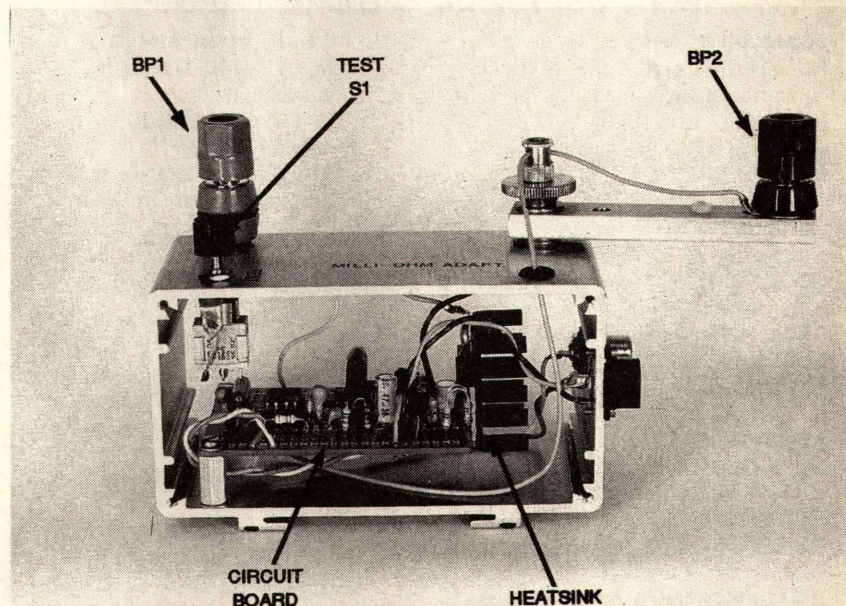A piece of a PC board that matches a solderless board supports most of the circuit's parts. Layout is not critical; however neatness is important.



A view of the Milliohm Adapter before the side covers are installed. Note that the heat sink has been attached to the Darlington transistor Q1 and stands free of any metallic contact.

the 1% duty-cycle voltage pulse generated across "R<sub>x</sub>" to a steady DC voltage having the exact magnitude of the pulse's peak voltage value. Thus, the output at J1 is a DC voltage with the transfer function of 1.0-ohm-per-volt across R<sub>x</sub>.

**Construction.** The only critical sections of the adapter are the binding-post connections to the resistance to be measured. Use a pair of jumbo (5-way) binding posts rated for 15 amps or more; the posts specified in the Parts List have large-area gold-plated




contacts that make the physical and electrical securing of "R<sub>x</sub>" very good. Once you have selected the binding posts, the next thing you must decide is how to mount them. The spacing between BP1 and BP2 must be mechanically variable to allow easy adjustment for various resistor sizes, wire lengths, etc.

The best method for mounting the binding posts is to leave the positive terminal (BP1) fixed, and have the negative ground terminal (BP2) movable. There are three different options to accomplish this: leave BP2 dangling from its leads without any mechanical mount; cut a slot in your cabinet so that BP2 can slide back and forth in the slot; or mount BP2 on an arm that pivots on a stud, thus rotating away from BP1 for adjustment. The last method was used for the prototype. Pick any of the methods and mount the binding posts so that they are level with each other, using shims or washers where needed. Be sure to insulate BP1 from the cabinet (which has to be aluminum), while BP2 should

be electrically connected to the cabinet.

The prototype uses a cabinet made from extruded aluminum having a 3/32-inch thick wall for drilling and tapping for machine-screw attachments. For chassis boxes made from aluminum sheet metal, you can use ordinary machine screws, lock washers, and nuts.

The prototype cabinet measures 2-inches wide by 4 3/8-inches long by 2 3/8-inches high. Binding post BP1 is mounted at one end of the cabinet top, with a 10-32 x 1-inch screw protruding out of the other end. On this stud rides the swing arm, which is made from a piece of 1/4-inch thick by 5/8-inch wide by 3-inch long aluminum bar. One end of the arm has a clearance hole for the 10-32 stud, and BP2 is mounted at the other end, along with a lug for the Kelvin connection. The arm rides on washers and is locked in place with a 3/4-inch diameter, 10-32-thread knurled nut (a wing nut works fine, also). At its closest position, the binding post terminal spacing is

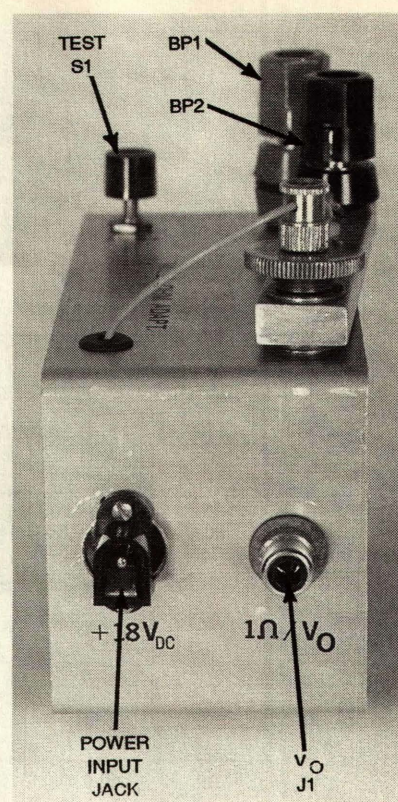

The power input jack (optional, see text) and insulated RCA phono jack (J1) that supplies the output signal to the DVM mounts on one side of the case

## PARTS LIST FOR THE MILLIOHM ADAPTER

### SEMICONDUCTORS

IC1—TLC555 or TLC555CN CMOS timer integrated circuit.  
IC2—78L12 12-volt, 100-mA, positive-regulator integrated circuit  
IC3—TLC272/TS272CN CMOS dual op-amp, integrated circuit  
Q1—TIP125 PNP Darlington transistor  
Q2—2N2222 PNP general-purpose transistor  
DI—1N4148 switching diode  
LED1, LED2—Light-emitting diode, red, T1 case

### RESISTORS

(All fixed resistors are 1/4-watt, 5% units, unless otherwise noted.)  
R1—33-ohm  
R2, R3, R<sub>C</sub>—4.02-ohm, 1%, metal film  
R4—10,000-ohm, one-turn potentiometer, PC mount, cermet (see text)  
R5—511-ohm, 1/4-watt, 1%, metal-film  
R6—120,000-ohm  
R7—1200-ohm  
R8—22,000-ohm  
R9—10,000,000-ohm

### CAPACITORS

C1—100-μF, 16-WVDC, electrolytic  
C2, C13—0.01-μF, monolithic ceramic  
C3—0.1-μF, polyester (Mylar)  
C4, C7, C12—1-μF, 35-WVDC, solid tantalum  
C5, C8, C9, C11—0.1-μF, monolithic ceramic  
C6—47-μF, 35-WVDC, electrolytic  
C10—0.22-μF, polyester (Mylar)

### ADDITIONAL PARTS AND MATERIALS

B1—See text  
BP1, BP2—Binding post, insulated, 30 ampere (H.H. Smith #257)  
J1—RCA phono jack, isolated (Mouser#16PJ050, or equiv.)  
S1—Mini-push-button, spdt, momentary, 3 A  
S2—Mini-toggle switch, spdt, 1-amp (optional)  
Prototyping board (RadioShack 276-150, or equiv.), 8-pin IC socket (2), TO-220 heat sink, post spacers (2, threaded holes at ends with matching screws), threaded ends with screws to match, aluminum cabinet (see text), aluminum bar (see text), wire, phono plug, DVM plug, etc.

**Note:** The semiconductors and precision resistors are available from Mouser Electronics and other sources. All other parts are available at most local electronics stores and electronics mail-order houses.

about 3/4 inch apart, which can be opened to a maximum of about 5 1/2 inches. Output jack J1 and an optional power-input jack are mounted on one end of the cabinet with normally-closed push-button switch S1 (TEST) mounted on the top, near BP1. Jack J1 has to be isolated from ground. Use fiber shoulder washers or an insulated phono jack made for the purpose. If you use POWER switch S2, mount it near S1 for the most convenience.

Assemble the circuit board, following the parts location shown in the photos, on a 1 7/8-inch by 2 7/8-inch circuit board (see Parts List) starting with Q1 on one end of the board. Attach a small heat sink to Q1. Install two 8-pin DIP sockets and potentiometer R4 as shown; then add the rest of the components and interconnects leaving long leads for connecting the jacks and switches. The positive Kelvin lead is a separate wire connected directly from pin 3 of IC3 to binding-post BP1, and the collector tab of Q1 is also connected directly to BP1 via a separate wire.

(Continued on page 79)



Get picture-perfect results every time with this easy-to-build, easy-to-use darkroom aid.

# BUILD A ZONAL ENLARGING METER

MICHAEL A. COVINGTON

**M**ost enlarging exposure meters tell you how many seconds to expose print paper. The Zonal Enlarging Meter described here does not! Instead, it tells you how light or dark each area of the picture will turn out, based on a selected standard exposure time for your enlarger.

When in the photo darkroom, you position the Zonal Enlarging Meter with one hand and adjust the lens

opening of the enlarger with the other hand. The exposure setting technique using the Zonal Enlarging Meter is much faster than twisting the dials on a conventional enlarging meter and it assists in obtaining a correctly exposed enlargement that fits all the brightness zones of the negative into the response range of print paper, from stark white to jet black. Ordinary enlarging meters measure only one zone which is usually a high-

light or skin tone, and just guess where the other zones will fall. The Zonal Enlarging Meter lets you measure any area of the enlarger's project image on the paper surface and adjust the lens opening until that area is as light or as dark as you want it to be.

**How it Works.** The heart of the Zonal Enlarging Meter circuit (Fig. 1) is a National Semiconductor LM3915 LED bargraph driver IC, which lights any-

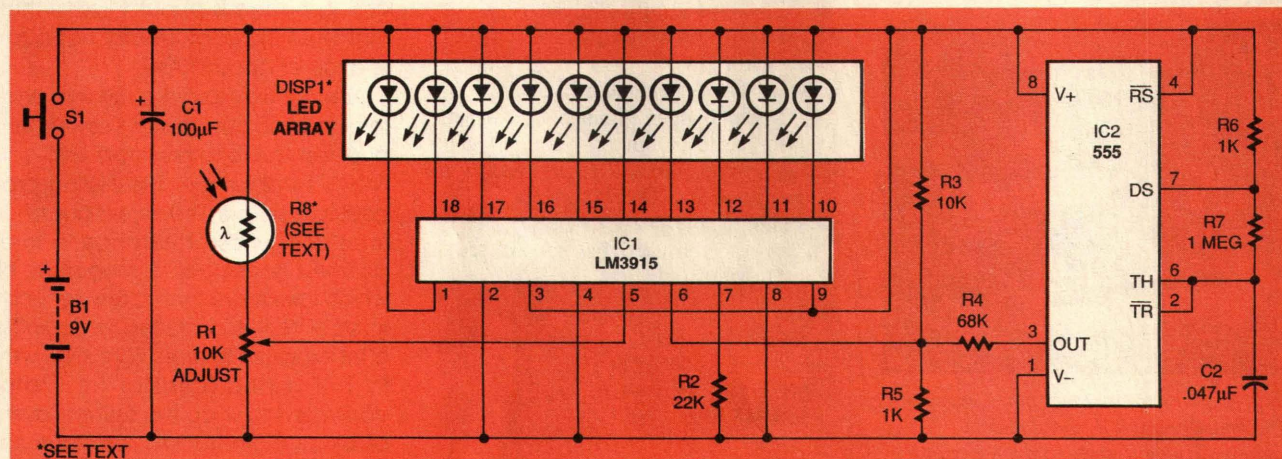


Fig. 1. Here's the schematic diagram for the Zonal Enlarging Meter. Light falling on photoresistor R8 causes LEDs in the bar-graph display DISP1 to illuminate. The number of LEDs that come on is logarithmically proportional to the light intensity.



where from 0 to 10 LEDs depending on the ratio of the input voltage on pin 5 to the reference voltage on pin 6.

The trigger voltages for the LEDs in bar-graph display (DISP1) are arranged along a logarithmic scale, just like photographic exposures, and the total voltage range is 10 to 1. Because of some nonlinearity in the photoresistor's response to light-intensity change, the range of light levels that the meter actually covers is more like 30 to 1, which is ideal because it slightly exceeds the density range of a properly exposed negative.

Each LED in DISP1's bargraph display has three states, off, flashing, and fully on; that feature lets you read a total of 20 steps rather than just 10. The flashing effect is produced by the 555 oscillator (IC2), which makes the reference voltage at pin 6 of IC1 fluctuate

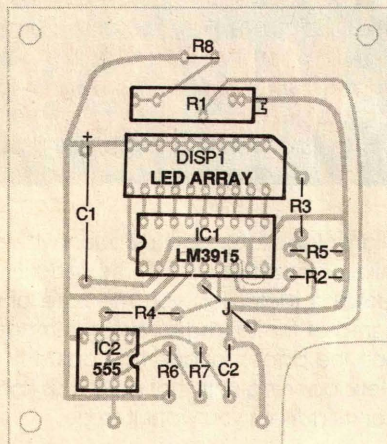


Fig. 2. Parts location diagram shows that the PC board is uncluttered and easy to assemble. Mounting holes align with the screws used to close the plastic case.


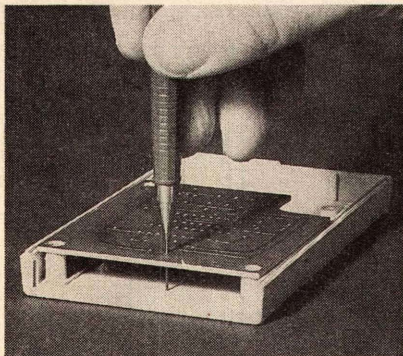


Fig. 3. Prior to inserting parts onto the PC board, extend the lead of an automatic pencil through the holes in the board to locate openings in the case cover for the LED bar-graph display DISP1 and photoresistor R8.

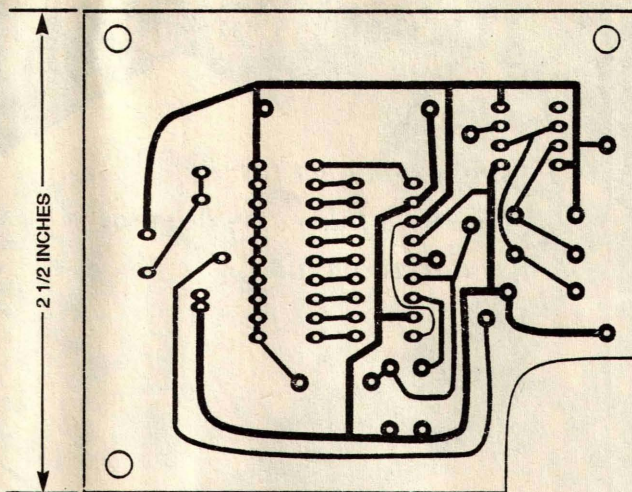

Same-size foil-pattern diagram for the meter's PC board. Carefully drill holes so that integrated-circuit chips and display chip mount quickly.

## PARTS LIST FOR THE ZONAL ENLARGING METER

### SEMICONDUCTORS

DISP1—10-LED bar-graph display, red (Mouser 351-2402 or equiv.)  
IC1—LM3915 LED logarithmic-bargraph driver integrated circuit (National Semiconductor)  
IC2—555 timer-oscillator integrated circuit

### RESISTORS

(All fixed resistors are 1/8-watt, 5% units.)

R1—10,000-ohm, 10-turn, 3/4- to 1-inch long, trimmer potentiometer  
R2—22,000-ohm  
R3—10,000-ohm  
R4—68,000-ohm  
R5, R6—1,000-ohm  
R7—1-megohm  
R8—Cadmium sulfide photoresistor (see text and note below).

### ADDITIONAL PARTS AND MATERIALS

B1—9-volt transistor-radio battery  
C1—100-μF, 16-WVDC, electrolytic capacitor  
C2—0.047-μF, ceramic capacitor  
S1—Normally-open, momentary-contact, push-button switch  
Plastic-case enclosure (includes battery connector; Pac-Tec HML-9VB, RadioShack 270-211, or equiv.), PC circuit-board material as needed (see text), wire, solder, etc.

**NOTE:** A suitable photoresistor, type 76C59, is available from Mouser Electronics, 2401 Highway 287 North, Mansfield, TX 76063, phone 800-346-6873.


feature by omitting IC2, R4, R6, R7, and C2.

**Choosing a Photoresistor.** The choice of cadmium sulfide photoresistor (R8) used in the meter depends on what is available and what kind of paper and exposure time you like to use. You'll need one whose resistance is somewhere between 50K and 500K at the light level corresponding to a mid-gray tone in a picture printed on your paper with your exposure time.

One commercially available photoresistor that works well is the type 76C59 available from Mouser Electronics (see the Parts List). It's rated for a resistance of 20K to 50K ohms at a light intensity of 10 lux (1 foot-candle), and 20 megohms in total darkness. The light level for a mid-gray tone in a 5-second exposure on most fast enlarging papers is about 1 lux; at that light level, this photoresistor has a resistance of about 300K.

Another way to get a suitable photoresistor is to buy a surplus assortment and test the photoresistors until you find a suitable one. The testing procedure is simple. First, reject any photoresistors whose resistance in total darkness is less than 2 megohms, or which take more than a few seconds to stabilize when placed in darkness after exposure to room light. One way to put a photoresistor into total darkness is to wrap it in several layers of black cloth, plastic, or electrical tape. Avoid aluminum foil; it reflects light and tends to develop cracks that will throw your readings awry.




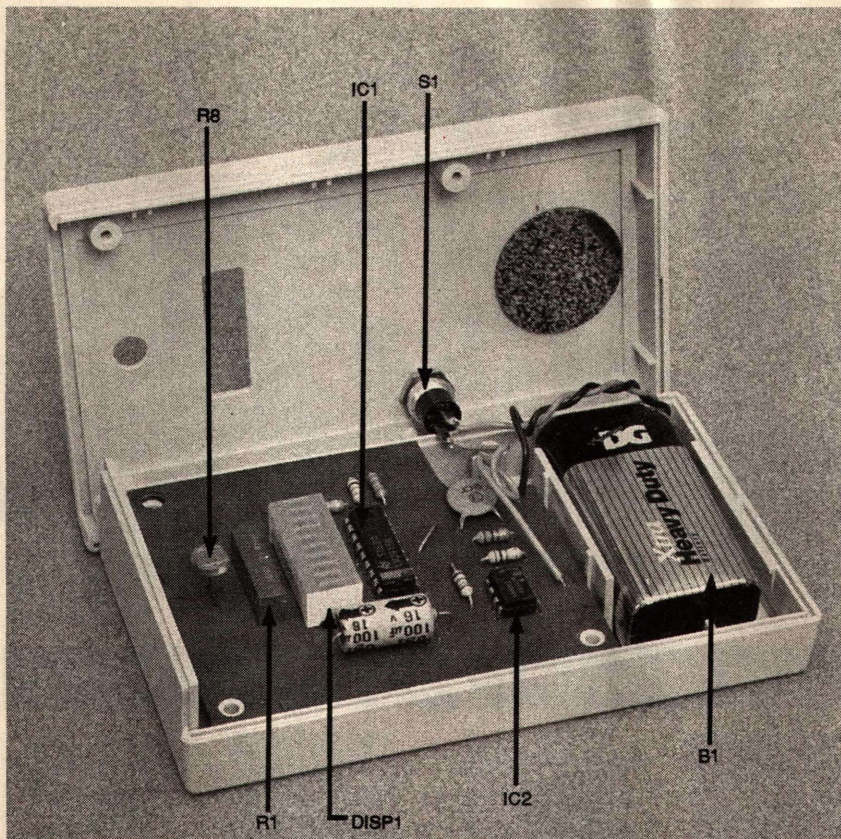

The Zonal Enlarging Meter with PC circuit board and battery B1 in position just prior to closing the plastic case. Note the holes cut for the photoresistor R8 and LED bargraph display DISP1. The photoresistor is mounted above the PC board to be flush with the inside surface of the case's cover.

Next, set up your enlarger to make a properly exposed print on your usual paper with your usual exposure time. Then put the photoresistor on a mid-gray area of the projected image, turn off the safelight, and measure the resistance. If it's between 50K and 500K, and the resistance in total darkness is at least 10 times higher, you have a workable photoresistor. If the photoresistor's test measurements are outside that range specified above, you can still use the photoresistor by substituting a different value for R1. The resistance of R1 should be about 1/50 to 1/2 that of the photoresistor.

**Putting it Together.** The Zonal Enlarging Meter is housed in a Pac-Tec HML-9VB plastic enclosure (see Parts List). The illustration of the foil-side pattern of the printed-circuit board provided is same-size and can be used to produce a PC board using any of the photographic techniques available. You can assemble the project equally well on perfboard or a universal, pre-drilled circuit board. The parts loca-

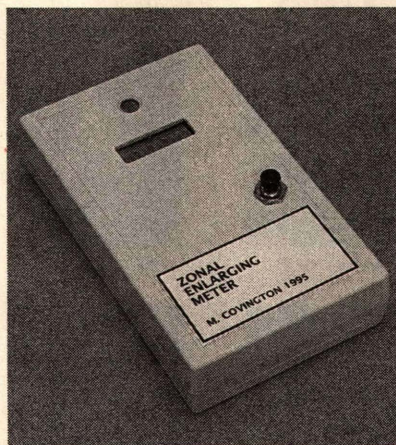

Here's the Zonal Enlarging Meter all closed up and ready for use.


tion diagram in Fig. 2 should be followed closely no matter what circuit board you use.

The photograph in Fig. 3 shows how to locate the holes for the photoresistor and the LED display in the plastic case cover once you've made the circuit board. To cut the rectangular opening for the LED bargraph display (DISP1) in the case, drill

holes in the corners directly over the display, then join them with a jeweler's saw if you have one. If you don't have a jeweler's saw, simply drill more holes until you have an approximately rectangular opening. Either way, finish the hole carefully with a file. Even though it is not attached to the hole in the cover, the photoresistor should stand up high enough on its leads so that it doesn't pick up stray light from the LEDs.

**Calibration.** Set up your enlarger to make a properly exposed print with your usual paper and exposure time. Place the meter on a mid-gray area of the image, turn off the safelight, and press S1. Adjust R1 so that five of the ten LEDs are on.

Now explore the rest of the picture. You will probably find that two or three LEDs come on in the densest areas of the negative that will show detail on the print, and eight LEDs are illuminated in the thinnest areas that will show detail. You may find it useful to make a set of strips of paper exposed at the light level of one LED, two LEDs, up to ten, so that you can see the exact shade of gray that corresponds to each meter reading. Once you have the desired adjustment for your darkroom operation, close up the meter's case. You are now ready to produce quality, full-tonality photographs at a rapid pace on the first try with each negative.  $\Omega$

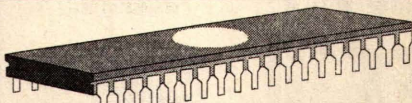

## CABLE CONVERTER DIAGNOSTIC TEST CHIP

**LOAD FULL ACTIVATION OF CABLE CONVERTER**

**WE STOCK A COMPLETE LINE OF CHIPS, TOOLS, WIRELESS QUICK INSTALL TEST BOARDS AND DIAGNOSTIC CUBES FOR ALL CONVERTERS!**

**\*\*\*ANYONE IMPLYING ILLEGAL USE WILL BE \*\*\* DENIED SALE. WE SELL PRODUCTS ONLY!! TO TECHNICIANS OR CABLE REPAIR FACILITIES!!**

**#1 IN CUSTOMER SERVICE & TECH. SUPPORT!**

**\*ALL ORDERS SHIP WITHIN 24HRS, UPS/ FED-X.**

**\*PRIORITY NEXT DAY SHIPPING AVAILABLE!**

**\*SALE- BUY 5 TEST BOARDS AND GET 1 FREE.**

**MONDAY THRU FRIDAY - 8AM-7PM EST.**

**HTTP://WWW.AMERICANINTERNET.COM/GOCABLE**






**COMMUNICATIONS INC.**


**FOR ORDERS 1-800-GO-CABLE**

**CATALOG & TECH. SUPPORT 717-620-4363 EST. 1976**






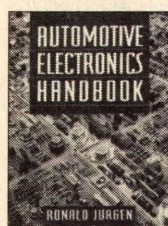
**The leading source of information for electronics hobbyists for over 30 years!**




0331898-XX \$89.50  
Counts as 2

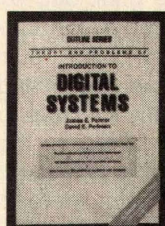


0484392 \$13.95

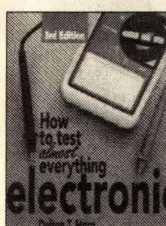


0304068 \$15.95

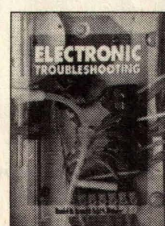


0650780 \$24.95

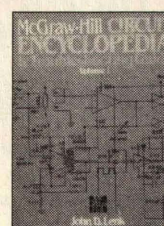

0376115-XX \$36.95  
Counts as 2

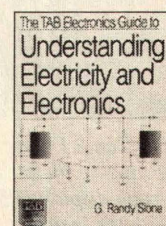

0582165 \$16.95

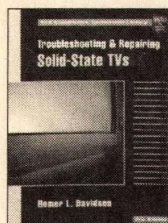


0157537-XX \$44.95  
Counts as 2




0634955 \$11.95




1570519 \$17.95

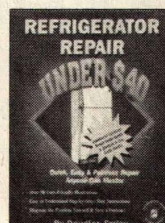


5869179 \$12.95

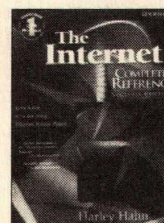


882138X-XX \$36.95  
Counts as 2

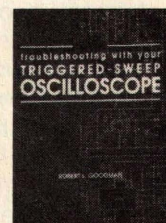


1576568 \$21.95

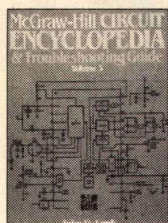


0377162-XX \$59.50  
Counts as 2

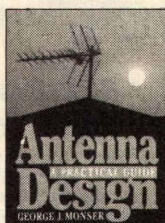


0428433 \$60.00

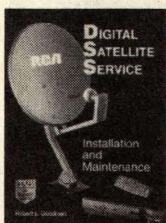


0242046 \$39.95

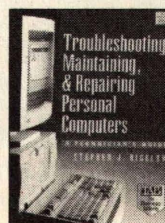

9120989-XX \$70.00  
Counts as 2

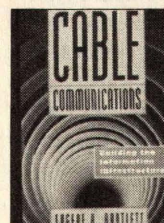

0053553 \$50.00

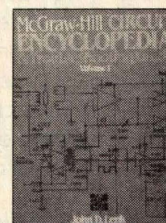

0380767-XX \$36.95  
Counts as 2


**As a member of the ELECTRONICS BOOK CLUB®** you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off the regular publishers' prices. If you want the Main selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. Your only obligation is to purchase 3 more books during the next 12 months, after which you may cancel your membership at any time. And you'll be eligible for FREE BOOKS through our Bonus Book Program.

A shipping/handling charge and sales tax will be added to all orders. All books are softcover unless otherwise noted. If you select a book that counts as 2 choices, write the book number in one box and XX in the next. (Publishers' Prices Shown) ©1996 EBC



# 5 BOOKS FOR ONLY \$4.95


VALUES TO \$243.90

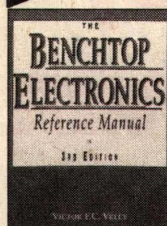

0673764-XX \$54.95  
Counts as 2/Hardcover




1573119 \$19.95

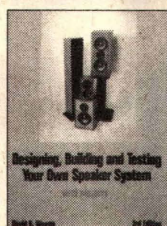

1561579 \$17.95




0156492 \$34.95

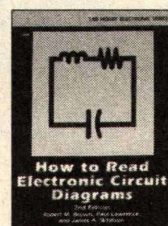

1554637 \$16.95



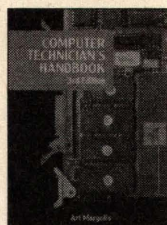
0376581XX \$39.50  
Counts as 2/Hardcover




1575472 \$27.95




0707618 \$19.95

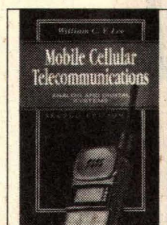

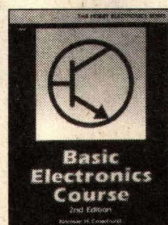
0380899-XX \$60.00  
Counts as 2/Hardcover




1574875 \$19.95

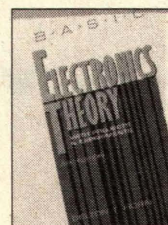


0304084-XX \$24.95  
Counts as 2

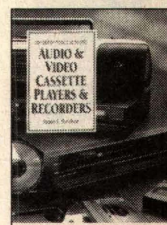

1577564 \$22.95

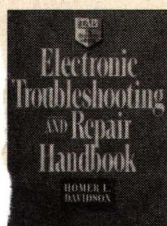


015676X-XX \$69.00  
Counts as 2

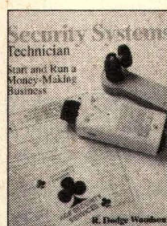

0717753 \$19.95




0497060 \$29.95

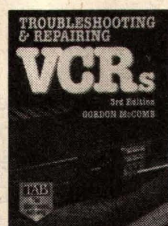


155016X \$34.95  
Hardcover




9122264-XX \$39.95  
Counts as 2

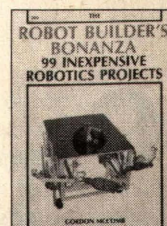


1571469 \$18.95

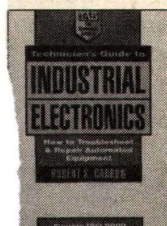

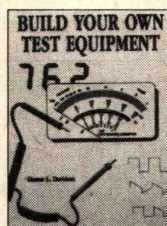
0112738-XX \$45.00  
Counts as 2/Hardcover




0155593 \$22.95

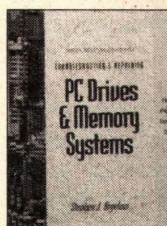


0053146 \$24.95

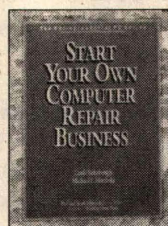

9119018-XX \$32.95  
Counts as 2

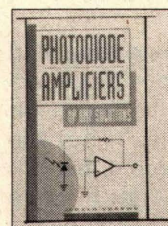

024247X \$49.00

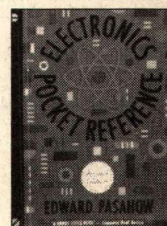

0487375 \$24.95

If coupon is missing, write to: Electronic Book Club, A Division of The McGraw-Hill Companies, PO Box 549, Blacklick, OH 43004-9918

**Electronic Book Club**

A Division of The McGraw-Hill Companies,  
P.O. Box 549, Blacklick, OH 43004-9918

**YES!** Please send me the books listed below, billing me just \$4.95 plus shipping/handling & tax. Enroll me as a member of the **Electronic Book Club** according to the terms outlined in this ad. If not satisfied, I may return the books within 30 days without obligation and have my membership cancelled.

|  |  |  |  |  |
|--|--|--|--|--|
|  |  |  |  |  |
|--|--|--|--|--|

If you select a book that counts as 2 choices, write the book number in one box and XX in the next.

Signature \_\_\_\_\_ (required on all orders)

Address/Apt. # \_\_\_\_\_


City/State \_\_\_\_\_

Phone \_\_\_\_\_

Offer valid for new members only, subject to acceptance by EBC. U.S. orders are shipped 4th Class Book Post. Canada must remit in U.S. funds drawn on U.S. banks. Applicants outside U.S. and Canada will receive special ordering instructions. Publishers' prices shown. A shipping/handling charge & sales tax will be added to all orders. RE1196C

November 1996, Electronics Now



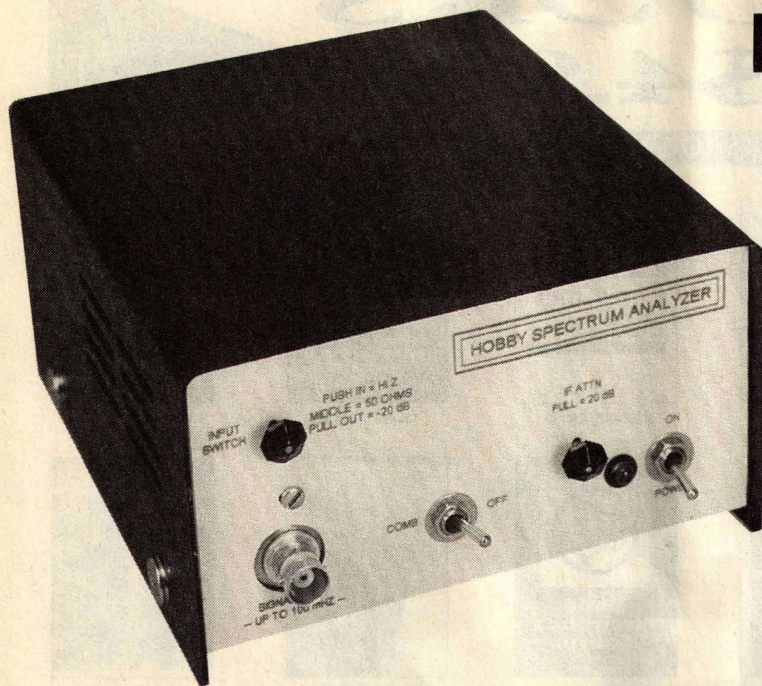

BOB KOPSKI

# BUILD THIS Hobby Spectrum Analyzer

*At less than \$100 to build,  
this spectrum analyzer is  
a must for every hobbyist!*

Over the last two months we have discussed the theory behind the \$100 *Hobby Spectrum Analyzer* and built and tested its various boards and subassemblies. Now it's time to put everything together and finish up the project.

**Functional Interconnection and Test.** Connect all four functional modules together on the bench top for a final check. This is not the *cleanest* RF arrangement, but it is workable for initial inter-module checkout.

Hook up the bench supply and current meter to the DC/DC converter and regulators battery lead. Turn on the HSA power switch but not the comb generator switch, and slowly run up the variable supply from zero, watching the current drain behavior as you advance to 12-volts DC. Look for a current draw of 26-31 mA. Turn on the comb generator; the current draw should increase 5-8 mA. Turn the comb generator off.

Connect the log amplifier output temporarily to the oscilloscope input, and the trigger output to the oscilloscope's trigger input. Set the vertical coupling to AC, and the range to 0.1 volts/division. Set the sweep to 1-mS per division. Set the IF ATTN to normal, and the INPUT SWITCH to mid-position (50

ohms). You should see a noisy baseline trace having about 0.1 volt peak-to-peak of noise. Be sure the oscilloscope is triggered for a stable display. Turn on the comb generator. You can expect a mess of vertical lines to appear on the oscilloscope. If so, you're now ready to do final assembly and alignment.

**Cabinet Assembly.** All modules and related parts easily fit in the specified cabinet; nevertheless, care is required in marking, drilling, and installing everything.

Start by flattening the dimples in the cabinet bottom where the feet screws were intended to go. The rubber feet can be glued on later. Hold a Universal prototyping board on the cabinet floor and mark four hole locations for the stack bolts. The rear board edge should be located 0.5-inch inside the rear panel, and as far to the right side of the cabinet as possible. Drill the holes. The stack screws are #6 machine screws. It is easier to slip the Universal prototyping boards over the #6 screws if the holes in the boards are drilled out to 5/32-inch diameter.

Next, drill the holes for the four phono jacks on the rear panel located on a line 1 3/8-inch up from the cabinet floor to clear the stacked boards inside. Jack-to-jack spacing and elec-

trical assignment are not critical. Glue or double stick tape a 1/4-inch thick, 3/4-inch wide, 2 1/2-inch wood or foam spacer block on the rear cabinet wall right behind the battery box location. Attach a strip of self-adhesive-backed Velcro tape to the battery box bottom and the cabinet inside floor, and trial mount the battery box.

The front panel is the most difficult mechanical task. With the RF circuit

## PARTS SUPPLIERS

### DC Electronics

PO Box 3203  
Scottsdale, AZ 85257-3293  
Tel: 800-467-7736

### Digi-Key Corp.

701 Brooks Ave So.  
Thief River Falls, MN 56701-0677  
Tel: 800-344-4539

### Electronix Express

365 Blair Road  
Avenel, NJ 07001  
Tel: 800-972-2225

### Hosfelt Electronics Inc.

2700 Sunset Blvd.  
Steubenville, OH 43952-1158  
Tel: 800-524-6464

### Ocean State Electronics

PO Box 1458  
6 Industrial Drive  
Westerly, RI 02891  
Tel: 401-596-3080




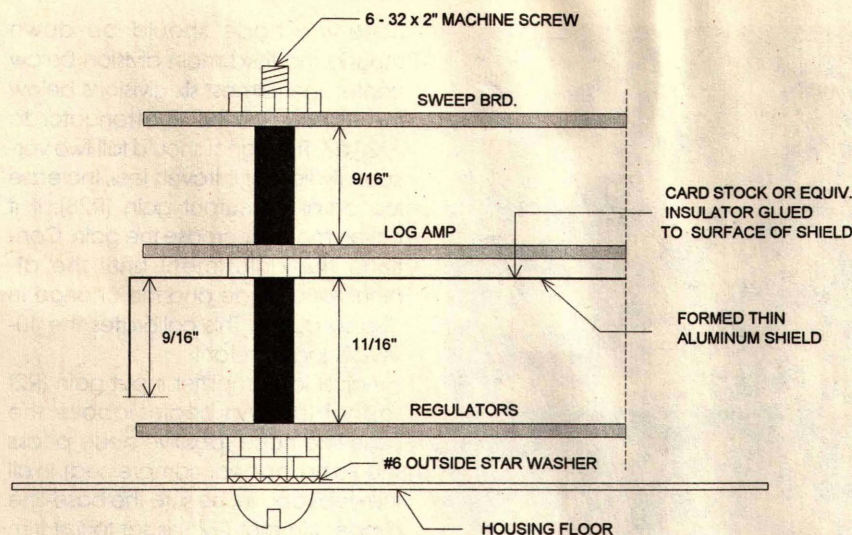


FIG. 12—MODULE STACK ASSEMBLY details are illustrated here (not to scale). Aluminum shields between the log amplifier module and DC/DC converter and regulators module provides RF shielding from stray radiation generated in the DC/DC converter circuitry.

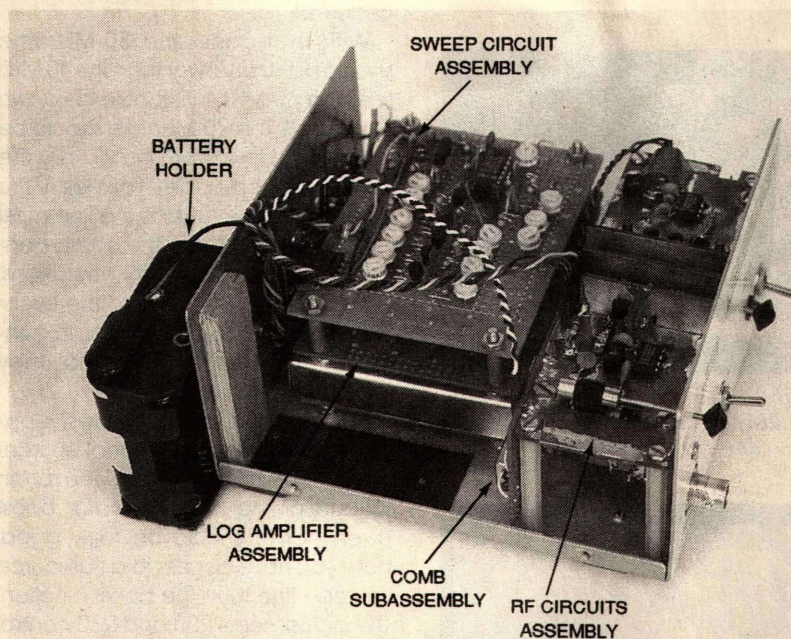

FRONT PANEL OF THE HSA mounts four switches and a BNC connector for the input signal. The rear panel (not shown) has four RCA phono jacks that provide three output signals and a battery test point.

module in hand, mark off the various hole centers in the front panel. There are two critical hole locations: the  $\frac{5}{64}$ -inch holes for the switch push rods (discussed in a moment). Make sure the alignment is correct before you drill. Use a  $\frac{5}{8}$ -inch chassis punch to make the clearance opening for the BNC connector. Finally, the panel screw just above the BNC connector is a 4-40- $\frac{1}{4}$ -inch screw. It screws into a tapped hole in the BNC mounting plate to draw the latter snug against

the rear surface of the cabinet front panel.

Locate and drill the four mounting holes in the cabinet floor for the RF circuit module spacers ("legs"). The mounting holes for the toggle switches and POWER LED2 are not critical. Make push rods for the switches using  $\frac{1}{16}$ -inch brass rod, a decorative bead glued on for a knob, and model-plane wheel collars to capture the sliding switch knobs themselves. Install all the electronics/interconnections in

the cabinet as in the drawings and photos. Temporarily omit the topmost stack nuts (Fig. 12), so that the sweep board can be lifted to access the log amplifier.


**Final Alignment.** Temporarily connect the unused preamplifier output test point to the oscilloscope vertical, and connect the trigger output to the oscilloscope trigger input. Power up. Connect a lead to a source of 145-MHz signal and allow the lead to radiate near the double-tuned 145-MHz filter. Tune the second local oscillator trimmer capacitor C27 and the filter capacitor trimmers C13 and C17 iteratively (again and again) for both a visible audio frequency heterodyne and maximum signal as well. Remove the 145-MHz signal.

Position the start of the baseline sweep precisely at the left most graticule line on the oscilloscope. Turn on the comb generator. Readjust the sweep circuit board adjustments (in the same sequence as before) to progressively locate the spectral lines on subsequent graticule divisions. The sweep offset (R7) and sweep gain (R10) board-mounted controls are used to set the lines from zero to mid-screen (50-MHz) beginning with the 10-MHz component on the first graticule line. The remaining adjustments cover the last 50 MHz. Unlike the earlier rough tuneup, you can now use the segment gain adjustments (R17, R19, R21, and R23) for fine-fitting the entire sweep shape. Work with all the screw adjustments; you can't hurt anything, and you'll observe that sweep alignment goes easily.

If you find that you can't quite hit the highest and/or one or two of the lowest frequencies, note that the HSA will likely not tune below 1-2 MHz. As for the high-end difficulties, try adjusting RF circuit module capacitor C6 in conjunction with re-spacing the loops in inductor L2. The trick is to have a suitable ratio of L and C and enough motion in C (via varactor D1) to cover the band.

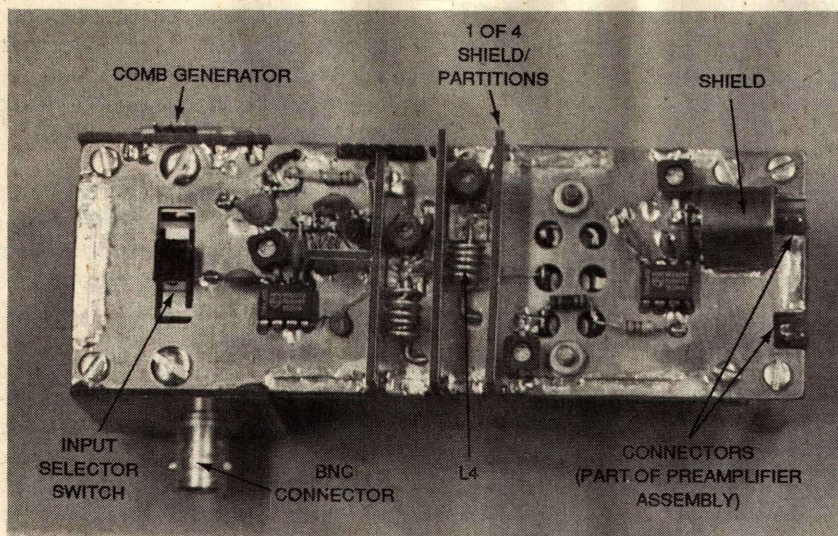Fine tune the HSA using one of the comb generator's spectral lines. The 30-MHz line is good, or an external source can be used. Connect the unused preamplifier output to the oscilloscope vertical input and the trigger output to the oscilloscope trigger input. Power up. Center up the






THE RF CIRCUITS MODULE has two subassemblies—preamplifier and comb generator. Note the partition/shield area in the center that isolates the two sections of 145-MHz bandpass filter. Inductor L4 has a tap on the first turn (bottom in photo) that is difficult to see in this view.

desired spectral line on the oscilloscope display, and then use the scope magnifier if it has one. You should see a symmetrical heterodyne bubble including a "suck out" at zero beat. Fine tune the IF trimmer capacitors C13 and C17 iteratively for a smooth sharp passband peak with the heterodyne dead center.


Switch in the IF attenuator and increase signal or oscilloscope gain as necessary to re-display the bubble. It will likely be detuned. Adjust attenuator-compensation capacitor C18 to reshape the display. Note that the bubble should have  $\frac{1}{10}$  the amplitude of the original signal (it is 20 dB down).

The adjustment of the V+ level is somewhat subjective and somewhat quantitative. Lower voltages reduce the overall HSA gain; the highest values increase it significantly. However, along with higher gains comes more noise, jitter and trash near the base-line. The baseline may also take on an undulating or curvy appearance. Another indication is an unaccounted baseline spike located at about 72 MHz. Setting V+ to a compromise level eliminates all the above unpleasantness and provides for very good operation as well. The prototype's V+ setting is about 5.7 volts.

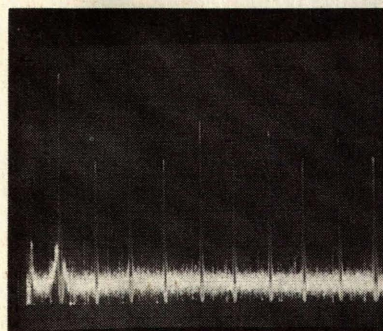The spectral line at the 10-MHz position can be used to help adjust HSA amplitude performance. Locate the top of that line on an upper oscilloscope's graticule line at three



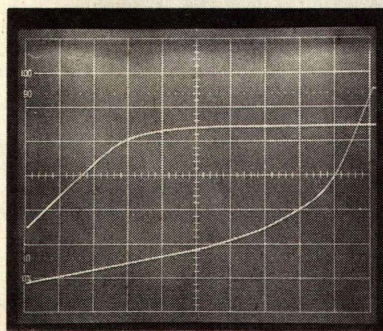A VIEW OF THE HSA comb generator oscilloscope display after the alignment procedure is completed.



THE SWEEP-CIRCUIT OUTPUTS as viewed on an oscilloscope. The lower-most curve is the varactor (sweep) drive waveform—the bottom grid line is 0.0 volts, 5-volts per division. The upper-most waveform is the local-oscillator boost waveform—1-volt/division, top of trace is 4.5 volts. Both curves are displayed on a 1-ms/division time base.

main graticule divisions up from center face. This is the -30-dBm level. The

base-line noise should be down around the third main division below center line (almost six divisions below the signal). Set the IF attenuator to -20 dB. The signal should fall two vertical divisions. If it travels less, increase log amplifier output gain (R28); if it travels more, decrease the gain. Continue the adjustment until the attenuator change and the change in display agree. This calibrates the 10-mV/dB log constant.

Adjust log amplifier input gain (R2) so that logging begins above the base-line noise (positive noise peaks should not appear compressed). In all the steps above, be sure the base-line clipper trimmer (R26) is set to just trim off negative going spectral lines and not infringe on the magnitude of the base-line noise. Trimmer R26 will require resetting during the above procedures.

With that done, the 30-MHz line should be 10 dB lower than the 10 MHz line. The 50-MHz line should be down 5 more dB. The 70-MHz line should be about 3 dB down from that. Finally, the 90-MHz line should be 21 dB below the 10-MHz line. The latter is the line most likely to be off due to the comb-generator-waveform quality limitations. Finally, pay no attention to the even-order spectral lines; if the comb generator waveform were ideal they would not be present at all.

Frequency flatness is best confirmed with a quality signal source/power meter combination. The rough tuneup of the local oscillator boost given earlier should be fairly good, but if you have access to a flat source you can fine tune the boost function. The adjustments R33 and R30 control boost waveform "zero" and ramp rate respectively. The setting of R35 controls the waveform effect on local oscillator power.

**Hints.** The Hobby Spectrum Analyzer just begins to overload for signals exceeding -30 dBm. This is about 20 mV peak-to-peak on 50-ohm lines. Distortion manifests itself in several ways including baseline "buckling" at the base of such a spectral line, and "splatter" across the display. This situation can often be controlled with the input and/or IF attenuators.

It is sometimes convenient to transformer couple RF energy into the HSA.

(Continued on page 118)





# PHONE LINE SENTINEL

***Put an end to phone-call interruptions with the Phone-Line Sentinel—it will let others know when you're on the line.***

MORDECHAI SAAD

WE ALL KNOW HOW ANNOYING IT CAN be when you're in the middle of an important phone call and somebody else picks up the line and says "Oh, I didn't know you were on the phone." And it's all the more annoying when they start dialing without first checking for a dial tone. Of course, such an interruption can be devastating to a fax or modem transmission. If you are regularly plagued with such interruptions, then you need one of our Phone-Line Sentinels placed next to every phone in your house. The PC board measures only 1 × 1.8 inches.



## **How it works**

The nominal voltage of a telephone line, when not in use, is about 50 volts DC. As soon as the line is in use, meaning that a telephone on the line has been picked up, the line drops to about 5 volts DC. Therefore, all we need is a voltage-level sensor to detect whether or not the line is in use. The Phone-Line Sentinel is just that; it monitors the phone-line voltage and lights an LED to let you know when the telephone line is in use.

At the heart of the circuit, shown in Fig. 1, is IC1, an ultra-low-current voltage-level sensor.

Using that IC, the circuit draws "no" current (about 5  $\mu$ A) when the phone line is not in use, and negligible current (about 3 mA) when the line is in use. Power for IC1 is supplied from the phone line via R2, D1, and C1. Transistor Q1, which powers LED1, is driven directly from IC1 whenever the proper voltage level has been detected. Resistor R1 limits the current flow through LED1, and R3, R4, and D2 divide the phone-line voltage down to a proper level for IC1. Protection from phone-line transients is provided by resistor R5 and varistor R6.




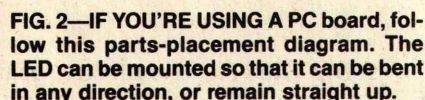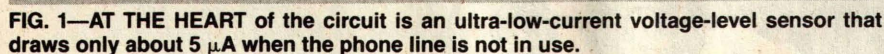

The Phone-Line Sentinel is available as a kit (or completed unit) from the source mentioned in the parts list. However, if you can dig up all of the parts on your own, you can point-to-point wire the circuit, or make your own board from the foil pattern we've provided.

A photograph of a vintage electronic circuit board, likely a radio receiver. The board is populated with several vacuum tubes, including a large 6X4 tube at the top, a 6AR5 tube in the middle, and a 6X4 tube at the bottom. There are also several smaller tubes and components like capacitors and resistors. A large speaker is mounted on the left side of the board. The board is housed in a metal chassis.

**FIG. 3—THE COMPLETED BOARD** should look something like this.

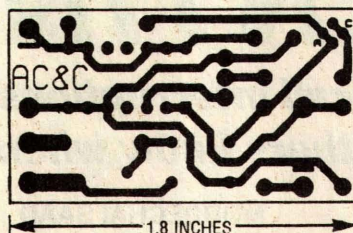

**USE THIS FOIL PATTERN** to make your own PC board.

two positions, so that it can be bent in any direction, or remain straight up. You can also mount the LED on leads as long as you like, allowing the board to be hidden from view, or perhaps inside a telephone if there's enough room, leaving only the LED indicator in view. We'll leave the details up to you. Just be sure to observe the LED's polarity on the board regardless of how you install it.

Connecting the unit to a phone line is easy. If you have a spare

**All resistors are 1/4-watt, 5%.**

R1—1500 ohms

R2, R3—2.2 megohms

R4—3.3 megohms

R5—5.1 ohms

R6—MOV022 varistor

## Capacitors

C1—0.1  $\mu$ F, 50 volts, ceramic

## Semiconductors

IC1—OP8602 ultra-low-current voltage-level sensor

D1—1N5245B 15-volt Zener diode

D2—1N5253B 25-volt Zener diode

BR1—DB103 bridge rectifier

LED1—light-emitting diode

Q1—ST91A NPN transistor

**Miscellaneous:** PC board, modular phone cord or hookup wire, solder, etc.

**Note:** The following items are available from TelMore, 11 Market Dr., Syosset, NY 11791: A complete kit, including PC board and all parts in Parts List (above), \$14.99. An assembled and tested unit, \$19.99. With the assembled units, you must specify which way you want the LED positioned. With the LED pointing straight up, order LIUD-UP; with it pointing to the long side of the board, order LIUD-LS; with it pointing to the short side, order LIUD-SS; and with it mounted off the board on wire leads, order LIUD-W. Add \$1.75 for the -W model. Please add \$7.50 for shipping and handling to all orders. NY State residents must add appropriate sales tax.


jack in a desirable location, all you have to do is solder the tip and ring (green and red) wires of a modular phone cord to the board as shown in Fig. 2. Otherwise you can use whatever wire you like and connect it to the line however you see fit. Figure 3 shows the completed board.

Testing the circuit is as simple as using it. Just connect it to the phone line; the LED should be off if the line is on-hook. Then, if you pick up any phone on the line, the LED should light. After the operation of the circuit checks out, it's time to decide what you're going to do with it. Because of the extremely compact size of the board, the neatest thing you can do is mount one inside every phone you own, with only the LED left exposed. If you do a neat job, it will look like it was factory installed.  $\Omega$



*The 7107 A/D converter/display driver has been on the market for so long, its versatility tends to be overlooked. Get re-acquainted with this amazing voltmeter-on-a-chip: the device with a thousand-and-one uses.*

CARL J. BERGQUIST

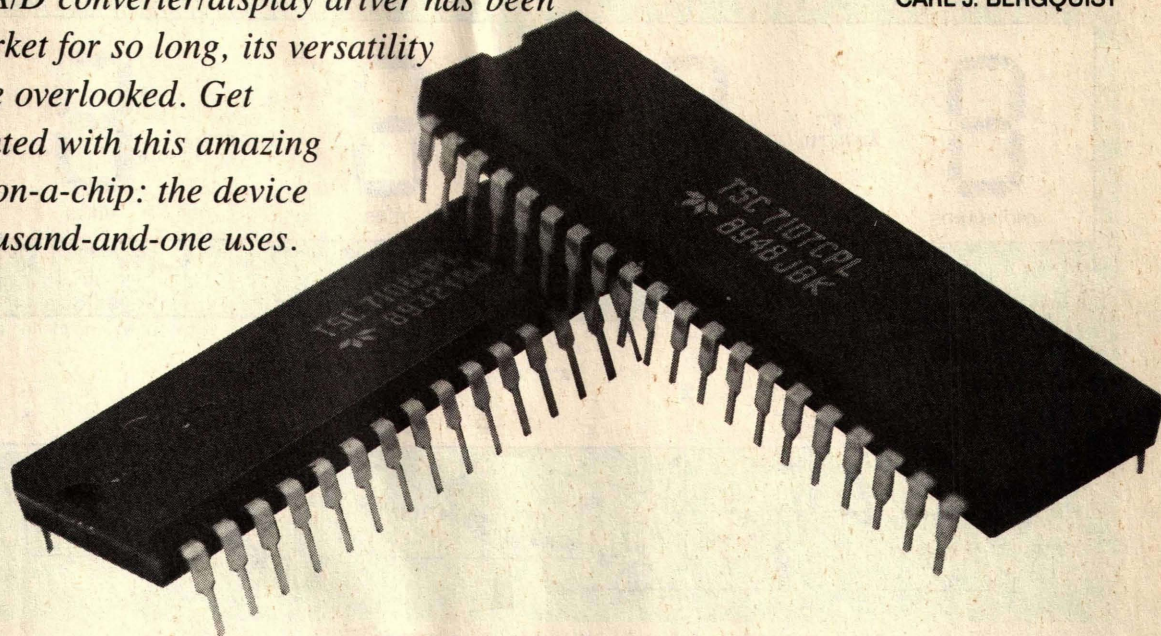

## USING THE 7107

**W**ith the invention and introduction of the seven-segment light-emitting diode (LED) display, adding an information display to the front panel of almost any project has become commonplace. Digits are easier to read than analog meters, and tend to "dress up" the appearance of the completed unit.

Those displays, of course, do not light themselves, but rely on logic and driver circuitry to display the desired information. The combination of a binary or decade counter with a decoder/driver is one way to display information on the LEDs, especially in clock applications, but a more versatile method is an analog-to-digital converter.

A number of options are available along that line. Combining a Motorola 14433 3½-digit A/D converter or an RCA CA3162 A/D converter with an RCA CA3161 BCD-to-7-segment decoder/driver chip is one way to go, but for ease of use, low cost, and low component count, it's hard to beat the Intersil/Harris ICL7107/7106 3½-digit A/D converter/display driver.

Originally designed primarily as a voltmeter, the 7107 is a combination analog-to-digital converter, reference voltage, timing clock, and decoder/driver circuit all on a single CMOS IC. It features high accuracy, low power consumption, and directly

drives instrument-sized, common-anode, 7-segment LED displays. The 7106 is the liquid-crystal display (LCD) version of that device and incorporates a backplane driver.

The number of support components needed for operation of the 7107 are minimal: five capacitors, four resistors, a potentiometer, and the display. Add a split five-volt power supply, and the 7107 becomes a complete 3½-digit voltmeter with a full-scale reading of either 200 mV (199.9) or 2 volts (1.999), depending on the values selected for the support components. Another attractive feature is that since both chips have been on the market for several years, their price through catalog distributors has dropped to below four dollars each.

With the basic voltmeter circuit, any measurement, value, or quantity that either exists as a voltage or can be converted to a voltage will provide the input. The 7107 is then easily calibrated to display that measurement or value digitally.

So, the possibilities are limitless. Volt-

age, current, resistance, inductance, light, temperature, speed, capacitance, frequency, etc., can all be directly displayed through simple transducer circuits. We'll show you how to do that, and armed with that knowledge, it is very convenient to either equip projects and new designs with digital displays, or modernize older gear.

**7107 Circuit Operation.** Figure 1 is the schematic for a basic 2-volt configuration. Power for the chip is applied to pin 21 for ground, pin 26 for -5 volts, and pin 1 for +5 volts. Pins 2-20, and 22-25 connect the device to the LED display, with pin 19 driving the ½ digit, or the leading "1", on the display. Pin 20 indicates when the input voltage drops below 0 volts, so it can be used to drive a minus sign on the display.

Pins 30 and 31 accept the negative and positive inputs, respectively, while pins 35 and 36 handle the reference voltage generated by a resistor-potentiometer divider network. The lo



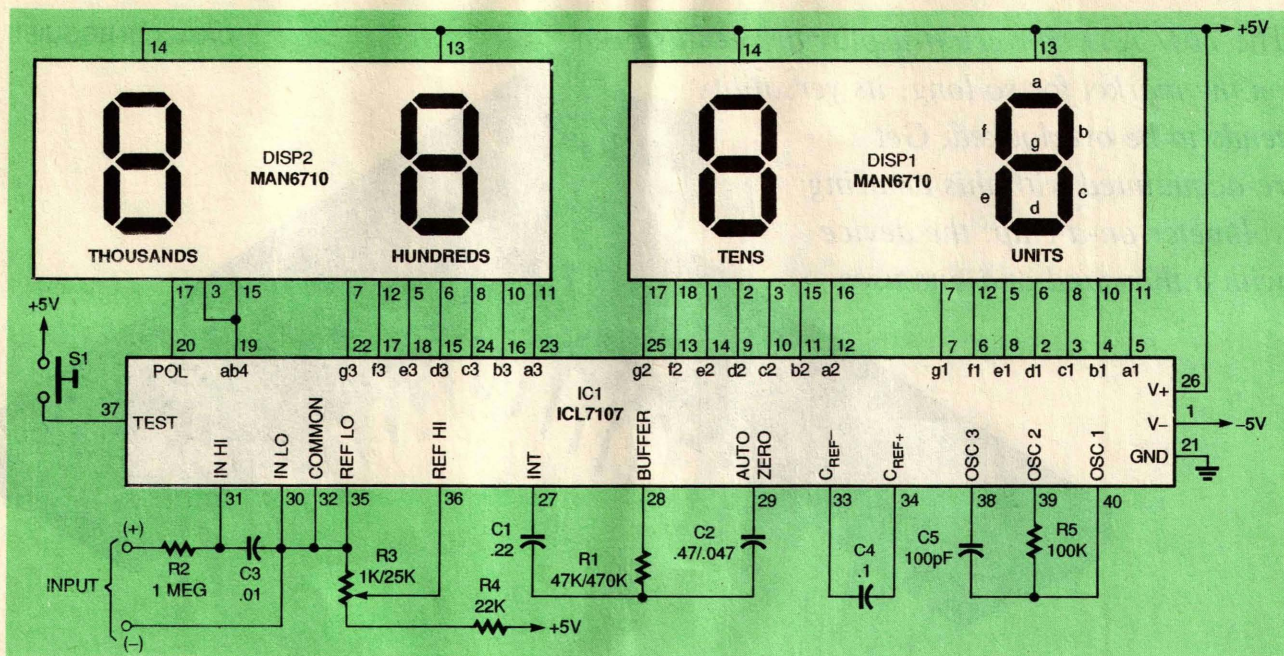


Fig. 1 The 7107 was originally designed to be a self-contained, highly accurate voltmeter. By changing the values of C2, R1, and R3, the 7107 can have a range of 200-mV or 2 volts.

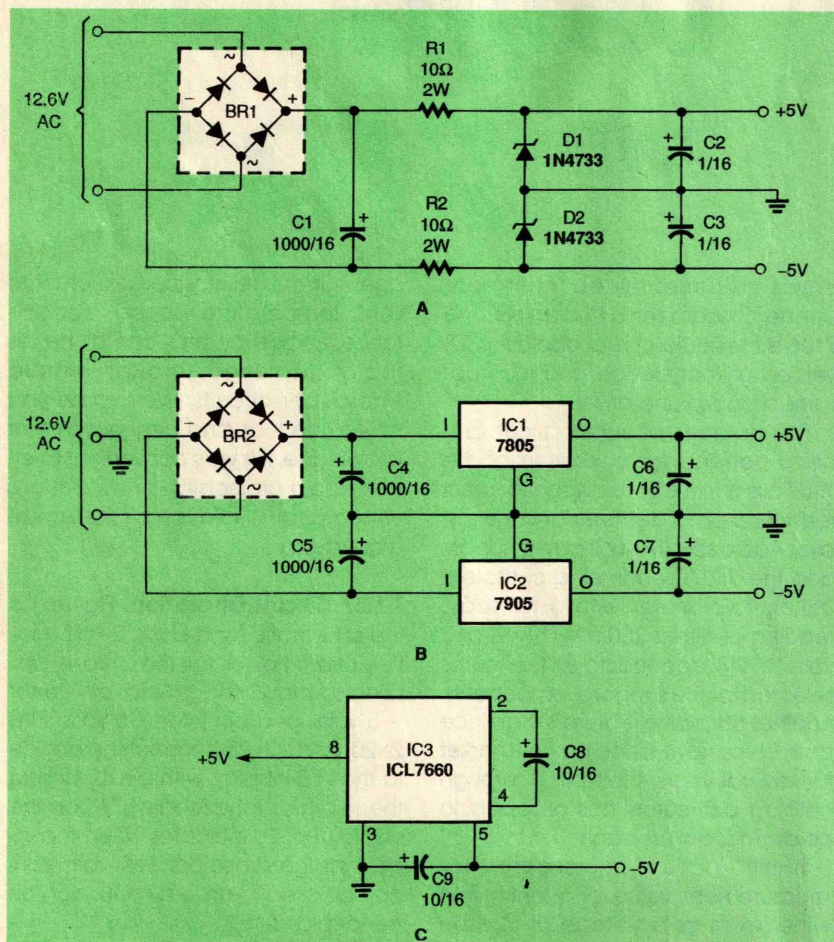


Fig. 2. Here are a few different methods of generating the + and -5-volt power required by the 7107. A pair of Zener diodes (A) are handy if the transformer you want to use does not have a center tap. A pair of three-terminal regulators (B) and a center-tapped transformer also work well. An interesting alternative is the ICL7660 chip (C), which generates a negative-voltage output from a positive-voltage input.

reference (pin 35), analog common (pin 32), and negative input (pin 30) are tied together in any application where the input signal is "floating" with respect to the power supply. The analog common also provides the reference voltage for the auto zero feature, which maintains a zero reading for a 0-volt input.

Pins 38, 39, and 40 provide access for the clocking circuit. The recommended values result in a frequency of 48-kHz (3 readings per second), which generally gives excellent performance. If a different frequency is desired, the equation  $f = 45/RC$  can be used to find the component values needed. If you keep R at 100,000 ohms, the formula will select the correct value for C. In addition to the RC arrangement, a crystal can be connected between pins 39 and 40, or an external oscillator signal can be fed into pin 40.

With the exception of R1, C2, and R3, component values are common to both the 200-mV and 2-volt configurations. Resistor R1 provides linearity over the input range. Recommended values are 47,000 ohms for a 200-mV range, and 470,000 ohms for the 2-volt range.

Auto-zeroing capacitor C2 has an effect on noise in the circuit. For the 200-mV scale, a value of 0.47-μF improves noise immunity, while 0.047-μF is adequate for the 2-volt version. That



smaller value also improves recovery speed of the circuit. A value of 1,000 ohms for potentiometer R3 in the lower-voltage meter is increased to 25,000 ohms to provide a wider reference range for the higher-voltage meter.

For maximum accuracy and stability, it is best that all capacitors, with the exception of C5, be of the Mylar variety. With its lower dielectric absorption, that type of capacitor will provide superior performance. Capacitor C5 can be a standard ceramic disc or silver-mica type, and all resistors are 5% carbon film.

One disadvantage of the 7107 is the need for a split 5-volt power supply, but there are several simple ways to meet that requirement. If a bench supply is at hand, it usually has  $\pm 5$  volts available, either as a separate output or through the use of the adjustable supplies. If that source is not convenient, or a separate self-contained supply is preferred, Fig. 2 shows three different approaches.

In Fig. 2-a, input power from a small step-down transformer is first rectified by bridge rectifier BR1 and smoothed by capacitor C1. A pair of 1N4733 Zener diodes (D1 and D2) regulate the input power to the needed 5 volts.

## PARTS LIST FOR THE 7107 VOLTMETER

### SEMICONDUCTORS

IC1—ICL7107CPL A/D converter/LED display driver, integrated circuit  
DISP1, DISP2—dual 7-segment common-anode LED display (MAN6710 or similar)

### RESISTORS

(All fixed resistors are 1/4-watt, 5% units.)


R1—47,000-ohm/470,000-ohm  
R2—1-megohm  
R3—1000-ohm/25,000-ohm, potentiometer, (see text)  
R4—22,000-ohm  
R5—100,000-ohm

### CAPACITORS

C1—0.22- $\mu$ F, Mylar  
C2—0.47- $\mu$ F/0.047- $\mu$ F, Mylar (see text)  
C3—0.01- $\mu$ F, Mylar  
C4—0.1- $\mu$ F, Mylar  
C5—100-pF, ceramic-disc

### ADDITIONAL PARTS AND MATERIALS

IC sockets, hookup wire, etc.

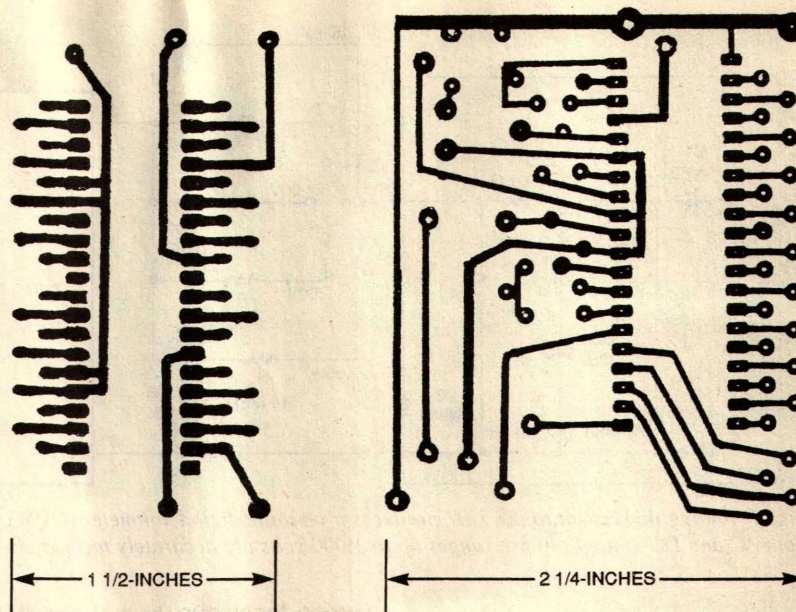

Here are the foil patterns for the basic 7107 voltmeter and the LED display. A split power supply and a handful of passive components turn the 7107 into an accurate, easy-to-use instrument. Putting the display on a separate board makes the project more versatile in terms of mounting arrangements. You can also combine both boards into one if you need to.

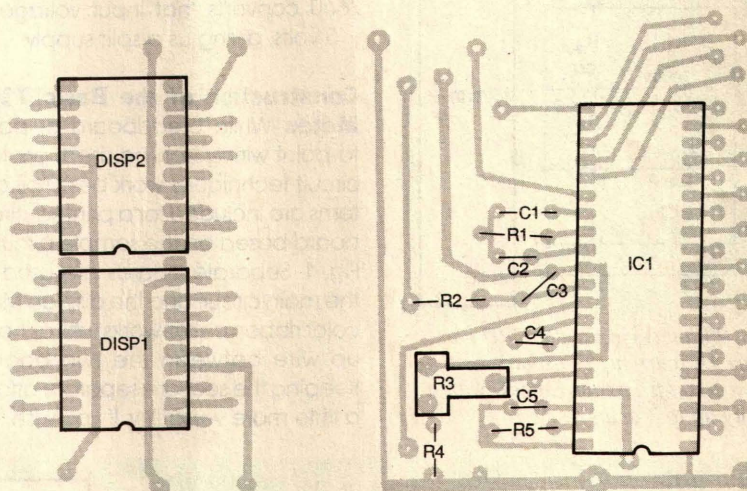


Fig. 3. If you want to build your own 7107 voltmeter, you can follow the parts placement diagrams here. Using sockets for the 7107 and the displays make troubleshooting easy.

Actually, the diodes are rated at 5.1 volts, which is well within the 7107's tolerance. Resistors R1 and R2 limit the current that flows through the Zener diodes themselves. The remaining circuitry is a standard "rail" power supply.

Figure 2-b illustrates a similar configuration utilizing positive- and negative-output linear voltage regulator ICs. However, we are using a center-tapped transformer to form a true split power supply. A disadvantage of a center-tapped transformer is the added expense. However, never try to

get around that by using a non-center-tapped transformer and connecting one side of the AC input to ground. Although that would work, it would create a "hot" ground: a potentially dangerous situation. Any extra money spent on the proper transformer will be far cheaper than spending several days in a hospital should some component in the circuit fail. Be sure both the 7805 and 7905 voltage regulators have adequate heat sinks.

Figure 2-c uses a voltage-con-



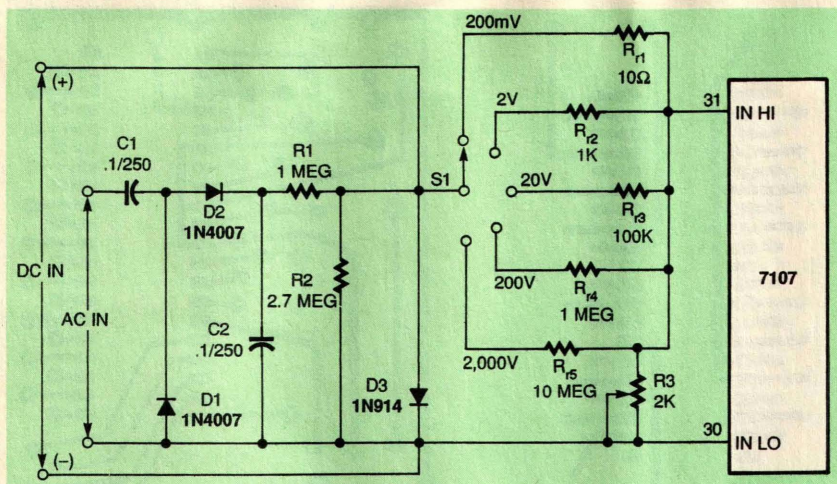


Fig. 4. Adding this circuit to the 7107 produces a versatile digital voltmeter (DVM). Both AC and DC voltages in five ranges up to 2,000 volts are accurately measured.

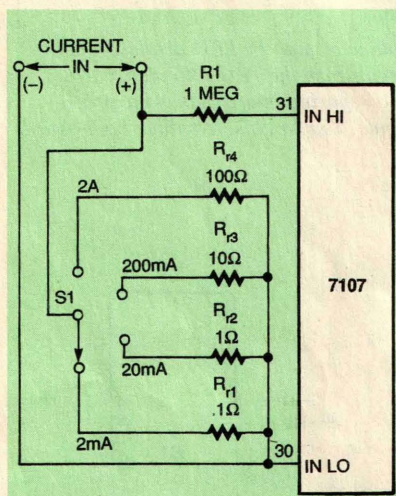


Fig. 5. With this circuit, the 7107 can measure DC current. The rotary switch lets you select from four ranges, with a capacity up to 2 amps.

version technique. In that circuit, either the Teledyne TSC7660 or the Intersil/Harris ICL7660 will work. Both are 8-pin DIP packages with identical pinouts. If a 7660 is used, the power supply need only deliver +5 volts. The 7660 converts that input voltage to -5 volts, giving us a split supply.

**Construction of the Basic 7107 Meter.** While breadboard or point-to-point wiring can be used, printed-circuit techniques work best. Foil patterns are included for a printed-circuit board based on the sample circuit in Fig. 1. Separate boards are used for the main circuit and the display. Multi-color ribbon cable works well as hook-up wire between the two boards. Keeping the sections separate affords a little more versatility. If you wish, the

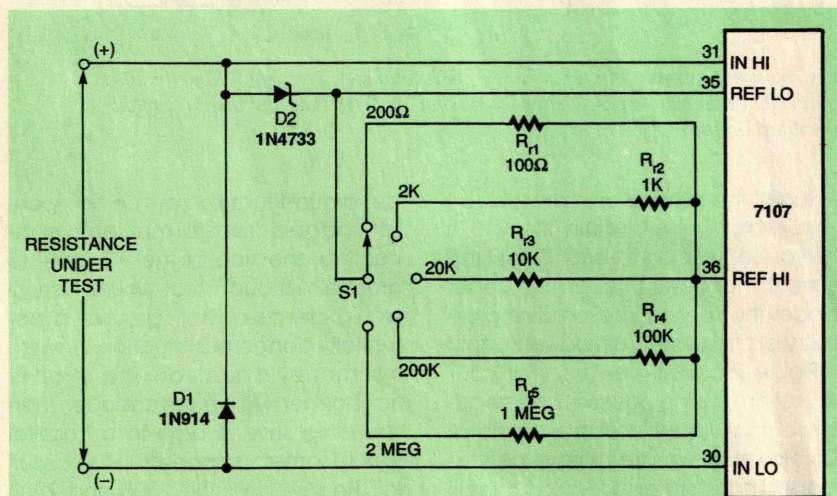


Fig. 6. Although you could measure resistance with a simple voltage-divider circuit, the use of a Zener diode and a switch-selectable resistor to change the 7107's reference voltage makes it easier to measure resistances up to 2 megohms.

LED readouts and main circuit can be combined onto one board. It's a simple matter to merge the two patterns together.

Regardless of how you handle your PC boards, use a 40 pin IC sockets for both the 7107 and the LED displays. That makes changing the 7107 or the displays easy if you need to. The parts-placement diagram in Fig. 3 will aid in component insertion at the proper locations. When installing the discrete components, the only orientation to observe is the IC itself, as the capacitors are non-polarized.

Like the display circuit, the power-supply circuit can either be put on the main PC board or kept separate. Convenience or personal preference will, of course, influence which way you decide to go. With all three sections completed and connected together, we can move on to the next step.

### Testing and Operation of the 7107

**Meter.** Before installing the 7107 chip itself, confirm that the correct voltages are present at the power supply, and at pins 1, 21, and 26 of the 7107 socket. If a problem is encountered, double-check the wiring and component placement for errors. Once the proper voltages are verified, disconnect the power and plug the 7107 into its socket. Turn the power back on, and the display should read "000".

Apply +5-volts to pin 37, and "-1888" should be displayed. Pin 37 is the test input and activates all segments. A permanent switch can be added if the test function is to be used often. However, do not leave the test on for more than a few minutes if you're using the 7106. The test function on that chip applies straight DC instead of squarewaves to the LCD segments. That might cause the image to "burn" into the LCD.

Apply a known, stable voltage to the + and - inputs. Adjust potentiometer R3 until the display reads that voltage. The meter is now calibrated and ready to go.

Another method of calibration is to read the actual reference voltage at pins 35 (REF LO) and 36 (REF HI). For the 200-mV meter, that reading should be as close to 100 mV as possible. For the 2-volt meter, 1 volt is the needed measurement.

That procedure will also be useful if



an abnormal voltage reference is needed. In some applications where the transducer output is above or below the standard meter parameters, it is easier to adjust the reference voltage to accommodate the transducer, rather than attempt to correct the transducer's output voltage. In any event, always adjust the reference to one half the input voltage.

Additionally, a decimal point can be displayed by hard wiring a 470-ohm resistor from ground to the pole of a four-position rotary switch. With the four contacts connected to the four decimal points on the display, the decimal point can easily be placed wherever it is needed.

### Applications and Input Transducers.

With the basic digital meter built and tested, it's time to put the unit to work. As we mentioned earlier, any value or measurement that is a voltage or can be converted to a voltage can be displayed, but only if we connect what we need to measure to the meter properly. That is where the input circuits and transducers come into play.

**Voltage Measurements.** Since the 7107 is a voltage-measuring device, let's look at that application first. Figure 4 is a circuit for a digital voltmeter (DVM) that will measure voltages from 0 to 2,000 volts in five ranges. The circuit can measure both alternating and direct current, with C1, C2, D1, D2, R1, and R2 acting as a rectifier/filter for AC measurement. Resistors  $R_x$  and R3 form a selectable input-voltage divider. Rotary switch S1 connects any one of the five resistors,  $R_{r1}$ – $R_{r5}$ , for the selected voltage range.

Once that input circuit has been connected to the 7107, choose a known voltage source, either AC or DC. Select the appropriate range with S1, and adjust R3 to obtain a display that matches the known source. That will fine-tune the circuit for future voltage measurements.

**Current Measurements.** The next basic measurement to consider is current. We do that by passing the current through a shunt resistor. The shunt develops a voltage across itself in proportion to the amount of current flowing through it. That voltage can be measured by the 7107 meter.

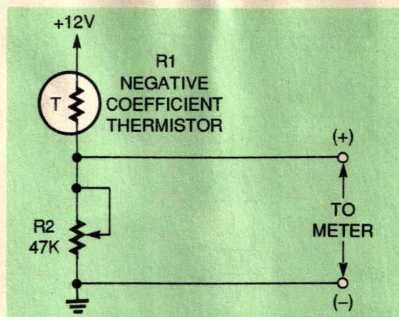


Fig. 7 A simple voltage-divider circuit using a negative-temperature-coefficient (NTC) thermistor is a low-cost and accurate method of measuring temperature with the 7107. An NTC thermistor's resistance drops as its temperature rises. If you switch the locations of R1 and R2, the reading on the 7107 will drop with rising temperature.

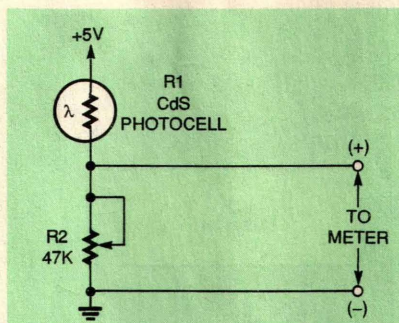


Fig. 8. We can measure light intensity the same way we measure temperature by substituting a cadmium-sulfide (CdS) photocell for the thermistor in Fig. 7. In most CdS photocells, resistance will drop with an increase in brightness. Should you need to have the 7107's display reading drop as the photocell gets brighter, or if you have a photocell that increases in resistance with exposure to light, simply switch the positions of R1 and R2.

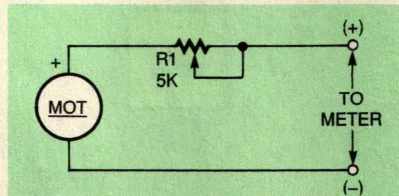


Fig. 9. You can use a small permanent-magnet motor as a tachometer. Attach the motor's armature to whatever spinning shaft you want to measure, and the voltage generated by the motor can be read directly by the 7107.

Figure 5 is the schematic of a four-range system, where  $R_{r1}$ – $R_{r4}$  controls the range and acts as the shunt. Resistors R1 and  $R_{r1}$ – $R_{r4}$  form a voltage divider that provides the input for the

meter. A rotary switch arrangement similar to the range selector in Fig. 4 works nicely for the ammeter as well. The values for the shunt resistor are selected by S1. Using 1% precision metal-film resistors gives the greatest accuracy.

**Resistance Measurements.** The last type of value commonly measured by most digital multimeters (DMMs) is resistance, and Fig. 6 illustrates a method for that. Zener diode D2 develops an external reference voltage, allowing S1 to select one of  $R_{r1}$ – $R_{r5}$  to control the on-chip reference voltage. A DC voltage is generated across the unknown resistance, and that value is then processed by the 7107 and displayed.

That measurement could also be done with a standard voltage-divider circuit, but the problem with that method is that  $R_{r5}$  would have to be in the 500-megohm range for the 200,000- to 2-megohm setting. That is a difficult value to obtain, especially at precision levels. Adjusting the reference voltage results in a workable value for  $R_{r1}$ – $R_{r5}$ .

**Temperature Transducer.** There are a number of ways to measure temperature. Figure 7 is a simple and surprisingly accurate method. In that configuration, a 47,000-ohm potentiometer provides as calibration, and a negative-temperature-coefficient (NTC) thermistor acts as the temperature probe. By applying 12 volts and setting the decimal point on the display between the units and tens digit, readings to an accuracy of  $\frac{1}{10}^\circ$  can be achieved. Again, the circuit is a voltage divider.

### Light Measurement Transducer.

The light transducer in Fig. 8 is almost identical to the temperature sensor. The only differences are a 5-volt supply voltage and the use of a cadmium-sulfide (CdS) photocell in place of the thermistor. Changes in ambient light shining on the photocell changes the resistance of the cell. That in turn changes the voltage produced by the divider. Any change in light intensity will be shown in the display. The display can be calibrated to indicate "f-stops" for photography work, or can be an arbitrary numerical value for which a chart or graph



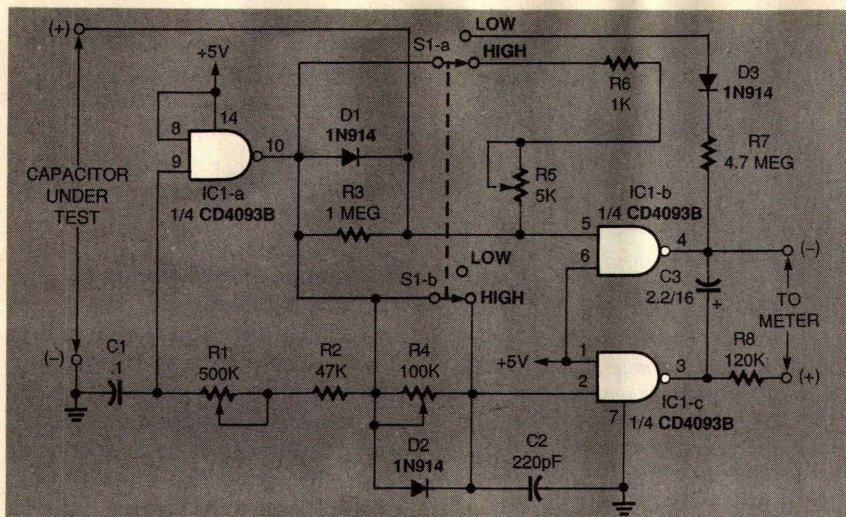


Fig. 10. With this circuit, the 7107 gains the ability to measure the value of capacitors from 2 pF to 2  $\mu$ F. Potentiometer R4 adjusts the circuit for a zero reading, while R1 and R5 calibrate the low and high ranges.

can be developed as appropriate. By using a photocell with a range of 500-ohms illuminated to 2- to 3-megohms dark, very sensitive results can be achieved with the circuit.

Those two circuits illustrate how any device that changes resistance due to any circumstance can be plugged into the divider network. You can try replacing the CdS photocell with a 1,000-ohm potentiometer. After calibrating with the 47,000-ohm variable resistor, the exact value of the potentiometer between 0 and 1,000 ohms will be displayed.

**Speed Measurements.** Figure 9 shows a method of measuring rotary speed. Since the 7107 is a voltmeter, and electromagnetic motors produce a voltage when their armatures are rotated, the measurement circuit is extremely simple. A 5,000-ohm potentiometer is used for calibration, with one end connected to the positive motor pole, and the other tied to the HI input (pin 31). The negative side of the motor goes to the LO input (pin 30). When the motor shaft is coupled to a rotating object, the voltage developed is proportional to the speed of rotation. That system can be used for tachometers, wind-speed indicators, generator-voltage monitors, and the like.

**Capacitance Meter.** One of the most useful bench tools around is the digital capacitance meter. Those meters will save not only time, but money as well. Surplus capacitors are

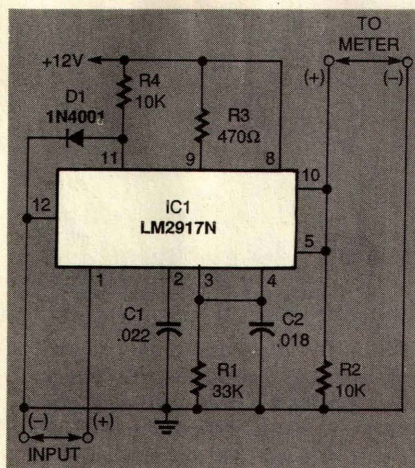


Fig. 11 Adding an LM2917 to the 7107's inputs lets you measure lower frequencies up to about 10 kHz.

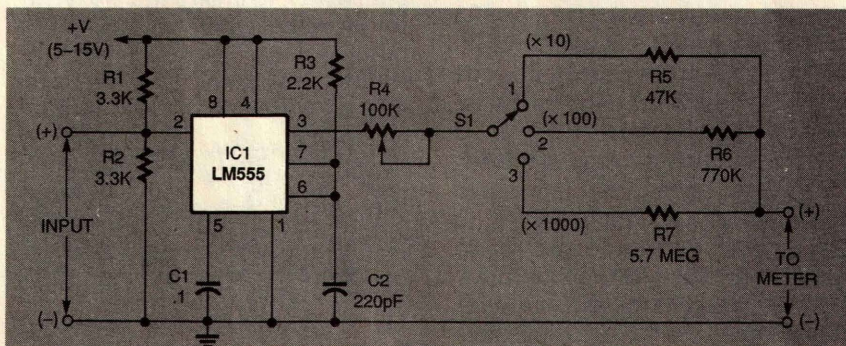


Fig. 12 To measure higher frequencies than the LM2917 can handle, this circuit does the job quite well. Frequencies in 3 ranges up to 2 MHz (1.999 x 1000) can be measured.

often sold by the pound at a greatly reduced price, but due to factory marking, or no marking at all, it can be hard to determine the values of those. A capacitance meter solves the problem, but most commercial meters are

relatively expensive.

Figure 10 is the schematic for a unit that makes use of a 4093 quad 2-input NAND Schmitt trigger, and will measure capacitors from 2 pF to 2  $\mu$ F in two ranges. The low setting handles 2 to 1,000 pF while the high setting is for capacitor values from 0.001 to 2  $\mu$ F. The circuit hooks up directly to the 7107.

Once connected to the 7107, calibration is simple. Turn the unit on and adjust R4 for a zero reading. With S1 in the low setting, connect a 100-pF capacitor to the test leads, and adjust R1 for a reading of "0100". Then switch S1 to the high setting, and with a 1- $\mu$ F capacitor connected to the test leads, adjust R5 for a "1000" display. With that done, the meter is now ready to test and measure capacitors within the meter's range.

It is a good idea to conduct those last two steps with several known capacitors to fine-tune the calibration. While not shown in the schematic, it is common practice when using CMOS-technology ICs to connect the inputs of any unused logic gates (e.g., pins 11 and 12 of IC1) to either ground or the positive voltage. That will reduce power consumption and interference. On a final note, be sure the +5-volt supply is well regulated to maintain accuracy.

**Frequency Measurements.** Figure 11 uses the LM2917N frequency-to-voltage converter in a standard configuration. That device is a simple and

inexpensive way of displaying frequency with the 7107. The 2907/2917 series was originally designed for tachometer systems, and is limited to frequencies from DC to about 10,000 (Continued on page 79)



# Understanding Digital Filters, Using Your Time Profitably, and More

RECENTLY GOT A HELPLINE CALL FROM SOMEONE WHO STRONGLY FEELS THAT THEY HAVE ONCE AND FOR ALL SOLVED THE CELLULAR-PHONE FRAUD PROBLEM. THAT SOLUTION WAS BASED ON THE USE OF HIS ELEGANT SYSTEM-software modification. The question was how to profitably market the concept. Well, maybe, or maybe not.

Without a closer look, and even if it did not have any obvious or hidden flaws, the chances are that this caller's simple solution would only further escalate the cell wars a notch. But that's not the problem.

The problem is that certain things can be sold by small-scale start-ups or independent individuals, while some can not. Whenever you come up with what you think is a solution to an industry problem, it seems to me that there are

three key questions you should ask:

- **Are you an industry insider?** Do you aggressively subscribe to all the field's trade journals, read its books, attend its shows, and network with its experts? Do you thoroughly *grok* the fundamental technical and marketing principles of the industry?

If not, the odds are overwhelming that you're developing a non-solution to a non-problem. You probably do not possess the skills or the tools to even understand the real-problem, let alone correct it. And that the "gotchas" here are certain to "git ya."

- **Does the field welcome innovation?** If the industry 1) has areas that are highly regulated; 2) has a complex infrastructure; 3) is controlled from a solidly entrenched oligopoly; or 4) requires major changes for your concept to fly, it is not a reasonable place for you to be spending your time and effort. Also, avoid investing time in fields populated by lawyers eager to eat innovators for lunch, or one that is subject to lawsuits, etc.

- **Can you sell six of them?** Your best concepts are those you can sell to real people who have real wallets in their back pockets, with real credit cards in them. If you cannot sell a few of your designs to your friends, there is no way you will ever sell lots of them to your enemies.

Let's look at some "for instances." If reasonably priced, your improved laptop battery would be instantly gobbled up as a sure-fire winner. But that very same battery technology for an electric car is pretty near certain to get ruthlessly stomped upon.

A new personal-airplane design is guaranteed to bankrupt you—every time. But a variant sold as a quarter-sized R/C model kit could be a very popular product, especially when it doubles as a video platform.

More to the point: A snap-on accessory that an end-user can attach to a phone to eliminate cellular fraud is workable. But fundamental changes in the cellular standards and distribution are not. At least not for most small scale startups or outside individuals.

Sure, it's real difficult not to get excited about a new concept. Long ago, I allowed low-pressure pneumatic

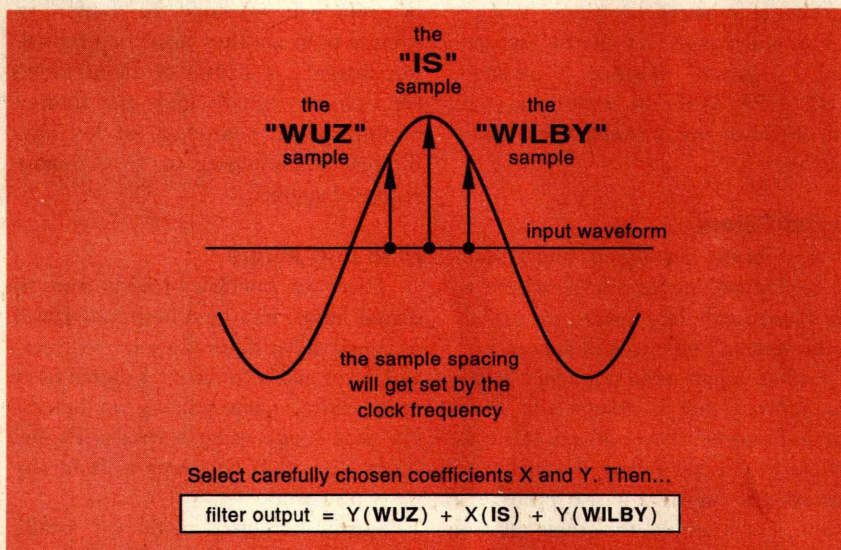


**FIG. 1—THE "TRISAMP"** is a useful building block that can let you understand, design, test, debug, and apply digital filters.



# DON LANCASTER

## ACTIVE FILTER COOKBOOK

## CMOS AND TTL COOKBOOKS

**INCREDBLE SECRET**

## LANCASTER CLASSICS LIBRARY

## LOTS OF OTHER GOODIES

## POSTSCRIPT SECRETS

## BOOK-ON-DEMAND PUB KIT

## THE CASE AGAINST PATENTS

## BLATANT OPPORTUNIST

**RESOURCE BIN 1**

## FREE SAMPLES

FREE US VOICE HELPLINE VISA/MC

# SYNERGETICS

**Box 809-NV**

**Thatcher. AZ 85552**

**(520) 428-4073**

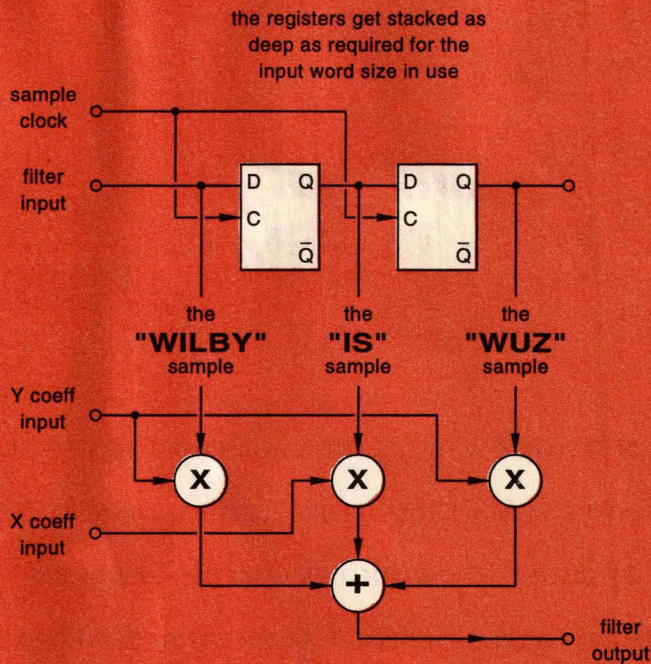


**FIG. 2**—DIGITAL FILTERS can be much more powerful than analog ones because they can look both forward and backward in time. The need for a "time machine" is avoided by using the shift-register scheme shown here.

robotics to gobble up all sorts of time and resources. And my magic sinewave development is currently using as much as twenty hours a day of my time. But, as hard as it is to do, you must focus on stuff that is technically challenging and still marketable by a small scale start-up if you are to be successful. Asking the fundamental questions outlined above ahead of time can save you lots of hours and grief and lets you focus your time and energy in better directions.

For much more on all this, see my *Case Against Patents* package, WHEN2PAT.PDF on [www.tinaja.com](http://www.tinaja.com), and, of course, my *Incredible Secret Money Machine*.

# Digital Filters

A filter is just some frequency-selective network that is designed to favor certain frequencies over others. It is usually used to isolate a desired signal or to improve the signal-to-noise ratio of a system. For example, the treble control on your hi-fi is a low-pass filter, the bass control is a high-pass filter, and AM radio tuning uses a bandpass filter.

Traditional filters were originally built with capacitors and inductors. Many of those were replaced long ago by active filters—combinations of resistors, capacitors, and op-amps that exactly fake inductors. You can find more details on that in my *Active Filter Cookbook*.

In contrast, a digital filter takes an existing pile of numbers and runs multiply-and-add calculations upon them to create a new pile of numbers whose behavior will, we hope, be “better” in some way or another than the original. For instance, a stream of digital video can become digitally high-pass filtered to improve its sharpness, or low-pass filtered for softening or to eliminate slanted “jaggies”.

## Plus and Minus

Special circuitry could be totally eliminated if the digital filtering gets done inside a stock microprocessor or a DSP digital signal processor.



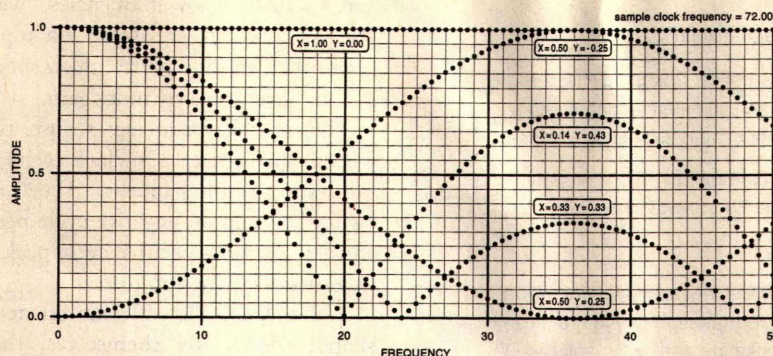


**FIG. 3—HOW A TRISAMP'S FREQUENCY RESPONSE varies when its X and Y coefficients are changed.**

Best of all, a digital filter can do certain tasks that end up being difficult or impossible when using classic analog designs. For one thing, in a sense, they can look forward and backward in time. That is, unlike capacitors and inductors, they can react to currents and voltages that are yet to happen; classic analog components can only react to things that have already occurred.

Examples here include "brick-wall" filters with extremely sharp cutoffs and linear-phase filters that attenuate a waveform's harmonics without any time-shifting distortion.

There are also disadvantages and limitations to digital filters. While they are a lot simpler than some may have you believe, they still are rather hard to understand.

You do already have to have your pile of numbers before you can filter them. Thus, A/D and D/A conversion might be needed in your system.

There is a really ugly property of digital filters called aliasing. If you sample any waveform less than twice per cycle, you might "fold over" and generate lower-frequency noise and artifacts. Very rarely, aliasing can be a valuable tool, one that lets you do digital mixing, downsampling, or a downconversion. But far more often, aliasing is a major nuisance that must be dealt with by pre-filtering.

Here's a rule to follow when working with digital filters: Input signals to a digital filter must get prefiltered so that zero energy exists above one-half of your sample frequency. That is, unless you have some really good reason to be doing otherwise!

The dynamic range of any digital filter is limited by several factors. Those

include your input and output word sizes, truncation errors, and any round-off errors.

Because you are often adding up very small differences between large values, the internal word size usually has to be much larger than that of the input or output. Thus, digital filters are much more suited to larger input signals than to very small ones.

Simpler digital filters apply integer math or fixed-point arithmetic. Such filters are faster and easier to implement, but have reduced dynamic range.

Exotic digital filters can use a full floating-point processing for all their math. While more accurate, floating-point filters often run much slower, either restricting the maximum input frequency or forcing you to move to non-real-time applications.

Finally, if your filter only works with a small number of samples, you might get into some ugly windowing problems. Softening the edges of a window or making sure that the edges happen where they don't cause problems are two

possible cures. Watch out for that windowing detail, or it will nail you every time.

## Trisamp Building Blocks

My approach in the *Active Filter Cookbook* was to use a basic analog building block called a second-order section. No matter how exotic your filter response, all you really ended up with was a pile of those cascaded sections. And each section only had two possible adjustments—the cutoff frequency and its damping.

Let's try something similar here. I'll call our basic building block a "trisamp," and it is shown in Fig. 1. Just as you can use and cascade second order analog sections, you can use and cascade trisamps.

A trisamp gathers in three samples of a waveform. Which I will call "wuz," "is," and "wilby." It then scales them and adds them all together by using this fairly simple rule:

$$\text{output} = Y(\text{was}) + X(\text{is}) + Y(\text{wilby})$$

Since a digital filter is a linear type of "thingy," it should not matter what frequency or what phase we use for our analysis. Thus, we can apply just one frequency at a time to determine our overall response and arbitrarily pick an "is" phase of 90 degrees.

For a single-frequency sinewave input, your output should be a scaled amplitude clone of your input. The output will be larger or smaller than the input, depending on the values and signs of X and Y, and upon the ratio of your input frequency to the sample-rate clock.

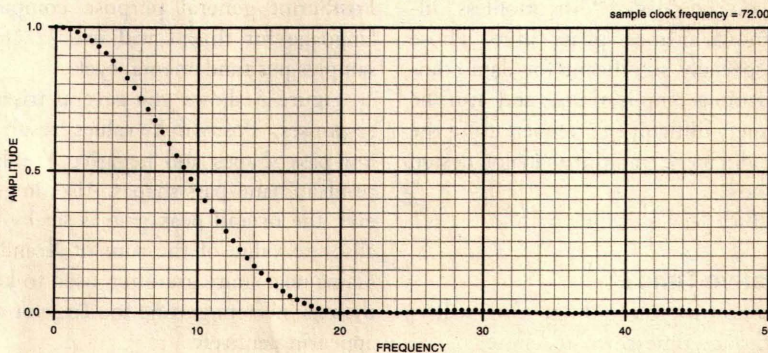


**FIG. 4—A LOW-PASS FILTER built by cascading three trisamps. This is a "distortionless" or linear-phase filter that is extremely difficult to build using older analog techniques. To simplify your final design, using ordinary algebra easily reduces three cascaded trisamps into a single, seven-sample "septsamp." Additional samples improve response shape.**



```
% PostScript triple cascaded trisamp digital filter designer v 2.04

% Copyright c 1996 by Don Lancaster and Synergetics, Box 809, Thatcher, AZ
% 85552 (520) 428-4073 http://www.tinaja.com All commercial rights and all
% electronic media rights are fully reserved. Reposting is expressly forbidden.

% For best results, improve with Guru Gonzo PostScript utilities. Enhanced and
% fully annotated version available as TRISAMP.PS on www.tinaja.com

% draw a graph:
110 350 translate 8 dup scale 0.03 setlinewidth 1 setlinecap gsave 0 0 moveto 51
{0 0 moveto 0 20 rlineto 1 0 translate} repeat stroke grestore gsave 0 0 moveto 21
{0 0 moveto 50 0 rlineto 0 1 translate} repeat stroke grestore 0.12 setlinewidth
gsave 3 { -0.5 0 moveto 50.5 0 rlineto 0 10 translate} repeat stroke grestore gsave
6 { 0 -0.5 moveto 0 20.5 rlineto 10 0 translate} repeat stroke grestore

/dot { newpath 0.150 0 360 arc fill } def % dot utility

/tripletrisamp {0 0.5 50 {/freq exch store 180 freq mul sampfreq 2 div div cos
coeffB mul 2 mul coeffA add /firsthold exch store firsthold abs 20 mul freq exch
dot 180 freq mul sampfreq 2 div div cos coeffD mul 2 mul coeffC add /secondhold
exch store secondhold abs 20 mul freq exch dot 180 freq mul sampfreq 2 div div
cos coeffF mul 2 mul coeffE add coeffC coeffD 2 mul add div /thirdhold exch store
thirdhold abs 20 mul freq exch dot firsthold secondhold mul thirdhold mul abs 20
mul freq exch dot} for} def

% //// demo - remove or alter before reuse. ////

/sampfreq 72 def % set sample clock frequency

/coeffA 2.0 4 div def % center of first trisamp
/coeffB 1.0 4 div def % pair
/coeffC 1.0 3 div def % center of second trisamp
/coeffD 1.0 3 div def % pair
/coeffE 1.0 7 div def % center of third trisamp
/coeffF 3.0 7 div def % pair

tripletrisamp showpage quit % do it and flaunt it
```

**FIG. 5**—THIS POSTSCRIPT TRIPLE TRISAMP exploration utility could make you an instant digital-filter-design expert. The code shown here can be easily expanded.

The X and Y values are known as coefficients. And while you could select different coefficients for “was” and “wilby,” that change would add or remove time delay to your response.

Forcing the coefficients for “was” and “wilby” to always be identical can give you the class of “distortionless” filters known as linear-phase filters. Those are especially significant for data communications applications, and can be extremely difficult to do when using the older and more traditional analog design methods.

Which leaves dealing with . . .

### Negative Time?

So how do you find out who “wilby” is without a time-travel machine?

Simply look one stage previous in the shift register scheme of Fig. 2, or access one sample address earlier in a memory data bank. This is sort of the same way

any vertically delayed scope lets you look at the waveform edge you have just triggered on.

Let’s look at the responses we can expect from a trisamp as we vary its coefficients and the input frequency. Naturally, I prefer to use the superb PostScript general purpose computer language for this. I will use 72 clock samples per fundamental cycle.

Figure 3 shows you several trisamp responses. Positive Y values result in low-pass shapes and negative Y values result in band-pass shapes. Also, in general, the overall peak gain is set by the absolute value of the sum of X and Y. Gains near unity are often used to keep the results from getting too large or disappearing entirely.

For instance, a Y value of zero and an X value of one simply copies the peak value to the output for a flat or an all pass response. Next, consider  $Y = 0.25$

and  $X = 0.50$ . At low frequencies, “wuz,” “is,” and “wilby” are nearly on top of each other, so they pretty much sum to 1.0 and give us nearly unity gain.

But at the frequency whose time period equals exactly 36 clock cycles, an interesting result happens. “Wuz” and “wilby” end up on negative cycle peaks, and “is” sits on a positive cycle peak. In other words, they sum to zero!

Other X and Y coefficients create the shapes shown. By themselves, those shapes may be interesting. But they aren’t all that useful. So, to get useful response shapes, you must cascade your trisamps.

Figure 4 shows a highly desirable linear-phase, low-pass filter made by cascading the three trisamps shown. Note the excellent stopband response. And the modest droop in the passband is fairly typical of linear-phase filters. Most important, there is zero excess phase shift to higher frequency harmonics. That property is very important in telecomm filters and for wave analysis.

Yes, you can easily re-graph this result in semi-log frequency-vs.-decibels for a more traditional-appearing, classic response plot. Among other features, that re-plot would make the stopband zeros more obvious.

Actually, nobody really cascades trisamps. Go through some simple algebra and you can quickly prove that any two cascaded trisamps are the same as a five-coefficient filter. And three cascaded trisamps are the same as a seven-coefficient filter. So you apply a pentsamp or a septsamp instead. All digital filtering amounts to is finding the right coefficients to use for the result you are after.

PostScript code to do a seven-coefficient filter made from three cascaded trisamps is shown in Fig. 5. You could easily use that routine to explore fancier digital-filter response shapes on your own. Just modify the coefficients with your favorite word processor or editor. Then send it to GhostScript or route it to almost any PostScript printer.

Lots more PostScript-as-language details are found on [www.tinaja.com](http://www.tinaja.com) For an amazing range of applications, PostScript can completely blow away the more traditional general purpose computer languages.

Incidentally, more coefficients are normally chosen for fancier shapes.





***Plug a Friend into***  
***Electronics***  
***NOW***<sup>®</sup>  
***and Save \$26.03\****

***This Christmas give an electrifying gift ... plug a friend into Electronics Now and brighten the whole new year! Whether electronics is your friend's livelihood or hobby, your gift will illuminate the whole spectrum of electronics throughout the coming year and provide a monthly reminder of your friendship.***

Electronics Now will keep your friend informed and up-to-date with new ideas and innovations in all areas of electronics technology ... computers, video, radio, stereo, solid-state devices, satellite TV, medical electronics, communications, robotics, and much, much more.

We'll provide great plans and printed circuit patterns for great electronic projects. In just the last few years, Electronics Now has presented amateur TV equipment, robots, computer peripherals, microcontroller programmers, test equipment, audio amplifiers, telephone projects, relay circuits, and much more.

PLUS ... equipment troubleshooting techniques ... circuit design ... reports on new technology and products ... equipment test reports ... in-depth coverage on computers, video, audio, vintage radio ... and lots more exciting features and articles.

SAVE \$26.03\* ... OR EVEN \$52.06\* ... For each gift of Electronics Now you give this Christmas, you save a full \$26.03\* off the newsstand price. And as a gift donor, you're entitled to start or extend your own subscription at the same Special Holiday Gift Rate—you save an additional \$26.03\*!

No need to send money ... if you prefer we'll hold the bill till January, 1997. But you must rush the attached Gift Certificate to us to allow time to process your order and send a handsome gift announcement card, signed with your name, in time for Christmas.

So do it now ... take just a moment to fill in the names of a friend or two and mail the Gift Certificate to us in its attached, postage-paid reply envelope. That's all it takes to plug your friends into a whole year of exciting projects and new ideas in Electronics Now!

\*Basic sub rate — 1 yr/\$19.97 2 yrs/\$38.97



## Names and Numbers

**American Institute of Organbuilders**  
PO Box 130982  
Houston, TX 77219  
(713) 529-2212

**Clement Engineering**  
PO Box 1086  
Severna Park, MD 21146  
(410) 268-6736

**Compu-Mart**  
899 Presidential, Ste. 110  
Richardson, TX 75081  
(800) 864-1155

**Dukane Ultrasonics**  
2900 Dukane Drive  
St Charles, IL 60174  
(708) 584-2300

**Genesis Microchip**  
2111 Landings Drive  
Mountain View, CA 94043  
(415) 428-4277

**Harris Semiconductor**  
Box 883  
Melbourne, FL 32902  
(407) 724-7000

**ICT**  
2123 Ringwood Avenue  
San Jose, CA 95131  
(408) 434-0678

**Mitel**  
2321 Morena Blvd., #M  
San Diego, CA 92110  
(619) 276-3421

**Qualcomm Inc**  
6455 Lusk Blvd.  
San Diego, CA 92121  
(619) 587-1121

**Redmond Cable**  
15331 NE 90th Street  
Redmond, WA 98052  
(206) 882-2009

**Schott**  
3 Odell Plaza  
Yonkers, NY 10701  
(914) 968-8900

**Seagate**  
920 Disc Drive  
Scotts Valley, CA 95066  
(408) 438-6550

**Synergetics**  
Box 809  
Thatcher, AZ 85552  
(520) 428-4073

**Thomson CFS**  
40G Commerce Way  
Totowa, NJ 07511  
(201) 812-9000

**Wale Apparatus**  
400 Front Street  
Hellertown, PA 18055  
(800) 334-WALE

**Western Reserve Games**  
21651 Tungsten Road  
Euclid, OH 44117  
(800) 531-1230

Typical hardware building-block chips offer four coefficients each. Those can get cascaded "wide" to handle twelve to sixteen or more coefficients. Or, they can be cascaded "deep" to handle the number of bits in a fixed-point word. Harris and Qualcomm are two big sources for these dedicated chips, but you can easily do the same thing with a PIC microprocessor.

I've been using digital filters as an important part of my magic-sinewave research. Magic sinewaves are my brand new way for simplifying and dramatically improving the efficiency of such products as variable-speed induction-motor drives, solar panels, and electric cars. You can find a lot more about them and all the new research opportunities they present on my Magic Sinewave shelf, which is in the [www.tinaja.com](http://www.tinaja.com) reference library.

### 5SiMX Hard Drives

As we saw a couple of months or so ago, the Hewlett-Packard 5SiMX is an ideal mid-range PostScript laser printer,

one well suited to book-on-demand publishing. Its many features include genuine Adobe PostScript Level II, 24 pages-per-minute print speed, a page-flipping duplexer, 11 × 17 capability, refillable toner cartridges (offering excellent economics), 600 DPI resolution, and photo halftone enhancements; and all the service manuals and parts are readily available.

It also has, at least in theory, a hard disk.

Scant few printer users appreciate how absolutely crucial a local hard disk is for a PostScript printer (though Apple and QMS have had them for years). First, your hard disk lets you store lots of fonts. Second, it lets you stash all of your book-on-demand files so you'll never have to tie up a network resending them. That same storage lets you do a run unattended for overnight BOD publishing.

The same goes in spades for often-used forms or patterns. When a diskless PostScript printer is first turned on, all of those needed font bitmaps have to be laboriously built up into a font cache.

Your first few printouts (and anything "new" after that) will always be very slow.

A local hard disk instead saves a font cache for you. There is normally not any speed-difference slowdown on your first few files.

Hard disks are also real useful for PostScript-as-language apps where they can serve as your primary I/O. They are also quite handy to log what is coming into your printer, to solve interface hassles, to convert formats, or to grab otherwise inaccessible data or commands. Once you have used a PostScript printer that offers a hard disk, it is unthinkable to ever again so much as walk through a room housing a printer that lacks one.

The only tiny 5SiMX problem is that the HP disk drive has been undeliverable—and it appears permanently so now as HP has gone completely out of the hard-drive business. Well, it turns out you can easily substitute your own hard drive—for as little as \$35—after you know and understand a few simple things.

Let's excerpt some key info from the HPs *LaserJet 5SiMX Developer's Quick Reference Guide*:

"The standard 2½-inch ATA IDE disk drive interface is supported. (ATA stands for 'AT Attachment, as in the IBM PC-AT bus. And IDE stands for Intelligent Drive Electronics.) This printer is designed to allow these drives to be mounted directly to the formatter board.

"The disk drive attaches to four standoffs. It is electrically connected via a ribbon cable.

"The Seagate ST9420AG is the disk that has been qualified to work in the LaserJet 5SiMX printer."

The developer's guide is available through HP Developers. My favorite source for custom cables is Redmond Cable. The oddball 2-millimeter bulk ribbon cable and connectors are sold by Digi-Key or Mouser (this is sometimes called a mini-IDE or "European" cable).

Bargain drives often show up in *Compu-Mart*, *Computer Hot Line*, and similar publications. Note that non-Seagate drives may be larger and have different mounting holes. Older and larger 3½-inch drives are most likely not worth the hassle. Besides needing excess supply current, their larger pinouts take a special adaptor.



## Navigation Resources

### Advanstar Communications

7500 Old Oak Blvd.  
Cleveland, OH 44130  
(800) 598-6008

### GPS World

859 Willamette St.  
Eugene, OR 97401  
(503) 343-1200

### Institute of Navigation

1800 Diagonal Rd., #480  
Alexandria, VA 22314  
(703) 683-7101

### ITS World

859 Willamette Street  
Eugene, OR 97401  
(503) 343-1200

### NASA Tech Briefs

41 E 42nd St., #921  
New York, NY 10017  
(212) 490-3999

### Navtech Books & Software

2775 S Quincy St., #610  
Arlington, VA 22206  
(800) NAV-0885

### SAE

400 Commonwealth Drive  
Warrendale, PA 15096  
(412) 776-4841

### Trimble

585 N Mary Avenue  
Sunnyvale, CA 94086  
(408) 481-8000

The last three digits of the Seagate part number are apparently its size. In the case of the unit referenced above, it is 420 megabytes.

Be extremely careful when you experiment here on your own! Any crossed cable can destroy both your drive and the printer electronics. Do not attempt to interface a SCSI drive. Unless you know all about fancy and expensive IDE to SCSI conversions. And, of course, never hot swap an IDE drive! Always turn power off.

On your PostScript software side, the drive is called "%disk0%." Fonts usually go in a fonts subdirectory. Although half a gig is vastly more storage than you are likely to need for this, there's one curious limitation: You are only allowed 1000 different files on your drive. Filenames can be one to 100-characters long. Nulls, backslashes, percents, end-of-file, and spaces are disallowed characters.

Again, much more on BOD in general can be found in my *Book-on-Demand Publishing Kit*.

## Navigation Resources

I just got a flyer from Advanstar Communications on their brand new bookstore. This one focuses on GPS Global Positioning System and GIS Geographical Info System texts.

Because of that flyer, and since it's been a while, I thought we might summarize several of the better navigation info sources as this month's resource sidebar.

A good place to start is with the Navtech Bookstore. Then go on to those shows and publications from the

Institute of Navigation. Two important trade journals in this area are *GPS World* and *ITS World*; the latter focuses on "Intelligent Transportation Systems."

Finally, here's a reminder that Trimble has a great nav tutorial it calls *GPS—A Guide to the Next Utility*. Hot links to several useful GPS and nav sources are also found on [www.tinaja.com](http://www.tinaja.com).

## New Tech Lit

New from Thomson-CSF, a new data book on their CCD Image Sensing Products. From Mitel comes an analog and digital Telecomm data book.

The PC1802 Stereo Enhancement Processor chip from ICT uses 3-D psychoacoustics to "spread out" the apparent source of stereo sounds. The new GMVLD10, from Genesis Microchip, is a real-time video-line doubler integrated circuit that is useful for de-interlacing. Uses for it include TV-to-monitor conversions and video walls.

The MIM Module from Clement Engineering can be useful for balloon telemetry and other remote sensing apps. Original jukebox manuals are sold by Western Reserve Games.

Some info on power ultrasonics appears in the *Waves* newsletter from

## NEED HELP?

Phone or write all your US Tech Musings questions to:

Don Lancaster  
Synergetics  
Box 809-EN  
Thatcher AZ, 85552  
Tel: 520-428-4073

US email: [don@tinaja.com](mailto:don@tinaja.com)  
Web page: <http://www.tinaja.com>


Dukane. Bunches of traditional pipe-organ building info gets sold by the American Institute of Organbuilders, who offer various newsletters and conferences.

Two unusual glass topics: Glass paints are newly available through Wale Apparatus, while Foturan is a new photo-etchable glass product line from the Schott folks.

That long unclaimed \$10,000 prize for anybody able to convincingly demonstrate dowsing techniques to locate a buried water pipe has just been upsized to \$640,000. Contact [www.randi.com](http://www.randi.com) for details. There's more on pseudoscience bashing in general on [www.tinaja.com](http://www.tinaja.com)

For more on the fundamentals of digital integrated circuits, read my *CMOS Cookbook* and *TTL Cookbook*, either by themselves or as part of my bargain *Lancaster Classics Library*, per my nearby Synergetics ad.

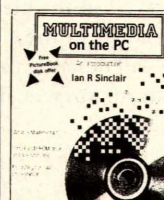As usual, many of the mentioned resources appear in our Names & Numbers and Navigation-Resources sidebars. A reminder that a no charge technical helpline is available per the Need Help box. Funding and time constraints strictly limit that service to U.S. callers only. Let's hear from you! **EN**



## MULTIMEDIA on the PC!

What is Multimedia? What can it do for you? It can do lots of nice things! This 184-page book helps you create your own multimedia presentation.

Multimedia applications by people like you can revolutionize educational and business applications as well as bring more FUN, FUN, FUN into your leisure computer activities.

Mail coupon to:

**Electronics Technology Today, Inc.**

**P.O. Box 240**

**Massapequa Park, NY 11762-0240**

Please send me my copy of *Multimedia on the PC* (PCP120). I enclose a check or money order for **\$18.95** to cover the book's cost and shipping-and-handling expenses. NY state resident must add local sales tax.

Name

Address

City  State  Zip

All orders must be paid in U.S. funds only. Sorry, no orders accepted outside of USA and Canada. Please allow 6-8 weeks for delivery. MA02

November 1996, Electronics Now



# Troubleshooting VCR Tape Path Alignment

**W**HEN EVERYTHING IS SET UP RIGHT IN A WELL-DESIGNED VCR, IT WILL RECORD AND PLAYBACK CLEAR, SHARP PICTURES. BUT EVEN MINOR MISADJUSTMENTS IN THE TAPE PATH COULD SEVERELY IMPACT THE QUALITY OF THE

video or the audio, or both. If there are severe misadjustments in the tape path, the tape itself can be damaged.

Figure 1 diagrams the tape path in a Hitachi VHS VCR. It is typical of, though not identical to, the path that VHS recording tape follows in many modern VCRs. The five key areas in the tape path that require adjustment to ensure that the tape travels in the proper vertical plane are shown in the diagram. As we go on we will describe each adjustment point and its importance in a properly aligned tape path.

## Reel Table Height

The first tape-path point in Fig. 1 is where the reel-table height is set. That setting determines the height of the tape as it is taken up or supplied from either the supply or take-up reel tables. If either table height is misadjusted, making the tape lower or higher than normal, the edge of the tape can be damaged. Figure 2 shows how a misadjustment there can cause tape curling. In that example the reel table is too high, affecting the height of the tape at the entry point to the guide. The result is tape curling at the top edge of the tape, which can permanently destroy or distort the audio or control tracks on the tape. As shown in Fig. 3, those tracks are at the top and bottom edges of the tape. That kind of problem shows up as dis-

torted audio, with level changes; intermittent speed changes; or tracking problems.

Another problem caused by improper reel-table height is that it could cause the tape to be rewound into its VHS cassette improperly. That rewinding can

cause the tape to bind, and in some instances stretch, causing symptoms similar to those of tape-edge damage.

## Tape Tension

Tape tension is the applied force of the tape at some particular point along the tape path of the VCR. In VHS VCRs, tape tension is regulated to insure video signal interchangeability between VCRs. Incorrect tape tension produces a number of different playback problems. Those problems show up as:

- **Tape Skew**—flagging or bending of the picture at the top of the viewing

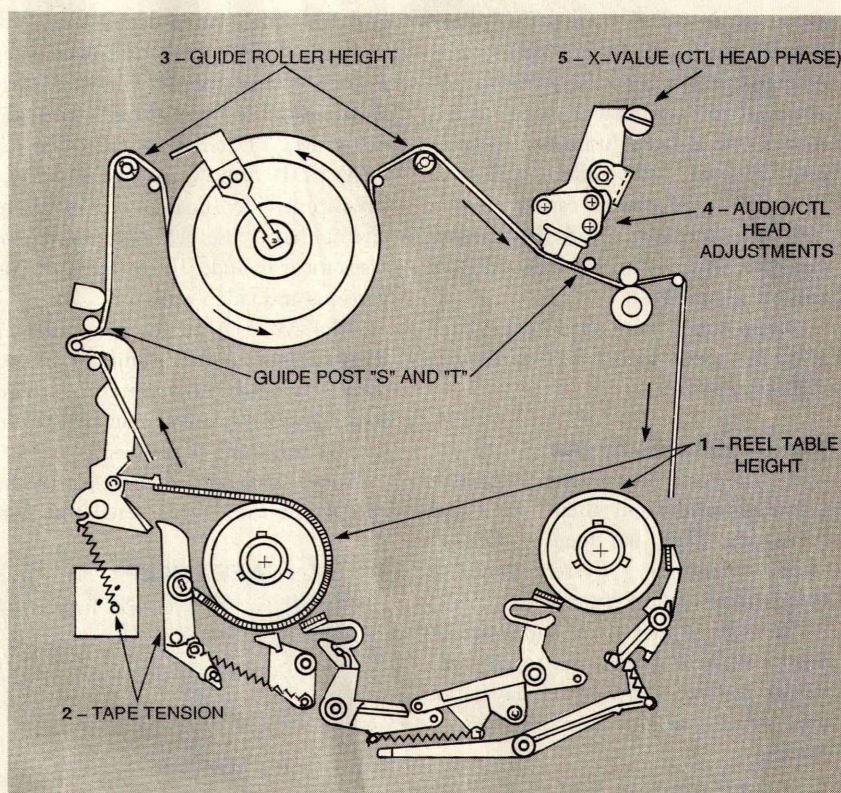


**FIG. 1**—THE VHS TAPE PATH shown here is from a Hitachi unit, but it is common to many VHS VCR's. Note the five major adjustment points.

\*FROM HITACHI Hi-lite Hitachi Home Electronics (America) Inc. Suwanee, GA



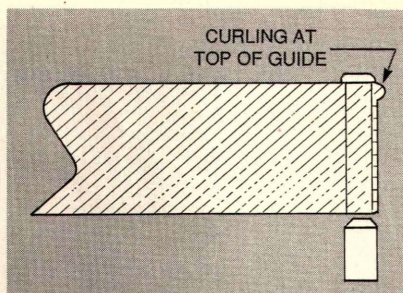


**FIG. 2—TAPE CURLING AT THE TOP of the tape guide can be caused by a misadjusted reel-table height. If severe, it can physically damage the tape.**

screen. That vertical bending is caused by horizontal time-base errors in the horizontal-sync pulses on the tape. Correct tape tension reduces horizontal time-base errors.

- **Intermittent Blue Screen**—triggered by the loss or excessive distortion of the playback video-sync signals. System-control microprocessors often monitor the sync signal, sending control codes to the character generator, which activates the blue screen whenever abnormalities are detected.

- **Upper Cylinder, Tape-Guide Damage**—severe, excessive tape tension can actually damage the upper cylinder and tape guides, causing surface scarring or excessive head wear.

Proper tape tension is clearly one adjustment that must not be overlooked. It is maintained throughout the tape path by a tension band, which is wound around the supply-reel table that continuously controls the braking force applied to the table. That braking force provides a variable resistance to the rotation of the supply reel when the tape is being withdrawn from the cassette-supply hub. To change the braking

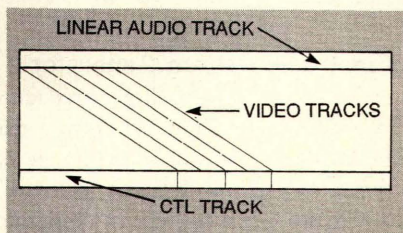


**FIG. 3—THE AUDIO SIGNAL SITS ALONG the top edge of the VHS tape. Control signals are placed along the bottom edge.**

force, a tension band is connected to a tension-arm assembly using a pole that is in continuous contact with the tape as shown in Fig. 4. The tape itself determines the pole position relative to the tape tension at any given point in time. As the tape is pulled from the supply-

reel table with more (or less) force, the pole position changes in proportion to the force, and the band around the supply-reel table alternately loosens (with increased tape-pull force) or tightens (with decreased tape-pull force) to maintain a constant back tension (resistance) against the tape.

## Guide Rollers

Figure 5 shows two additional components that play an important part in determining the position of the tape as it travels through the tape path. Since no two VCRs have precisely the same mechanical path for tape travel, the supply and take-up guide-roller heights are adjustable to maintain interchangeability when playing back prerecorded video-cassettes. The guide rollers determine the height of the tape at the entrance and exit of the video-drum assembly, and control the tape travel across its surface. That ensures the correct positioning of the video head with respect to the video signals recorded on the tape (particularly the proper placement of the video-sync signals), and the point at which the video heads were switched from CH1 to CH2 during the initial recording.

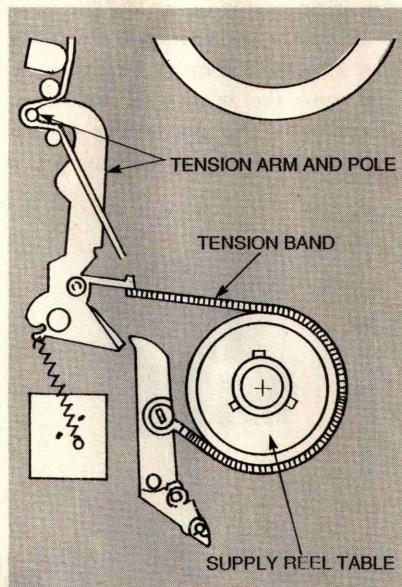


**FIG. 4—TAPE TENSION MECHANICS** are illustrated here. The tension band does most of the work.

Figure 6 shows what happens if a supply-guide roller is misadjusted. Note the noise bar that appears at the top of the screen. The particular guide roller that is misadjusted, and the degree of misadjustment, determines the number of noise bars and where they appear on

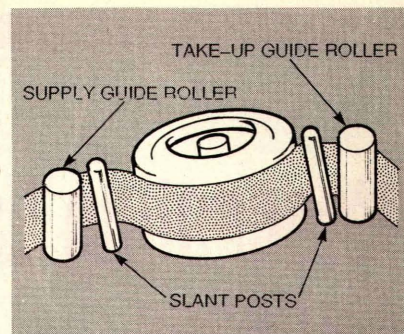


**FIG. 5—TWO GUIDE ROLLERS**—one before the video-drum assembly, one after—determine the tape position as it travels across the video heads.

the screen. A misadjusted guide roller can also cause tape curling, which results in distorted audio and distorted picture (noise bars, vertical jitter, and intermittent blue screen).

## ACE Head

The ACE-head assembly is shown in Fig. 7. It is comprised of three heads that together support the audio and servo functions of the VCR. Those are:

- **Audio Erase Head**—a high-frequency AC bias current flows through the erase head to remove any previously recorded audio signal.

- **Linear Audio Head**—records and plays back the linear audio signal.

- **Control Track Head**—records a 30-kHz signal onto the tape to form a video-head reference. When a tape is played back, the video-head phase is aligned with respect to that recorded control signal.

The ACE head is adjusted to assure proper playback of the linear audio signal and to insure proper tracking when playing back prerecorded tapes. When adjusting the ACE head assembly, two of

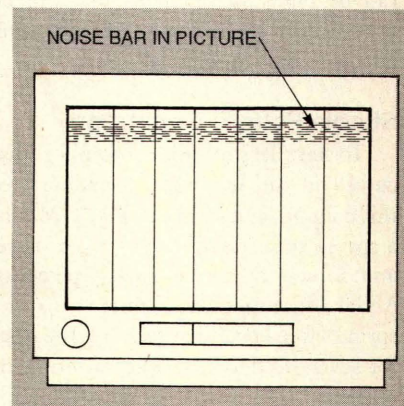


**FIG. 6—THE NOISE BAR THAT APPEARS** in the picture can be caused by a misadjusted guide roller.

continued on page 72 **69**



# Generating Laser-Light Patterns

**T**HIS MONTH, WE ARE GOING TO TURN OUR ATTENTION TO THE WORLD OF GEOMETRIC PATTERNS AND DESIGNS. THE LASER MARKET IS TEEMING WITH EQUIPMENT, RANGING FROM SIMPLE X-Y AXIS UNITS AND SCANNERS TO

elaborate, computerized professional controllers. All are designed to manipulate one or more laser beams into designs, patterns, moving artwork, lettering, or even sheets of light.

Such equipment is remarkable in terms of what it does, but costs start in the \$100 range for the most basic set-up and go up to \$15,000 and more for highly sophisticated machines.

While such specialized professional equipment is wonderful to work with, it is overkill for our experimentation purposes, and its cost puts it out of reach for many. But that doesn't mean that we can't experiment with laser special effects. Let's take a look at some of the simple and inexpensive equipment that can be built and methods that can be used to produce many of the same effects as the commercial units.

## Simple Pattern Generators

To start, let's re-visit a set-up first discussed in the July 1996 installment of this column, and shown in Fig. 1. Mount a spring to a stand, as illustrated there, and attach a 1-inch-square piece of Mylar or top-surface mirror to the spring's free end. That set-up is the basis for several different simple pattern generators.

One tip when working with springs is that the action can be adjusted by expanding or contracting the coil. As a

general rule, a spring becomes springier when stretched. Use that principle to control the amount of reaction to touch or vibration.

Once the set-up is assembled, aim your laser so the beam reflects off the Mylar or mirror onto a flat, light-colored surface, and then give the spring a tap. That tap will make the spring oscillate, and the beam will follow suit. Thanks to the persistence-of-vision characteristics of the human eye, the

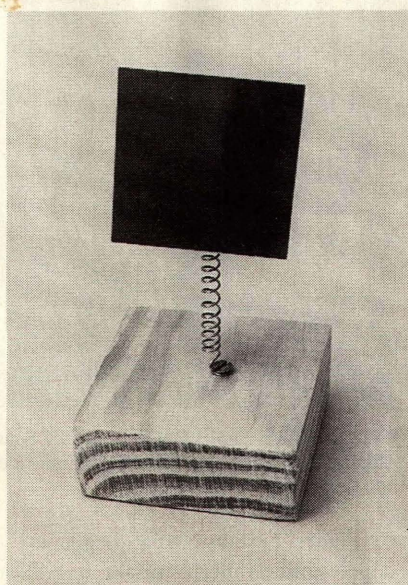


**FIG. 1**—A SQUARE MYLAR REFLECTOR attached to a spring that is anchored to a block of wood is one of the most basic laser-light reflectors.

## WARNING!!

This article deals with and involves subject matter and the use of materials and substances that may be hazardous to health and life. Do not attempt to implement or use the information contained herein unless you are experienced and skilled with respect to such subject matter, materials and substances. Neither the publisher nor the author make any representations as for the completeness or the accuracy of the information contained herein and disclaim any liability for damages or injuries, whether caused by or arising from the lack of completeness, inaccuracies of the information, misinterpretations of the directions, misapplication of the information or otherwise.

rapid movement of the spot generates random patterns and designs on the surface.

Repeat that step several times. Note that the patterns are never exactly the same twice. A blast of air or strong vibration can also vibrate the spring and create new light effects. Experiment with different forces and make note of what happens.

## Electronic Pattern Generator

If you set up a small gear-reduction motor, rigged with an arm (say, a nail, for example) that will gently nudge the spring on each revolution, you'll have a way to produce more repeatable patterns for longer periods of time. The photo in Fig. 2 shows one way that can be done.

An electromagnet or solenoid can also be used to pulse the spring and move the reflector. Those devices can be driven from the output of an electronic timer that is also used to control the frequency of the pulse. Figure 3 shows a suitable circuit for a simple timer.



For more dramatic effects, use a dual timer, like the one shown in Fig. 4. In that circuit, first one electromagnet, then the other, is activated, and the sequence repeats. If the two electromagnets are placed at right angles to each other, a north-south, east-west movement can be established. That movement can produce some very interesting designs, especially if you vary the oscillation rate by changing the capacitance and resistance values.

### Motorized Pattern Generators

Motors and mirrors make an excellent combination for generating graphics.

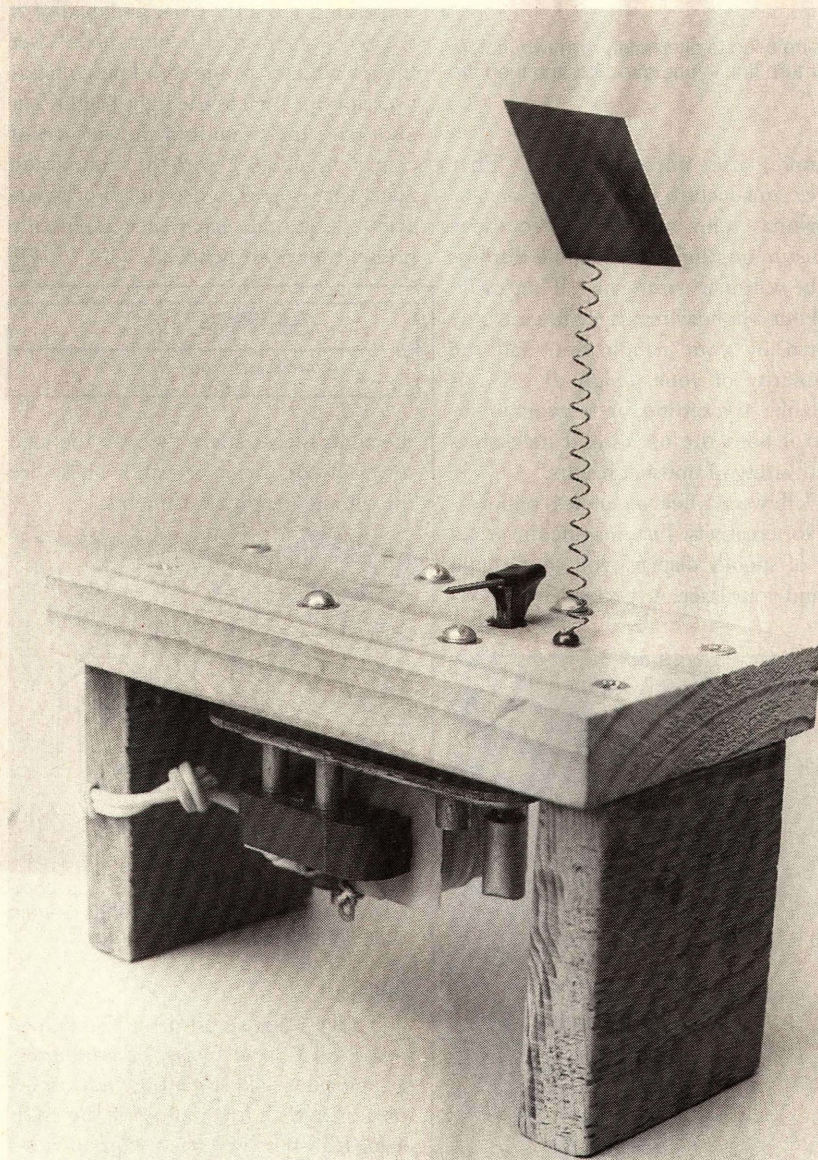


**FIG. 2**—FOR REPETITIVE VIBRATIONS, this simple set-up works well. A small gear-reduction motor rotates a nail, which strikes the spring one time each revolution. That rotation creates a repetitive movement in the reflector.

Attach reflective surfaces to the shafts of the motors. Then arrange the assemblies at various angles to each other. Now direct the laser beam between the mirrors and onto a screen. As the motors turn the mirrors, additional angle changes occur that vary the pattern.

Figure 5a shows a variation of the circuit in Fig. 4 that can be used to control a pair of motors. When the motors are connected to the circuit as shown in Fig. 5b, it will turn the individual motors on and off. If, on the other hand, you use the arrangement shown in Fig. 5c to control a single motor, it will make that motor first rotate in one direction and

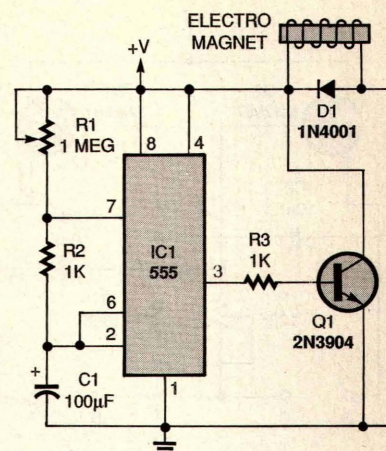


**FIG. 3**—A SIMPLE TIMER built around a 555 gives you a switching electromagnet to use to create laser-light patterns.

then the other. That set-up has all kinds of useful applications.

If you want to add yet another variable, you can provide a speed control by connecting a 5000-ohm potentiometer in series with the motor and power supply. Another variation would be to replace the flat mirrors with either convex or concave surfaces. One last area to consider is reflecting the laser beam off liquid surfaces such as water, oil, paint, etc. Different beam angles and vibrations of the substance being used as the

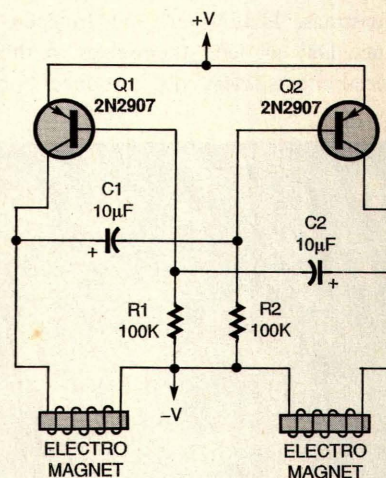


**FIG. 4**—IF THE ELECTROMAGNETS in this dual-timer circuit are arranged perpendicular to each other, a north-south, east-west motion can be established.

reflector can produce some delightful and interesting results.

It is obvious that a nearly endless variety of effects could be produced by making minor or more extensive



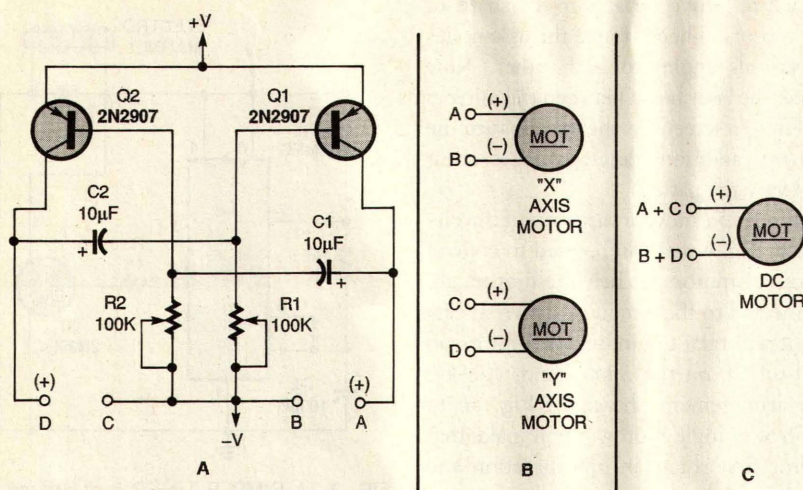


**FIG. 5—THE MOTOR-CONTROL CIRCUIT (A)** can be used to alternately turn two motors on or off (B). It can also be used to make one motor turn first in one direction and then the other (C).


changes to the basic set-up. Spend some time experimenting with the ideas presented, as doing so is a valuable source of knowledge.

### Holiday and Other Displays

So, aside from special effects at rock concerts, what practical applications are there for what we have learned? Well, how about using lasers to create holiday displays that would be the talk of the neighborhood. Holidays, such as Christmas, Halloween, and Independence Day all lend themselves to the special effects lasers could produce. For

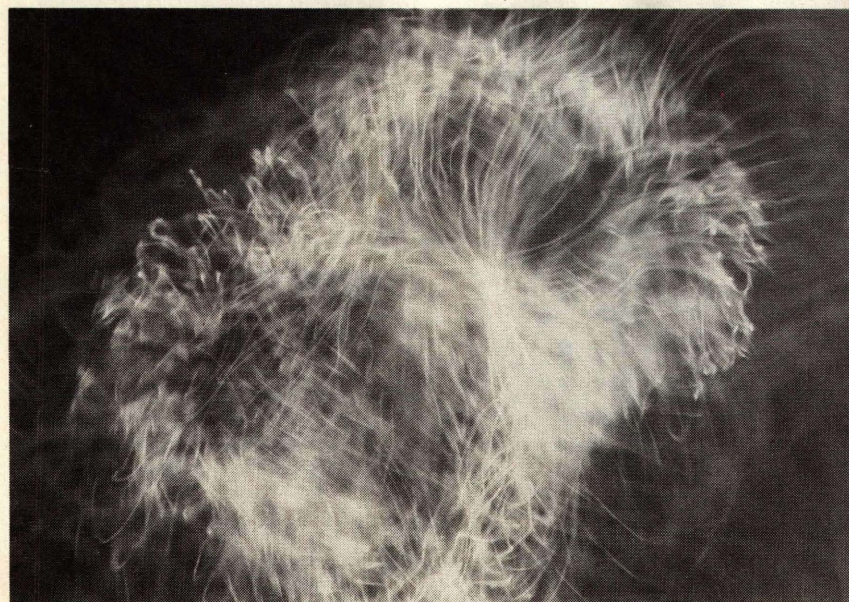example, use mirrors, lenses, fiber optics, and such to uniquely personalize Christmas trees and other decorations with stunning light shows. The displays can be stationary or moving. They could spell out a holiday message. You are only limited by your imagination and the complexity of your design. If a PC is available, try setting up a program to control both the optics and mechanics for a variety of unusual results.

Halloween offers an endless opportunity for creativity. Just imagine the selection of spooky displays you could build around your laser. A spectacular demon-



**THIS IS ONE EXAMPLE** of the kinds of light patterns that you can create using the information in this article.

stration for the Fourth of July could be assembled with the help of mirrors and motors to simulate fireworks. Let your imagination loose and when you do come up with a great idea, put it down on paper and send it to **Electronics Now**, Laser-Experiments Editor, 500 Bi-County Blvd., Farmingdale, NY 11735, or simply e-mail to [lartronics@aol.com](mailto:lartronics@aol.com).

While on the subject of gaining attention, why not take a look at the possibilities for advertising. A swirling, pulsating light show projected on a billboard or a showroom ceiling or wall will immediately attract people passing by. In addition to the movement, there is something about the color and quality of the red light from a helium-neon laser that is difficult to ignore. The collimation not only makes the light bright, but also gives the beam and the surfaces it comes in contact with a shimmering effect that is hard to describe. For whatever reason, the experience is visually pleasant for most people. **EN**

## SERVICING

*continued from page 69*

the adjustments affect the way the tape travels across the tape path. These are the tilt and height adjustments.

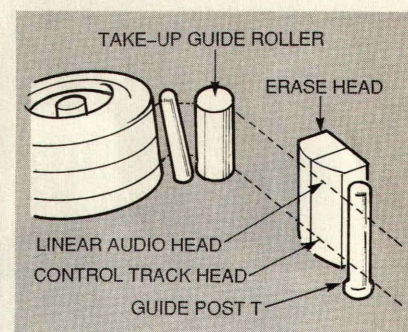


**FIG. 7—ACE-HEAD ASSEMBLY** is composed of three separate heads—audio erase, linear audio, and control track.

### X-Value

The X-value adjustment, also known as the CTL head phase, or tape-interchangeability adjustment, is used to set the position (horizontally) of the ACE head. It insures that the recorded video signal and control-signal phase relationship is maintained when playing back tapes from different VCRs. You can be sure that tracking linearity is correct when the X-value is properly set. **EN**



## EQUIPMENT REPORTS

continued from page 18


pressure or you can enter a new user. Each new user gets their own password and set of records. If you want, you can set the upper and lower pressure limits for each measurement—the smaller the range, the quicker each measurement can be made.

With everything connected and the software running, you simply follow software prompts to wrap the cuff around your arm, tighten the air valve on the bulb, start pumping, stop pumping and wait, and then to loosen the valve and release the air. The process takes about 30 seconds. All results appear on-screen and can be saved or printed.

The DynaPulse measures blood pressure in much the same way as a physician does. The inflatable cuff presses on the artery in your arm to the point where blood stops flowing. Then, as pressure is released, blood starts flowing at some point. At that point, the blood swirls in a turbulent flow causing a sound a doctor can hear with a stethoscope, and variations in pressure that DynaPulse can detect. The point where blood starts to flow is measured as the higher pressure point (systolic). At some point as pressure is released, the turbulence ceases; that's the lower pressure point (diastolic).

While it will not (and should not) replace a physician, DynaPulse is excellent for medical screenings by qualified personnel, or for home use to keep track of your blood pressure between doctor's visits. It also makes it very easy to store your results where they will never get lost. You can display long-term trends to monitor the effects of diet, exercise, medication, and so on (again, any diet or exercise regimen should first be discussed with and approved by your physician). Whether you're keeping track of just yourself, your whole family, or an entire organization, the DynaPulse 200M simplifies the task of taking and storing blood-pressure readings.
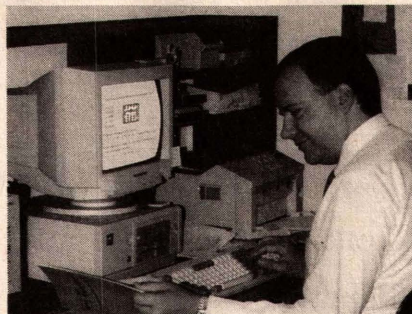
## EARN YOUR B.S. DEGREE IN COMPUTERS OR ELECTRONICS



### By Studying at Home

Grantham College of Engineering, now in our 46th year, is highly experienced in "distance education"—teaching by correspondence—through printed materials, computer materials, fax, modem, and phone.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand but complete and thorough lesson materials, with additional help from our instructors.

Grantham offers three separate distance-education programs, leading to the following accredited degrees:

- (1) The B.S.E.T. with Major Emphasis in Electronics.
- (2) The B.S.E.T. with Major Emphasis in Computers.
- (3) The B.S.C.S. — the Bachelor of Science in Computer Science.

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Write or phone for our free catalog. Toll free, 1-800-955-2527, or see mailing address below.

Accredited by  
the Accrediting Commission of the  
Distance Education and  
Training Council

**GRANTHAM**  
College of Engineering  
Grantham College Road  
Slidell, LA 70460

## You can Build Gadgets! Here are 3 reasons why!




### ☐ BP345—GETTING STARTED IN PRACTICAL ELECTRONICS \$5.95

If you are looking into launching an exciting hobby activity, this text provides minimum essentials for the builder and 30 easy-to-build fun projects every experimenter should toy with. Printed-circuit board designs are included to give your project a professional appearance.
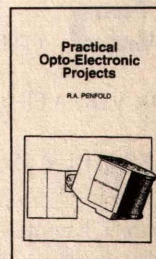
### ☐ BP349— PRACTICAL OPTO- ELECTRONIC PROJECTS \$5.95

If you shun opto-electronic projects for lack of knowledge, this is the book for you. A bit of introductory theory comes first and then a number of practical projects which utilize a range of opto devices, from a filament bulb to modern infrared sensors and emitters—all are easy to build.



### Practical Electronic Music Projects



### ☐ BP363— PRACTICAL ELECTRONIC MUSIC PROJECTS \$5.95

The text contains a goodly number of practical music projects most often requested by musicians. All the projects are relatively low-in-cost to build and all use standard, readily-available components that you can buy. The project categories are guitar, general music and MIDI.

Mail to:  
**Electronic Technology Today, Inc.**  
P.O. Box 240  
Massapequa Park, NY 11762-0240

### Shipping Charges in USA & Canada

|                               |                               |
|-------------------------------|-------------------------------|
| \$0.01 to \$5.00.....\$2.00   | \$30.01 to \$40.00.....\$6.00 |
| \$5.01 to \$10.00.....\$3.00  | \$40.01 to \$50.00.....\$7.00 |
| \$10.01 to \$20.00.....\$4.00 | \$50.01 and above.....\$8.50  |
| \$20.01 to \$30.00.....\$5.00 |                               |

Sorry, no orders accepted outside of USA and Canada. All payments must be in U.S. funds only.

☐ Number of books ordered.

Total price of books.....\$ \_\_\_\_\_  
Shipping (see chart).....\$ \_\_\_\_\_  
Subtotal.....\$ \_\_\_\_\_  
Sales Tax (NYS only).....\$ \_\_\_\_\_  
Total enclosed.....\$ \_\_\_\_\_

Name.....  
Address.....  
City.....State.....ZIP.....

Please allow 6-8 weeks for delivery.

Only You Can Prevent Forest Fires.

Ad  
Council





# Microphone Basics

**S**OUND IS GENERATED THROUGH A SPECIFIC MECHANICAL PROCESS. THAT IS, SOME PHYSICAL DEVICE MOVES OR VIBRATES, IN TURN MOVING THE AIR AROUND IT. ONE SIMPLE EXAMPLE IS A TUNING FORK. IF YOU HIT THE TUNING FORK

with a hammer (see Fig. 1), the fork vibrates at one specific frequency determined by its size and shape. The vibrations of the fork move the air around it. When those movements reach your ear, they are converted into electrical energy and sent to your brain to be processed and interpreted. (Of course, there is a lot more going on here than what we've just outlined; but, for our purposes, this simplified explanation will suffice).

Well, that process could also be used to describe how a microphone works. Like the ear, all microphones are sound conversion devices—they take sound and change it into electrical energy. There are three basic steps in this process:

1. Sound waves move the diaphragm inside the microphone.
2. The voice coil also moves, since it is attached to the diaphragm.
3. When the voice-coil moves, electrical energy is generated in the coil since it is located inside the microphone's magnet structure (magnet and magnetic housing).

The kind of microphone just described, shown in Fig. 2, is a dynamic or moving-coil type. The sound wave that reaches the microphone must be strong enough (or, rather, loud enough) to move the mass of the diaphragm and the coil assembly. That type of microphone works well, but does have some limita-

tions. It usually generates a small peak, sometimes called presence, somewhere between 2 and 5 kHz. Extremely-low and extremely-high frequencies can also give dynamic microphones some trouble. However, dynamic microphones are very durable and do not require any special handling. That's why they are so commonly used.

The amount of electrical energy that a microphone can put out partly depends on the amount of acoustical energy that reaches its transducer. In general, the louder the sound, the greater the electrical energy the microphone will produce, but there are limiting factors—the maximum possible movement of the voice coil for one.

Sound that we hear is usually measured in dB SPL (sound pressure level). That measurement ranges from 25-dB SPL (the level in a quiet broadcasting studio for recording music) to 140-dB SPL (a 50-HP siren). An average full symphony or orchestra has a dynamic

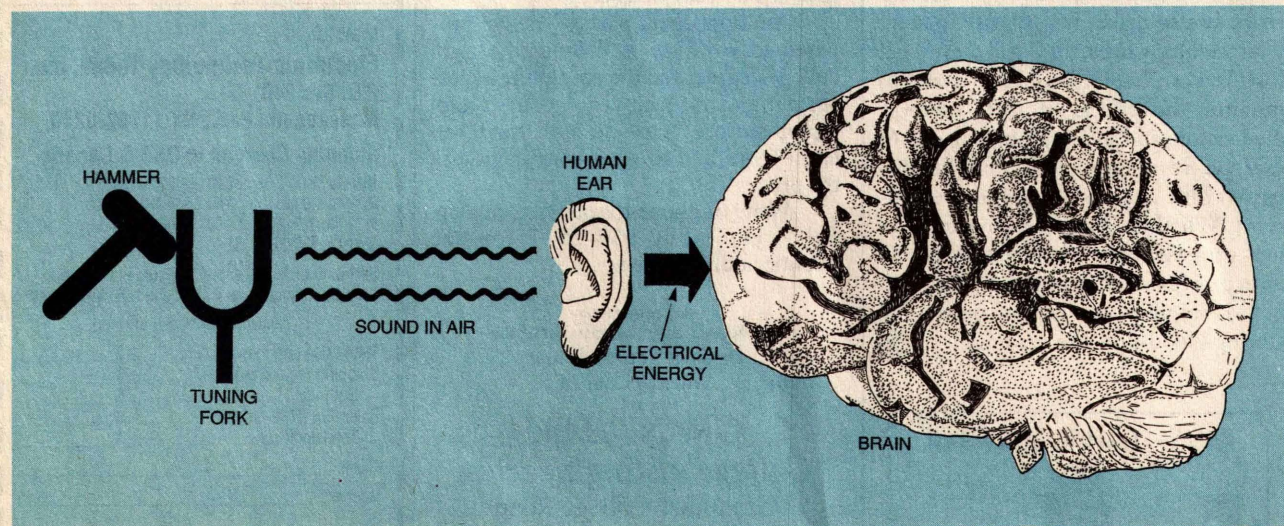


FIG. 1—HOW SOUND IS GENERATED. Striking a tuning fork is the method illustrated here.



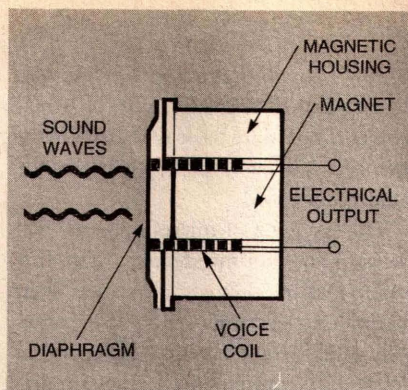


**FIG. 2—MICROPHONES CONVERT** sound waves into electrical signals.

range of 20 to 100 dB. The human ear has a dynamic range of about 120 dB, which is a ratio of a trillion to one. Analog recording has a 60-dB range (a million to one). Digital recording has a range of 90 dB (a billion to one).

As you can see from the above, the human ear is a very fine instrument indeed and should be treated with respect. Therefore, a microphone that can convert the air movement into an electrical signal within the very large dynamic range of the ear has a difficult job, at best.

### Microphone Efficiency

Microphones work best when they are positioned as close as possible to the sound-generating source. As shown in Fig. 3, the voltage produced by a microphone falls off with the inverse square of the distance. Put another way, the voltage the microphone produces increases geometrically as the distance from the sound source decreases. However, there is a limit. If the microphone is too close to the sound source, there is a proximity effect that causes the low frequencies to

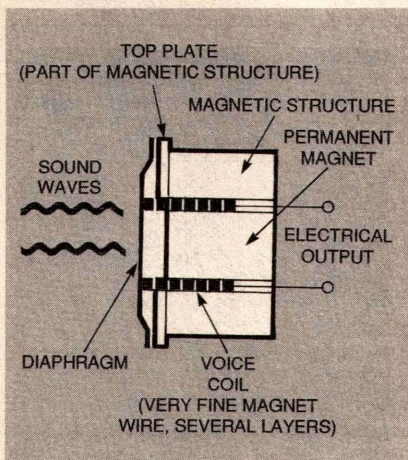


**FIG. 4—THE BASIC DYNAMIC MICROPHONE.** It is probably the most commonly used variety.

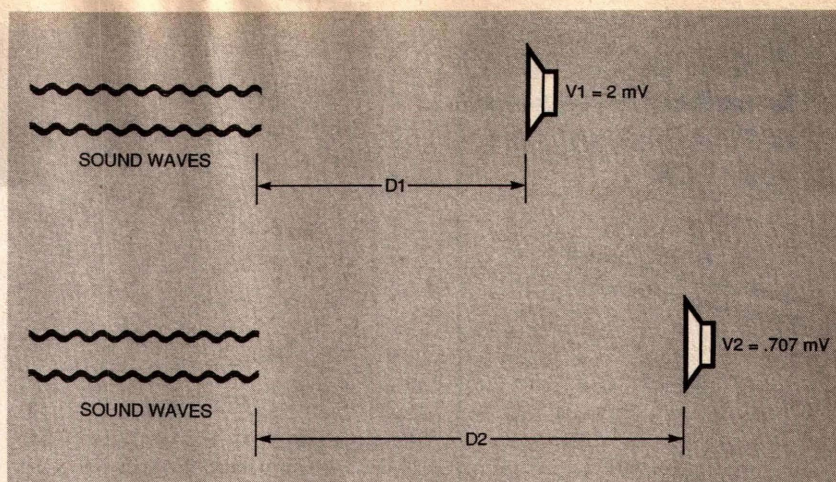


**FIG. 3—A MICROPHONE'S OUTPUT FALLS OFF** as it gets farther away from the source of the sound.

have a greater build-up than the high frequencies.

It is important to realize that microphones are never 100% efficient (their precise efficiency is not important to this discussion), and many factors come into play to reduce efficiency still further. For example, even temperature and humidity are important factors in the sound-reproduction process. That is one reason why studio recording is ordinarily very uniform, while remote recording can be quite variable. It is also why something that worked once might not seem right at another time. Most of those problems can be solved, but microphone users need to be aware that they can and do occur.

### Types of Microphones

There are several different types of microphones. The first and most common is the dynamic microphone that we have been talking about. It has a small diaphragm with a coil of magnet wire

attached to it (see Fig. 4) that sits in the field of a permanent magnet.

The electret condenser type is the next most popular in today's marketplace. It is a permanently charged capacitor type with an FET amplifier built in. It is shown in Fig. 5.

Another type of microphones is the capacitor type; it is the forerunner of the electret type. Its major drawback is that it needs a power supply to charge its plates. An RF capacitor microphone is another quality way to convert sound waves into an electrical signal.

### Acoustical Characteristics

Next, let's look at the acoustical characteristics of microphones, in order of their popularity. Figures 6, 7, and 8 are polar diagrams that show the pickup patterns of various microphone varieties. All three have some common elements and all are for a 1-kHz signal. At other frequencies the patterns might be different.


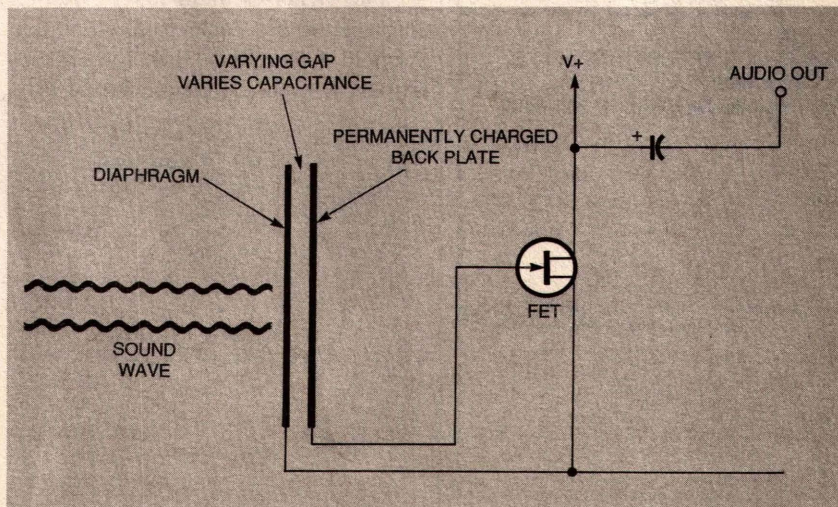


**FIG. 5—AN ELECTRET CONDENSER MICROPHONE** features a built-in FET amplifier.

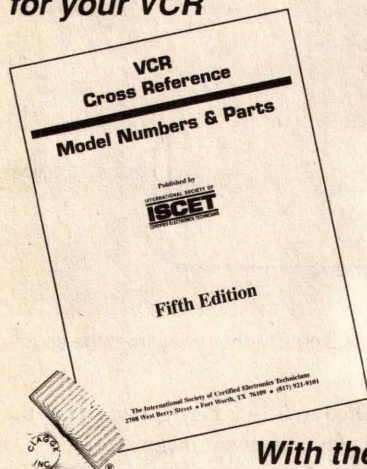

## VCR Cross Reference

**NOW Find the right Part  
for your VCR**



### With the ISCET VCR CROSS REFERENCE

This 119-page reference contains both model and part-number cross-references updated to include 1994 units.

VCR's are made in a few factories from which hundreds of different brand names and model numbers identify cosmetically-changed identical and near-identical manufactured units. Interchangeable parts are very common. An exact replacement part may be available only a few minutes away from you even though the manufacturer supplier is out-of-stock. You may be able to cannibalize scrap units at no cost!

The ISCET VCR Cross Reference is pre-punched for standard loose-leaf binding. . . \$38.00 plus \$3.00 for shipping for each Reference.

**Claggk Inc.  
VCR CROSS REFERENCE OFFER  
P.O. Box 4099  
Farmingdale, New York 11735-0793**

Name \_\_\_\_\_  
Business \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_  
Phone \_\_\_\_\_  
Enclose \$38.00 for the Fifth Edition of the ISCET VCR Cross Reference and \$3.00 for shipping for each Reference.  
The total amount of my order is \$ \_\_\_\_\_  
Check enclosed—do not send cash.  
or please charge my credit card.  
☐ Visa ☐ MasterCard Exp. Date \_\_\_\_/\_\_\_\_/\_\_\_\_  
Card No. \_\_\_\_\_  
Signature \_\_\_\_\_  
New York State residents must add applicable local sales tax to total. US funds only. Use US bank check or International Money Order. CB02

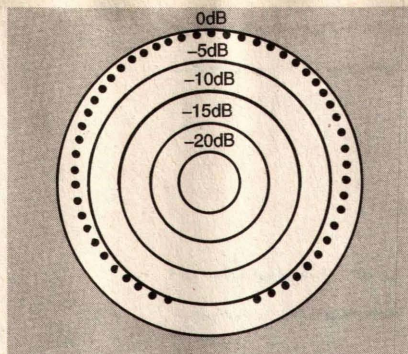


**FIG. 6—A MICROPHONE WITH AN OMNI-DIRECTIONAL pattern like this one picks up sounds from all directions.**

Every microphone has its own polar pattern. The manufacturer will generally supply it with the microphone, or the information might be in the catalog or other literature. The key to selecting the right microphone is to know which pattern is the correct one to use for a particular application.

The most common type is the omnidirectional. As its name implies, an omnidirectional microphone receives the acoustical waves in a pattern that is equal all around in a circular fashion. Note that the plot in Fig. 6 shows that the pickup in the rear does have some loss, but that loss is small enough to ignore.

The next type of pickup pattern is the cardioid. It has better pick-up from the front of the microphone than from the rear, as shown in Fig. 7. That type of pickup is very popular for live performances. That's because it greatly reduces the chance of acoustical feedback (although it is far from the total answer to that common problem).

The hyper-cardioid/super-cardioid microphone has some features of the cardioid microphone, but the pickup pattern is even more pronounced (see

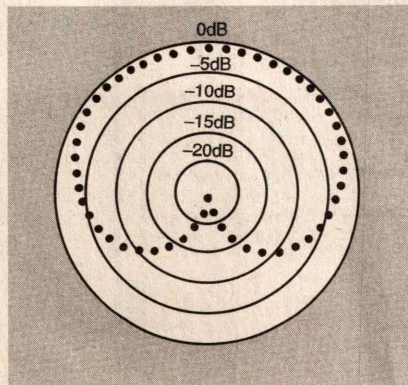


**FIG. 7—A CARDIOID PICKUP PATTERN reduces the likelihood of acoustic feedback.**

Fig. 8). Though that microphone is useful where feedback is likely to be a real problem, one drawback is that it might have too narrow a pickup pattern for some applications.

The last type of microphone we will discuss is the gun/interference tube. It is used to pick up sounds at a distance. That microphone has some special uses, especially in electronic newsgathering and in film and TV production, to pick up dialogue where a wireless microphone is impossible to use for some technical reason. While we have not shown a polar plot for that type, obviously, they are highly directional.

It is important to remember that

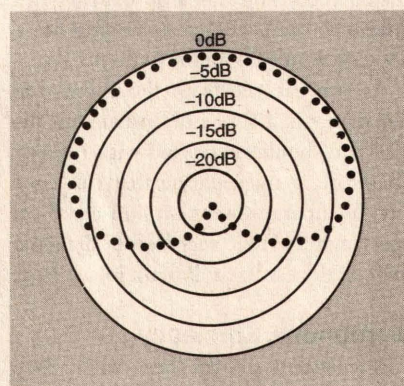


**FIG. 8—WHEN FEEDBACK PROBLEMS are severe, try a hyper-cardioid type that delivers the polar pattern shown here.**

there is no one microphone that can solve all acoustic problems. You must try different ones in different situations. After some practice, you will have a good understanding of what works for what situation. **EN**





# IP Addressing and HTML Coding

**T**HERE WERE SEVERAL MISLEADING AND INCORRECT STATEMENTS IN MY COLUMN ON INTERNET RESOURCES (AUGUST 1996). I THINK THAT THE TOPICS ARE IMPORTANT AND INTERESTING ENOUGH THAT WE'LL REVISIT THEM IN

somewhat greater depth for our discussion this month.

The first problem was my statement, "Thus, a textual address like jkh@acm.org eventually gets resolved to a numeric address like 127.0.0.1." Actually, the numeric address is a machine address, not some sort of user alias. As Lou Sortman pointed out, "There is a mapping between IP addresses and domain (host) names, but the user part of an e-mail address is resolved by the Mail Transfer Agent on the referenced host (or Mail eXchanger) and has nothing at all to do with any part of the IP address." Thanks also to Ron Dozier for information in this area.

Lou also clarified some details of where HTTP ends and TCP begins: "In the HTTP protocol, the client issues a request to the server and the server responds with the status, a header (which you described with the HEAD command), and any requested data (if applicable). Your description added two extra parts (client initiates "transfer" and server acknowledges the connection). Those are not part of HTTP. They are part of the transport protocol (TCP on the Internet)."


Regarding CGI (Common Gateway Interface), Lou stated, "CGI programs can be accessed with the GET method as well as the POST method. You specified that only the POST method can be

used. Later, you say that mostly what is transferred with the GET method is simple HTML files. Statistically, that is probably true, but it is also used quite a lot for other file types (sound files, images, etc.) and even CGI programs."

Lou also disagreed with my assessment of CGI: "CGI is not an awkward

hack. It is the most portable way of handling CGI programs on differing operating systems and written in differing languages, including interpreted ones such as Perl and the Bourne shell. There is a place for more efficient schemes for executing code on the server, but there are portability and resource consumption issues that would make CGI a better solution in many cases."

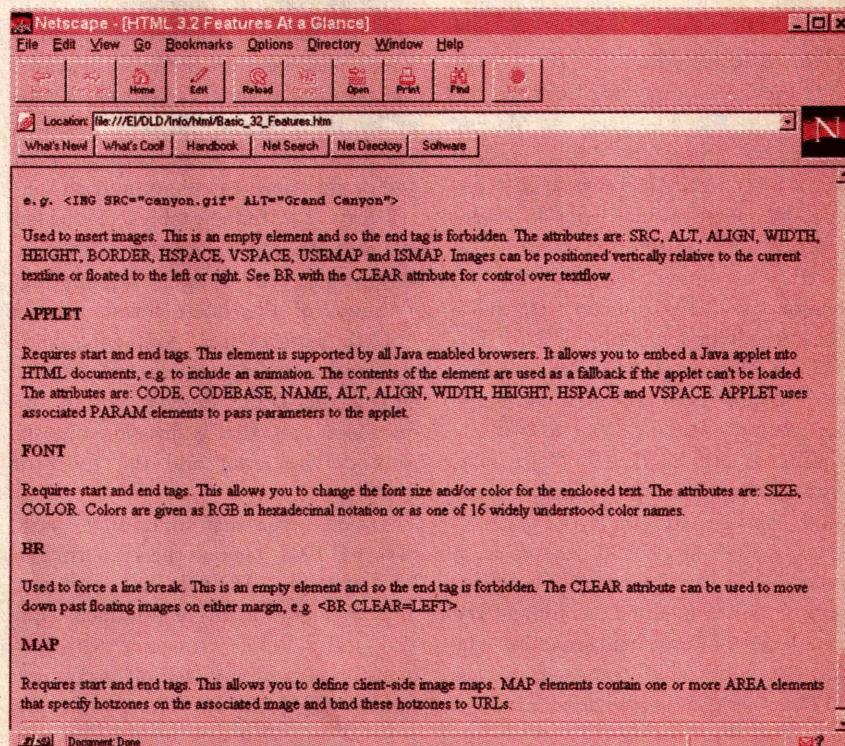I agree that CGI has the virtue of portability. However, it lacks elegance and performance. As the Microsoft steamroller overtakes Internet technology, I think we'll see the company's direct-access Internet Server Application Pro-



THE HTML 3.2 SPECIFICATION adds support for Java Applets, and several new tags for specifying text formatting. HTML 4.0 should be out by the end of the year.



gramming Interface (ISAPI) become much more widely used than CGI. And even if MS were to drop dead tomorrow, other vendors (e.g., Netscape) have comparable solutions.

Lou also disagreed with my assessment of HTML. "HTML was intended to be platform independent. It was quite intentional that there were no font or color tags in the original spec. Leaving the precise manner of interpreting the document content and markup up to the browser was a good thing. The reason that people have problems with documents looking different on different browsers is that they decided that they wanted to do things that HTML was never intended for. HTML is a markup language. It is not a page description language. Ask Don Lancaster (the world's biggest PostScript proponent) about the difference. There may be a need for an open page-description language with hypertext capabilities on the WWW, but the problems that you cite are not shortcomings of HTML."

Here Lou and I have a major disagreement. I'm certainly aware of the distinction between a markup language and a page-description language. The problem is that HTML is rapidly becoming a page-description language.

## HTML and SGML

HTML is an application of SGML (Standard Generalized Markup Language, defined by ISO Standard 8879:1986). SGML purposely separates document content from document structure and document formatting. An SGML "document" actually has two components: the document itself, and a Document Type Definition (DTD). The DTD is like a style sheet (in the MS Word sense). In a pure SGML document, the document has no direct formatting. Nothing is ever marked bold or italic; fonts are not specified by name, nor are colors; nor is any type of layout information (e.g., tab stops and line spacing) embedded in the document. The document never has anything but content and tags specifying format and structure. The tags are interpreted according to the DTD associated with the document.

In that way, the DTD can change without changing the underlying document. Thus, the same document can be presented in several different ways sim-

ply by associating the document with different DTDs.

That may seem like an esoteric feature, but it's not. For example, a big problem in creating software documentation is reuse of material. There are printed manuals and on-line, hypertext documents. Often, they share much of the basic content. But it is extremely rare for them to have a strict, two-way, one-for-one correspondence. The on-line stuff invariably needs something that the manual does not, and *vice versa*. Conversely, the manual invariably has stuff that you don't want in the online version, and *vice versa*. Similar types of problems are pervasive throughout every aspect of electronic publishing

### LISTING 1—TEMPLATE FOR DELPHI COMMAND-LINE UTILITY

```
program Test;
{$APPTYPE CONSOLE}
begin
  writeln('Howdy, world...')
end.
```

The problem with Web pages that look different on different browsers is that the details of the HTML DTD are interpreted differently by different browsers. Netscape interprets the DTD one way, Microsoft another, and so on. If it were just a question of fonts and colors, the graphics designers might be unhappy, but things would still work. It's when Microsoft and Netscape each goes off and defines new tags to accomplish special feats (e.g., frames, tables, embedded applications, and so on) that both page designers and end users end up suffering.

Some of the latest format-related HTML features (e.g., font tags, color tags, and cascading style sheets) in effect embed the DTD directly within the document, and that is directly contrary to both the letter and the spirit of SGML.

It's also true that some of the very oldest HTML tags do the same things. For example, HTML has tags for directly marking text as boldface, <B>, and italic, <I>. However, directly marking text in any fashion is counter to the SGML model. There are more general tags that are usually, but not necessarily, rendered as bold and italic: <STRONG> and <EM>, respectively. Those are the correct tags to use.

## Theory and Practice

Is this a theoretical discussion with no practical application? No. Many Internet citizens still browse with text-only browsers. And as the technology continues to infiltrate other areas (e.g., pagers, cell phones, PDAs), consistent understanding and interpretation of tagging conventions is important. By thinking at a more abstract, general level (e.g., emphasized rather than italic), page designers will better be able to serve a wider audience.

At the bottom of what I dislike about HTML is that it was not designed with a broad set of capabilities and long-term interests in mind. Rather it was a hack thrown together to prove a concept. The creators then lost control, and market evolution took over. Long term, that's probably best. But short term, it makes life difficult for end users, page developers, browser vendors, and new technologies, such as alphanumeric pagers. PostScript, though proprietary, was designed with a full set of capabilities. It has not shown the need to evolve every few months. But that's moot, because HTML is the standard for the Internet. How long will it be before we see HTML-based laser printers?

## Delphi Tip

Delphi is a Pascal-based visual development environment for Windows 32 (Win95 and NT). I compared it in some depth with MS Visual Basic in last month's column. Delphi can also be used to create traditional command-line utilities, although Borland has certainly deemphasized that capability, and has hardly documented how to do it.

Listing 1 shows a shell for such an application. The key is line 2, which tells the compiler that this is to be a console app, not a GUI app. To compile the program, use DCC32.EXE, which is located in Delphi's ..\BIN directory. Also, the compiler must be able to find SYSTEM.DCU, which is located in the ..\LIB directory. To do some really retro non-GUI command-line based development, all you need is the compiler, the system unit, and your favorite text editor. It'll all actually fit on a floppy disk with plenty of room to spare!

That's all for now. Until we meet again next time, you can stay in touch via [jkh@acm.org](mailto:jkh@acm.org).



## USING THE 7107

(Continued from page 60)

Hz. While it is not well-suited for frequency counters, it is an excellent choice for automobile tachometers, audio-frequency meters, pulse- and function-generator displays, and other such applications. The 2917 interfaces directly with the 7107, but might require a simple op-amp buffer at the input. If the output is erratic, a 0.1- $\mu$ F Mylar capacitor connected in series with the positive input will usually correct the problem.

For frequency counting, the LM555 timer is a better choice, as that chip will handle higher frequencies. Figure 12 is the schematic for a 555 frequency-to-voltage converter that can display up to a maximum of 1.999 MHz. The 100,000-ohm potentiometer (R4) functions as calibration, and S1 selects one of three resistors that determines range.

The display reading is multiplied by 10 for range 1, 100 for range 2, and 1,000 for range 3. A 1999 reading in range 2 would be equivalent to an input frequency of 199,900 Hz. A display of 0865 in range 3 would represent 865,000 Hz.

The range of the counter can be further expanded through the use of input pre-scalers. Those ICs will divide an input frequency, usually by 10, before applying it to the counter. A single pre-scaler would increase the input capability to 19,990,000 Hz, while cascading two pre-scalers would take it up to 199,900,000 Hz. Again, there is the multiplication factor to consider. When using pre-scalers, the displayed value is multiplied first by the range factor, then by the pre-scale factor to get the actual measurements.

The 11C90 and 95H90 ICs are two common pre-scalers, but the drawback with them is their expense. Those chips are not exactly economical, although the 95H90 can sometimes be found on the surplus market for as little as \$6 to \$10.

**Other applications.** Now that you're an expert on the 7107, the knowledge gained will perhaps prompt you to expand projects, designs, or equipment, and possibly inspire ideas for future projects. LED and LCD displays are highly informative, and can add

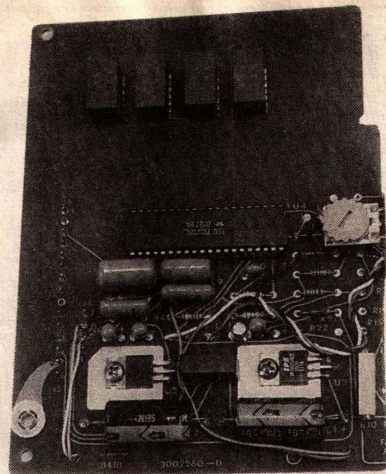


Fig. 13. A section of an alarm board, bought through surplus, that contains a 7107. This particular board also contains the  $\pm 5$ -volt power supply.

to the functionality of many types of electronic equipment. A project that takes advantage of the 7107's voltage-measuring capabilities is the author's "Versatile Power Supply" article in the December, 1995 issue of **Electronics Now**. That project is a bench-type power supply with a 7107-driven LED readout that displays the level of the output voltage.

Only a few applications were covered in this article. With a little thought or as practical needs arise, many other ideas will present themselves. For example, the Intersil data book illustrates a circuit for a digital torque meter, using a resistance-dependent strain gauge.

One area to watch for an economical source of devices is the surplus market, as the 7107 and 7106 can be found on many circuit boards. The surplus circuit board in Fig. 13 is an example of that type of source. The chip is usually mounted in a socket, and can be removed for use in one of your own projects. Frequently, the basic meter circuit is intact, and can be used as is with minor modifications. The 7107 can be found in some alarms, satellite receivers, antenna-positioning units, salvaged digital panel meters, counters, controllers, and a variety of other equipment. Be sure and keep an eye out for them when surplus "bargains" are advertised.

So, pick up a couple of 7107s and try adding one to your next project. The chip is quite easy to work with, and the results you could achieve can be very gratifying.  $\Omega$

## MILLI-OHM ADAPTER

(Continued from page 42)


Run a wire directly from the ground connection of C1 on the board to a lug on the 10-32 stud supporting the swing arm. The common connection including C10, C11, C12, R9, and J1 is the negative Kelvin lead, which is *not* to be connected to ground on the board. Connect the Kelvin lead in this fashion: Run an insulated lead from the common connection of C10, C11, and C12 through a grommet located in the top of the cabinet near the stud, then through an "eyelet" located on the stud itself, and finally make the connection to the lug on BP2.

Mount the completed board on a pair of 1/2-inch spacers in the bottom of the cabinet and connect the remainder of the panel components to the board. Install the ICs in their sockets and close the cabinet. Prepare an output cable using a twisted pair of wires (do *not* use coaxial cable) with an RCA phono plug on one end, and a suitable plug for your DVM on the other end. A 12-inch length is sufficient.

**Calibration.** Power up the adapter and allow it to warm up for about five minutes, allowing the temperature to stabilize in the cabinet. Connect the adapter to your DVM, open the cabinet, and connect a clip-lead jumper from the base lead of Q1 to its emitter lead. The resulting voltage, which can now be read on your DVM, is the *offset voltage* of IC3; make a note of that voltage, which can be anywhere from 0 volt to  $\pm 10$  millivolts. Remove the clip lead. Using your DMM, measure the exact value of  $R_C$  (4.02 ohm, 1%), minus your test lead resistance. Connect  $R_C$  to BP1 and BP2, push the TEST switch, S1, and adjust CAL potentiometer R4 so that the output from J1 (about 4.02 volts) indicates the exact value of  $R_C$  added to IC3's offset voltage. Re-assemble the cabinet and the milli-ohm adapter is complete and ready for use.

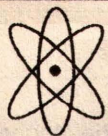In actual use, connect the unknown resistance ( $R_x$ ) at the exact points on its leads from which you want to measure, take the reading, and *subtract* IC3's offset voltage for the proper value at 1 ohm/volt. That procedure will ensure the best possible accuracy.  $\Omega$





# TECH-SYSTEMS

1309 Hwy. 71 Belmar, NJ 07719  
908-280-0007 FAX: 908-280-0111

# 800-435-1516

## BUY - SELL - TRADE

## VISA & MasterCard Accepted

### 90 Day Warranty / 10 Day Right of Return

### N.I.S.T. Traceable Calibration Available on Most Items

#### SPECTRUM ANALYZERS

|                                                                  |         |
|------------------------------------------------------------------|---------|
| TEK 492/01/02 Spectrum Analyzer 50KHz to 21GHz                   | \$6,995 |
| Option 01 Adds Internal Preselection and 02 Adds Digital Storage |         |
| TEK 492/02 Spectrum Analyzer 50KHz to 21GHz                      | 6,650   |
| Option 21 18GHz to 40GHz Waveguide Mixer Set                     | 1,775   |
| TEK 496 1KHz - 1800 MHz Spectrum Analyzer                        | 4,750   |
| TEK 7L12 100KHz to 1800MHz Spectrum Analyzer Plug-In             | 1,850   |
| TEK 7L13 1KHz to 1800 MHz Spectrum Analyzer Plug-In              | 2,495   |
| TEK TR503 Tracking Generator w/ TM503 Power Supply               | 1,450   |
| HP 1411/8552B/8555A 10 MHz to 18GHz Spectrum Analyzer            | 2,195   |
| HP 1411T Variable Persistence/Storage Display                    | 595     |
| HP 140T Non-Storage Display                                      | 425     |
| HP 8553B 1KHz to 110MHz RF Section                               | 450     |
| HP 8554L 100KHz to 1250MHz RF Section                            | 550     |
| HP 8554B 100KHz to 1250MHz RF Section                            | 795     |
| HP 8555A 10MHz to 18GHz RF Section                               | 995     |
| HP 8556A 20Hz to 300 KHz LF Section                              | 450     |
| HP 8552B IF Section                                              | 650     |
| HP 8552A Economy IF Section                                      | 295     |
| HP 8443A 0.1 to 110MHz Tracking Generator                        | 550     |
| HP 8444A 0.1 to 1300MHz Tracking Generator                       | 795     |
| HP 8444A/059 0.5 to 1500MHz Tracking Generator                   | 1,350   |
| HP 8445B 1.8 to 18GHz Preselector                                | 650     |
| HP 182T Mainframe                                                | 495     |
| HP 182T/8557A 10KHz to 350MHz Spectrum Analyzer                  | 1,495   |
| HP 182T/8558B 100KHz to 1500MHz Spectrum Analyzer                | 3,350   |
| HP 8557A 10KHz to 350MHz Spectrum Analyzer Plug-In               | 1,250   |
| HP 8558B 100KHz to 1500MHz Spectrum Analyzer Plug-In             | 2,395   |
| HP 8559A 0.01 to 21GHz Spectrum Analyzer Plug-In                 | 4,450   |

#### OSCILLOSCOPES

|                                            |       |
|--------------------------------------------|-------|
| TEK 465 100MHz Portable Scope              | \$595 |
| TEK 475 200MHz Portable Scope              | 795   |
| TEK 485 300MHz Portable Scope              | 995   |
| TEK 2465 300MHz Portable Scope             | 2,595 |
| HP 1741A 100MHz Portable Scope             | 495   |
| HP 1725A 275Hz Portable Scope              | 695   |
| HP 54200A 50MHz/200Msa/s Digitizing Scope  | 2,250 |
| HP 54200D 50MHz/200Msa/s Digitizing Scope  | 2,650 |
| HP 54201D 300MHz/200Msa/s Digitizing Scope | 2,995 |
| HP 54110D 1GHz/40Msa/s Digitizing Scope    | 5,995 |
| HP 54111D 500MHz/1Gsa/s Digitizing Scope   | 6,995 |
| TEK 7603 w/ 7A18 (X2) & 7B53A Scope        | 695   |
| TEK 7104 w/ 7A29 (X2), 7B10 & 7B15 Scope   | 5,995 |

Over 600 TEK 7000, 5000 & TM Series Mainframes and Plug-Ins

Call for pricing information

#### WAVE - DISTORTION - MODULATION

|                                                                             |       |
|-----------------------------------------------------------------------------|-------|
| HP 331A Distortion Analyzer 5Hz - 600 KHz                                   | \$195 |
| HP 332A Distortion Analyzer with AM Detector                                | 295   |
| HP 333A Distortion Analyzer with Auto Nulling & High Pass Filter            | 395   |
| HP 334A Distortion Analyzer with Auto Nulling/High Pass Filter/ AM Detector | 495   |
| HP 3581C Selective Level Meter                                              | 995   |
| TEK AA501 Distortion Analyzer                                               | 1,295 |
| BOONTON 82AD/01/03/04 Modulation Meter                                      | 995   |
| Marconi 2305 2.32GHz Modulation Meter w/ IEEE                               | 4,995 |

### OVER 3000 ITEMS IN STOCK !

### Inventory Changes Daily!

### OVER 500 DC & AC POWER SUPPLIES !

### Any Voltage - Any Current ! CALL

### CALL FOR FREE 40 PAGE CATALOG

#### COMPONENT TEST

|                                                                                    |         |
|------------------------------------------------------------------------------------|---------|
| HP 4342A Q Meter [22KHz to 70MHz]                                                  | \$2,495 |
| HP 4342A/001 Q Meter [10KHz to 32MHz]                                              | 1,650   |
| BOONTON 5110 LCR Meter 100Hz, 120Hz & 1 KHz Test Frequency                         | 1,450   |
| includes 5110-1 Test Adapter & 5110-4 Kelvin Clip Adapter                          |         |
| BOONTON 72BD Digital Capacitance Meter 1MHz Test Freq. 2pF to 2000pF               | 750     |
| TEK 576 Curve Tracer                                                               | 2,995   |
| TEK 577/D2 Curve Tracer                                                            | 1,695   |
| HUNTRON TRACKER 5000 Computer Controlled Troubleshooting System                    | 1,350   |
| SAUNDERS 150C/09 Crystal Test Oscillator Microprocessor Controlled/IEEE/1 to 60MHz | 1,695   |
| GENRAD 1630AV Inductance Measuring System                                          | 2,995   |

#### STANDARDS & CALIBRATORS

|                                                             |         |
|-------------------------------------------------------------|---------|
| FLUKE 5100B/03/05 Multifunction Calibrator                  | \$5,750 |
| FLUKE 3330B DC Calibrator                                   | 1,995   |
| FLUKE 515A Portable Calibrator AC/DC/RES                    | 1,695   |
| FLUKE 332B DC Calibrator                                    | 595     |
| FLUKE 5205A AC Amplifier                                    | 2,650   |
| FLUKE 5450A Resistance Calibrator 1 OHM to 100 megohms/8ppm | 1,995   |
| FLUKE 730A DC Transfer Standard                             | 450     |
| FLUKE 750A Reference Divider                                | 450     |
| FLUKE 720A Kelvin Varley Divider                            | 1,895   |
| ESI RV722 DC Divider 1ppm Accuracy                          | 1,295   |
| DATRON 4200/30/80 Autocal AC Standard                       | 2,495   |
| BOONTON 25A Power Meter Calibrator                          | 450     |
| BOONTON 2500A Power Meter Calibrator                        | 450     |
| HP 8477A Power Meter Calibrator                             | 495     |
| HP 11683A Range Calibrator                                  | 775     |
| TEK PG50B Calibration Generator                             | 1,350   |
| TEK TG501 Time Mark Generator                               | 1,350   |
| TEK SG503 Leveled Sine Wave Generator 250KHz to 250MHz      | 1,350   |
| TEK SG504 Leveled Sine Wave Generator 245MHz to 1050MHz     | 2,650   |
| RFL 829G Multi-Function Calibrator                          | 1,495   |

#### FREQUENCY COUNTERS

|                                                             |       |
|-------------------------------------------------------------|-------|
| HP 5314A 100MHz Universal Counter                           | \$225 |
| HP 5315B 100MHz Universal Counter                           | 495   |
| HP 5316A 100MHz Universal Counter                           | 695   |
| HP 5328A/011/030 512MHz/IEEE Universal Counter              | 695   |
| HP 5328A/011/031 1.3GHz/IEEE Universal Counter              | 895   |
| HP 5340A/011 18GHz/IEEE Microwave Counter                   | 1,950 |
| HP 5342A/011 18GHz/IEEE Microwave Counter                   | 2,750 |
| HP 5300B/5303B 525MHz Counter                               | 450   |
| HP 5257A Transfer Oscillator for HP 5245 Counters           | 175   |
| HP 5255A 3 to 12.4GHz Frequency Converter                   | 175   |
| HP 5359A Time Synthesizer                                   | 1,895 |
| SYSTRON CONNER 6054B 20Hz to 26.5GHz IEEE Microwave Counter | 2,295 |
| TEK DC5009 Programmable 135MHz Universal Counter            | 695   |
| TEK DC505A 225MHz Universal Counter Plug-In                 | 295   |
| TEK DC508 1.3GHz Universal Counter Plug-In                  | 450   |

#### SIGNAL SOURCES

|                                                                       |         |
|-----------------------------------------------------------------------|---------|
| HP 8640B/003 512MHz Signal Generator w/Reverse Power                  | \$1,895 |
| HP 8640B/001/002 1024MHz Signal Generator w/Audio Oscillator          | 2,795   |
| HP 8656A 100KHz to 990MHz Synthesized Signal Generator                | 2,995   |
| HP 8660C/86603A/86632B 2600MHz Synthesized Signal Generator           | 3,995   |
| HP 8660A/86602A/86632B 1300MHz Synthesized Signal Generator           | 2,350   |
| HP 8620C Sweeper Mainframe                                            | 395     |
| HP 86222A 0.01 to 2.4GHz RF Plug-In                                   | 1,495   |
| HP 86222B/001 0.01 to 2.4GHz RF Plug-In w/Crystal Markers & 70dB ATTN | 1,795   |
| HP 86290C 2 to 18.6GHz RF Plug-In                                     | 2,395   |
| HP 86260A 12.4 to 18GHz RF Plug-In                                    | 995     |
| HP 8697A 26.5 to 40GHz RF Plug-In                                     | 1,450   |
| HP 214B Pulse Generator                                               | 1,995   |
| HP 8005B 20MHz Dual Pulse Generator                                   | 450     |
| HP 8007B 100MHz Pulse Generator                                       | 695     |
| HP 8013B 50MHz Dual Pulse Generator                                   | 695     |
| HP 3312A 13MHz Function Generator                                     | 895     |
| BOONTON 2000 20GHz Sweep Generator                                    | 2,450   |
| TEK FG501 2Hz to 2MHz Function Generator                              | 195     |
| TEK FG502 1KHz to 11MHz Function Generator                            | 295     |
| TEK FG503 1 to 3MHz Function Generator                                | 195     |
| TEK PG501 50MHz Pulse Generator                                       | 250     |
| TEK PG502 250MHz Pulse Generator                                      | 495     |
| TEK PG508 50MHz Pulse Generator                                       | 795     |
| APPLIED MICROWAVE/EPSCO PG5KB 5KW/575 to 925MHz RF Pulser             | 2,995   |
| VELONEX 380 5KW High Power Pulser                                     | 2,995   |
| COBER 605/P27 2KW/10Hz to 1MHz High Power Pulser                      | 1,350   |

## We Buy & Sell Service Manuals Coax/Waveguide Components

# WANTED !

## Surplus Electronic Test Equipment

## FAX US YOUR LIST

# FAX: 908-280-0111



# Electronic SHOPPER<sup>®</sup>

## TEST EQUIPMENT SALES

customer  
satisfaction  
#1 priority!

WE BUY  
SURPLUS  
EQUIPMENT

MC & VISA  
ACCEPTED

NEW SCOPES  
IN STOCK

TEK SG504.....1 GHz SINE WAVE GENERATOR.....\$2795  
HP 8111A.....PULSE/FUNCTION GENERATOR.....\$1995  
TEK 2465.....300 MHz 4 CH. SCOPE.....\$2850  
TEK 2445.....150 MHz 4CH. SCOPE.....\$1850  
TEK 2465BDM...400 MHz 4 CH. SCOPE w/DMM...\$6695  
TEK 465.....100 MHz 2 CH. SCOPE.....\$475  
HP 1650B.....80 CH. LOGIC ANALYZER.....\$3595  
HP 3325A.....SYNTH/FUNC. GENERATOR.....\$1995  
TEK 7L5.....SPECTRUM ANALYZER P/L.....\$1495  
(INCLUDES L3 MODULE)

DIO 2900.....PROGRAMMING SYSTEM.....\$2195  
BMI 2400.....POWER LINE MONITOR.....\$1295  
ELGAR 251.....AC POWER SOURCE.....\$750  
TEK 2235.....100 MHz 2 CH. SCOPE.....\$995  
**NEW TEKTRONIX SCOPES W/ 3 YEAR  
MFG. WARRANTY !!**  
TEK THS 720...100 MHz 500MS/s HANDHELD  
SCOPE & DMM.....\$2195  
TEK TDS 340.....100 MHz 500 MS/s SCOPE  
W/DIGITAL REAL TIME & FFT .....\$2695  
TEK TDS 420A.....200 MHz 4 CH. SCOPE  
W/DRT, FFT & DISK DRIVE.....\$6295  
FLUKE 45.....DUAL DISPLAY BENCHTOP  
DIGITAL MULTIMETER.....\$679

P.O. BOX 986  
LONDONDERRY, NH 03053

PHONE (800) 684-4651  
FAX (603) 425-2945

ASK ABOUT OUR NEW  
TEKTRONIX & FLUKE  
PRODUCTS

### Weeder Technologies

Electronic KITS!  
from  
\$29 to \$55

FREE  
CATALOG!



### Pro-Kit<sup>™</sup>

PO Box 421, Batavia, OH 45103

weedtech@iglou.com

513-752-0279

#### Home Automation

Connects between a TW523 and an RS-232 serial port. Use your PC or Mac to receive and transmit all X-10 commands. Create your own program to control your home automation system, turning on/off any device plugged into an electrical outlet with response to time/date, other X-10 transmissions or any other computer input stimuli.

#### Caller ID / RS-232

Connects between a telephone wall jack and an RS-232 serial port. Decodes the caller ID data sent over the phone line and sends it to your PC or Mac, in a pre-formatted ASCII character string. Create your own program to log the name, number, date, and time of all incoming calls.

#### Telephone Call Restrictor

Connects to telephone wall jack. Disables all phones on the line if attempting to either: dial a number that has been stored in memory "Block" mode or, dial a number that has not been stored in memory "Allow" mode. Use touch-tone phone to enter telephone numbers into memory, and choose mode. Program from any phone on the line using your password.

#### 50 MHz Frequency Counter

Reads frequency from 1Hz to 50MHz and displays up to 7 digits on a 16x1 character LCD display. Auto-range feature provides floating decimal point and automatically affixes the correct suffix (Hz, KHz, or MHz). Microcontroller based provides for very small parts count, only 2" x 3" big.

#### Telephone Scrambler

Scrambles your voice before sending it over the telephone line. Prevent eavesdropping from an extension or tap. Connects between your telephone and wall jack. No modifications are required to your telephone. Full duplex operation.

#### IR Remote Control Receiver

Learns and records the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. Seven individual I/O pins can be assigned to any button on your remote, and can be configured for either "toggle" or "momentary" action.

#### Caller Block

Connects between your telephone and its wall jack. Prevents your telephone from ringing unless the calling party is one which you've entered into memory using your touch-tone phone. Can also be set to allow all callers "except" those which you've entered into memory.

#### DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Connects to your telephone wall jack. Decodes all 16 touch-tones and displays them on an LCD display. Holds the last 240 digits in a non-volatile memory. Scroll through and view all telephone numbers dialed, credit card numbers entered, etc.



# BLOWOUT! TIMELINE INC. BLOWOUT!

Over 10 years and 27,000 customers and still growing

## LIQUID CRYSTAL DISPLAYS

### 240x64 dot LCDs with built-in controller.

AND 4021 ST-EO. Unit is EL back-lit. \$79.<sup>00</sup> or 2 for \$149.<sup>00</sup>  
OPTREX. DMF5005 \$69.<sup>00</sup> or 2 for \$129.<sup>00</sup>

160 x 128 dot LCD with built-in controller (T6963C)

20 character x 16 line \$79.<sup>00</sup> or 2 for \$149.<sup>00</sup>

Mfr.: Toshiba TLX-1013-EO. Unit is EL back-lit. Dim: 5 1/4" L x 4 1/4" H.  
The built-in controller allows you to do text and graphics.

### Alphanumeric—parallel interface

|                              |                              |                        |
|------------------------------|------------------------------|------------------------|
| 16x1.....3 for \$25.00       | 20x2.....\$12.00             | 40x1.....\$8.00        |
| 16x1 (lg. char.).....\$12.00 | 20x4.....\$25.00             | 40x2.....2 for \$25.00 |
| 16x2.....\$8.00              | 20x4 (lg. char.).....\$25.00 | 40x4.....\$25.00       |
| 16x2 (lg. char.).....\$12.00 | 24x2.....\$12.00             | 4x2.....\$5.00         |
| 16x4.....\$15.00             | 32x4.....\$10.00             |                        |

5V power required • Built-in C-MOS LCD driver & controller • Easy "microprocessor" interface • 98 ASCII character generator • Certain models are backlit, call for more info.

### Graphics and alphanumeric—serial interface

| size              | Mfr.      | price   | size              | Mfr.    | price   |
|-------------------|-----------|---------|-------------------|---------|---------|
| 640x480 (backlit) | Epson     | \$35.00 | 480x128           | Hitachi | \$15.00 |
| 640x400 (backlit) | Panasonic | \$25.00 | 256x128           | Epson   | \$20.00 |
| 640x200           | Toshiba   | \$15.00 | 240x128 (backlit) | Optrex  | \$20.00 |
| 480x128 (backlit) | ALPS      | \$15.00 | 240x64            | Epson   | \$20.00 |
|                   |           |         | 160x128           | Optrex  | \$15.00 |

## LASER PRODUCTS

HeNe Laser Head (10mw max. output) TEMOO, 15.5" long MFG: NEC \$99.<sup>00</sup>

Laser Power Supply (for HeNe tube) \$89.<sup>00</sup>

LASER SCANNER ASSEMBLY \$29.<sup>00</sup>

Assembly intended for a laser printer. Includes laser diode, polygon motor (6 sided) and misc. optics and lenses.

LASER DIODE (5mw) with collimator \$20.<sup>00</sup>

VISIBLE LASER DIODE: 5mw at 670nm \$15.<sup>00</sup>  
Index guided. Threshold current 40 ma typical.

### POLYGON MOTOR UNIT & DRIVER \$79.<sup>00</sup>

Ten-sided first surface mirror mounted on an armature that spins at 125 revolutions per second yielding a beam sweep rate of 1250 sweeps per second. The driver for the polygon unit requires 24 volts and plus and minus 12 volts to operate. There is also an f-theta lens in front of the polygon scanning mechanism with a three inch diameter. Great for optical experiments, etc. Very high quality units. (MFR: JAPAN ELECTRONICS)

## NETWORK

### Proton ProNet-4 Model p1347 Token Ring Board \$49.<sup>00</sup>

16 bit • 4 Mbps • IEEE 802.2 and 802.5 compatible • twisted pair • interoperable with IBM Token Ring network

## POS & BAR CODE

### MAGNETIC CARD READER \$25.<sup>00</sup>

Includes: • 20 character dot matrix display with full alpha-numeric capability • keypad with full alpha-numeric entry • separate 7.5 VDC/0.5 Amp power supply • standard telephone interface extension cord • lithium battery and flat-cone speaker.

HP bar code wand (HBCS 2300).....\$25.00

## POWER SUPPLIES

SWITCHING POWER SUPPLIES \$12.00 or 2 for \$20.00 115/230 Volts  
73 WATT (2) 4 pin power connectors attached • Dim: 8.5" L x 4.5" W x 2" H

Output: +5V @ 2-9.75 A, +12V @ 0-1.5 A, -5V @ 0-0.4 A, -12V @ 0-0.5 A

68 WATT Dim: 5.5" L x 3.2" W x 1.7" H • Output: 5V @ 4 A, 12V @ 4 A

60 WATT Dim: 8 1/4 x 4 x 3 • Output: 5V @ 6A + 12V @ 1A - 5V @ 1A - 12V @ 1A

## CHARGE COUPLED DEVICES



"The Spy In The Sky" \$29.<sup>00</sup>

MATRIX TYPE

Sony CCD Imager - designed for black and white composite video cameras. Picture elements: 384 (H) x 491 (V)  
Chip size 10.7 (H) x 9.3 (V) mm<sup>2</sup> • Unit cell size 23.0 (H) x 13.4 (V) um<sup>2</sup>.  
Ceramic 24 pin DIP package • Mfr: Sony, Part# 016AL

4096 element CCD \$19.00

1024 element CCD \$15.00

2048 element CCD \$15.00 • 1728 element CCD \$15.00

LINEAR TYPE

23605 Telo Ave., Torrance, CA 90505

Order desk only: USA: (800) 872-8878 CA: (800) 223-9977

L.A. & Technical Info: (310) 784-5488 Fax: (310) 784-7590

OEM INQUIRIES WELCOME

## MONITORS

### Non-Enclosed TTL

Comes with pinout. 12V at 1.4 Amp input • Horizontal frequency 15KHz. • Ability to do 40 and 80 column.

5 inch Amber \$29.00 • 7 inch Amber \$39.00

9 inch Amber or Green \$29.95

### 5" COLOR MONITOR \$49.<sup>00</sup>

• Flat Faceplate • 320 x 200 Dot Resolution • CGA & Hercules Compatible

• 12 VDC Operation • 15.75 KHz Horiz. Freq. • 60 Hz Vert. Sync. Freq.

• Open Frame Construction • Standard Interface Connector • Degaussing Coil included • Mfr. Samiron



## MISCELLANEOUS

ADAPTEC 4070A (RLI) OR 4000A (MFM), SCSI Controller, your choice \$25.<sup>00</sup>

IBM 370 option XT and AT emulation boards \$35.<sup>00</sup>

## HACKER CORNER

### POINT OF SALE BANK TERMINAL \$49.<sup>00</sup> or 2 for \$89.<sup>00</sup>

• LCD Display 20 Char. x 4 Line • Printer 16 Column Dot Matrix • Epson • 24 Key Domed Membrane Keypad • Intel 80C32 Processor • 2 PCMCIA Sockets (ICC Slots) • Dallas DS1287 Realtime Clock • 2 Solid State Buzzers (Piezo Electric) • 4 Crystals • Rockwell Modem Chip • Telephone Line Interface (4 Pin "RJ" Connector) • RS-232 Interface (8 Pin "RJ" Connector) • NI-CAD Battery Pack Inside

Note: We have not been able to bypass an access code in the software. Thus, while time of day and other introductory things are displayed on LCD, the full original capabilities of this unit cannot be guaranteed. Also, we do not have a source for the smart cards that were to go in the PCM CIA sockets. Requires 12 volt adapter for power. (Not included) Dimensions: 9-1/2 L x 6-1/4 W x 2-1/2 D • Original cost over \$450.00

### CAMERA BLOCK \$149.<sup>00</sup>

#### FOR ROBOTICS AND EVERYTHING ELSE

Unit is for Hi Band 8mm CamCorders, includes 8X zoom lenses, D/D converters, built-in CCD 2/3 in, 420 thousand picture elements, complementary mosaic filters. Excellent performance. High resolution, high sensitivity, low lag, low smear, good color reproduction, no distortion, 1/60-1/10000sec variable speed digital shutters, TTL auto focus, auto white balance, one-push auto white balance, auto/manual iris and gain up switch. Can be controlled by a 4bit micro computer. Remote controlling is possible for zoom and focusing. NOTE: These are PAL (European Standard) Units. SONY PART #EVI-101 (PAL)

### CELL SITE TRANSCEIVER \$79.<sup>00</sup> 2 for \$149.<sup>00</sup>

These transceivers were designed for operation in an AMPS (Advanced Mobile Phone Service) cell site. The 20 MHz bandwidth of the transceiver allows it to operate on all 666 channels allocated. The transmit channels are 870.030-889.980 MHz with the receive channels 45 MHz below these frequencies. A digital synthesizer is utilized to generate the selected frequency. Each unit contains two independent receivers to demodulate voice and data with a Receive Signal Strength Indicator (RSSI) circuit to select the one with the best signal strength. The transmitter provides a 1.5 watt modulated signal to drive an external power amplifier. Channel selection is accomplished with a 10 bit binary input via a connector on the back panel. Other interface requirements for operation are 26 VDC (unregulated) and an 18.990 MHz reference frequency for the digital synthesizer. The units contain independent boards for receivers, exciter, synthesizer, turnable front end, and interface assembly (which includes power supplies and voltage-controlled oscillator). Service manual, schematics and circuit descriptions included.

### Encased Black & White Composite CCD Camera with Adapter

IR viewing to 1000 nm 7 1/2 L x 2 1/2 W x 1 1/4 H

Comes complete with CCD camera, mounting nut on bottom of casing,

12VDC power supply. Excellent low light capability, standard RCA NTSC video out.

Great for: entryway security/remote monitoring,

video conferencing/desktop video conferencing

This miniature camera is perfect for multimedia computer applications as well as security and surveillance. NTSC output allows use with all popular video digitizing boards for Apple Macintosh and Microsoft video for Windows. Connects directly to any composite monitor or VCR with "video" input. Its razor-sharp wide-angle lens focuses from two inches to infinity and its state-of-the-art CCD technology accurately captures 16 level grayscale images for Quick Time movies and still pictures. Records at 30 frames per second and 260 lines resolution with excellent low light capability. Uses 12VDC (adapter supplied) and standard RCA cable.

### Portable Micro Terminal \$99.<sup>00</sup> or 2 for \$149.<sup>00</sup>

Flip up LCD display (9-16 VDC) • Can communicate with any computer having RS 232 port • Can communicate with another Microterminal • Easy to use as a desktop terminal • On-board microprocessor, data RAM (32K) and Video RAM (64K) • Easy to set up and use • Includes all necessary cables and set up capabilities. • Original intention for POS applications. • display size 40x16 (256 x 128 pixels). Dimensions: 6.3" W, 11" L, 2" H. (With LCD up height is 7.1")



### BAREBONES 286-12 COMPUTER \$49.00 (2 FOR \$79.00)

Slimline desktop case, 100 watt supply, math co-processor support. On board IDE, & Floppy controllers. 2 COM ports and 1 parallel port with software setup. Supports up to 8 Megs using standard 30 PIN SIMMs. Internal room for (1) 3 1/2 inch IDE hard drive and (2) 3 1/2 inch floppies. Four 16 BIT ISA slots, accepts full length AT size cards. Keyboard can be set to no test at boot. Case size is 15.5" W x 16" D x 4" H. (Motherboard can be purchased separately: \$29.00 or 2 for \$49.00)

### .6" COMPOSITE MINIATURE COLOR DISPLAY \$149.<sup>00</sup>

Fully encased. Dim: 1.3" x 1.3" x 4". 12 Volts DC power. NTSC signal.

250 H x 300 V resolution. Focus adjustable eyepiece. Applications include camcorder viewfinder, helmet mounted display, etc... Original cost over \$600.00

Minimum Order: \$20.00. Minimum shipping and handling charge \$5.00. We accept cashiers checks, MC or VISA. No personal checks or COD's. CA residents add 8.25% sales tax. We are not responsible for typographical errors. All merchandise subject to prior sale. Phone orders welcome. Foreign orders require special handling. Prices subject to change without notice. 20% restocking fee for returned orders.



**FREE CATALOG  
CALL TOLL FREE  
1-800-338-0531**

E-Mail: [xpress@parts-express.com](mailto:xpress@parts-express.com)



**Parts  
Express™**

**30 DAY MONEY  
BACK GUARANTEE!**

340 E. First St., Dayton, OH 45402-1257  
Phone: 513-222-0173 • Fax: 513-222-4644

### Amplified Indoor FM Antenna

17" tall, amplified FM antenna. Improves reception with weak FM signals. 18 dB of gain. Includes AC adaptor, gain control, and 75 ohm coaxial cable terminated with an "F" connector.

**HOT  
NEW  
ITEM!**



#EN-219-055 ..... **\$12<sup>90</sup>**

### Cable TV Stereo Decoder

When used in conjunction with a cable TV converter or cable ready VCR, this handy device allows you to feed the cable TV stereo signal into your home sound system for superb audio reproduction of your favorite shows, movies, and sporting events.



#EN-189-110 ..... **\$19<sup>90</sup>**

### Digital Video Stabilizer


The digital video stabilizer will eliminate the constant picture distortion caused by the copyright protection on movie videotapes. This unit is fully automatic and operates on one 9V battery which is included.



#EN-180-320 ..... **\$17<sup>95</sup>**
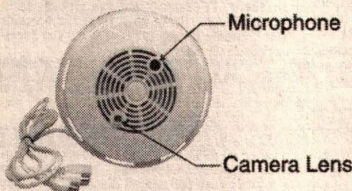
### Decoy Cameras

These 1/3" CCD cameras offer a clever means of disguise. Both feature a 3.6mm wide angle lens, built-in electronic shutter, and a 12 VDC power supply. Minimum illumination: 0.3 lux. 400 line resolution. Smoke detector decoy camera includes an audio output.



| Part #     | Description          | Price    |
|------------|----------------------|----------|
| EN-335-535 | Smoke detector decoy | \$249.50 |
| EN-335-540 | Decoy clock camera   | 299.95   |

**AFFORDABLE  
HIGH TECH  
SURVEILLANCE!**



### "The Sound Bridge" FM Stereo Wireless Transmitter

The Sound Bridge is a mini FM wireless transmitter that can be used to broadcast stereo sound from any audio source like portable CD players, TVs, electronic games, CD-ROM, even computer soundcards, to your home stereo receiver! Adjustable from 89 to 95.5 MHz.



**HOT  
NEW  
ITEM!**

#EN-249-220 ..... **\$14<sup>95</sup>**

### Portasol/Weller Butane Soldering Tool

**NO CORDS.  
NO BATTERIES!**




This cordless, refillable, butane powered soldering tool is ideal for any on-site soldering job. Provides up to 35 watts with a temperature range up to 700 degrees F. Includes flint igniter in plastic case, safety cut off switch, and C-2 chisel tip.

#EN-372-150 ..... **\$25<sup>95</sup>**
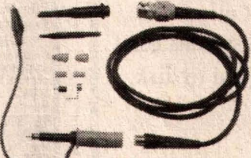
### 150 MHz Oscilloscope Probe Kit

Deluxe probe kit features a modular design for longer life, switchable 10:1 probe with 150 MHz bandwidth, 2.8 ns rise time, and adjustable capacitance from 10-35 pF. 60" in length.




**GREAT  
VALUE!**

#EN-390-100 ..... **\$29<sup>95</sup>**
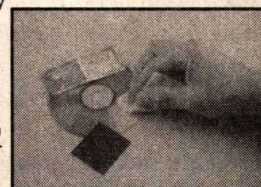
### Memorex CD Repair And Maintenance Kit

Don't throw away expensive CDs because of annoying mistracking and skipping errors! The Memorex CD Repair kit contains enough solution and materials to clean and repair 12 compact discs.



#EN-249-032 ..... **\$1<sup>95</sup>**

### 5" Sealed Back Midrange

5" heavy duty sealed back midrange with deluxe mesh grill. 1" aluminum voice coil. Popular midrange for auto sound installations. ♦Power handling: 35 watts RMS/50 watts max ♦Voice coil diameter: 1 inch ♦Impedance: 8 ohms ♦Frequency response: 800-10,000 Hz.



#EN-280-030 ..... **\$7<sup>50</sup>**

### 1", Titanium Dome Tweeter

Features a ferro fluid cooled Kapton voice coil and a rubber surround. Very natural sounding high frequency reproduction with extended response to 30KHz.

♦Power handling: 50 watts RMS/75 watts max  
♦Voice coil diameter: 1" ♦Impedance: 8 ohms  
♦Frequency response: 2500-30,000 Hz.



**RESPONSE  
TO 30KHz!**

#EN-275-050 ..... **\$16<sup>50</sup>**

**Dayton Loudspeaker Co.®**

### 3 Channel Color Organ Kit

This sound to light unit features three separate outputs, which can be controlled independently. Each output reacts to three different bands of the musical spectrum: bass, midrange, and treble. Has built-in microphone, so no connection is required to music source, but a line input is provided.

**High-Q  
velleman-kil®**



**SUPER  
QUALITY  
KIT!**

#EN-320-210 ..... **\$59<sup>95</sup>**

### 6-1/2" Woofer

Polymer resin treated paper cone with poly foam surround. Long throw voice coil design helps to deliver powerful bass output. Perfect for bookshelf type speakers. Mfg. #C16L020-51F. ♦Power handling: 60 watts RMS/120 watts max. ♦Voice coil diameter: 1-1/4 inches ♦Impedance: 8 ohms ♦Frequency response: 57-7000 Hz.

**PIONEER**



#EN-290-023 ..... **\$19<sup>95</sup>**



♦30 day money back guarantee ♦\$20.00 minimum order ♦We accept Mastercard, Visa, Discover, and company C.O.D. orders ♦24 hour shipping ♦Shipping charge = UPS chart rate + \$1.90 (\$5.00 minimum charge) ♦Hours 8:00 am - 8:00 pm ET, Monday - Friday ♦9:00 am - 5:00 pm Saturday. Mail order customers, please call for shipping estimate on orders exceeding 5 lbs. ♦Foreign destination customers please send \$5.00 U.S. funds for catalog. ♦Quantity pricing available.

CIRCLE 262 ON FREE INFORMATION CARD

**1-800-338-0531**




# DIGITAL STORAGE OSCILLOSCOPE

WITH  
SPECTRUM  
ANALYZER,  
DVM, FREQ.  
COUNTER,  
AND DATA  
LOGGER.

from  
**\$189.**

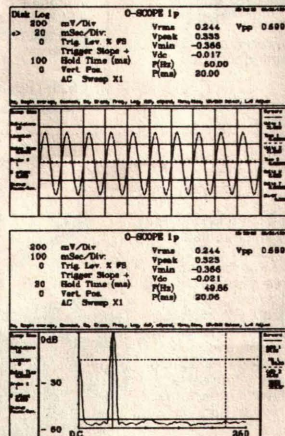O-SCOPE  
MODULES  
CONVERT PC'S  
INTO  
MULTIPURPOSE  
TEST AND  
MEASURING  
INSTRUMENTS.



No room on the bench? Too much to carry? Why lug a scope around? Just toss an O-SCOPE into laptop case or tool kit. When you need a Digital Storage Scope, Spectrum Analyzer, Data Logger, or DVM, plug the O-SCOPE into a PC printer port and see it all on the monitor. Continuous, delayed, or triggered sweeps can be frozen on the screen, printed out, or saved to disk. Frequency spectrums DC to 500KHz.

Both single and dual channel models accept standard scope probes and works on 286 or faster desktop and laptops.

## FEATURES:

- ♦ SMALL & PORTABLE
- ♦ USES PRINTER PORT
- ♦ USES STD. PROBES
- ♦ DC TO 500 KHz (O-Scope II)
- ♦ 10v/div. TO 50 mv/div.
- ♦ X-Y DISPLAY (O-Scope II)

## OPTIONS:

- ♦ PROBE SETS
- ♦ EXTERNAL TRIGGER
- ♦ DUAL TRACE
- ♦ AUTOMOTIVE PROBES
- ♦ BATTERY PACK
- ♦ SOFT & HARD CASES

MADE IN U.S.A.

SAME DAY SHIPPING

INCLUDES CABLE, SOFTWARE & MANUALS

O-SCOPE Ip (DC-50KHz, single trace) ..... \$189.  
O-SCOPE II (DC-500KHz, dual trace) ..... \$349.  
SHIPPING: ..... \$7.50 (2ND DAY \$11.50)

SEND CREDIT CARD INFO., M.O., or CHECK, OR CALL

**1-800-980-9806**

Allison Technology Corporation

8343 CARVEL, HOUSTON, TX. 77036 U.S.A.

PHONE: 713-777-0401 FAX: 713-777-4746 BBS: 713-777-4753

<http://www.atcweb.com>

# TOP SECRET

**CONSUMERTRONICS**  
2011 Crescent Dr., P.O. Drawer 537  
Alamogordo, NM 88310

--- Please order by Mail or Fax only ---  
Fax: (505) 434-0234, 439-1776 (orders only; if you get voice, enter #11#11 any time). 24-hr

**Customer Service & Tech Support:**  
(505) 439-8551 (8AM-6PM MST, Mon-Sat)

Relates directly to your order or prospective order.  
**Web Site:** Visit our popular site (tell your friends) at: <http://users.aol.com/wizguru/hl-tech.html>

**10% OFF on orders \$100+ 15% OFF over \$200+**  
Add \$5 total SH (US, Canada). All items in stock.

Postal M.O. is fastest. VISA, MC CC OK. COD (\$49-\$999), add \$8. New Catalog (200+) offers \$2 w/ order, \$5 w/o (no CC), \$24 foreign. NO dealers.

Since 1971. As seen on CBS "60 Minutes". Forbes, etc. By John Williams - former Lockheed Senior Engineer, NMSU CS Professor, DOD Electronic Weapons Engineer, NIH Health Physicist. Sold for educational purposes only.

**Wanted:** 5 MAC Ilix, PC486 (or better), peripherals, new surplus electronic parts, test equipment - buy, trade.

**\*All software supports all IBM-PC systems**

## Off-the-Shelf HARDWARE

Van Eck Systems\*Data Card Reader/Writers\* ATM3\*Security/Surveillance\*RF/EM/UV/Wave/Radar/Ultrasonic/IR/Light/Sound Detectors/Receivers/Xmitters/Jammers/Blasters\*Neurophone/RIFe/Hieronymus/Resonant Crystal Radionics\*EM Lab/Weaponry/Countermeasures\*ESS Infinity Devices\*Voice Disguisers\*Lineman's Hand-sets\*Buy/Tap Detector/Blaster\*Phone Color Boxes\*DTMF Decoders\*Carjack/Kidnap Foller\*Bumper Beeper/Child Finder\*Panic Button\*Shrik Module\*TENS\*Subliminal Mixer/Amp (Ultrasound & Infrasonic)\*Electronic Dowers\*Hidden Presence Detectors\*Hearing Assistor\*Vortex Generator\*6th Sense Communicator\*Noise Cancel. System\*Levitor - many more! See our New Catalog!

## SPECIAL PROJECTS

We design/build/obtain/repair/modify/maintain/consult on any device/system/process/project - electronic/computer/mechanical/optical (ex: phone/auto/security/radionics/lab/energy/HV/EM/RF/radar/ultrasonic/IR/UV/commo/consumer) for business/personal/invention needs. Describe & include \$30 pre-engineering fee (no obligation). Time & cost estimates 7-10 days. Confidentiality guaranteed.

## CELLPHONE MODS

See our Catalog for our infamous cellphone modification guide (\$69) - detailed, comprehensive, covers all makes - 1.0 times more info than competitor's "guide". (Do Special Projects above to get up-to-date hardware/software). **Free Data Search:** As a special FREE service to our C&CP customers, we will perform one FREE search of our massive cellphone database if requested within 30 days of your purchase of C&CP. Data now on cellphones is so great, we can fit in C&CP only that in greatest demand. Search results not guaranteed. Request by mail (don't fax); include a #10 SASE.

## PAGER (Beeper) MANUAL

Describes in detail how Pagers work, different types and uses, frequencies, advantages over and uses with cellphones, and tips and tricks. And how Pagers are hacked and countermeasures. Includes the plans for your own Personal Pocket Paging System (transmitter and receiver). \$49.

## HACKING FAX MACHINES

Describes in detail how Fax machines are hacked and countermeasures (hacking Faxes is much more complex than just connecting a third Fax to the phone line). Includes Fax protocols, comms parameters, and 2-1 and 4:1 compression. And insights into designing Fax interception devices and modifying existing Faxes into Stealth Faxes do the job. \$49.

## VOICE MAIL HACKING

How Voice Mail Box (VMB) systems are used and the specific ways they are hacked. Includes ASPEN, MESSAGE CENTER, BIX, GENESIS, EZ, SYDNEY, PHONE MAIL, AUDIX, CINDY, CENTAGRAM, SPERRY LINK, RSVP, etc. Absolutely required for all users, sysops and security personnel! \$29.

## PBX HACKING

1,000s of PBXs are hacked to the tune of \$ Billions/yr! While "VOICE MAIL HACKING" details how VMBs are hacked for "phun" and profit - including VMS methods for hacking PBXs themselves - "PBX HACKING" addresses ALL issues relating to PBX hacking, including countermeasures! Can your business or agency afford a \$90,000 phone fraud loss (the average loss due to hacked PBXs)? As described in Forbes Magazine. \$29

## PHREAKING CALLER ID & ANI

Details on how they work and dozens of effective ways of defeating Caller ID, ANI, \*69, \*87, and Call Blocking and \*67. Also describes Caller ID, Orange, Beige, Cheese and GF Boxes, ESS, S87, E-811, various CLASS services, CWA, NOW PUB DA, CAMA, DNR, 800-ECR, Diverters, Extenders, Centrix - more. \$29.

## COMPUTER PHREAKING

Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS, etc are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system (Ed. Choice, PC Magazine). BBS advice, password defeats, glossary - much more! Manual + Disk\* \$39.

## Beyond PHONE COLOR BOXES

Dozens phone color boxes described - many circuits. Plus Call Forwarding, Conferencing, Phreak History, Glossary, Diverters, Extenders, Loops, REMOBS, Bridging Heads & Cans, Optocom, 3rd Party and many other non-box methods - more. \$39.

## HACKING ANSWERING MACHINES

How answering machines are hacked to listen to - even erase - messages, and to convert them into mini-VMBs. And countermeasures - protect yourself from snoops, stalkers, burglars and pranksters! \$29.

## CREDIT CARD SCAMS

Cardholders, merchants, banks suffer \$ Billions in losses annually because of credit card fraud. Describes every known means of credit card fraud and scams. Protect yourself! \$29.

## AUTOMATIC TELLER MACHINES

ATM crimes, abuses, vulnerabilities and defeats exposed! 100+ methods detailed. Include: Physical, Reg. E, cipher, PIN compromise, card counterfeiting, magnetic stripe, false front, TEMPEST, Van Eck, tapping, spoofing, inside job, super-cool, vibration, pulse, high voltage - others. Case histories - law countermeasures, detailed security checklist, labeled internal photos, figures. ATMs contain up to \$250,000 in cash! Recent \$350,000 ATM crime spree still unsolved! \$39.

## CONS, SCAMS & SWINDLES

Cons & scams and related swindles fleeces Americans of \$100+ Billion per year! The most comprehensive survival manual on cons & scams of all kinds - from the classic to hi-tech. Details on 100s and many variations. And countermeasures. Protect yourself! \$39.

## INTERNET CONS & SCAMS

Internet cons, scams and related frauds now rake in \$2+ Billion annually! Most are done anonymously and with little fear of prosecution (difficult to prove and to find the perpetrators). Described in detail, includes countermeasures. \$29.

## Beyond VAN ECK PHREAKING

Eavesdropping on TV and computer video signals using an ordinary TV described in detail. Includes security industry reports. Range up to 1 KM. Plans include both the Consumertronics and the original Top Secret Van Eck designs! \$29.

## The HACKER FILES

Compilation of 100s of the best articles written (in ASCII) by top hackers & phreakers. Covers every major topic in hackerdom! 3 HD Disks\* \$59.

## STOPPING POWER METERS

As reported on CBS "60 Minutes": How certain devices can slow down - even stop - without meters - while loads draw full power! Device simply plugs into one outlet and normal loads into other outlets. Also describes meter creep, overload drop, etc. Plans \$29. **I.Q. MANUAL:** External magnetic ways (applied to the meter itself) to slow down and stop without meters while drawing full loads. Plans. \$25. **KW-HR METERS:** How without meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow and stop meters by others. \$25. Any 2. \$47. All \$49.

## UNDER ATTACK!

Electromagnetic Interference and Electronic Weapon Attacks cause: Cancer, birth defects, and profound psychological, neurological, cardiovascular and immune system disorders! Destructive to people, animals, plants, equipment! Includes ACTUAL CASES OF EM ATTACKS (we investigated)! Includes how to verify and pinpoint EM and electronic attack sources, and effective countermeasures. \$29. **EM BRAINBLASTER:** Tutorial and plans for powerful ELECTROMAGNETIC WEAPONS and LAB DEVICES. Optimum circuits, freqs, waveforms, duty cycles. Intensities. Thorough. \$29. Both \$49.

## MIND CONTROL

Concern and fear increases over EM and ultrasonic mind (and body) control technologies - especially implants! Unfortunately, there is much more misinformation and disinformation published than facts. Some victims are controlled and exploited by arm-chair "experts" and so-called victims' assistance groups - one even demands the poisoning of the Internet to prevent and remove postings it doesn't approve of! \$39. Visit our site at: <http://users.aol.com/wizguru/mindcontrol.html>

## RADIONICS MANUAL

Exciting electrical, electronic, electromagnetic therapeutic, diagnostic & preventive devices (mostly experimental). History, descriptions, plans (dozens), availabilities of Radionics Devices from early to modern. While drugs cost \$100s, electricity costs pennies! \$29. **HEAL THYSELF:** Plans for 3 major electronic therapeutic devices of types approved by FDA. \$19. Both \$39.

## HIGH VOLTAGE DEVICES

HV devices plans: Blum Blum, Yagor, Prod, Cane, Blaster, Flasher, Zapper, Audio-RF, Hammer, Fence Charger, Plasma & Van de Graaff Gens., Jacob's Ladder, Geiger Counter, Ozone Gen., Fish Stunner, Plant Stim., Kirlian, more! All plans for only \$29.

## STEALTH TECHNOLOGY

Police radar is fascinating! It also has error rates of 10-20%! Every known error mode - stealth method and material used to minimize radar reflections - tactic and strategy to fight unjust radar tickets (that cost you \$100s in insurance and risk cancellation) - methods to detect and jam signals - fully described! \$29.

## SECRET & SURVIVAL RADIO

Optimum survival and security radio equipment, methods, freq allocations and voice/data scrambling/encoding. Includes small receivers/transmitters, telemetry, antenna optimizations, remote monitoring and control, security, surveillance, and ultrasonic, fiber-optic and infrared commo. 70+ circuit plans, tables. \$29.

## CRYPTANALYSIS TECHNIQUES

Five powerful menu-driven crypto programs (in .COM and .BAS source code) to analyze, decrypt "secure" cipher texts. Worked-out examples. Recommended by prestigious "Computers & Security." Manual + Disk\* \$29.



## WHITE-STAR ELECTRONICS

TEL: 405-631-5153 FAX: 405-631-4788

|                                        |           |           |             |
|----------------------------------------|-----------|-----------|-------------|
| <b>CONVERTERS:</b>                     | <b>20</b> | <b>50</b> | <b>100+</b> |
| Regal CR-83                            | 45        | 39        | 35          |
| * New, Panasonic TZPC 145              | 75        | 69        | 65          |
| DQN-5 (2 or 3) (unmodified)            | 45        | 39        | 35          |
| DRZ-3 PJ (unmodified) 70 Channel Plain | 35        | 32        | 29          |
| DRX-3 PJ (unmodified) 60 Channel Plain | 32        | 30        | 27          |

Call for **FREE** catalog.  
405-631-5153




### REMOTE CONTROL

|                                 |           |           |             |
|---------------------------------|-----------|-----------|-------------|
| <b>HAND UNITS:</b>              | <b>20</b> | <b>50</b> | <b>100+</b> |
| Jerrold Replaces: 400/450/550   | 4.95      | 4.50      | 4.25        |
| Scientific Atlanta: 075/175/475 | 4.95      | 4.50      | 4.25        |
| 8600: On screen display         | 7.50      | 7.00      | 6.50        |
| Pioneer: BR 81, 82              | 4.95      | 4.50      | 4.25        |
| Panasonic: Call for model #     | 7.50      | 7.00      | 6.50        |
| Zenith: All                     | 4.95      | 4.50      | 4.25        |
| Tocom: 5503-VIP, 5503-A         | 7.00      | 6.50      | 6.25        |
| Universal: 4 in 1 R/M           | 7.50      | 7.00      | 6.50        |

Call for Oak, Hamlin, Regal-83, Regency, Texscan, and all others.

### Tamper-Bit tools: (10-lot)

|                          |         |
|--------------------------|---------|
| Jerrold compatible bits: |         |
| 1/4" Stacom Bit          | \$8.00  |
| Oval Round D             | \$20.00 |
| <b>Torx Bit:</b>         |         |
| Tocom T-8                | \$8.00  |
| Zenith T-10, T-15        | \$8.00  |
| Pioneer T-20             | \$8.00  |
| Scientific Atlanta T-20  | \$8.00  |
| Pio 63XX Oval            | \$20.00 |
| Bit Driver Handle        | \$4.00  |

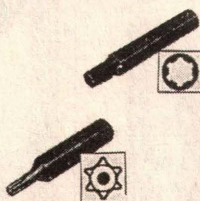

We carry most remote hand units. If you don't find the one you're looking for, we can locate for you.

*Specializing in large quantities.*

HOURS: Monday thru Friday 9 am to 5 pm Central Time.

Call for **FREE** catalog.

CIRCLE 314 ON FREE INFORMATION CARD

## RF POWER TRANSISTORS AND TUBES


In depth stocking of popular and hard-to-find Electronics Parts for Transmitters & Linear Amplifiers

### Popular Transistors

2SC1969  
2SC2166 • 2SC2290  
2SC2312C • 2SC2879  
MRF454 • MRF455  
MRF455A • MRF477  
MRF492 • MRF497  
SRF3749 • SRF7000-90
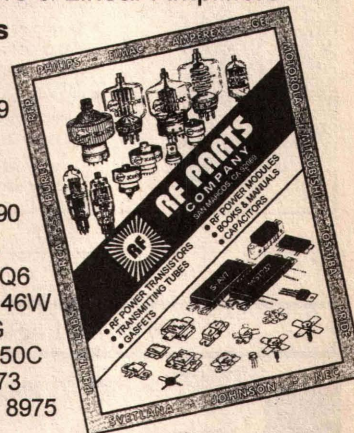
### Popular Tubes

6KD6 • 6JS6C • 6LQ6  
M2057 • 6146B • 6146W  
3-500Z • 3-500ZG  
811A • 572B • SV6550C  
7558 • 8417 • 8873  
8874 • 8875 • 8877 • 8975



Order your **FREE** copy of our new Catalog by writing or calling us now.

(619) 744-0700 • (800) 737-2787


Fax: (619) 744-1943



## RF PARTS

435 SOUTH PACIFIC STREET  
SAN MARCOS, CA 92069

## REMOTE CONTROL A/B SWITCH

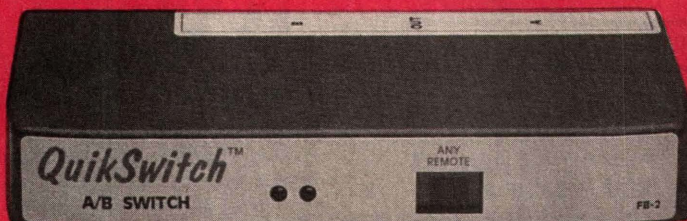

\$ **29**<sup>95</sup>

**A/B/C SWITCH \$39**<sup>95</sup>

Plus Shipping - Money Back Guarantee  
DEALER PRICING ON REQUEST

## CONTROLLED BY ANY REMOTE!

Now you can switch between two TV signal sources without getting up or even reaching for a different remote control! Simply press any button on any remote control and hold it down for two seconds. QuikSwitch contains a patented sensor that causes it to switch sources each time it receives an uninterrupted infrared signal for two seconds. And you won't need a spare AC outlet, because QuikSwitch operates a full year on 2 "AA" alkalines, 3 years on lithiums!

HIGH ISOLATION

100% SOLID STATE

MADE IN U.S.A.



## MILESTONE PRODUCTS


5698 WESTBOURNE AVE - COLUMBUS, OH 43213

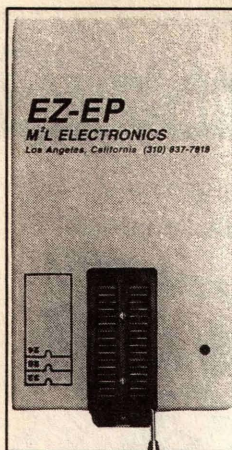**1-800-535-7827**



Licensed Under U.S. Patents 4,935,733 and 5,047,765 Other Patents Pending





### EZ-EP DEVICE PROGRAMMER - \$169.95

**Fast** - Programs 27C010 in 23 seconds.

**Portable** - Connects to PC Parallel Port.

**Versatile** - Programs 2716-080 plus EE and Flash (28F,29C) to 32 pins.

**Inexpensive** - Best for less than \$200

- Correct implementation of manufacturer algorithms for fast, reliable programming.
- Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web page.
- Full over current detection on all device power supplies protects against bad chips and reverse insertion.
- Broad support for additional devices using adapters.

#### Adapters Available


|                                  |         |
|----------------------------------|---------|
| EP-51 (8751,C51)                 | \$39.95 |
| EP-11 (68HC11 E/A)               | \$59.95 |
| EP-PIC (16C5x,61,62x,71,84)      | \$49.95 |
| EP-PIC64 (16C62,63,64,65,73,74)  | \$39.95 |
| EP-PEEL (ICT 22V10, 20G10, 18V8) | \$59.95 |
| EP-SEE (93x,24x,85x)             | \$34.95 |
| EP-16 (18bit 40 Pin EPROMs)      | \$49.95 |
| EP-49 (8742,48,49)               | \$49.95 |
| EP-750 (87C750,751,752)          | \$59.95 |
| EP-Z8 (286E03,04,05,06,07)       | \$39.95 |
| EP-55 (8755)                     | \$39.95 |
| EP-51-PLCC (8751,C51)            | \$59.95 |
| EP-PIC-SOIC (16C5x,61,62x,71,84) | \$59.95 |
| EP-PLCC (PLCC EPROMs)            | \$49.95 |
| EP-SOIC (SOIC EPROMs)            | \$49.95 |
| EP-LCC (LCC EPROMs)              | \$49.95 |

#### M<sup>2</sup>L Electronics

3526 Jasmine #4; Los Angeles, CA 90034  
310/837-7818 Fax/BBS: 310/841-6050

<http://www.cs.ucla.edu/csd-grads-gs3/moving/www/m2l.html>  
CA orders add 8.25% sales tax. Ground shipping - \$5; 3 Day - \$7; 2 Day \$10; Overnight \$17; COD \$4.75.

### NEW!! Checker 12 E Monitor tester

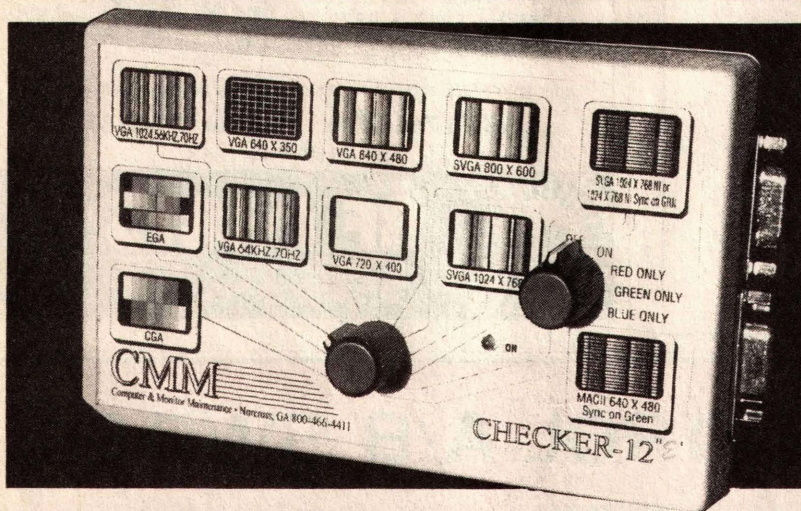

### COLOR BARS, GRAY SCALE & SWEEPS TO 64 K hz!!!!!!

The "Checker 12" is an easy to operate, hand held, battery, or AC operated computer color monitor pattern generator. With its support of CGA(15.75khz), EGA(22khz), MACII(35khz), and VGA modes 1,2,3 (31.5khz), 800X600(35khz), 1024X768 interlaced (35khz), 1024X768 non-interlaced, & 1024X768NI with sync on Green (48khz), ++ 2 NEW VGA MODES>>> 56 kHz x 70 Hz & 64 kHz x 70 Hz. With its' single mode switch, you know exactly what type of monitor you are testing. Its' front panel color pictures, show just what you should be seeing on the monitor under test. You can quickly tell if the monitor is a VGA, SVGA, or a SVGA/NI. guessing. The "Checker 12" provides various test patterns for VGA monitors. X-hatch, for size and linearity and convergence set-up. White screen, for purity and CRT burn evaluation. Color bars and 8 step gray scale for color tracking and balance. There is also a single color mode that allows for single color channel operation.

**Price: \$339.00 + \$5.00 S&H.**

Includes battery, AC adapter, Mac adapter and 1 year warranty  
(upgrade your Checker 12 to a 12 E for \$49, call for details)

Please call about our other monitor test products, and offers, or visit our Webb site.



Computer & Monitor Maintenance

6649 Peachtree Ind., Blvd., Suite N-1 • Norcross GA 30092

1-800-466-4411, 770-662-5633 (Voice), 770-840-8814 (Fax)

We're on the WEBB at <http://www.computermonitor.com>

CIRCLE 331 ON FREE INFORMATION CARD

### BEST DEALER PRICING!

## CABLE DIRECT

CONVERTERS • FILTERS  
DESCRAMBLERS

IMPROVE YOUR IMAGE WITH  
VIDEO STABILIZERS



100%  
MONEY BACK  
GUARANTEE!

30 DAY  
FREE  
TRIAL!

FREE Cable TV Catalog.




Now you can tune-in your favorite  
cable TV programming and  
**SAVE \$100'S - EVEN \$1000'S**  
on premium **CABLE TV EQUIPMENT.**

## MODERN ELECTRONICS

**1-800-906-6664**

2125 S. 156TH CIRCLE • OMAHA, NE 68130

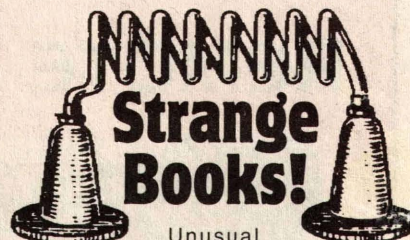

Unusual,  
detailed how-to books, manuals, references,  
old & new, for experimenters, builders, and  
mad scientists on high voltage, Tesla, crystal  
sets, very early radio and television, vacuum  
tube gear, plastics, chemistry, lasers, more!  
Repair cameras! Make neon signs! Make  
whiskey! Hydrogen fuel! A solar cell! A wind-  
mill! Electric bicycle! More! Highest quality!  
Guaranteed! Big illustrated catalog! Write!

### Lindsay's Technical Books

PO Box 538-EBA, Bradley IL 60915

fax:815/935-5477 • [lindsay@keynet.net](mailto:lindsay@keynet.net)

### Prototype it..... FAST!

Run prototype applications or experimental hardware from the serial port - WITHOUT PROGRAMMING!

with ProtoQuick 8051 or Z8

- Complete single board computers
- Up to 32K EPROM and 8K RAM
- 12 sq. in. plated-through proto area
- RS232 C serial port w/ DB25 conn.
- Op sys. in EPROM w/ source code
- Assembled, ready to run - 5v. only
- MS-DOS cross-assembler included

**\$99.00** each

Software Science  
1750 Roundbottom Road  
Cincinnati, OH 45244 USA  
(513) 561-2060



# MCM ELECTRONICS®

**ELECTRONICS NOW READERS ONLY!**  
Save up to 50% on select items!  
Take advantage of  
this tremendous offer.  
Call today, time is limited!

To take advantage of this offer,  
you must supply this special price code:

**CODE: ENS28**

**20<sup>th</sup>  
Anniversary  
1996**

## Value And Selection From One Source...

- Test Equipment from Tenma, Fluke, Hitachi, Leader, B+K
- Name Brand and Low Cost Generic Technician's Tools
- OEM and Generic TV/VCR repair parts
- Over 10,000 American and Original Japanese Semiconductors

**MCM offers a comprehensive line of tools and test equipment engineered for the repair of computers, TVs, VCRs and more. In addition, you will find a wide variety of OEM and low cost generic TV/VCR parts, passive components and semiconductors, over 25,000 items in all, stocked and ready to ship.**



**SAVE  
23%**

### IR Remote Control A/B Switch

Allows wireless switching between two 75ohm inputs. Ideal for cable, antenna, dish or dual cable systems. Requires 12VDC, 100mA, AC adaptor included. Remote requires two "AA" batteries, not included. UL listed.

**#32-4425** Reg. \$25.75 Sale **\$19.75**

Prices effective

October 3 through November 16, 1996

Hours: M-F 7 a.m.-9 p.m., Sat. 9 a.m.-6 p.m., EST.

**For Complete Information On the items listed, or a FREE catalog, Call...**

## 1-800-543-4330



**MCM ELECTRONICS®**

650 CONGRESS PARK DR.  
CENTERVILLE, OH 45459-4072

A PREMIER Company


**RITE  
OFF**

### Projection Television (PTV) Coolant

Popular fluid is used by many large screen TV manufacturers and is a must when replacing CRTs in projection televisions. Direct replacement for Magnavox #4835-310-57233 and RCA 212072. 7.5 oz. can, 24 cans per case.

**#20-2040**

Reg. \$4.99

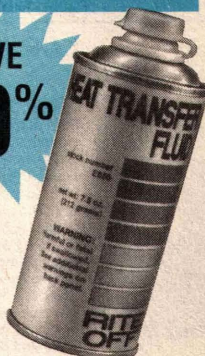

**SAVE  
20%**

Sale **\$3.99**

**SAVE  
50%**



**#22-1145**



**#22-1150**

### Security Bit Drivers For Nintendo and Sega

Driver bits allow easy removal of security screws found on many home video games, cartridges and accessories. 1/4" hex size fits standard 1/4" nut driver (MCM #22-1620) and most rechargeable screwdrivers. Available in two sizes.

**#22-1145 3.8mm** Reg. \$7.99 Sale **\$3.99**

**#22-1150 4.5mm** Reg. \$7.99 Sale **\$3.99**



**FREE  
Catalog**

**RCA/GE**

Premier  
Distributor

**Authorized  
Panasonic  
Quasar/Technics  
Original Parts  
Distributor**

**Fast Delivery From Distribution Centers Near Reno, NV and Dayton, OH.**

**CODE: ENS28**

CIRCLE 327 ON FREE INFORMATION CARD



# ALFA ELECTRONICS


HIGH QUALITY TEST EQUIPMENT  
BEST PRICE



## DMM 89 \$179.00
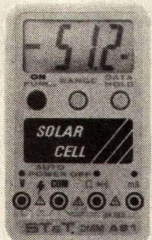
### Most Advanced DMM

All Purpose & Communication  
-80.7 to 81.4 dBm with 4Ω-1200Ω  
20 reference impedances  
True RMS  
Frequency counter: 0.01Hz-10MHz  
Capacitance: 1pF-50,000μF  
Measure AC volt to 20kHz  
5000 counts, 0.1% accuracy  
Auto/manual range, fast bar graph  
Min/Max/Ave/DH/Relative/Zoom  
Auto power off  
Input warning  
Splash proof  
Volt, amp, ohm, logic, diode, continuity  
Ruggedized case  
Rubber holster included



## DMM A91 \$49.95

### NOW \$45.00

### Plus Free Case Solar Cell Powered Large Display

Diode, Continuity  
Volt, Amp, Ohm  
Data Hold  
Auto power off  
7 functions, 19 ranges  
3.5 Digit, 0.8% accuracy  
Auto/Manual ranging  
Energy saver  
Student & hobbyist's favor



## DMM 20 \$74.95

Inductance: 1μH-40H  
Capacitance: 1pF-200μF  
Frequency: 1Hz-20MHz  
Volt, amp, ohm, diode,  
20 Amp AC/DC current  
Transistor HFE  
Continuity, duty %  
Peak hold/Max  
Ruggedized case  
Rubber holster \$8.00

Full line of DMMs,  
economy, compact,  
ruggedized, solar cell,  
automotive, heavy  
duty, industrial,  
starts from \$19.95

Fluke Multimeter  
Fluke 12 \$84.95  
Holster C-10 \$10  
Fluke 70 II \$75.95  
Fluke 73 II \$97.50  
Fluke 75 II \$129  
Holster C-70 \$16  
Fluke 77 II \$155  
Fluke 79 II \$175  
Fluke 29 II \$175  
Fluke 76 \$175  
Fluke 87 \$287  
Fluke 867 \$1199  
Fluke 97  
Scope Meter \$1785  
Fluke 105  
Scope Meter \$2799



## LCR Meter 131D \$229.95

### Most Advanced LCR

Dual display: L/Q or C/D  
Inductance: 0.1μH-1000H  
Capacitance: 0.1pF-10,000μF  
Impedance: 1mΩ-10MΩ  
0.7% basic accuracy  
Auto/manual range  
Dissipation factor & Q factor  
Serial & parallel mode  
Relative mode for comparison  
and to remove parasitics  
Statistics, tolerance,  
Best for design, incoming  
testing & production  
SMD and chip component  
test probe \$25.00




## LCR Meter 814 \$189.95
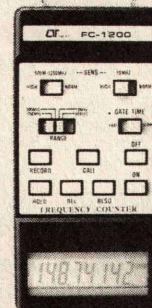
### Best Resolution LCR

Inductance: 0.1μH-200H  
Capacitance: 0.1pF-20,000μF  
Resistance: 1mΩ-20MΩ  
1% basic accuracy  
Dissipation factor indicates leakage  
in capacitor and Q factor in inductor  
Zero adjustment to reduce parasitics  
Best for high frequency RF  
SMD and chip component test probe  
\$25.00



LIMITED QUANTITY SPECIAL  
DIGITAL LCR 680 \$74.95  
0.1pF, 1μH, 10mΩ resolution


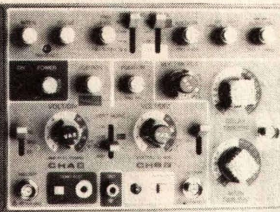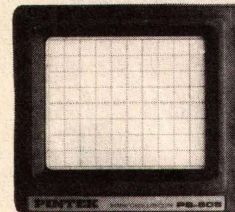
## Frequency Counter FC-1200 \$129.95

Frequency: 0.1Hz-1.25GHz  
Display: 8 digit LCD  
Period: 0.1μs-0.1s  
Records Max/Min/Average  
Data hold, relative mode  
Telescoping antenna \$8.00  
Deluxe case \$5.00

Also Available:  
AC/DC clamp meter, Light meter,  
Thermometer, pH meter, High  
voltage probe, Digital caliper,  
Anemometer, Electronic scale,  
Force gauge, Tachometer,  
Stroboscope, Humidity & EMF  
adapter, Sound level meter,  
Frequency counter, SWR/field  
strength/power meter, Dip meter



## 20 MHz Oscilloscope with Delay Sweep PS-205 \$429.95


Dual Trace, Component test, 6" CRT, X-Y Operation, TV  
Sync, Z-Modulation, CH2 Output, Graticule Illum, 2 probes  
each has x1, x10 switch. Best price with delay sweep.  
PS-200 20 MHz DUAL TRACE \$339.95  
PS-400 40 MHz DUAL TRACE \$494.95  
PS-405 40 MHz DELAY SWEEP \$569.95  
PS-605 60 MHz DELAY SWEEP \$769.95  
PS-1000 100 MHz DUAL TRACE \$999.95  
Scope Probe: 60MHz x1, x10 \$15, 100MHz x1, x10 \$22  
250MHz x1, x10 \$29, 250MHz x100 \$39

## Digital Storage Scope

DS-303 30MHz, 20M Sample/sec \$849.95


DS-303P with RS-232 interface \$1,049.95

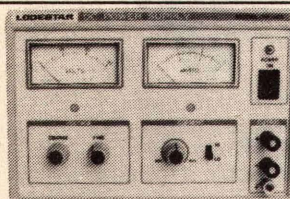Switchable between digital and analog modes  
2 K word per channel storage  
8 bit vertical resolution (25 Lere/div)  
Expanded Timebase 10ms/div - 0.5 s/div  
Refresh, Roll, Save all, Save CH2, Pre-Trig  
Plotter control




## DC Power Supply PS-303 \$159.00

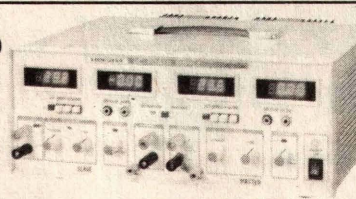0-30 VDC, 0-3A output  
Constant voltage & constant current mode  
0.02% + 2mV line regulation  
0.02% + 3mV load regulation  
1 mVrms noise and ripple  
Short circuit and overload protected  
PS-8200 with digital voltmeter \$179.00  
Also available: 30V/5A, 60V/3A, 60V/5A  
16V/10A, 30V/10A


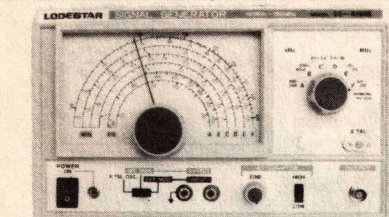
## DC Power Supply Triple Output PS-8202 \$499.95

Two 0-30 VDC, 0-3A outputs  
One fixed 5VDC, 3A output  
Capable of independent or tracking operation  
Constant voltage and constant current mode  
Four digital meters for volt and current display  
Excellent regulation and low ripple  
Short circuit and overload protected  
Also available: 30V/5A triple output \$549.95  
Dual tracking 30V/3A, 30V/5A, 60V/3A, 60V/5A



## RF SIGNAL GENERATOR SG-4160B \$124.95

100 kHz-150MHz sinewave in 6  
ranges  
RF Output 100mVrms to 35 MHz  
Internal 1kHz, External 50Hz-20kHz  
AM modulation  
Audio output 1 kHz, 1 Vrms

## AUDIO GENERATOR AG-2601A \$124.95

10Hz - 1MHz in 5 ranges  
Output: 0-8Vrms sinewave  
0-10Vp-p squarewave  
Synchronization: ±3% of oscillation  
frequency per Vrms  
Output distortion:  
0.05% 500Hz - 50kHz  
0.5 % 50Hz - 500kHz  
Output impedance: 600 ohm

## FUNCTION GENERATOR FG-2100A \$169.95

0.2 Hz - 2 MHz in 7 ranges  
Sine, square, triangle, pulse and ramp  
Output: 5mV-20Vp-p  
1% distortion, DC offset ± 10V  
VCF: 0-10V control frequency to 1000:1

## FUNCTION GEN/COUNTER FG-2102AD \$229.95

Generates signal same as FG-2100A  
Frequency counter 4 digits  
Feature TTL and CMOS output

## SWEEP FUNCTION GEN/COUNTER \$329.95

0.5Hz to 5 MHz in 7 ranges  
Sweep: Linear 10:1/Log 10:1 20ms to 2s  
AM Modulation  
Gated Burst, Voltage Control Generator  
Generator Control Voltage & 6 digit counter  
1Hz-10MHz for internal & external sources



## RF SIGNAL GEN./COUNTER SG-4162 AD \$229.95

Generates RF signal same as  
SG-4160B  
6 digit frequency counter 1Hz - 150  
MHz for internal and external  
source Sensitivity <50mV

## AUDIO GEN./COUNTER AG-2603AD \$229.95

Generates audio signal same as  
AG-2601A  
6 digit frequency counter 1Hz-  
150MHz for internal and external  
sources Sensitivity <50mV

# ALFA ELECTRONICS

741 Alexander Rd., Princeton, NJ 08540

(800) 526-2532/(609) 520-2002

FAX: (609) 520-2007

Visa, Master Card, American Express, COD, Purchase Order Welcome

15 DAY MONEY BACK GUARANTEE. 1 YEAR WARRANTY


CALL OR WRITE FOR FREE CATALOG

CIRCLE 213 ON FREE INFORMATION CARD



**100 MHz Cursor Readout Scope  
4 ch, 8 traces OS-6101 \$1,499.95**


- \* 4 independent channels, 8 traces
- \* Time/Voltage cursor measurement
- \* ALT triggering function for 4 ch.
- \* Sweeps to 2ns/div, Delayed Sweep
- \* TV Sync., Ch. 1 output, Z-axis input
- \* 2 probes(x1, x10)

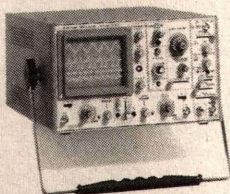**100 MHz Scope, 4ch. 8 traces  
Best value all purpose scope  
OS-6100B \$1,329.95**


- \* 4 channels, 8 traces
- \* High sensitivity 500µV/div
- \* Sweeps to 2ns/div, Delayed sweep
- \* 20 kV accelerating voltage
- \* TV sync., Z-axis input
- \* A and B gate output
- \* Best price 100 MHz scope
- \* 2 probes(x1, x10)

**50 MHz Triggering Oscilloscope  
OS-653 \$699.95**


- \* Dual Channel
- \* Hold Off Function
- \* Delayed Sweep
- \* Built-in Delay Line
- \* TV Sync
- \* ALT Triggering
- \* High sensitivity 1 mV/div
- \* Trigger level lock function
- \* Z-axis input, CH1 output
- \* 2 probes(x1, x10)

**20 MHz Oscilloscope  
OS-622B \$344.95**


- \* Dual trace, X-Y operation
- \* TV Sync., Z-axis input, CH1 output
- \* High sensitivity 1 mV/div
- \* Trigger level lock
- \* 2 probes (x1, x10)

OS-623B - 20 MHz w/Delayed Sweep.....\$ 449.95  
OS-935 - 5 MHz One channel.....\$ 209.95

**DC Linear Power Supplies  
Single Output**


- \* Constant voltage and constant current mode
- \* Voltage regulation  $\leq 0.01\%$
- \* Current regulation  $\leq 0.2\%$
- \* Low ripple and noise
- \* Overload and reverse polarity protection
- \* Features 2 analog or 1 digital meter (PS series)
- \* 2 analog or 2 digital meters (PR series)

|                            |          |
|----------------------------|----------|
| PS-1830 : (0-18V, 0-3A)    | \$209.95 |
| PS-1830D : Digital Display | \$219.95 |
| PS-1850 : (0-18V, 0-5A)    | \$219.95 |
| PS-1850D : Digital Display | \$244.95 |
| PS-3030 : (0-30V, 0-3A)    | \$224.95 |
| PS-3030D : Digital display | \$254.95 |
| PS-6010 : (0-60V, 0-1A)    | \$209.95 |
| PR-1810H : (0-18V, 0-10A)  | \$349.95 |
| PR-3060 : (0-30V, 0-6A)    | \$314.95 |
| PR-6030 : (0-60V, 0-3A)    | \$314.95 |
| PR-6030D : Digital Display | \$399.95 |

**Triple Output DC Power Supplies**


- \* Two variable 0-30VDC, 0-3A outputs
- \* One fixed 5VDC, 3A output
- \* Auto tracking
- \* Auto serial and parallel operation
- \* Constant voltage and constant current mode
- \* Continuous/dynamic load can be selected
- \* Features 4 analog or 2 digital displays

|                            |          |
|----------------------------|----------|
| PC-3030 : (0-30V, 0-3Ax2)  | \$499.95 |
| PC-3030D : Digital display | \$549.95 |

**Programmable DC Power Supplies**

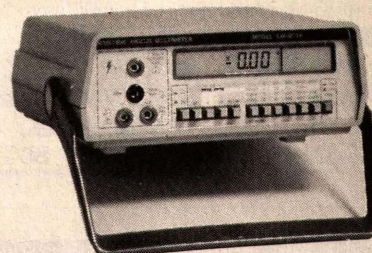

- \* High stability, low drift, 4 digit display
- \* Front/rear output-sense switch selectable
- \* Auto step running w/timer settings
- \* 100 point programmability (PPS series)
- \* 50 point programmability (PPT series)
- \* Auto serial and parallel operation (PPT series)
- \* Auto tracking (PPT series), IEEE-488.2 and SCPI compatible command set (optional)

|                                           |           |
|-------------------------------------------|-----------|
| PPS-1860G : (0-18V, 0-6A)                 | \$1099.95 |
| PPS-3635G : (0-36V, 0-3.5A)               | \$1099.95 |
| PPS-6020G : (0-60V, 0-2A)                 | \$1099.95 |
| PPT-1830G : (0-18V, 0-3Ax2, 0-6V, 0-5A)   | \$1399.95 |
| PPT-3615G : (0-36V, 0-1.5Ax2, 0-6V, 0-3A) | \$1399.95 |

**Digital Display Function Generator  
FG-8016G \$239.95**

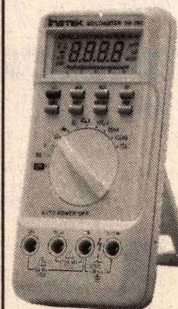

- \* Frequency Range: 0.02Hz to 2MHz
- \* Three Instruments in one: Function generator, Pulse generator & Frequency counter
- \* Sine, Triangle, Square, TTL Pulse and CMOS output
- \* Built-in 6 digit counter with INT/EXT function
- \* 1000:1 tuning range
- \* Variable DC offset control

|                                          |          |
|------------------------------------------|----------|
| FG-8015 Function Generator               |          |
| * 0.02Hz-2MHz (No Counter).....          | \$189.95 |
| FC-8131 Intelligent Counter 1.3GHz ..... | \$469.95 |
| FC-8270 Intelligent Counter 2.7GHz.....  | \$629.95 |
| UC-2010G Universal Counter.....          | \$294.95 |

**Digital Multimeter & C Meter  
DM-8034(3½ digits) \$179.95**


- \* 8 Function, AC/DC voltage, AC/DC current, resistance
- \* Built-in C meter, diode test and audible continuity check
- \* High voltage 1000V and 20A range
- \* 0.5% basic accuracy

|                                      |          |
|--------------------------------------|----------|
| DM-8040 (3½ Digits, True RMS)        |          |
| * Measures ACV to 50 kHz.....        | \$339.95 |
| DM-8055 (5½ Digits).....             | \$649.95 |
| * 0.006% basic accuracy              |          |
| * 1µV, 1mΩ, 1nA resolution           |          |
| * dBm measurement                    |          |
| * Auto range, relative mode, Max/Min |          |
| DM-8055G(5½ Digits, GPIB).....       | \$889.95 |

**Model DM-392  
(3½ digits) \$109.95**


- \* Auto/Manual ranging(38 ranges)
- \* 42 Segment analog bar graph
- \* Data Hold/Min-Max memory /Relative mode
- \* Auto power off
- \* Overload protection
- \* Audible continuity check /diode test
- \* Capacitance: 1pF-40µF
- \* Frequency: 0.1Hz-1MHz
- \* 20 Amp range
- \* Double high energy fused (1A, 20A)
- \* 0.3% DCV accuracy

|                                                   |          |
|---------------------------------------------------|----------|
| DM-351 : 3½ Digits w/Continuity, Auto Off.....    | \$54.95  |
| DM-352 : 3½ Digits, Cap. Freq. hFE, 20 Amp.....   | \$79.95  |
| DM-353 : 3½ Digits, Cap. Freq. Temp. hFE.....     | \$84.95  |
| DM-391 : 3½ Digits, Auto, Cap. Freq. Min/Max..... | \$99.95  |
| DM-392 : 3½ Digits, Hold, Min/Max 20Amp.....      | \$109.95 |
| DM-393 : 3½ Digits, Peak, Logic, hFE, Freq.....   | \$119.95 |

**ALFA ELECTRONICS**  
741 Alexander Rd., Princeton, NJ 08540


(800) 526-2532/(609) 520-2002 15 DAY MONEY BACK GUARANTEE. 2 YEAR WARRANTY  
FAX:(609) 520-2007  
CALL OR WRITE FOR FREE CATALOG AND QUANTITY DISCOUNT.  
Visa, Master Card, American Express, COD, Purchase Order Welcome

CIRCLE 213 ON FREE INFORMATION CARD


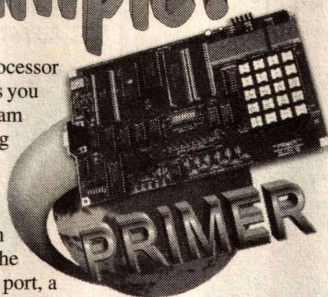
# Learn by Example!

The PRIMER 8085 Based Microprocessor Training and Control System shows you how to program by example. Program examples take you from writing simple programs to controlling motors. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The Upgrade includes: an RS232 serial port, a serial cable, 32K of battery backed RAM and Assembler/Terminal software.



## EXPERIMENTS USING THE PRIMER INCLUDE:

- Measuring Temperature
- Using a Photocell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Using the Primer as an EPROM Programmer


The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed.

# ENAC, inc.

P.O. BOX 2042, CARBONDALE, IL 62902  
618-529-4525 Fax 457-0110 BBS 529-5708

1985 - 1996  
OVER  
**10**  
YEARS  
OF SERVICE
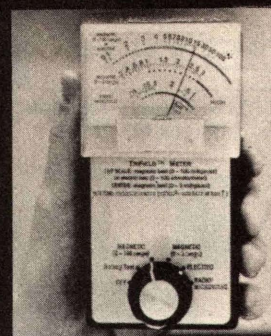
## NOW YOU CAN "SEE" INVISIBLE FIELDS AND AVOID THEM



Most homes and offices have hot spots with strong artificial electro-magnetic fields, where chronic exposure may cause mental or physical problems. Even the EPA names these fields as suspected carcinogens. You can reduce your risk by avoiding these high-field areas.

The **TriField™** meter detects *far more* of these fields than any other electromagnetic pollution meter. It's the only one that independently reads AC electric fields, AC magnetic fields, and radio/microwaves. It also reads field strengths in *all directions simultaneously*. Every other meter that sells for under \$500 reads only magnetic and only in one direction — they can entirely miss a magnetic field unless pointed correctly and are blind to radio/microwaves and electric fields, both of which cause biological effects.

The **TriField™** meter reads all three types of fields numerically and with a **SAFE/BORDERLINE/HIGH SCALE**, weighted proportional to effect on the body. Thresholds are based on epidemiological and laboratory studies. (While no *absolute* hazard thresholds have been established, reduction of *relative* exposure is prudent.)

The **TriField™** meter comes ready-to-use with battery, instructions, and one-year limited warranty. The cost is \$144.50 postpaid.

AlphaLab, Inc. / 1280 South Third West / Salt Lake City, UT 84101-3049  
For literature and information, call (503) 543-6545

## VOICE CHANGERS! ELECTRONIC KITS AND MORE!

### PUT 15 YEARS OF EXPERIENCE TO WORK FOR YOU

Ever since we started in 1981, people have been telling us what they want, and we've delivered. We are pleased to offer a line of quality engineered kits, an iron clad guarantee, Fast, Fast delivery, great prices, and a highly competent Technical support staff that's just a phone call away if you need help. Prices subject to change without notice. Shipping and handling extra. In general our products are available in one or more of the following forms:

#### COMBO-KIT

Indicated by a **C** in the part number. Includes all electronic parts, a printed wiring board, and assembly instructions.

#### E-Z KIT

Indicated by an **E-Z** in the part number. These are mostly assembled and require some simple assembly before they can be used.

#### ASSEMBLED

These products are assembled, tested and ready to use.

### 143.79 MHz CRYSTAL CONTROLLED TRANSMITTER KITS



**XTR300 E-Z** \$79.95  
**XTL3000 E-Z** \$99.95  
**XTL1000 E-Z** \$69.95

#### CRYSTAL TRANSMITTER KITS

- Ultra-miniature surface mount construction.
- E-Z kit approach makes assembly a snap.
- Miniature battery and holder mounted directly to the circuit board.
- Transmit to any scanner type receiver

**XTR300 E-Z TRACKING TRANSMITTER KIT**  
Transmits continuous beep-beep tone. Ideal for locating lost or stolen items. Range up to 1/2 mile. Simply install the battery holder and the antenna wire and the unit is ready to use. Custom frequencies available. 3 Volt photo battery included.

**XTL3000 E-Z LONG RANGE TRANSMITTER KIT**  
Sensitive built in microphone with amazing audio sensitivity. Picks up sounds at the level of a whisper. With a range of up to 1 mile, this is our longest range transmitter. Custom frequencies available. 3 Volt photo battery included.

**XTL1000 E-Z TRANSMITTER KIT**  
Sensitive built in microphone with amazing audio sensitivity. Picks up sounds at the level of a whisper. Up to 1/2 mile range. Custom frequencies available. 3 Volt photo battery included.

## ELECTRONIC KITS!

## BUY WITH CONFIDENCE FROM XANDI ELECTRONICS, INC. ASK ABOUT OUR COMPLETE CATALOG

### 88-108 MHz FM TRANSMITTER KITS



**XST 500 E-Z** \$49.95  
**XWB 1000 E-Z** \$46.95  
**XFM 100 Combo E-Z** \$21.95  
**XSP 250 E-Z** \$34.95  
**XTR 100 Combo E-Z** \$29.95  
**XTT 100 Combo E-Z** \$19.95

**XST 500** Voice transmitter. Range up to 1 mile. Supersensitive mic. Uses 9 volt battery. Uses surface mount components.  
**XWB 1000** Voice transmitter. Range up to 1/2 mile. Includes mic and battery on circuit board. Uses surface mount components.  
**XFM 100** Voice transmitter. Range up to 1 mile. 9 v battery and leaded components.  
**XSP 250** Super-miniature telephone transmitter. Range 1/4 mile. Powered by phone line. Uses surface mount components.  
**XTR 100** Tracking transmitter. Range up to 1 mile. Uses 9 volt battery. Transmits a BEEP - BEEP - BEEP tone  
**XTT 100** Telephone transmitter. Range up to 1 mile. Uses 9 volt battery.

**ORDER BY PHONE:** COD, CHK, MO  
**ORDER LINE:** 1-800-336-7389  
**FAX:** 1-602-731-4748  
**TECH SUPPORT:** 1-602-894-0992

**BY MAIL:**  
**XANDI ELECTRONICS, INC.**  
1270 E. Broadway Rd. #113  
Tempe, AZ 85282

#### PHONE VOICE CHANGER

16 levels of digital voice changing. Sound tougher, older or younger, female or male. Powered by 4 AA batteries. (Batteries not included.)

Works with regular or multi-line phones. Connects between handset and phone. Note: will not work with cordless or handset type telephones.  
T-2001 Assembled \$69.95

### 88-108 MHz FM RECEIVER

**XMR2000 Assembled \$29.95**  
• Works smallest FM radio.  
• As small as a hearing aid.  
• Weighs less than 1/4 oz.  
• Digital touch tuning.  
• Ideal for use with our 88-108MHz FM transmitters

### XANDI ADVANCED HOBBY KITS

**XFS 108 Combo E-Z** \$39.95  
**XLC 900 Combo E-Z** \$49.95  
**88-108 MHz FM STEREO TRANSMITTER KIT**  
• Separate level control for both left and right channels.  
• Output level circuit with test points for quick and easy tuning.  
• Transmit from any stereo audio source to most any FM stereo receiver.  
**800-950MHZ SCANNER CONVERTER KIT**  
• Uninterrupted coverage of the 800 to 950 MHz band!  
• Works with any 400-550MHz scanner.  
• Gain: 6 dB typical.  
• Noise figure: 3 dB typical.  
**VOICE-STRESS ANALYZER KIT**  
• See at a glance if your being lied to!  
• Subject need not be present. Works with voices from recordings, TV or radio.  
• Has built-in microphone.  
• Easy to use LED display output.  
**PROJECT BOX**  
Ideal project box to give your kits that professional look. Available custom drilled for the following kits: XFS108, XPS1000, XLC900, and XVA250. \$14.95

#### BUG DETECTOR

**XBD500 Assembled \$149.95**  
• Professional quality.  
• Not a kit, ready to use.  
• Covers 1 to 2,000MHz.  
• Uses new Microwave Integrated Circuit amplifier.  
• Adjustable sensitivity.  
• Audio jack for privacy ear phone.  
Any intercepted signal causes an audio tone that increases from a low pitched growl to a high pitched squeal as the signal strength increases.



## Electronic CAD for Windows

Professional Windows EDA tools at an affordable price with powerful features to make designing faster. WinBoard PCB layout delivers sophisticated interactive routing for complex designs, plus it has the tools needed for high-speed circuits, analog, RF and SMT designs.

### WinDraft® Schematics


- ◆ Use True-Type fonts. Quickly copy and paste into other applications.
- ◆ Supports hierarchical designs, electrical rules checking, Annotation & Bill of Materials.
- ◆ Thousands of library parts and symbol editor included.

### WinBoard™ PCB layout

- ◆ Supports 16 layers, multiple copper pours, and advanced features for RF designs.
- ◆ SMD & through hole library with on-line graphical editor.
- ◆ CAM outputs include BOM, in-circuit test, NC Drill, Gerber, Pick & Place, & Advanced Design Rule Checking (DRC).

With our unique **pin capacity** versions you only pay for what you need. You choose the base configuration to suit your needs today, and expand that configuration to handle increased pin capacity as your design requirements change.

**New Versions Available Now**

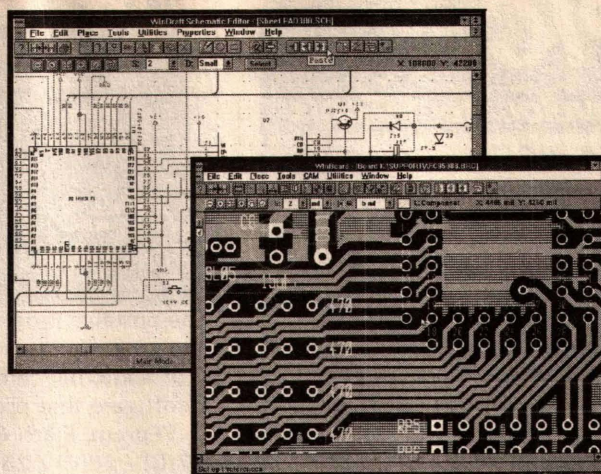

**\$ 250** WinDraft or WinBoard - P650  
**\$ 495** WinDraft or WinBoard - unlimited

**\$ 895** WinBoard P650 with CCT  
 Spectra® autorouter.

Thousands of satisfied customers are using this new generation of powerful and affordable Windows EDA tools from Ivex. Your satisfaction is guaranteed!

**World Wide Web: <http://www.ivex.com>**

Information and free evaluation version is available on the Ivex WW Web, FTP and BBS.

**Tel: (503) 531-3555**  
**Fax: (503) 629-4907**  
**BBS: (503) 645-0576**



Ivex Design International. 15232 NW Greenbrier Parkway. Beaverton, Oregon 97006. USA.

ADV2\_1

CIRCLE 329 ON FREE INFORMATION CARD

## ROBOTIC MACHINING

ROUTE, MILL, DRILL, CARVE, ENGRAVE, PAINT . . . .  
 IN WOOD, PLASTIC, VINYL, PC BOARD, & LIGHT METALS!

- 4 & 5 MOTOR GANTRY MILL CONFIGURATIONS
- PC COMPUTER CONTROLLED CNC/DNC
- IMPORT/EXPORT FILES TO OTHER CADS
- AUTO-BACKLASH COMPENSATION
- PRE-MACHINED HEAVY CASTINGS
- SIMULTANEOUS 4 AXIS MOTION
- FREE 3D CAD/CAM SOFTWARE
- AVAILABLE IN KITS OR ASSEMBLED
- EXPEDITE SERVICE ALSO AVAILABLE
- OPTIONAL ALUMINUM WAY COVERS
- .0005" RESOLUTION / AMERICAN MADE



**STARTING AT  
 \$695.00**

**3 & 4 AXIS UNITS  
 FROM 12" X 12" TO  
 66" X 66" MACH. AREA**

**U.S. CYBERLAB, INC. 14786 SLATE GAP RD., WEST FORK, AR 72774**

**CALL NOW FOR INSTANT SPECS 501-839-8293 24 HR. FAX-BACK**



## PIC Programmer Development Tools

### JM-PICE \$245

- Programmer for PIC 16C5X, 16C6X, 16C7X, 16C84, and 17C4X in DIP packages.
- Assembler and Simulator.
- Emulates program memory, registers, and I/O for the PIC 16C5X.
- Instruction-level emulation for the PIC 16C71 and 16C84.
- Programmer only \$155, Complete package \$245. 15 day money-back guarantee.
- Adapters for emulating 16C6X and 16C7X will be available soon.

## 80C552 Development System

- 8051 core processor with 8 channel 10-bit A/D and PWM.
- 24 more I/O and RS-232 port.
- 32K ROM and 64K RAM.
- \$130 each SBC. High performance development system includes assembler, disassembler, real-time execution and debugging, monitor program, and examples (\$70 more).
- 80C31 Development System is also available.

## ROMY-16 EPROM EMULATOR


Emulates ROM or RAM in 8- and 16-bit systems. \$195 (2716-27256) or \$245 (2716-27010). Window/menu driven interface. 15 day money-back guarantee. Optional assembler, disassembler, and ROM debugger \$100 each CPU.

## 68HC11 Development System

- Eight channel 8-bit A/D converter.
- 32K ROM and 32K RAM.
- \$120 each SBC. 40x2 LCD \$20.
- Add \$70 for the real-time integrated development system.
- Microprocessor Simulator/Debugger and Custom design are available.

**J&M** Microtek, Inc.  
83 Seaman Road, W Orange, NJ 07052  
Tel: (201)325-1892 Fax: (201)736-4567

## The Pocket Programmer Only \$129.95

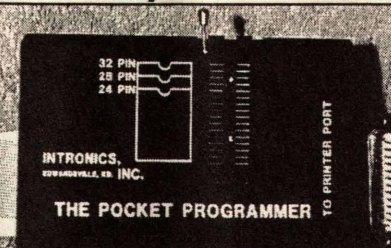

The portable programmer that uses the printer port of your PC instead of an internal card. Easy to use software that programs Eprom, EEprom, Flash & Dallas Ram. 27(C) / 28(C) / 28F / 29F / 29C & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, PLCC, 5-Gang, 874X, 875X MCU's, 40-Pin X 16 & Serial Eprom's, and Eprom Emulator to 32K X 8.

Same Name, Address & Phone # for 13 Years... Isn't it Amazing ?

### Intronics, Inc.

Box 13723 / 612 Newton St.  
Edwardsville, KS 66113 Add \$4.75 COD  
Tel. (913) 422-2094 Add \$4.00 Shipping  
Fax (913) 441-1623 Visa / Master Charge



## Write your PIC programs in BASIC!

Still \$99<sup>95</sup>

The PicBasic Compiler converts your BASIC programs and BASIC Stamp I programs into hex files that can be programmed directly into a PIC microcontroller. New Peek and Poke instructions let you access PORTA, A/D converter and other on-PIC features in BASIC.

- ♦ Expanded BASIC Stamp I compatible instructions
- ♦ True compiler provides faster program execution and longer programs than BASIC interpreters
- ♦ In-line assembler and Call support
- ♦ Supports PIC16C6x, 62x, 7x and 8x micros
- ♦ Pocket PIC Programmers from \$34.95
- ♦ PICProto prototyping boards \$9.95 - \$19.95

\*BASIC Stamp is a trademark of Parallax, Inc.

**microEngineering Labs**

Box 7532 Colorado Springs CO 80933  
(719) 520-5323 FAX 520-1867  
<http://www.melabs.com>




## INTERFACE TO YOUR PC KEYBOARD INPUT!


Our KE-18 Keyboard Encoder converts input from switches and keypads into PC compatible keyboard signals.

- Use with or without your own PC's keyboard
- Scans 9 x 9 matrix or 18 individual inputs
- PCXT, AT, PS/2 and Compatibles
- Looks like a Keyboard to your Computer

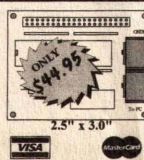**Hagstrom Electronics**  
2 Green Lantern Boulevard  
Endicott, NY 13760 (607) 786-7523



## BAC552ES CONTROLLER

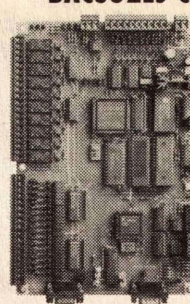

- Enhanced BASIC Language
- Phillips 80C52 MCU
- 6"x9" circuit board
- 10 5A relay outputs
- 3 LED or logic outputs
- 16 opto-isolated inputs
- 8 ch. 10 bit analog inputs
- 2 ch. 8 bit analog outputs
- Real Time clock/calendar
- 128K Static RAM
- 128K FLASH memory
- 256 byte serial EEPROM
- 3 serial ports (RS232C/485)
- IIC bus expansion
- Plug-on I/O terminal blocks
- Single 12Vdc operation

## APPLICATION READY ONLY \$334<sup>90</sup>

Includes \$14.95 Connector Package!

APPLICATIONS: Industrial control • HVAC systems • security  
• home automation • data logging • remote control & monitoring

**SYLVA Control Systems** a division of Sylva Energy Systems Inc.

519 Richard Street, Thunder Bay, Ontario, Canada P7A 1R2


Ph. 807-768-2487 Fax 807-683-6485 BBS 807-767-0587

WEB PAGE: <http://www.sylvacontrol.baynet.net>

Email: [sylva@mail.baynet.net](mailto:sylva@mail.baynet.net)

## 16 Bit Control

& Data Acquisition System

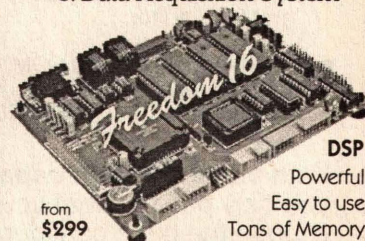

from \$299

DSP

Powerful,

Easy to use,

Tons of Memory,

I/O & features:

16.8MHz 68HC16  
RS-232 & RS-485  
RT clock option

34 digital I/Os (7 IRQ)  
+ LCD/Keypad port  
+ 8 ch 10b fast A/D

Affordable "C" compiler/library  
Multi-tasking kernel  
Up to 256K ea. SRAM, FLASH memory

**INTEC INOVENTURES INC.**

Ph: (604) 721-5150 FAX: 721-4191

<http://www.islandnet.com/~iii>

## WINDOWS 95

—One Step at a Time

Don't know what to do when confronted with Microsoft's Windows 95 screen? Then you need a copy of **Windows 95—One Step at a Time**. Develop your expertise with the straight-forward presentation of the frequently-used features that make Windows 95 so valuable to the PC user.



To order Book BP399 send \$6.95 plus \$3.00 for shipping in the U.S. and Canada only to **Electronics Technology Today Inc.**, P.O. Box 240, Massapequa Park, NY 11762-0240. Payment in U.S. funds by U.S. bank check or International Money Order. Please allow 6-8 weeks for delivery.



# Keep your PCs up & running with the 100% accurate fix...

**Loop-back Plugs**—9-pin serial, 25-pin serial and 25-pin parallel plugs, used for external I/O port testing.

## Universally Compatible

Works with any IBM or compatible computer and any operating system (DOS, Windows 95 & NT, OS/2, Unix, Novell, etc.

## Micro-Scope™ diagnostic diskettes

containing the best PC diagnostic tools on the market. Comes with both 3.5" and 5.25" disks to work with any PC.

## Durable Zip-up Leatherette Carrying Case

all your tools in one organized, easy to carry toolkit.

## Complete Micro-Scope Manual

easy to follow testing procedures and detailed error code descriptions. See the features list at left to view some of the incredible wealth of testing capabilities this program contains.

Revive Your Dead PCs

**Tri-State Logic Probe**—works with Post-Probe to enable testing down to individual chip level.

## Post-Probe™ Diagnostic Card

when Post-Probe detects an error, a 2-digit BIOS code will display on the card telling you exactly what's wrong with your PC. 100% compatible with all ISA, EISA, Compaq and Micro-Channel PCs.

## Micro-Channel Adapter Card

(behind Post-Probe card) allows Post-Probe to be used with Micro-Channel equipped computers.

## Extensive Post-Probe Manual

exhaustively complete, containing BIOS error codes for most PCs on the market. Look up the 2-digit error code in this manual and instantly diagnose your PC's problems. Also contains common chip diagrams, descriptions and complete troubleshooting tips.

# Micro-Scope™

UNIVERSAL DIAGNOSTIC SOFTWARE

**Fully O/S Independent diagnostic software...**

Call for Current Upgrade

Call for upgrade pricing & complete new features list!

**Jerry Pournelle** awarded MICRO-SCOPE & POST-PROBE the User's Choice Award in the May 1994 issue of Byte Magazine, stating: **"You name it, this tests it. If you maintain PCs you'll love it."**

◆ **LOW-LEVEL FORMAT**—Performs low-level format on all hard drives including IDE drives. ◆ **TRUE HARDWARE DIAGNOSTICS**—Accurate testing of CPU, IRQ's, DMA's, memory, hard drives, floppy drives, video cards, etc. ◆ **RELOCATES TRACK 0** on hard drives that support relocation. ◆ **IRQ CHECK**—Talks directly to hardware and shows I/O address and IRQ of devices that respond. ◆ **O/S INDEPENDENT**—Does not rely on O/S for diagnostics. Talks to PC at hardware level. All tests are full function regardless of O/S (i.e. Windows, Novell, UNIX, OS/2). ◆ **IRQ DISPLAY**—Show bits enabled in IRQ chip for finding cards that are software driven (Network, Sound Card, etc.). ◆ **MEMORY DISPLAY**—Displays any physical bit of memory under 1 MB. Very useful for determining memory conflicts and available memory space. ◆ **AND MUCH MORE...** We don't have enough space here for everything this software can do!

Govt. Orders: NSN-7030-01-421-6459

Professional Diagnostics from

**MICRO 2000**

Call Now for Latest Pricing  
**1-800-864-8008**

© 1996 Micro 2000, Inc. All Rights Reserved.

CIRCLE 325 ON FREE INFORMATION CARD

# Post-Probe™

First Ever Universal P.O.S.T. Card for All PCs!

**PC won't boot up? Find out why fast with our universal POST card...**

2000 Technician Newsletter  
Call for a FREE NEWSLETTER & subscription

"This is the only card that will function in every system on the market. The documentation is extensive...covers the expected POST Codes for different BIOS versions...includes a detailed reference to the bus signals monitored by the card." —**Scott Mueller** from *Upgrading & Repairing PCs, 2nd Edition*

◆ Includes pads for voltmeter to attach for actual voltage testing under load. ◆ 4 LEDs monitor +5vdc -5vdc +12vdc -12vdc. ◆ Monitors Hi & Lo clock and OSC cycles to distinguish between clock chip or crystal failure. ◆ Monitors I/O Write and I/O Read to distinguish between write and read errors. ◆ Accurately monitors progress of POST for computers *without* POST codes. ◆ Reads POST codes from any IBM or compatible that emits POST codes. ISA/EISA/MCA. ◆ Compatible with Micro Channel computers. ◆ Dip switch allows easy selection of I/O ports to read. ◆ Includes **TRI-STATE LOGIC PROBE** to determine actual chip failures. ◆ Manual includes chip layouts and detailed POST procedures for all major BIOSs. ◆ **AND MUCH MORE...** call for more details.

Govt. Orders: NSN-7025-01-421-6467

Web Site: <http://www.micro2000.com>

GSA Approved

PCUPGRADE  
UTILITY OF THE MONTH

SERVICE NEWS  
PRODUCT OF THE MONTH

1993  
**BYTE**  
POURNELLE'S  
USER'S CHOICE  
AWARD

Windows 95  
COMPATIBLE


VISA  
MasterCard  
AMERICAN EXPRESS  
DISCOVER

Award Winning


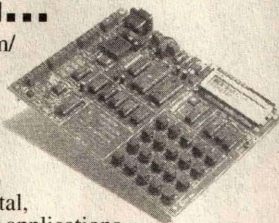
## Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING...

...with the AES learning system/  
embedded control system.  
Extensive manuals guide you  
through your development  
project. All programming and  
hardware details explained.  
Complete schematics. Learn to  
program the LCD, keypad digital,  
analog, and serial I/O. for your applications.



**THREE MODELS AVAILABLE. Choose from an  
Intel 8051, Intel 8088, or Motorola 68HC11  
based system. All models come with:**

- 32K Byte ROM, 32K Byte RAM • 2 by 16 Liquid Crystal Display • 4 by 5 Keypad • Digital, Analog, and Serial I/O • Interrupts, timers, chip-selects • 26 pin expansion connector • Built-in Logic Probe • Power Supply (can also be battery operated) • Powerful ROM MONITOR to help you program • Connects to your PC for programming or data logging (cable included) • Assembly, BASIC, and C programming (varies with model) • Program disks with Cross Assembler and many, well documented, program examples • User's Manuals: cover all details (over 500 pages) • Completely assembled and ready to use • Source code for all drivers and MONITOR • Optional Text Book

Everything you need. From \$279.  
Money Back Guarantee


Call for Free Info Pack, or see  
WEB at <http://www.aesmicro.com>  
714-550-8094, FAX 714-550-9941



**Call 1-800-730-3232**

AES 970 W. 17TH STREET, SANTA ANA, CA 92706, USA


## 386 SBC \$83

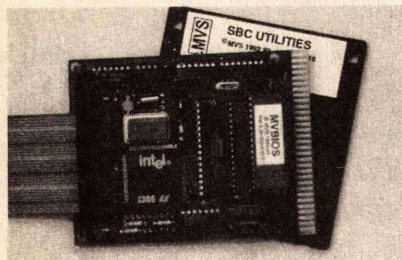

OEM (1K) PRICE  
INCLUDES:  
- 5 SER (8250 USART)  
- 3 PAR (32 BITS MAX)  
- 32K RAM, EXP 64M  
- STANDARD PC BUS  
- LCD, KBD PORT  
- BATT. BACK. RTC  
- IRQ0-15 (8259 X2)  
- 8237 DMA 8253 TMR  
- BUILT-IN LED DISP  
- UP TO 8 MEG ROM  
- CMOS NVRAM  
USE TURBO C,  
BASIC, MASM  
RUNS DOS AND  
WINDOWS  
EVAL KIT \$295
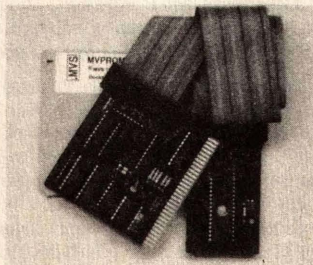
## \$95 SINGLE PIECE PRICE UNIVERSAL PROGRAMMER

- DOES 8 MEG EPROMS
- CMOS, EE, FLASH, NVRAM
- EASIER TO USE THAN MOST
- POWERFUL SCRIPT ABILITY
- MICROCONT. ADAPTERS
- PLCC, MINI-DIP ADAPTERS
- SUPER FAST ALGORITHMS



OTHER PRODUCTS:  
8088 SINGLE BOARD COMPUTER ..... OEM \$27 ... \*95  
PC FLASH/ROM DISKS (128K-16M) ..... 21 ..... 75  
16 BIT 16 CHAN ADC-DAC CARD ..... 55 ..... 195  
WATCHDOG (REBOOTS PC ON HANGUP) ..... 27 ..... 95

\*EVAL KITS INCLUDE MANUAL  
BRACKET AND SOFTWARE.  
5 YR LIMITED WARRANTY  
FREE SHIPPING  
HRS: MON-FRI 10AM-6PM EST




**MVS BOX 850  
MERRIMACK, NH  
(508) 792 9507**

## DATA ACQUISITION


and Control Hardware for PC's

ANA100 Analog I/O ..... \$ 99

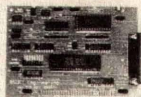

- 8 Channel 8-Bit
- 0 to 5 Volt Input
- 14 TTL I/O lines
- Analog Output
- 400KHz Sampling

DIG100 Digital I/O ..... \$ 39

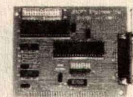

- 8255 PPI
- 24 or 48 TTL I/O Lines option
- Selectable Base Address

ANA150 Analog/Counter... \$ 89



- 8 Channel 8-Bit
- 0 to 5 Volt input
- 3 16-Bit Counters
- 400KHz Sampling

DIG200 Counter I/O ..... \$ 79



- 3 16-Bit Counters
- 8 TTL Input lines
- 8 TTL Output lines
- Selectable Clock Frequency input

ANA200 Analog I/O ..... \$ 79



- 1 Channel 12-Bit
- 0 to 5 Volt input optional bi-polar
- 100KHz / 300KHz Sampling rate
- 24 TTL I/O lines

ANA201 Analog ..... \$ 129



- 8 Channel 12-Bit
- x1, x5, x10, x50 Programmable Channel gain
- 100KHz/300KHz Sampling rate

## Engineering Software - PC/MSDOS

Easy-PC Professional XM - Integrated Electronics cad system, Schematic Capture, Circuit Analysis, and PCB Design in one software package ..... \$ 399.00

PC-SCOPE - Digital Storage Oscilloscope, 1, 2, 4, or 8 Channel Capture and Data Display. Works with ANA100, ANA150, and ANA201 Boards ..... \$ 39.00

MasterCard/Visa orders accepted


More hardware and software items available. Call for information or

See our catalog on the internet: <http://www.bsof.com>

E-mail: [sales@bsof.com](mailto:sales@bsof.com)
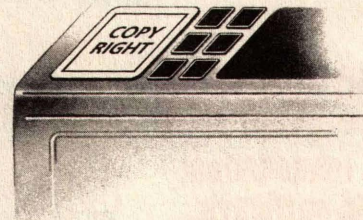
## BSOFT Software, Inc.

Phone 614-491-0832 \* Fax 614-497-9971  
444 Colton Road \* Columbus, OH \* 43207



*The Most*  
**AN IMPORTANT PART  
OF YOUR PHOTOCOPIER  
ISN'T PART OF  
YOUR PHOTOCOPIER**

Having a machine may not permit you to photocopy  
books, journals, newsletters and magazines.

The Copyright Clearance Center CAN.

Contact us to find out  
how you too can COPY RIGHT!<sup>SM</sup>

## COPYRIGHT CLEARANCE CENTER

222 Rosewood Drive, Danvers, MA 01923 ☐ Tel. (508) 744-3350 ☐ Fax (508) 741-2318

© 1993 Copyright Clearance Center



**"Get the skills you need at a price you can afford!"**

# Earn up to \$45 an hour or more as a skilled Computer Programmer.

**Cash in on the explosion of opportunities. Start your new career or even open a business of your own as a highly-paid computer programmer.**

**C**omputer programmers today can almost write their own ticket to financial well-being and job satisfaction. Only Foley-Belsaw's unique in-home training programs can give you the skills you need at a price you can afford.

You'll learn the three hot computer languages — QBasic, C and Visual Basic. You'll even work with the hot new C++. With this easy-to-learn knowledge, you'll write your first QBasic program by the end of the first SkillPak of lessons. Soon you'll be programming sound and graphics, and even learning how to program for the Windows environment — the most popular application program today.

## It's easy to cash in!


Look at some of the things professional computer programmers do. "Wrote a C program to clean up a WordPerfect file; edited the resulting file as data errors were found." This work would take a trained programmer less than five hours to complete, and they could make over \$200 for the work. That's money you could be making — and soon — with training from the Foley-Belsaw Institute of Computer Programming.

## Everything is included!

We provide you with all the materials you'll need to become a professional computer programmer. You'll receive 37 lessons, designed for you by the Foley-Belsaw Professional Programmer Staff. Other valuable materials include a *Programmer's Handbook*, *Programmer's Examples* on two 3.5 inch disks, *Programmer's Flowchart Template*, and a booklet, *Selecting the Right Computer*.

Other schools force you to buy a complete computer package as part of their training program. At Foley-Belsaw we understand that your needs as a programmer may not fit into a "one size fits all" approach. Why should you pay hundreds of dollars for a computer system that you may not need?

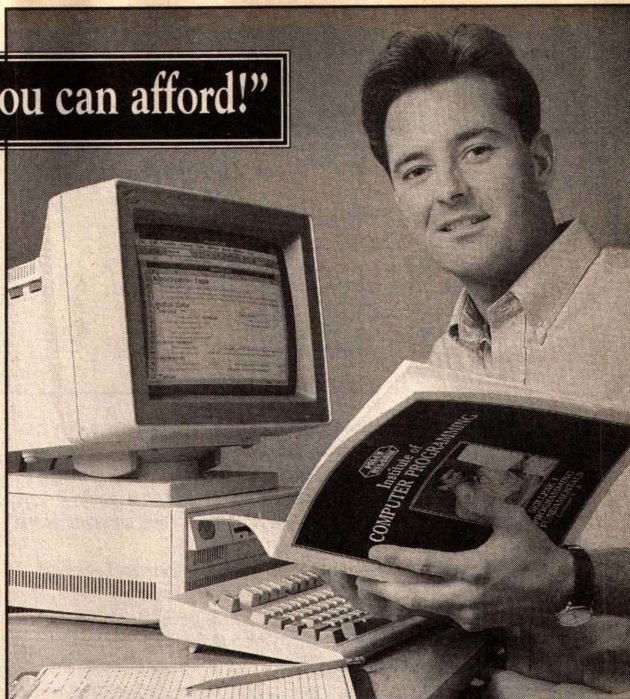We'll tell you what you need to know so that when you're ready to buy your own computer, you can get the machine that fits your needs at the lowest possible price. That's the Foley-Belsaw way.



## Get the free facts today.

Whether you want to change careers, have a profitable part-time job or start your own business, Foley-Belsaw Institute's new computer programming course is the first step. A profitable future in computer programming can be yours. Call or write today for a fact-filled information kit including a free copy of *Computer Programming — A Profitable Career In Your Spare Time*. See how easy it is to begin a money-making career as a sought-after computer programmer. Our free full-color information kit outlines the steps of the computer programming course and shows you everything you will receive as part of your training.

**Mail this coupon or call today**

**Toll Free 1-800-487-2100!**

**Your free opportunity kit will be rushed to you!**

If coupon is missing, write to: Foley-Belsaw Company, 6301 Equitable Road, Kansas City, MO 64120

Call or complete & return this coupon to: Foley-Belsaw Institute, 6301 Equitable Road, Kansas City, MO 64120

☐ **YES! Rush me a free information kit on Computer Programming right away. Dept. 35281**

Other career courses:


- ☐ Locksmithing, Dept. 12871
- ☐ Small Engine Repair, Dept. 52747
- ☐ Saw & Tool Sharpening, Dept. 21687
- ☐ VCR Repair, Dept. 62561
- ☐ Computer Repair, Dept. 64458
- ☐ TV/Satellite Dish Repair, Dept. 31333
- ☐ Gunsmithing, Dept. 92361
- ☐ Woodworking, Dept. 43619
- ☐ Upholstery, Dept. 81288
- ☐ Vinyl Repair, Dept. 71221
- ☐ Electrician, 95136
- ☐ Computer Specialist, 38129
- ☐ Networking Specialist, 39116

I understand that there is ABSOLUTELY NO OBLIGATION and NO SALESMAN WILL CALL.

Name

Address

City  State  Zip

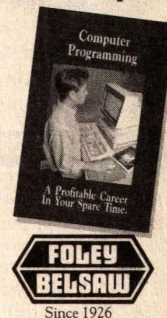


**P  
C  
P  
L  
A  
C  
E**

November 1996, Electronics Now



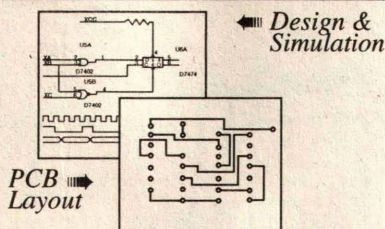
## Low Cost CAD Software Now In Windows™95



- Easy to use schematic entry program (**SuperCAD**) for circuit diagrams, only \$149. Includes netlisting, bill of materials, extensive parts libraries.
- Digital simulator (**SuperSIM**) allows you to check logic circuitry quickly before actually wiring it up. Works directly within SuperCAD and displays results in "logic analyzer" display window. Starting at \$149 this is the lowest cost simulator on the market. Library parts include TTL, and CMOS devices.
- Analog simulator (**mentalSPICE**) for \$149. Allows AC, DC and transient circuit analysis. Includes models of transistors, discretes, and op amps.
- Circuit board artwork editor and autorouter program (**SuperPCB**), starting at \$149. Produce high quality artwork directly on dot matrix or laser printers. You can do boards up to 16 layers including surface mount. Includes Gerber and Excellon file output. Autorouter accepts netlists and placement data directly from the SuperCAD schematic editor.
- **New!**—Complete electronic design package (**SuperMAX**) including schematic editor, analog and digital circuit simulation, and printed circuit board layout with autorouter for only \$549!

Write or call for free demo disks:  
**MENTAL AUTOMATION, INC.**  
5415 - 136th Place S.E.  
Bellevue, WA 98006  
(206) 641-2141  
Internet: <http://www.mental.com>

## PIC it $\mu$ P!

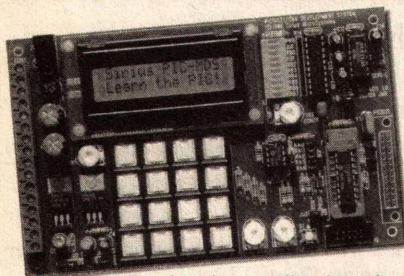

The PIC-MDS is a complete training and development environment for the mid-range PIC™ microcontrollers. Proven in classrooms, the PIC-MDS lets you learn to use and

develop applications for PIC microcontrollers quickly and easily. Our step-by-step examples guide you from simple programs through to keypad scanning, serial I/O, LCD display, A/D conversion, data logging, and interrupt routines.

### The PIC-MDS Professional Pack includes:

- PIC16C71 & PIC16C84 microcontrollers
- EPIC Programmer & PM assembler
- detailed training manual with disk
- in-circuit programming cable & socket
- ZIF socket • buffered LED port indicators
- 2 X 16 LCD display • 2 analog pots • RS-232 port
- 256 byte serial EEPROM • crystal/resonator socket
- 5V & variable DC power supply • AC voltage adapter
- all I/O pins on screw terminals & PICBUS connector
- all code examples in Microchip and Parallax™ syntax

**only \$299!**

### Also Available:

- Professional Board (no programmer) **\$259**
  - Hobbyist Pack **\$199** (kit, no ZIF, '84 only)
  - Hobbyist Board **\$139** (kit, no ZIF, '84 only, no programmer)
  - Teachers manual **Call**
- Prices exclude shipping. Parallax is a registered trademark of Parallax, Inc. PIC & Microchip are trademarks of Microchip Technology Inc.

**Sirius microSystems**

Visit our Web page: <http://www.siriusmicro.com>

172 Harvard Road  
Waterloo, ON N2J 3V3  
CANADA  
+1 519 886 4462 (ph.)  
+1 519 886 4253 (fax)  
support@siriusmicro.com

## EPROM+ PROGRAMMING SYSTEM USES PARALLEL PORT

**EPROMS** (24, 28, 32 & 40\* PIN PLUS 27CXXX)  
1702, 2708, 16, 32, 32A, 64, 64A, 128, 128A, 256, 512  
513, 011, 010, 101, 301, 1000, 1001, 1024, 210, 020  
2000, 2001, 220, 240, 2048, 4001, 4002, 040, 080, 8001  
2516, 32, 64, 68764, TMS2716

**FLASH EPROMS**  
28F256, 512, 010, 020 PLUS 29CXXX, 29FXXX

**EEPROMS & NVRAMS** (PLUS CXXX)  
2804, 16, 16A, 17, 2864, 64A, 65, 28256, 28C010  
X2210, X2212, DS1220, 1225, 1230

**SERIAL EEPROMS\*** (8 PIN PLUS CXX)  
2401, 02, 04, 08, 16, 32, 65, 2444, 59C11, 8572, 82, 92  
9306, 46, 56, 66, 16811, 911, 80011A, ER1400/58657

**BIPOLAR PROMS\*** (16 THROUGH 24 PIN)  
74SXXX AND 82SXXX FAMILY

**MICROCONTROLLERS\*** (UV, EE AND FLASH)  
8741, 02, 04, 48, 49, 8751, 87C51, 8752, C52, 87C5XXX  
87C75X, 89C51, 52, 68705, 68HC705, 68HC711E9  
PIC16C5X, PIC16C6X, PIC16C7X, PIC16C8X

\*ADAPTER REQUIRED - ASSEMBLED ADAPTERS AVAILABLE / DETAILED DIAGRAMS INCLUDED

- **SOFTWARE** - READ, VERIFY, PROGRAM, COPY, DISK FILE LOAD & SAVE, CHECKSUM, PLUS A FULL SCREEN BUFFER EDITOR WITH 20 COMMANDS
- **READS INTEL HEX**, MOTOROLA S-RECORD AND BINARY FILES
- **FAST!** - MANY DEVICES PROGRAM IN UNDER 10 SECONDS
- **RUGGED** (9" X 6" X 3"), PORTABLE ENCLOSURE WITH CARRY HANDLE DESIGNED FOR BENCH AND FIELD SERVICE.
- **ACCESSORY CONNECTOR** FOR FUTURE EXPANSION
- **LED INDICATORS** SHOW POWER, PROGRAMMING & SYSTEM STATUS
- **MADE IN THE USA** - 30 DAY MONEY BACK GUARANTEE - 1 YR WARRANTY
- **SYSTEM INCLUDES:** PROGRAMMING UNIT, POWER PACK, CABLE PRINTED MANUAL AND SOFTWARE

**ANDROMEDA RESEARCH**  
P.O. BOX 222  
MILFORD, OHIO 45150  
(513) 831-9708  
FAX (513) 831-7562

**SUPPORTS OVER  
600 CHIPS**




**\$289**



ADD \$5.00 SHIPPING - \$5.00 C.O.D.
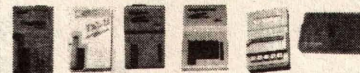
## PROGRAMMERS OVER 50 MODELS

ADVANTECH EETOOLS NEEDHAM DATA I/O ICE TECHNOLOGY HILO  
SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK



PROMAX EMP-20 MEGAMAX MEGAMAX4 SIMM/SIP TESTER EMUPA

- |                          |                       |
|--------------------------|-----------------------|
| CALL ADVANTECH LABTOOL   | 629 EETOOLS SIMMAX    |
| 689 ICE TECH MICROIV     | 795 CHROMA SIMM/SIP   |
| 669 EETOOLS ALLMAX +     | 350 MOD-MCT-EMUPA/R   |
| 429 EETOOLS PROMAX       | 279 MOD-MCT-EMUP/R    |
| 439 EETOOLS MEGAMAX      | 49 EPROM 1G TO 512K   |
| 539 EETOOLS MEGAMAX4     | 79 EPROM 1G TO 1MEG   |
| 429 XELTEK SUPERPRO II   | 99 EPROM 4G TO 1MEG   |
| 529 XELTEK SUPERPRO II P | 199 EPROM 16G TO 1MEG |
| 269 XELTEK SUPERPRO L    | 99 EPROM 1G TO 8MEG   |
| 179 XELTEK ROMMASTER II  | 129 EPROM 4G TO 8MEG  |
| 479 MOD-MCT-EMUPA        | 250 EPROM 8G TO 8MEG  |



LABTOOL48 MICROMASTER SUPERPRO ALLMAX PLUS ROMMASTER2

### General Device Instruments

Sales 408-241-7376 Fax 241-6375 BBS 983-1234  
Web [www.generaldevice.com](http://www.generaldevice.com) E-Mail [icdevice@best.com](mailto:icdevice@best.com)




**-SPY, INC.**  
ELECTRONIC SURVEILLANCE &  
PRIVACY ASSURANCE DEVICES

Cell & Home Phone Scammers, Covert  
Video Cameras, State of the Art Electronic Devices  
"YOU NEVER KNOW WHO'S WATCHING OR LISTENING"

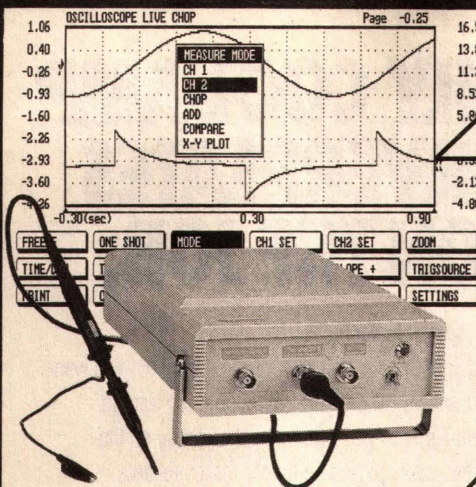
For a Full Catalog Send \$5 Check or M.O. to  
**T-SPY, Inc.**, PO Box 1707EN Amherst, NY 14226  
or call (716) 874-1707




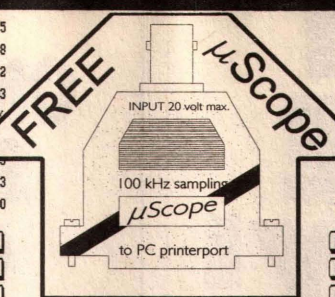
### TiePieSCOPE HS508

- > interface PC parallel printer port
- > sampling speed 50 Msamples/sec
- > resolution 8 bits
- > input range 50 mV/div - 20V/div
- > record length 32KByte/channel
- > price US\$1054 incl. software, user manual and 2 probes (1:1/1:10 switchable)



You get a free  $\mu$ Scope when you buy a TP508 or a HS508 until september 1st 1996


resolution 8 bits  
sampling speed 100 kSamples/sec  
input range 2.5V, 5V, 10V and 20V  
connects to PC parallel printer port

### Software for the PC-based instruments

contains an Oscilloscope, a Spectrum analyzer, a Voltmeter, and a Transient recorder. All instruments are controlled in the same intuitive way and provide for saving and recalling waveforms and settings, cursor measurements, hard-copy on matrix / laser printer and online help. Minimum requirements: a 80286-based PC with 2MByte and running MSDOS 3.3 or higher.


Call toll-free 1-800-626-6929 for a free demo disk and our catalog

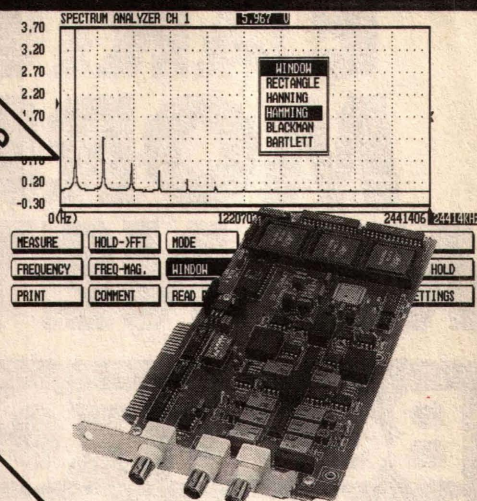Easy installation: just plug in and measure


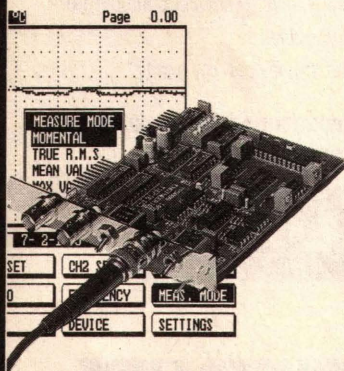
### TP508

- > interface PC-XT/AT ISA slot
- > sampling speed 50 Msamples/sec
- > resolution 8 bits
- > input range 5 mV/div - 20 V/div
- > record length 32 KByte/channel
- > price US\$1098 incl. software, user manual and 2 probes (1:1/1:10 switchable)




### TP5008

- > interface PC-XT-AT ISA slot
- > sampling speed 200ksamples/sec
- > resolution 8 bits
- > input range 125 mV/div - 5 V/div
- > programmable analog output channel
- > price US\$307 incl. software, user manual


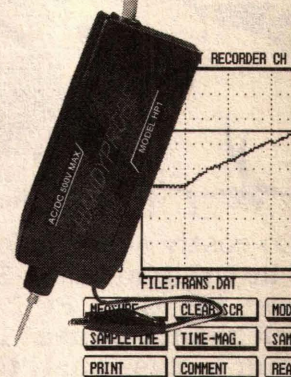
### HANDYSCOPE

- > interface PC parallel printer port
- > sampling speed 100ksamples/sec
- > resolution 12 bits
- > input range 125 mV/div - 5 V/div
- > no external power required
- > price US\$499 incl. software, user manual and 2 probes (1:1/1:10 switchable)



### HANDYPROBE

- > interface PC parallel printer port
- > sampling speed 100ksamples/sec
- > resolution 8 bits
- > input range 125 mV/div - 100 V/div
- > no external power required
- > price US\$169 incl. software, user manual

## CONWAY Engineering, Inc.

8393 Capwell Drive, Oakland, California USA 94621-2113

Tel: (510) 568-4028 Fax: (510) 568-1397

BBS: (510) 568-6533 Internet: <http://www.crl.com/~conway/>

Call toll-free 1-800-626-6929 for a FREE demo disk and a catalog of all our instruments!



CIRCLE 320 ON FREE INFORMATION CARD



# EARN MORE MONEY!

## Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

**No Need to Quit Your Job or Go To School**  
This proven course is easy, fast and low cost! **GUARANTEED PASS**—You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

Or, Call 1-800-932-4268 Ext. 210

### COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 210  
P.O. Box 2824, San Francisco, CA 94126  
Please rush FREE details immediately!

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

## ONLY COOL-AMP SILVERPLATES ON THE JOB.

From a customer testimonial:

"Ok, your edge connectors don't connect. Or you want to plate your own PC creations, but you don't want to bother with electro-plate solutions. The plating on the socket...has worn off and no longer makes reliable contact...what are you going to do now?"

"Give the people at Cool-Amp a call. They have a silver plating compound I have used for the past couple of years that solves all of the above problems and more. This white powder has an infinite shelf life...and is easy to use.

"It will actually put a permanent silver plate on copper, brass or bronze...There are no messy or dangerous chemicals. Application could not be easier. Use a clean rag and a little bit of water and just rub it on a clean surface. In minutes you can permanently silver plate a circuit board or replate a power amp tube or socket.

"It has saved me time, money and my sanity."

**Cool amp has even outperformed electroplating in recent tests. It is time-proven since 1944.**

**COOL-AMP**

## AND CONDUCTO-LUBE. THE SILVER-BASED CONDUCTIVE LUBRICANT.


The upstart, since 1952. Developed for switches, uses continue to expand to all applications needing a conductive lubricant.

*Conducto-Lube*

**ORDER FACTORY DIRECT:**  
**503-624-6426 or FAX 503-624-6436**


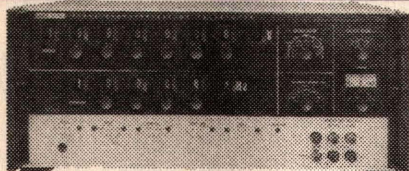
# Quality Reconditioned Test Equipment from Danbar



## Fluke 5200A

Programmable ac calibrator, outputs from 100  $\mu$ V rms to 120 V rms at 50 mA. Frequency range 10 Hz to 1 MHz, amplitude range is 1 mV to 1000 V.

**Special \$1500.00**

## Fluke 5215A

Power Amplifier, output voltages to 1100 Vrms, max output of 200 W, frequency from 10 Hz to 100 kHz.

**Special \$1500.00**

## Fluke 5220A

Transconductance Amplifier, lets you calibrate meters and shunts, 20 amps output dc or rms ac, 0.25% basic dc accuracy.

**\$2800.00**

## Fluke 720A

Kelvin-Varley Voltage Divider, 0.1 ppm resolution, 0.1 ppm of input absolute linearity.

**Special \$1000.00**

## Fluke 5100B Calibrator

Calibrator for analog and digital multimeters up to 4.5 digits, five functions: direct or alternating voltage or current plus resistance. Opt 03, 05.

**\$4350.00**

## Fluke 5101B Calibrator

Similar to 5100B but has procedure storage feature. Opt Y5000 Interface buffer for 5205A, 5215A and 5220A.

**\$5000.00**

## Fluke 335D

Dc Standard Null Detector, 1  $\mu$ V to 1000 Vdc with .001% accuracy.

**\$750.00**

## ESI RV622A Dekavider

Decade voltage divider, 6 dial, 10,000  $\Omega$ .

**\$199.00**



## Fluke 5440B

Direct Voltage Calibrator, 0 to 1100V range, completely automatic internal calibration, procedure storage module for single button set-up, completely programmable through the GPIB/ IEEE-488 interface.

**\$5600.00**

## Fluke 931B

True RMS Voltmeter, measures .01 to 1100 V in 5 ranges over 2 Hz to 1 MHz frequency range.

**\$450.00**

## Fluke 5450A

Resistance Calibrator, 17 standard resistors in 1 box, decade values from 1.0 $\Omega$  to 100 M $\Omega$ , 1.9 multiples from 1.9 $\Omega$  to 19 M $\Omega$ , GPIB/IEEE-488 programmable.

**\$1250.00**

## Fluke 343A

Dc Voltage Calibrator, 7 decade instrument with a basic accuracy of 20 ppm and a resolution of 1  $\mu$ V on the 10  $\mu$ V range, 0 to 1100V output, 0 to 25 mA, 0.1 ppm resolution.

**\$1000.00**

## Fluke 752A

Reference Divider, 10:1 and 100:1 division ratios, ratio accuracy of 0.2 ppm on 10:1 ratio, ratio accuracy of 0.5 ppm on 100:1 ratio, built-in calibration bridge.

**\$1750.00**

## Fluke 332D


DC Voltage Calibrator, output voltage ranges from 0 to 1111.111V Vdc and is set by 7 in-line decade switches.

**\$149.00**

## Fluke 5205A

Precision Power Amplifier, extends the range of 5700A, 5100B series, 5200A or 5400B calibrators, output voltages to 1100V rms,  $\pm$ 1500V dc, max output power 220 watts, dc to 100 kHz.

**Special \$2000.00**

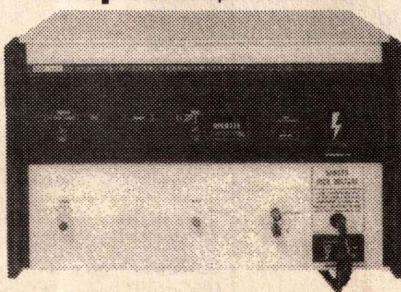

## Fluke 540B

Transfer Standard, this is a thermal instrument used for precise measurement and calibration of ac voltage and current, voltage transfers from 0.25 to 1000 Vrms in 14 ranges with a frequency from 5 Hz to 1 MHz.

**\$550.00**

## ESI DB62

Variable Resistor, 6 decades, 11,111,100 $\Omega$ , 10 M $\Omega$  max in .01 $\Omega$  steps.

**\$199.00**

## Fluke 515A

Portable Calibrator provides dc voltage, ac voltage and resistance standards in a compact unit. 0 to 100 Vdc, 2  $\mu$ V resolution, 0 to 100 Vac, 0 to 10 mA rms.

**\$1500.00**

## Fluke 845AR


Voltmeter/ Null Detector, high input impedance, 1  $\mu$ V to 1000V in 19 ranges, input resistance 100 M $\Omega$  on 300 mV and above, 10 M $\Omega$  on 100 mV and below.

**Special \$300.00**

## Datron 4000A

Autocal Standard, high-precision calibrator with exceptionally high stability and full system capability. Provides dc voltage calibration facilities in 8 decade ranges from  $\pm$  100  $\mu$ V to 1000 V, 7.5 digit, IEEE 488.

**\$5000.00**

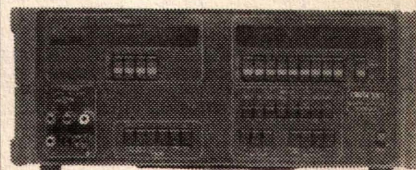

## Fluke 8922A


True RMS Voltmeter, 2 mV to 700V ranges, 4 digit display, relative dB, 2 Hz to 11 MHz.

**\$700.00**

## Fluke A55 Set of 9

High Frequency Thermal Converters, set of 9 pieces.

**\$1500.00**

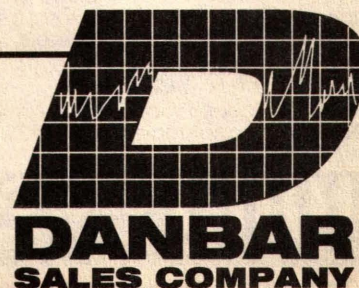

Please call for our Free 1996 Catalog

14455 NORTH 79TH STREET • UNIT C • SCOTTSDALE • ARIZONA 85260  
(602) 483-6202 • FAX (602) 483-6403

CIRCLE 235 ON FREE INFORMATION CARD



SEE US  
NOW AT  
http://www.cir.com

**CIRCUIT  
SPECIALISTS  
INC.**

**Check Out  
What  
We  
Have  
To Offer:**

### Fantastic DMM Offer!!!

Don't let the price fool you. This meter is a digital multimeter designed for engineers and hobbyists. Equipped with 5 functions and 19 ranges. Each test position is quickly and easily selected with a simple turn of the FUNCTION/RANGE selector rotary switch.

**General Rubber Boot Included**

**Display:** 3-1/2 Digit LCD, 21mm Figure Height with Automatic Polarity

**Overrange Indication:** 3 Least Significant Digits Blank

**Temperature for Guaranteed Accuracy:**

23°C±5°C RH<75%

**Temperature Ranges:**

Operating: 0°C to 40°C (32°F to 104°F)

Storage: -10°C to 50°C (14°F to 122°F)

**Power:** 9V Alkaline or Carbon-Zinc Battery (NEDA1604)

**Low Battery Indication:** BAT on Left of LCD Display

**Dimensions:** 188mm long x 87mm wide x 33mm thick

**Net Weight:** 400g

**DC Voltage (DCV)**

**Range:** Resolution: Accuracy:

200mV 100µV

2000mV 1mV

20V 10mV ±(1%rdg+2dgt)

200V 100mV

1000V 1V

**Maximum Allowable Input:** 1000V DC or Peak AC.

**DC Current (DCA)**

**Range:** Resolution: Accuracy:

200µA 100nA

2000µA 1µA

20mA 10µA

200mA 100µA

10A 10mA ±(1.2%rdg+2dgt)

**Overload Protection:** mA Input. 2A/250V fuse.

**AC Voltage (ACV)**

**Range:** Resolution: Accuracy:

200V 100mV ±(1.2%rdg+10dgt)

750V 1V

**Frequency Range:** 45Hz-450Hz

**Maximum Allowable Input:** 750V rms

**Response:** Average Responding. Calibrated in rms of a Sine Wave.



Our  
Best  
Offer  
Ever  
on a

High  
Quality  
Full Sized  
DMM

**\$19.00**  
any qty

**Resistance (Ω)**

**Range:** Resolution: Accuracy:

200Ω 100mΩ

2000Ω 1Ω

20KΩ 10Ω

200KΩ 100Ω

2000KΩ 1KΩ

20MΩ 10KΩ ±(1.2%rdg+2dgt)

**Maximum Open Circuit Voltage:** 2.8V


**Diode Test**

Measures forward voltage drop of a semiconductor junction in mV test current of 1.5mA Max.

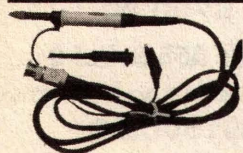**hFE Test**

Measures transistor hFE.

**CAT NO DESCRIPTION PRICE**  
**9300G Rugged High Quality DMM with Rubber Boot \$19.00**



### Switchable Scope Probe Sets

(Selectable X1/Ref/X10) These high quality scope probe sets are for oscilloscopes up to 60MHz (model HP 9060) or 150MHz (model HP 9150). Both sets include a handy storage pouch and include an IC test-hook adapter for

the probe. The BNC connector rotates to avoid cable tangle or kink. Cable length is 1.4 meters.

**PRICE EACH**

| CAT NO  | DESCRIPTION               | 1       | 10      | 100     |
|---------|---------------------------|---------|---------|---------|
| HP-9060 | Scope Probe Set DC~60MHz  | \$16.49 | \$14.49 | \$11.58 |
| HP-9150 | Scope Probe Set DC~150MHz | 24.95   | 21.95   | 18.62   |



### Positive Photo Resist Pre-Sensitized Printed Circuit Boards

These pre-sensitized printed circuit boards are ideal for small production runs. They provide high resolution and excellent line width control. High sensitive positive resist

coated on 1oz. copper foil allows you to go direct from your computer plot or art work layout. No need to reverse art.

**Single-Sided, 1oz. Copper Foil on Paper Phenolic Substrate**

| CAT NO | DESCRIPTION                  | PRICE EACH |        |        |
|--------|------------------------------|------------|--------|--------|
|        |                              | 1          | 10     | 50     |
| PP101  | 100mm x 150mm/3.91" x 5.91"  | \$2.55     | \$1.90 | \$1.70 |
| PP114  | 114mm x 185mm/4.6" x 6.6"    | 2.98       | 2.45   | 1.98   |
| PP152  | 150mm x 250mm/5.91" x 9.84"  | 5.40       | 3.98   | 3.60   |
| PP153  | 150mm x 300mm/5.91" x 11.81" | 6.15       | 4.48   | 4.10   |

**Single-Sided, 1oz. Copper Foil on Fiberglass Substrate**

| CAT NO | DESCRIPTION                  | PRICE EACH |        |        |
|--------|------------------------------|------------|--------|--------|
|        |                              | 1          | 10     | 50     |
| GS101  | 100mm x 150mm/3.91" x 5.91"  | \$ 3.90    | \$2.98 | \$2.60 |
| GS114  | 114mm x 185mm/4.6" x 6.6"    | 4.80       | 3.49   | 3.20   |
| GS152  | 150mm x 250mm/5.91" x 9.84"  | 8.69       | 5.98   | 5.78   |
| GS153  | 150mm x 300mm/5.91" x 11.81" | 10.20      | 7.20   | 6.80   |

**Double-Sided, 1oz. Copper Foil on Fiberglass Substrate**

| CAT NO | DESCRIPTION                  | PRICE EACH |        |        |
|--------|------------------------------|------------|--------|--------|
|        |                              | 1          | 10     | 50     |
| GD101  | 100mm x 150mm/3.91" x 5.91"  | \$ 5.07    | \$3.68 | \$3.38 |
| GD114  | 114mm x 185mm/4.6" x 6.6"    | 5.95       | 4.29   | 3.99   |
| GD152  | 150mm x 250mm/5.91" x 9.84"  | 10.47      | 7.39   | 6.98   |
| GD153  | 150mm x 300mm/5.91" x 11.81" | 11.95      | 8.69   | 8.30   |

### Etching Chemicals/Ferric Chloride

A dry concentrate that mixes with water to make 1 pint of etchant, enough to etch 400 sq. inches of 1oz board.

| CAT NO | DESCRIPTION  | 1      | 5      |
|--------|--------------|--------|--------|
| ER-3   | Makes 1 pint | \$3.50 | \$2.75 |



**Developer** This product is used as the developer on our positive photo-resist printed circuit boards. Includes instructions. 50 gram package, mixes with water,

| CAT NO | DESCRIPTION        | 1      | 10     | 25     |
|--------|--------------------|--------|--------|--------|
| POSDEV | Positive Developer | \$ .95 | \$ .80 | \$ .50 |



**Etching Tank** This handy etching system will handle PC boards up to 8" x 9", two at a time. Ideal for etching your PCB's! System includes an air pump for etchant agitation, a thermostatically controlled heater for keeping etchant at optimum temperature and a tank that holds 1.35 gallons of etchant. A tight fitting lid is also supplied to prevent evaporation when system is not being used. Typical etching time is reduced to 4 minutes on 1oz. copper board!

**REDUCES ETCHING TIME!**

| CAT NO | DESCRIPTION      | PRICE   |
|--------|------------------|---------|
| 12-700 | Etch Tank System | \$37.95 |

### Desoldering Pumps

These powerful plastic body desoldering pumps are designed for easy one hand operation for fast, efficient desoldering. Double O-ring piston seals for maximum suction.

| CAT NO    | DESCRIPTION              | 1       | 5       | 10      |
|-----------|--------------------------|---------|---------|---------|
| 08-366S   | Large Desoldering Pump   | \$15.89 | \$13.49 | \$11.95 |
| 08-366E   | Regular Desoldering Pump | 10.89   | 8.59    | 7.39    |
| 08-366TIP | Replacement Tip          | 1.95    | 1.95    | 1.95    |

SEE OUR ON-LINE CATALOG AT  
http://www.cir.com




**Electronic Soldering System** Here's the ideal solution when **Temperature Control** is required. Easy to use slide control allows user to set system from 300°F to 840°F. Voltage to iron from control unit is 24V Iron heating power is 48W. Replaceable 5.3mm tip is standard. Replacement irons and tips are available.

| CAT NO | DESCRIPTION                    | PRICE EACH |         |
|--------|--------------------------------|------------|---------|
|        |                                | 1          | 5       |
| SL10   | Temp Controlled Soldering Iron | \$56.00    | \$50.00 |
| SL24V  | Spare 24V Soldering Iron       | 10.50      | 7.50    |



**Electronic Soldering System with LED Display** Deluxe temperature controlled system with LED display for maximum accuracy. Temperature is adjustable from 160°-480°C (320°-900°F). Iron heating power is 48 Watts. Runs on 24V from controller unit. Replacement irons and tips are available. Tip size is 5.3mm.

| CAT NO | DESCRIPTION                               | PRICE EACH |         |
|--------|-------------------------------------------|------------|---------|
|        |                                           | 1          | 5       |
| SL30   | Deluxe Soldering System w/LED             | \$86.00    | \$75.00 |
| SL24V  | Spare 24V Soldering Iron for SL10 or SL30 | 10.50      | 7.50    |

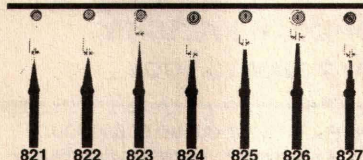






#### Replacement Tips for SL10/SL30

| CAT NO | DESCRIPTION      | PRICE EACH |        |
|--------|------------------|------------|--------|
|        |                  | 1          | 5      |
| 821    | 1/32" Pencil Tip | \$1.39     | \$1.19 |
| 822    | 1/32" Pencil Tip | 1.39       | 1.19   |
| 823    | 1/64" Pencil Tip | 1.39       | 1.19   |
| 824    | 1/16" Chisel Tip | 1.49       | 1.29   |

We now offer a variety of replacement tips for the SL10/SL30 soldering stations.

| CAT NO | DESCRIPTION      | PRICE EACH |        |
|--------|------------------|------------|--------|
|        |                  | 1          | 5      |
| 825    | 1/8" Chisel Tip  | \$1.49     | \$1.29 |
| 826    | 3/64" Chisel Tip | 1.49       | 1.29   |
| 827    | 3/64" Pencil Tip | 1.59       | 1.39   |

#### Ball Bearing 12V DC Fans

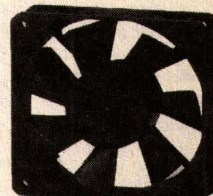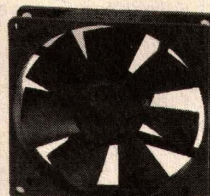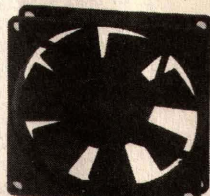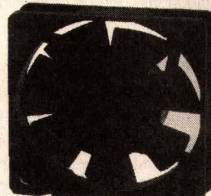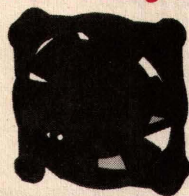

These High Quality Fans feature Ball Bearings and Brushless DC Motors. All of them are designed to meet UL, CSA & VDE Standards. Design these fans into power supplies, computers or other equipment requiring additional air flows for heat removal. These fans are regular Circuit Specialists stock items — they are not surplus.

#### INDUSTRY BEST PRICING!

##### Specifications


| CAT NO      | DIMENSIONS (MM) | RATED VOLTAGE (V) | START VOLTAGE (V) | INPUT CURRENT (A) | AIR FLOW (CFM) | STATIC PRESSURE (INCH-H <sub>2</sub> O) | SPEED (RPM) | NOISE LEVEL (dB) | WEIGHT (g) |
|-------------|-----------------|-------------------|-------------------|-------------------|----------------|-----------------------------------------|-------------|------------------|------------|
| CSD 4010-12 | 40x40x10mm      | 12                | 7                 | 0.06              | 5.1            | 0.19                                    | 5,500       | 26               | 20         |
| CSD 6025-12 | 60x60x25mm      | 12                | 5                 | 0.13              | 13.7           | 0.165                                   | 4,500       | 28               | 65         |
| CSD 8025-12 | 80x80x25mm      | 12                | 5                 | 0.16              | 37.8           | 0.177                                   | 3,000       | 31               | 80         |
| CSD 9225-12 | 92x92x25mm      | 12                | 5                 | 0.32              | 42             | 0.18                                    | 2,800       | 37               | 95         |
| CSD 1225-12 | 120x120x25mm    | 12                | 5                 | 0.35              | 62             | 0.180                                   | 2,500       | 42               | 135        |

**SOLDER • SOLDER • SOLDER • SOLDER • SOLDER • SOLDER • SOLDER • SOLDER • SOLDER • SOLDER**

We stock high quality 60/40(Sn%/Pb%), .031" and 63/37, .031" diameter. This is prime JIS certified solder that we maintain as a regular stock item (It is not "Left-overs, Rejects or Surplus") and you can buy it from us at a fraction of the price that you are used to.

#### Tired of Paying Inflated Prices for Solder?

| CAT NO    | DESCRIPTION                 | 1       | 10      | 25      |
|-----------|-----------------------------|---------|---------|---------|
| RH60-1    | 1-lb. Spool, .031", 60/40   | \$ 6.90 | \$ 5.96 | \$ 5.30 |
| RH63-1    | 1-lb. Spool, .031", 63/37   | 6.95    | 6.10    | 5.41    |
| RH60-4    | 4.4-lb. Spool, .031", 60/40 | 24.00   | 21.90   | 17.92   |
| RH60-TUBE | 6-oz. Tube, .031", 60/40    | .99     | .89     | .79     |

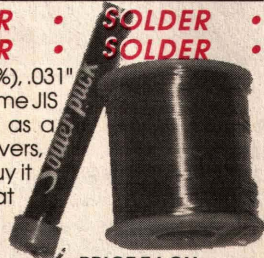

#### CCD Camera - IR Responsive As Low As \$109!!

This black and white monochrome CCD Camera is totally contained on a PCB (70mm x 46mm). The lens is the tallest component on the board (27mm high from the back of the PCB) and it works with light as low as 0.1 lux. It is IR Responsive for use in total darkness. It comes with six IR LED's on board. It connects to any standard monitor, AUX or video input on a VCR or through a video modulator to a TV. Works with a REGULATED 12V power supply (11V-13V). Hooks up by connecting three wires: red to 12V, black to ground (power & video) and brown to video signal output.



| CAT NO  | DESCRIPTION              | 1        | 5        |
|---------|--------------------------|----------|----------|
| CA-H34A | PCB Mounted IRCCD Camera | \$125.00 | \$109.00 |

!!!!!! SEE OUR ON-LINE CATALOG AT <http://www.cir.com> !!!!!!

**CIRCUIT SPECIALISTS, INC.**  
SINCE 1971

**800-811-5203**  
**602-464-2485**  
**602-464-5824(FAX)**

WE ACCEPT:



#### RECEIVE OUR LATEST 132 PAGE CATALOG!

It's chock full of all types of electronic equipment and supplies. We've got I.C.'s, capacitors, resistors, pots, inductors, test equipment, breadboarding supplies, PC supplies, industrial computers, data acquisition products, personal computers and computer parts, plus much, much more. FAX us your name and address or call **800-811-5203, ext. 5**, to leave a message on our catalog request line.





# BRIGAR ELECTRONICS

100 N. BINGHAMTON, NY 13904

PHONE: (607) 723-3111  
FAX: (607) 723-5202  
E-MAIL: BRIGAR2@aol.com

SEND FOR  
FREE  
CATALOGUE



**CREDIT CARD DISCOUNT**  
\$ 0.00 - \$ 99.99 NET  
\$100.00 - \$249.99 LESS 10%  
\$250.00 - \$499.99 LESS 15%  
\$500.00 - \$999.99 LESS 20%  
\$1000.00 AND UP LESS 25%

**WHY  
PAY  
MORE ?**

SERVING: ■ INDUSTRY ■ SCHOOLS ■ HOBBYISTS ■ EXPERIMENTORS ■ CONSUMERS


OPEN: MONDAY THRU FRIDAY 7:30AM TO 4:30 PM, SATURDAY 7:30AM TO NOON

## PORTABLE FLUORESCENT - MINI LIGHT Plug in anywhere - No Wiring - as bright as a 20-Watt Bulb.

- Energy efficient fluorescent bulb costs only pennies a day.
- Plugs into any standard outlet
- Convenient ON/OFF switch
- Completely portable - plugs into any standard outlet.
- Lasts up to 3 years with normal use.
- UL Listed. - 3.5watt - 120vac
- Size: 5-1/4" Long x 1-1/4"H x 1-3/4" deep
- Color: White

Use at Home: kitchen, hallway, stairway, bedroom etc.  
Use away: RV, Boat, Motel room, Camp

**BRAND NEW - DISPLAY PACKED.**

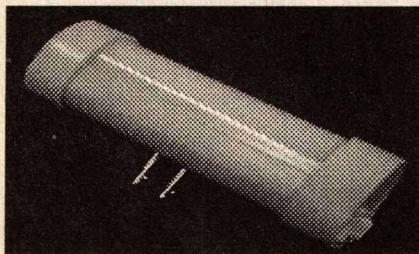

**SNAPIT**  
A LEVITON DIVISION


**SALE....  
\$4.95 EA.**

**ULTRASONIC LIGHT SWITCH MFG: LITRONIC**  
REPLACES EXISTING WALL SWITCH - OPERATES  
FROM 120VAC POWER. GREAT FOR HOME  
ALARM SYSTEMS OR CONTROLLING LIGHTS &  
SMALL APPLIANCES - ADJUSTABLE TIME &  
SENSITIVITY, ON-OFF SWITCH -  
LED TRIP INDICATOR - COLOR: WHITE  
SIZE: 5"W x 5"H x 1-3/8"D  
CAN BE USED WITH SINGLE OR DOUBLE  
SWITCHES.  
ON/AUTO SWITCH TURNS LIGHTS OFF  
MANUALLY WHEN NECESSARY OR LEAVES  
LIGHTS IN UTOMATIC CONTROL MODE.

- VOLTAGE 120 OR 277VAC 50/60HZ
  - MIN LOAD 80 WATT 120V
  - MAX LOAD 1000W 120V
  - SENSOR LOW POWER ULTRASONIC 25KHZ
  - SENSOR COVERAGE: 250 SQ. FT. WITH  
180 DEG. DETECTION FIELD
  - ADJUSTMENT: SENSITIVITY & TIME OUT  
(0 TO 25 MINUTES)
  - DOCUMENTATION & SCHEMATIC INCLUDED.
- ENERGY SAVINGS 30 TO 60%  
ORIGINAL PRICE \$100.00

**SPECIAL SALE PRICE**  
..... \$12.95 EA.  
5 FOR \$60.00

**MOTION SENSING  
AUTOMATIC SWITCH**

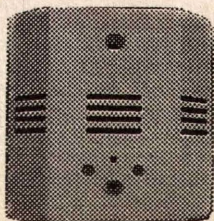

**OPTREX #DMF50140NF-SEW INTELLIGENT GRAPHIC LCD MODULE**  
"SUPERTWIST" Modules utilize surface mount technology. Displays Blue  
pixels on White backuond. Modules have E-L Backlighting - Graphic  
Figure Character Display. Unit comes complete with built in drivers & 8 bit  
tti interface.

•CONTROL LSI T6963C TOSHIBA

•VIEW ANGLE: 6:00 •DOT SIZE: .44(W) x .57(H) mm

•DIT PIXELS 143(W) x 153(H) mm •VIEW AREA 74.8(W) x 98.4(H) mm

•DC VOLTAGE: 5VDC •GRAPHIC, FIGURE & CHARACTER DISPLAY


•HIGH CONTRAST & WIDE VIEW ANGLE •FILM TYPE BACKGROUND

Using this information, one should be able to interface the  
LCD to any microcontroller or a microprocessor.

PROGRAM DISKETTES contains list of all commands, a file that contains list of  
initialization steps, and a text file that has the 68hc11 program

LIST PRICE... \$119.95

**BRIGAR SPECIAL \$59.95**

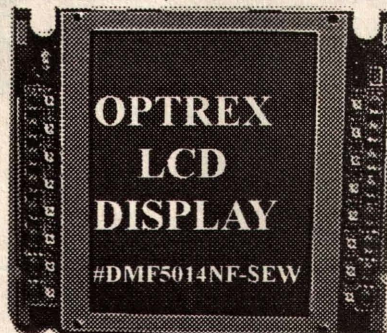

**DISPLAYS COMES COMPLETE  
WITH 3.5"  
DISKETTE. FILES CONTAIN  
68HC11 PROGRAM, LIST OF  
COMMANDS AND Initialization  
steps, Schematic, and pin out**



## AEROVOX

# P2066601YR

1.9 UF @ 660V 50/60 HZ  
SIZE: 2-1/4"H x 2"W x 1"D  
PRICE..... .90 EA.


**AEROVOX # N20R7001YR**

1.6 UF @ 700V 60HZ  
SIZE: 2-1/16"H x 2"W x 1"D  
PRICE.... \$1.00 EA.



## CHICAGO MINIATURE LAMPS
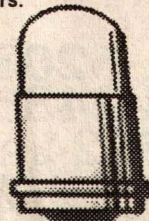
# CM385 - Base Style: midget flanged  
Brand New - Packed 100 pcs./card  
28 volts .04 amp - 50,000 life Hours  
Bulb style: T-1 3/4 - Same as 387 Lamps  
except has twice the life hours.  
Regular Price .. 60¢ ea.  
**BRIGAR SPECIAL  
SALE 20¢ EA.**



## 5 - 9 WATT DC/DC CONVERTER PART # EM951S

OUTPUT: ± 12 VDC ± 375 MA  
INPUT: 5 VOLT DC  
PC MOUNTABLE  
500V ISOLATION  
REGULATED LINE: 1.2%  
REGULATED LOAD: 8%  
REFLECTED RIPPLE: 75MA P-P  
Size: 2" square x .4" thick  
REGULAR PRICE ... \$20.00  
**PRICE SLASHED ....\$4.95**






# BASIC ELECTRICAL SUPPLY & WAREHOUSING CORPORATION

P.O. Box 8180 ■ Bartlett, IL 60103 ■ 800-577-8775

HOURS: Monday-Saturday 9-5 C.S.T.

We handle NEW equipment ONLY - Don't trust last year's OBSOLETE and UNSOLD stock!  
COMPETITIVE PRICING—DEALERS WELCOME

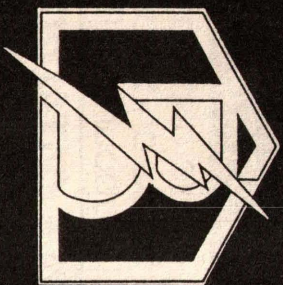It is not the intent of B.E.S.W. to defraud any pay television operator; an we will not assist any company or individual in doing the same.  
\*Refer to sales personnel for specifications.



## ❖ ATTENTION CABLE VIEWERS ❖ CABLE VIEWERS... get back to your BASIC Cable Needs


Call 800-577-8775

For information regarding all of your BASIC cable needs.

- 5 GOOD REASONS TO BUY OUR FAR SUPERIOR PRODUCT
- ❖ PRICE
- ❖ EFFICIENT SALES AND SERVICE
- ❖ WE SPECIALIZE IN 5, 10 LOT PRICING
- ❖ ALL FUNCTIONS (COMPATIBLE WITH ALL MAJOR BRANDS)
- ❖ ANY SIZE ORDER FILLED WITH SAME DAY SHIPPING
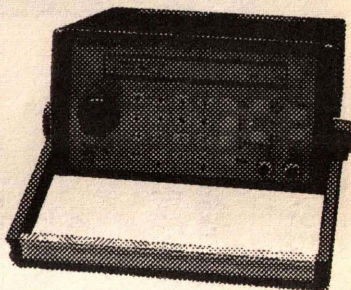
### AT LAST! DC-20 MHz SYNTHESIZED PERFORMANCE FOR ONLY \$795!

- DC-20 MHz, .1 Hz resolution, DC offset
- Linear/Log Sweep
- Internal/External AM
- Internal/External FM
- Internal/External PM
- Internal/External SSB
- Internal/External BPSK
- Dualtone Generation
- Internal/External FSK
- Burst
- DTMF Generation
- DTMF Detection
- Power Level Measmt



**\$795** Quantity 1  
Made in U.S.A.

The SG-100 gives you .1 Hz synthesized precision and a wide diversity of modulation functions all of which can be performed using an internally generated or externally applied signal. You also get signal analysis functions that are just not offered on any other signal source such as DTMF Detection and Power Level Measurement. And because you can download new instrument functions to Flash memory, you can ensure that your SG-100 will never become obsolete.

The SG-100 is available NOW and is ready to turn your engineering bench into a real powerhouse!



C.O.D. P.O.

Telulex Inc.

2455 Old Middlefield Way S, Mountain View, Ca. 94043 (415) 938-0240

Fax: (415) 938-0241 <http://www.telulex.com> email:sales@telulex.com

CIRCLE 290 ON FREE INFORMATION CARD

The **Smallest,**  
Most **Secure,**  
Best **Range,**  
**3 Channel**  
Remote Receiver.



**Security Receiver for...** Home Automation, Garage Doors, Home Security Add On, Auto Convenience Package (Door Locks, Trunk Pop, Windows-Up/Down, Car Start), W/O or W/C Contacts.

**Security** - 70 billion hopping codes with anti-scan processing. Unbreachable security; never repeats the same code twice. Double EEPROM memory.  
**Incredible Range** - No cross talk or blockage. Range up to 1000 feet.  
**3 Channel** - Our universal receiver controls up to 3 items with only one receiver (optional relay needed). Push both buttons together for third channel output.  
Interfaces with most home and auto security systems for easy remote integration.  
Comes with (1) three channel receiver, (1) long range three channel remote,  
(1) universal 120 VAC transformer.

**ALL FOR ONLY \$99.95 + shipping & sales tax.**

**Street Smart Security**  
**(619) 462-1167**


7147 University Avenue • La Mesa, CA 91941

Send, Fax or Call Order In - Use Credit Card or Check. Fax (619) 462-0652



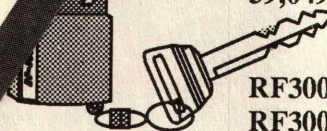
## Miniature Transmitters and Receivers

Small, Attractive, High End Quality, 2 Channel 318 MHz Transmitter  
59,049 Settable Codes, 120'-300' Range, 1-1/4" x 2" x 9/16", Assembled



|         |                        | Qty | 1     | 5     | 10    |
|---------|------------------------|-----|-------|-------|-------|
| RF300T  | 150' Range Transmitter |     | 24.95 | 19.95 | 15.95 |
| RF300XT | 300' Range Transmitter |     | 29.95 | 24.95 | 19.95 |

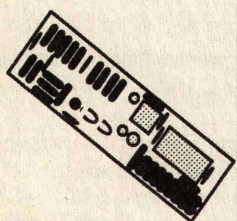Small, High End Quality, 2 Channel Receiver for the RF300 Transmitters  
1-1/4" x 3-3/4" x 9/16" PCB w/ .1" spaced pads for standard connectors  
Input: 8-24 vdc Output: Gated CMOS Momentary and Latching Lines



|         |                              | Qty | 1     | 5     | 10    |
|---------|------------------------------|-----|-------|-------|-------|
| RF300R  | Receiver, Fully Assembled    |     | 24.95 | 20.95 | 16.95 |
| RF300RK | Receiver, Complete Parts Kit |     | 19.95 | 15.95 | 12.95 |
| RF300PA | Pre-Amplifier. Doubles Range |     | 14.95 | 11.95 | 9.95  |

Small, Economical, Single Channel Transmitter and Receiver Set  
Set Code, 60' Range, 1-7/8"x2-3/8"x7/16" (T), 2"x2-3/4"x9/16" (R)  
Receiver Input: 5 vdc Output: Gated TTL Momentary Line



|      |                              | Qty | 1     | 5     | 10    |
|------|------------------------------|-----|-------|-------|-------|
| RF60 | Transmitter and Receiver Set |     | 24.95 | 19.95 | 14.95 |

Add \$4 shipping for first item + \$1 for each additional item. Ca. residents add 8.25% tax  
Visa, Mastercard, Money Orders Personal Checks and Cash C.O.D.s

### Visitect Inc.

P.O. Box 14156 Fremont, CA. 94539 (510) 651-1425 Fax (510) 651-8454

CIRCLE 316 ON FREE INFORMATION CARD

## WORLD'S SMALLEST UHF X-tal Locked Video Transmitters \$99.00

**So small the transmitter, camera and battery will fit into a cigarette pack!!!**

Used by hundreds in covert CCTV, R/C models, movie Special Effects, and Law Enforcement. "I've utilized your transmitters in covert video installations for about one year... previously, I used costly wireless units from Pelco, MVP, and Supercircuits. Nothing approaches the VidLinks in terms of power, picture quality, size, and value. Thank you." R. Leslie, CCTV Installer, NY.

"Incredible color, resolution... easy to use, convenient. Very cool." P. Davis, Props, CA.  
"... like having a TV station in your pocket." J. Ramsay, Electronic Hobbyist, FL.

**LIVE REMOTE VIDEO FROM: \$99.00 ACTUAL SIZE !!!**

**VidLink 100: 100mW Power- upto 1/4 Mile \$199.00 New! High-Power!**

**VidLink 15: 15mW Power- upto 150 Feet \$99.00 New! Low Price- Same Size!**

**Covert Camera: 1 1/4" sq. Pinhole Lens \$169.00 Pro Grade Japanese Quality!**

\*\*\* Audio Module Now Available. Call. \*\*\*

Check/MO, COD +\$5.00, S&H \$5.50



**AEGIS  
RESEARCH**

#671-1225 E. Sunset Dr.  
Bellingham, WA  
98226-3529 USA

**1-604-224-0416**

Visit our virtual catalog on the INTERNET at:  
<http://www.lynx.bc.ca/virtualspy>

WE SELL RED, BLUE-GREEN & IR

## LASERS

HUNDREDS OF UNITS TO CHOOSE FROM!  
PRICES AS LOW AS \$40.00!

- \* Experiments
- \* Laser Light Shows
- \* Cutting & Burning
- \* Communications

We also carry  
books and plans  
about LASERS.

**CALL FOR FREE CATALOG!**

**TEL (909) 278-0563**

**FAX (909) 278-4887**

**MWK INDUSTRIES**

1269 W. Pomona, Corona, California 91720

See our catalog on the internet.

[HTTP://WWW.PWEB.COM/MWK/MAIN.HTM](http://WWW.PWEB.COM/MWK/MAIN.HTM)

EMAIL: [MKENNY1989@AOL.COM](mailto:MKENNY1989@AOL.COM)




# DALBANI



**\$20 MINIMUM ORDER**  
CALL NOW FOR YOUR  
232 PAGE FREE CATALOG  
**1-800-325-2264**


## HOT PRICES ON POPULAR SEMI'S

| Order N°  | Brand   | Min | Price  |
|-----------|---------|-----|--------|
| BU-208    | TESLA   | 10  | \$1.49 |
| BU-208/O  | TOSHIBA | 1   | 4.50   |
| 2N-3055   | TESLA   | 10  | 0.60   |
| 2N-3773   | TESLA   | 5   | 1.20   |
| 2SD-1398  | SANYO   | 10  | 1.49   |
| 2SD-1650  | SANYO   | 5   | 1.69   |
| STRD-1005 | SANKEN  | 1   | 4.15   |
| STR-30130 | SANKEN  | 1   | 2.66   |
| STRS-6301 | SANKEN  | 1   | 8.50   |
| TA-7777N  | TOSHIBA | 1   | 6.96   |
| TDA-2005  | SGS     | 5   | 1.49   |

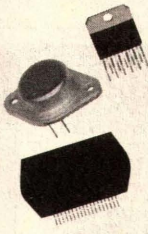
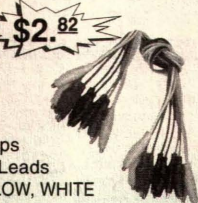
## COLOR CODED LEADS HEAVY DUTY ORDER N° 56-500

- 11" Long Wire Lead
- Insulated 1<sup>1/2</sup>" Alligator Clips
- 20 Gauge Wire Size • 10 Leads
- BLACK, GREEN, RED, YELLOW, WHITE



## SOLDER WICK

- Solder Remover
- Length 5 Feet

ORDER N° 51-1050 Min. 2 pcs.



## TEMPERATURE CONTROLLED SOLDERING STATION

- Adjustable Temp.: 300°F - 790°F - 150°C - 480°C
- Grounded Tip for Soldering : Static Sensitive Devices, Heater Aid.
- Led Power Temperature Indicator
- Overheat Protection W/ Temperature Control
- Auxiliary Grounded Terminal
- Comes in digital LED display
- 48 Watts soldering iron

ORDER N° 51-1035



## CODE EN96 PLEASE MENTION WHEN ORDERING

Items are subject to availability.  
Prices are subject to change without  
any prior notice.

## FLYBACK TRANSFORMERS



Replaces  
GOLDSTAR 154-074R  
ORDER N° 63-0189

**\$12.50**

## TUN-O-WASH® ORDER N° 30-0100

**\$7.50**  
(CFC Free)

**Fast drying electronics  
grade cleaner for tuners,  
controls and PC boards.**

TUN-O-WASH is excellent cleaner and  
degreaser for tuners, controllers and PC boards.

- Designed for cleaning and degreasing consumer electronics • Cleans in one step, no rinsing required • Contains no ozone depleting compounds • CFC and HCFC free
- Not for use on energized equipment
- 12.5 Oz aerosol (12 cans per case)



## VCR ALIGNMENT TOOL KIT ORDER # 50-888

The most popular

- VCR Head puller
- Retaining ring remover
- Spring hook
- Micro screwdriver
- Hex key set • Fitted vinyl • Soft zippered case
- Dimensions: 9 1/2"(W) X 12 1/4"(L)
- 7 Assorted head & guide aligners
- 3 Reverseable screwdrivers (Small-Flat-Phillips)



**\$24.99**

## UNIQUE REALTIME OSCILLOSCOPE BUILT-IN FUNCTION GENERATOR

Order N° 50-820



## 1 MHZ FUNCTION GENERATOR

### Features

- Wider than specified frequency response • High deflection factor of 1mV/div. • Wide dynamic range up to 30MHz without waveform distortion • Algebraic sum of CH1 and CH2 • Low drift with compensation circuit • Superb trigger sensitivity • Maximum sweep rate of video signals with internal TV sync. separator • Jitterless trigger circuitry • CH1 signal output terminal available • Variable trigger hold-off • High precision X-Y phase difference measurement up to 50kHz • Built-in function generator with BNC output of 50Ω and TTL • Three kinds of waveform are available with 50Ω output • Flat output waveform frequency up to 1MHz

### Specifications:

- Vertical deflection:** • Bandwidth :DC coupled (DC to 20MHz normal), AC coupled : (10Hz to 20MHz normal) • Deflection factor: 5mV/div to 5V/div in 10 calibrated steps of 1-2-5 sequence • Rise time: 17.5nS or less
- Horizontal deflection:** • Time Base A: 0.2μs to 0.2S/div in 19 calibrated steps. 1-2-5 sequence • Uncalibrated continuous control between steps of at least 1: 2.5.



**\$498.00**


## DIGITAL MULTIMETERS

NEW! Digital

- Overload protect 1000VDC or peak AC on all other ranges
- Input impedance 10M Ohm on all ranges • Base accuracy range ± 0.5 % to ± 1.0 % • Resistance 200Ω, 2K, 20K, 200K, 2M, 20M
- Audible continuity response lower than 50Ω • DC Voltage 200mV, 2V, 20V, 200V, 1000V
- AC Voltage 200mV, 2V, 20V, 200V, 700V

ORDER N° 50-815

## DALCO

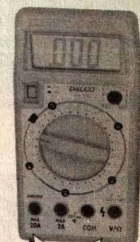

**\$19.95**

## LOGIC Probe

ORDER N° 51-1015

- Length: 8 inches
- Range: 4.5 To 15 VDC
- Includes Test Leads • Compatible With TTL, DTL, RTL, HTL, CMOS, NMOS Logic




**\$8.99**

## SOLDER ROLL

- 1 LB Spool
- 370 deg F melting point
- Fastest solder
- Alloy 60/40, tin lead, non corrosive flux, Diam. 1.2mm

ORDER N° 51-1005

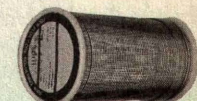

**\$3.95**

## Universal Audio/video Remote ORDER N° 82-1055

- Controls basic functions of TV, VCR, cable box, and CD or laser player • Ergonomic design! Main buttons are in line with natural thumb motion • Two-minute memory allows time to replace batteries without re-programming • Programming reminder sticker inside battery compartment • Sleep time for 60, 30, or 15 minutes (according to your TV) • Set key recessed to prevent accidental deprogramming • Spanish instruction included. • Requires four AAA Batteries (not included)



## MAGNAVOX Smart. Very smart

**\$9.95**

- Cable (11 brands)
- VCR (68 brands)
- TV (77 brands)
- Compact disc and Laser Disc (94 brands)

4225 N.W. 72nd AVE MIAMI, FLORIDA 33166 TEL : (305) 716-1016 FAX : (305) 594-6588

CIRCLE 234 ON FREE INFORMATION CARD



Tel: (954) 974-6864  
Fax: (954) 974-6818

# Gateway Products Corp.

Please mail orders to:  
P. O. Box: 93-6397  
Margate, FL 33093

|                                                                                                                                                                                                                                                                                                       |                                                                                                                                                                                                                                                                                               |                                                                                                                                                                                                                                                                                                                    |                                                                                                                                                                                                                                                                                                              |                                                                                                                                                                                                                                                                                                                |                                                                                                                                                                                                                                                                                                           |                                                                                                                                                                                                                                                                                                        |                                                                                                                                                                 |
|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <b>Popular I.C.s</b><br><br>LM324...45¢<br>LM339...45¢<br>LM358...45¢<br>NE555...40¢<br>LM556...50¢<br>LM741...40¢<br>Deal U3: 12 pcs total,<br>(2pcs of each)...\$5.00                                              | <b>Transistors</b><br><br>PN2222A...8¢<br>PN2907A...8¢<br>2N3904...8¢<br>2N3906...8¢<br>2N4401...8¢<br>2N4403...8¢<br>Deal N8: 60 pcs total,<br>(10pcs of ea.)...\$4.50                                      | <b>Semiconductors</b><br><br>74LS174...40¢<br>74LS244...45¢<br>74LS245...45¢<br>74LS374...45¢<br>LM3886N...45¢<br>LM393N...40¢<br>MC1488...45¢<br>MC1489...45¢                                                                    | <b>DIODES</b><br><br>1N914...4¢<br>1N4148...4¢<br>1N4001...1A/50V...4¢<br>1N4004...1A/400V...5¢<br>1N4007...1A/1kV...6¢<br>Deal P7: 50 pcs total,<br>(10pcs of ea.)...\$2.00                                                | <b>RADIAL LYTICS</b><br><br>1uF/50V...8¢<br>2.2uF/50V...8¢<br>3.3uF/50V...8¢<br>4.7uF/50V...8¢<br>10uF/50V...8¢<br>22uF/50V...10¢<br>33uF/50V...11¢<br>47uF/50V...12¢<br>Deal A2: 40 pcs total,<br>(5pcs of each)...\$3.00    | <b>Ceramic Disc</b><br><br>(All caps rated 50V)<br>10pF...7¢<br>22pF...7¢<br>27pF...7¢<br>33pF...7¢<br>47pF...7¢<br>100pF...7¢<br>150pF...7¢<br>220pF...7¢<br>Deal R4: 40 pcs total,<br>(5pcs of each)...\$2.50        | <b>Toggle Switches</b><br><br>Miniature size<br>1/4" Panel hole<br>on-on...SPDT...50¢<br>on-off-on...SPDT...80¢<br>on-on...DPDT...70¢<br>on-off-on...DPDT...80¢<br>Deal S3: 8 pcs total,<br>(2pcs of each)...\$5.00 |                                                                                                                                                                 |
| <b>Popular CMOS</b><br><br>CD4001B...30¢<br>CD4011B...30¢<br>CD4013B...40¢<br>CD4017B...40¢<br>CD4028B...40¢<br>CD4050B...40¢<br>CD4068B...40¢<br>CD4069B...40¢<br>Deal V8: 16 pcs total,<br>(2pcs of each)...\$5.00 | <b>More Transistors</b><br><br>MPSA05...15¢<br>MPSA13...15¢<br>MPSA27...15¢<br>MPSA42...15¢<br>MPSA56...15¢<br>MPSA92...15¢<br>Deal Q2: 30 pcs total,<br>(5 pcs of ea.)...\$4.00                             | <b>V. Regulators</b><br><br>LM317T...69¢<br>7805...48¢<br>7808...48¢<br>7812...48¢<br>7815...48¢<br>7818...48¢<br>7824...48¢<br>7905...48¢<br>7908...48¢<br>7912...48¢<br>7915...48¢<br>78L05...39¢<br>79L05...39¢<br>78L12...39¢ | <b>Power Diodes</b><br><br>1N5401...3A/100V...10¢<br>1N5404...3A/400V...11¢<br>1N5408...3A/1kV...12¢<br>6A10...6A/100V...32¢<br>6A100...6A/1kV...42¢<br>Deal H8: 25 pcs total,<br>(5pcs of ea.)...\$4.00                    | <b>RADIAL LYTICS</b><br><br>10uF/25V...8¢<br>22uF/25V...8¢<br>33uF/25V...8¢<br>47uF/25V...9¢<br>100uF/25V...10¢<br>220uF/25V...12¢<br>330uF/25V...19¢<br>470uF/25V...23¢<br>Deal A7: 40 pcs total,<br>(5pcs of each)...\$4.00 | <b>Ceramic Disc</b><br><br>(All caps rated 50V)<br>270pF...7¢<br>330pF...7¢<br>470pF...7¢<br>.001uF...7¢<br>.01uF...7¢<br>.022uF...7¢<br>.047uF...9¢<br>1uF...10¢<br>Deal R7: 40 pcs total,<br>(5pcs of each)...\$2.50 | <b>DEAL W2...\$2.50</b><br><br>120 pcs total (20 pcs of<br>each: 10, 47, 100, 470,<br>1k, 4.7k, All 1/4W 5%.                                                                                                        |                                                                                                                                                                 |
| <b>DEAL M3...\$5.00</b><br><br>7805 7812<br>7905 7912<br>12 pcs total<br>(3pcs of each)                                                                                                                              | <b>More Transistors</b><br><br>2N2222A...30¢<br>2N4124...11¢<br>2N4126...11¢<br>2N5401...14¢<br>MPSH10...13¢<br>2N3055...69¢<br>TIP31C...55¢<br>TIP32C...55¢<br>TIP117...55¢<br>TIP120...60¢<br>TIP125...65¢ | <b>Crystals...99¢ea</b><br><br>3.5795MHz, 4.000MHz<br>11.0MHz, 11.0592MHz                                                                                                                                                         | <b>1W Zener Diodes</b><br><br>1N4728A...3.3V...10¢<br>1N4733A...5.1V...10¢<br>1N4739A...9.1V...10¢<br>1N4742A...12V...10¢<br>1N4744A...15V...10¢<br>1N4746A...18V...10¢<br>Deal Z5: 30 pcs total,<br>(5pcs of ea.)...\$2.50 | <b>1A SCHOTTKY</b><br><br>1N5817...1A/20V...22¢<br>1N5818...1A/30V...23¢<br>1N5819...1A/40V...24¢<br>Deal Y6: 9 pcs total,<br>(3pcs of each)...\$2.00                                                                         | <b>Mono Caps...9¢ea</b><br><br>.01uF/50V .047uF/50V<br>.022uF/50V .1uF/50V<br>Deal B5: 40 pcs total,<br>(10pcs of ea.)...\$2.50                                                                                        | <b>400V BRIDGES</b><br><br>1Amp 4Amp<br>1.5Amp<br>DF04M...DIP...40¢<br>W04M...Round...35¢<br>KBL04...In-line...89¢<br>Deal X8: 6pcs total,<br>(2pcs of each)...\$3.00                                               |                                                                                                                                                                 |
| <b>DEAL J1...\$3.50</b><br><br>78L05<br>78L12<br>10 pcs total<br>(5pcs of each)                                                                                                                                      | <b>5mm (T1 3/4) Diffused LEDs</b><br><br>Red...8¢<br>Green...10¢<br>Yellow...12¢<br>Deal L3: 30 pcs total,<br>(10pcs of ea.)...\$2.50                                                                        | <b>3mm (T1) Diff. LEDs</b><br><br>Red...8¢<br>Green...10¢<br>Yellow...12¢<br>Deal L6: 30 pcs total,<br>(10pcs of ea.)...\$2.50                                                                                                    | <b>CHEAP STUFF</b><br><br>TO-220 heat sink...29¢<br>Mini push-button...29¢<br>30W solder iron...\$3.95<br>6ft printer cable...\$3.95<br>6ft VGA cable...\$3.95<br>3-b serial mouse...\$8.95                                 | <b>Germanium Diodes</b><br><br>1N34A...15¢<br>1N80...15¢<br>1N270...30¢<br>Deal G5: 18 pcs total,<br>(6pcs of ea.)...\$2.50                                                                                                   | <b>3A SCHOTTKY</b><br><br>1N5820...3A/20V...32¢<br>1N5821...3A/30V...36¢<br>1N5822...3A/40V...39¢<br>Deal Y9: 9 pcs total,<br>(3pcs of each)...\$3.00                                                                    | <b>Tantalum Caps</b><br><br>1uF/35V...18¢<br>2.2uF/35V...22¢<br>10uF/35V...49¢<br>Deal T6: 15 pcs total,<br>(5pcs of each)...\$3.50                                                                                 | <b>SOLDER ROLL</b><br><br>SN63/37<br>.031" dia<br>1 Lb Roll<br><b>\$7.80</b> |

  \$10.00 minimum order. We accept VISA, MC, MO, Check, No-CODs. Please add \$5.00 for shipping & handling (foreign addresses: \$8.50). Florida addresses add your applicable county sales tax. Hours: Mon-Fri: 9AM to 5PM (EST). All new premium parts. Send for free Catalog.

CIRCLE 330 ON FREE INFORMATION CARD

## The Hacker's Companion CD-ROM

Want a war-dialer program or something to crack a password? Do you want to learn how the phone company gets ripped off, or learn how to build a red box, or modify a cellular phone? Want to see what the security holes in a VAX are? Or how to compromise a Unix machine or a BBS? Want to learn how to use the system in ways you never imagined possible? This CD is the place to look! It contains all kinds of computer, telephone and general hacking information. Even a video of dutch hackers breaking into a classified US military computer! In all, 552 megabytes of fascinating information that's hard to get anywhere else!

**PC-Compatible CD-ROM \$49.95**  
Shipping \$3


**Call (800)719-4957 now!**

to order (Visa/MC/COD) or call or write for FREE CATALOG of hard-to-get information about computer viruses, computer hacking, security and cryptography!!

**American Eagle Publications, Inc.**  
P. O. Box 1507  
Show Low, AZ 85901

CIRCLE 315 ON FREE INFORMATION CARD

## Electronic Engineering Works 5.1

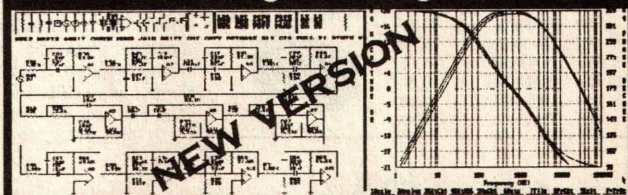

|                                                                                                                                                                                                                                                                                                                                                                                                                    |                                                                                                                                                                                                               |
|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <b>1 ANALOG CIRCUIT SIMULATOR</b><br>Fastest Simulator on the market. Active & Passive circuits. Up to 70 nodes, 225 elements. Programmable Models for active devices. 10 Programmable Input Transients. Edit circuits. Calc, Plot and Print AC voltages, AC currents, DC current, DC voltage, DC Sweep, Input and Output transients, power. Plots: Lin, Log, Semi, Polar, etc.                                    | <b>6 CONTROL SYSTEMS</b><br>Calc & Plot Root Locus, Nyquist, Bode of any H(s). Calc Gain/Phase Margins & stability. Add, delete poles or zeros.                                                               |
| <b>2 ANALOG SIMULATOR W/DRAW</b><br><b>3 ACTIVE FILTERS DESIGN</b><br>Design/Analyze active LPF, BPF, HPF, Butterworth, Chebyshev, Bessel & All pass filters. Plot response.                                                                                                                                                                                                                                       | <b>7 MAG/PHASE GRAPHICS</b><br>Calc, plot mag/phase of any H(s). More.                                                                                                                                        |
| <b>4 TRANSIENT SYSTEM ANALYSIS</b><br>Calc, plot transient response of system H(s). 14 Input Transients. Inverse Laplace. Edit H(s). More.                                                                                                                                                                                                                                                                         | <b>8 FUNCTION GRAPHICS</b><br>Calc, plot, edit any of 99 useful Math functions as desired. Multiplot. More.                                                                                                   |
| <b>5 POLYNOMIAL OPERATIONS</b><br>Calc polynomials Roots, Product & Coefficients.                                                                                                                                                                                                                                                                                                                                  | <b>9 DATA GRAPHICS</b><br>Plot up to 400 data points in 9 formats. Lin/Log, etc. Curve fit. More.                                                                                                             |
| <b>11 POWER SUPPLY DESIGN AND ANALYSIS</b><br>Design and analyze switching and linear supplies. Design AC/DC and DC/DC Converters. Design Power Transformers, with up to 60 windings. Design Power Inductors and Current Transformers. Switchers include Buck, Boost, Buck-Boost, Flyback. Perform Stability Analysis of Switchers. Design LC Filters. Includes Mag Core Tables. Gain/Phase Plots & Data. VGA req. | <b>10 CKT SCHEMATIC DRAW</b><br>Cut, Copy, Paste, Move, Merge, Check, Grid, Label, NetList, Add, Change, Delete, Print. Line & Text tools. 126 symbols. Up to 100 nodes, 1000 elements. More. Mouse Required. |
| <b>12 DIGITAL LOGIC SIMULATOR WITH DRAW</b><br>\$39.99<br>★ ANALOG CIRCUIT SIMULATOR (module 1) ..... \$ 69<br>★ ANALOG SIMULATOR W/DRAW (modules 1,2) ..... \$ 89<br>★ EE WORKS 5.1 STD (modules 1,2,3,10,12) ..... \$129<br>★ EE WORKS 5.1 PRO (All 12 modules) ..... \$295                                                                                                                                      | <b>Performance Guaranteed</b><br>PC AT, 540K BASE MEM. EGA/VGA COLOR DISP. WITH 200K VIDEO CARD. DOS 3.2 OR HIGHER. MS MOUSE. 5MB SPACE ON HARD DRIVE. LASER OR DOT MATRIX PRINTER.                           |

Call/Fax 1(619)384-3042 or send check/m.o.  
VISA/MC ACCEPTED, \$8.95 SHIPPING, CA ADD 7.25% TAX  
**FAST, ACCURATE & THOROUGH**  
GEOBAN ENGINEERING, P.O. BOX 658, RIDGECREST CA 93556



# PROFESSIONAL DESOLDERING with the

**Lane Norman - Normans Electronics Inc. Atlanta GA 404-451-5057**  
A cost effective solution to desoldering equipment at less than half the price of most equipment. Its performance is ASTOUNDING.

**Harold Smedberg - Smedberg Electronics - Custer MI**  
The SC7000 has reduced my damage to PC boards by 90%. It has also decreased my desoldering time by 50%. The best priced tool on the market.

**Mike Murphy - Service Center - Van Nuys CA 818-785-7805**

The single best investment of repair equipment we've made. It outperforms all other desoldering tools we've used. Easier to use and least expensive.

## DEN-ON SC7000

**Bob Monroe - M.A.R.C. Electronics - Virginia Beach VA 804-468-3932**  
Best investment we've made. Saves time, especially with multi-sided PCB's. Extremely pleased with warranty. Failed within 6 months and replaced by DEN-ON overnight.

**Dick Manning - Dicks Electronics - Hartland WI 414-367-8339**  
The ease & speed of component removal greatly increases productive time. The SMD kit makes SMD removal a breeze, even for inexperienced Techs.

**Dave Hayes - E-H Engineering Ltd - Lincoln NE 402-466-6720**  
Has been a durable & reliable desoldering unit. Our use has been both lab & field application over the last 2 yrs. with positive results.

**Bob Sorrels CET/CSM Polytronics Microcomputer - Shreveport LA**  
We've used our SC7000 almost every day for about three years with virtually no problems. Just clean it before you turn it off for the day.

**George Hefner - Hefner Electronics - Coleridge NE 402-283-4333**  
Being a one-men service center, I hesitated to spend the money on a desoldering tool, however all that changed when I nearly ruined a \$400 computer logic board. It has cut my desoldering time by 50 to 75%.

**Steven Gray - Electronic Wizards - Wichita KS 316-686-8324**  
By far the best desoldering tool we've ever used. Much more suction than other similar types we've tried. No trouble with postage stamp IC's or anything else.

**Dennis McMannis - Thorn Services International - Mabelton GA**  
The SC7000 has decreased my use of wick by 75% and at \$25 a roll, it pays for itself within months. My total bench time is reduced by approx. 20%.

**Don Cressin - Certified Electronics Service - Ellicott City MD 301-461-8008**  
We have obtained excellent results with the SC7000 including repairing high density U/V tuners. It is one of the best purchases we have made.

**Doug Pettit - LuRay Electronics - LuRay VA 703-743-5400**  
We found that the SC7000 not only saves money vs. wick, but saves valuable time in troubleshooting. It allows you to be more accurate in removing SMD's.

**Paul Horvat - Service Excellence Inc. - Bergenfield NJ 201-387-7776** It has made a almost impossible job (desoldering a 64 pin CPU) a piece of cake.

## Specifications

- ◆ Totally Self Contained diaphragm vacuum pump and AC motor for high vacuum suction or reversible hot air blow for SMD removal.
- ◆ 100Watt Ceramic heater with zero-crossover switching heater control circuit which prevents spikes and leakage currents.
- ◆ Unique patented long lasting filter cartridge design. Solder builds up on easily cleaned baffle, while air flows around the outside of baffle.
- ◆ Totally ESD Safe. The housing contains carbon and the tip is at ground potential for complete ESD Protection.
- ◆ Maximum vacuum of 600mmHg is attained in 0.2 seconds.
- ◆ Temperature adjustable from 300°C - 450°C or 572°F - 842°F


**Visa - M/C - Discover - American Express - Terms to Qualifying Companies**  
**30 Day Money Back Total Satisfaction Guarantee - One Year Parts and Labor Warranty**

**HOWARD**  
**HEINSTRUMENTS INC**  
6222 N. Oliver Wichita, KS 67220

**Toll Free U.S. and Canada**  
**1-800-394-1984**

**E-Mail sales@heinc.com**  
**Web Site www.heinc.com**  
**International (316) 744-1993**  
**or Fax (316) 744-1994**

CIRCLE 323 ON FREE INFORMATION CARD

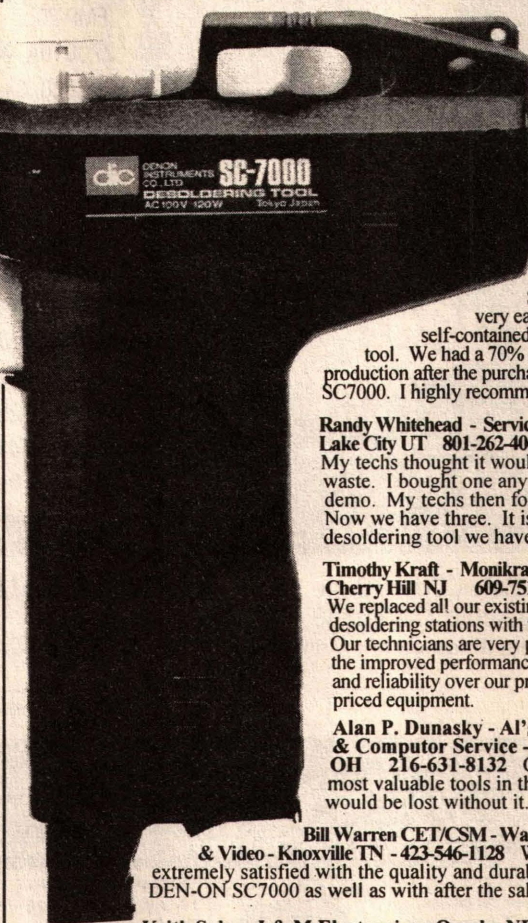

**Tom Mullett - JC Penny TD&S - Wausato se WI 414-259-2486**

The SC7000 is a

very easy to use, self-contained desoldering tool. We had a 70% increase in production after the purchase of the SC7000. I highly recommend it.

**Randy Whitehead - Service West - Salt Lake City UT 801-262-4069**

My techs thought it would be a waste. I bought one anyway after a demo. My techs then fought over it. Now we have three. It is the Best desoldering tool we have ever used.

**Timothy Kraft - Monikraft, Inc. - Cherry Hill NJ 609-751-3252**

We replaced all our existing desoldering stations with the SC7000. Our technicians are very pleased with the improved performance, portability, and reliability over our previous higher priced equipment.

**Alan P. Dunasky - Al's TV, VCR, & Computer Service - Cleveland, OH 216-631-8132** One of my most valuable tools in the shop. I would be lost without it.

**Bill Warren CET/CSM - Warrens Audio & Video - Knoxville TN - 423-546-1128** We have been extremely satisfied with the quality and durability of the DEN-ON SC7000 as well as with after the sale support.

**Keith Sahs - J & M Electronics - Omaha NE 402-291-7100** It's a must tool for my bench. I can desolder multiple pin IC's quickly and clean. It will even take up large solder amounts on tuner and case grounds.

**Ray Wurmnest - Ray's Electronics, Inc. - Bloomington IL 309-829-3238** The SC7000 saves time when changing out parts in the home or in the Service Center — Worth every penny we spent.

## FREE TRIAL

**Available on Request**

**Industrial User Price \$550.00**  
**Our Regular Price \$445.00**

**Sale Price \$395.00**


**Limited Supply at Sale Price**

Price includes  
Stand, two extra  
filter cartridges,  
tip wrench and  
tip cleaner.



**\$449<sup>95</sup>**

## Device Programmers

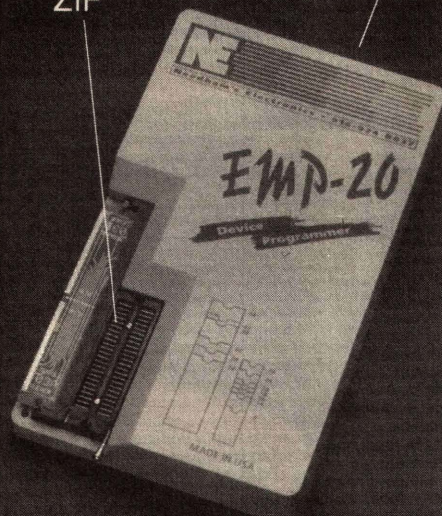**\$139<sup>95</sup>****48 PIN  
ZIF****Connects to standard  
PC parallel printer port**

9 1/2 x 5 3/4 x 1 1/4

**EMP-20**

- Easy to use software, on-line help, full screen editor

- **Fast Programming** (EMP-20)

27C010A, 23 seconds

28C020, 34 seconds

27C040, 95 seconds

- **Made in USA**

- 1 Year Warranty

- Technical Support by phone

- 30 day Money Back Guarantee

- FREE software upgrades available via BBS

- Demo SW via BBS (EM20DEMO.EXE) (PB10DEMO.EXE)


- **E(e)proms** 2716 - 8 megabit, 16 bit 27210-27240, 27C400 & 27C800,

- **Flash** 28F256-28F020, (29C256-29C010 (EMP-20 only))

- **Micros** 8741A, 42A, 42AH, 48, 49, 48H, 49H, 55, 87C51, 87C51FX, 87C751, 752

- **GAL, PLD** from NS, Lattice, AMD-16V8, 20V8, 22V10 (EMP-20 only)

### PB-10 Internal Card for PC

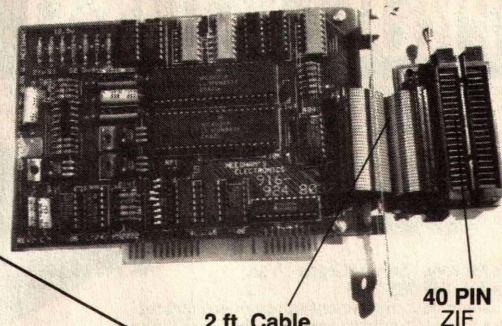

2 ft. Cable

**40 PIN  
ZIF****FOR MORE INFORMATION CALL**

4630 Beloit Drive, Suite 20  
Sacramento, CA 95838  
(Monday-Friday, 8 am-5 pm PST)

**NEEDHAM'S ELECTRONICS, INC.**

C.O.D.

**(916) 924-8037****BBS 916-924-8094****FAX 916-924-8065**

CIRCLE 257 ON FREE INFORMATION CARD

**Mark V Electronics, Inc.**  
8019 E Slauson Ave  
Montebello CA 90640

Free Catalog 213/ 888-8988  
Fax 213/ 888-6868

**Do-It-Yourself**  
**Audio Amplifier & Electronic Kits**  
**more than 60 items available!**

ORDER 1-800-521-MARK / 1-800-423-FIVE

- Low distortion, stability & superb transient response.
- 2 pairs MOSFET transistors.
- Highly sensitive & fool-proof.
- Loudspeaker protection circuit.

Kit: \$ 89.80

Asmb.: \$ 114.80



#### 120-250W MOSFET Power Mono Amp. # AF-2

- Field effect transistors.
- Symmetry circuit. Kit: \$ 64.00
- Wide frequency response & low distortion. Asmb.: \$ 80.00
- Power supply regulation.
- Time delay relay. # TA-388



#### Class A FET Dynamic Buffer Stereo Pre-Amp

It is short circuit proof & has overload protection. Output voltage is variable over a range of 0-50V. Current limit trip is adjustable up to max of 3A.

Kit: \$ 18.75

Asmb.: \$ 27.65



#### Regulated DC Power Supply # TR-503

##### School Project Kits Source...

|        |                             |          |
|--------|-----------------------------|----------|
| SM-36  | Dynamic Noise Reduction     | \$ 26.00 |
| SM-720 | AC/DC Stereo Pre & Main Amp | 77.00    |
| TA-006 | 6W Mini-Amplifier           | 9.50     |
| TA-120 | 36W Class A Power Amp       | 32.50    |
| TA-201 | Microphone Mixer Mono Amp   | 20.79    |
| TY-45  | 20 Bar/Dot Level Display    | 38.25    |

##### Clearance Sale...


|       |                            |         |
|-------|----------------------------|---------|
| TA-28 | Digital Voice Memo kit     | \$ 9.90 |
| TY-35 | FM Wireless Microphone kit | 6.99    |

- Input program source switching.
- Phono pre-amp stage with RIAA equalization. Kit: \$ 64.00
- 3 tone controls. Asmb.: \$ 80.00
- Built-in speaker protection circuit & power supply rectifier.


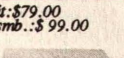
#### 120Wx2 Pre & Main Stereo Amp. # TA-800MK2

- Accurate & easy to operate. Kit: \$79.00
- Frequency 10Hz-150MHz. Asmb.: \$ 99.00
- Hold function available.
- A/D LSI circuitry.
- Input impedance 1M ohm.
- For adjustment, test & repair...



#### 150MHz 8 Digit Frequency Counter # SM-100

Super fast acting relay protects speaker against destructive DC voltage. Can connect directly to a power amp. or can use a separate power supply. Has a 3 sec turn-on delay to avoid turn-on thumps.

Kit: \$ 16.75

Asmb.: \$ 22.75



#### Stereo Loudspeaker Protector # TY-25

This unit provides 3 input jacks pairs. One pair accept a high impedance microphone. The two remaining pairs are for high & low level input sources. The unit is ready to plug into the AC power when assembled. Case & transformer are included.

Kit: \$ 85.00

Asmb.: \$ 104.00



#### 60W + 60W Stereo Power Amp # SM-302

### METAL CABINETS


#### Aluminium Front Panel

|         |              |          |
|---------|--------------|----------|
| LG-1273 | 3x12x6 3/4"  | \$ 26.50 |
| LG-1684 | 4x16x8"      | 32.50    |
| LG-1924 | 4x19x11 1/2" | 38.25    |
| LG-1925 | 5x19x11 1/2" | 42.00    |
| LG-1983 | 2 1/2x19x8"  | 35.25    |
| LG-1923 | 3x19x11 1/2" | 36.50    |
| LG-1927 | 7x19x11 1/2" | 50.50    |

LG- Black anodized rack cabinet

LL-1923B 2 3/4x19x12" \$ 69.50  
LL-1925A 5x19x12" 79.50

\*LL-Full Aluminum, Front .157" & other .078"  
\*LL-Gold plated cap screw for front panel

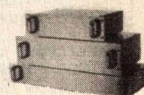**Best Buy****New**

### Alarm Box with Lock

|          |                     |          |
|----------|---------------------|----------|
| LB-1085  | 8 1/2x10 1/2x5"     | \$ 18.75 |
| LB-1395  | 9 1/2x13 1/2x5"     | 25.50    |
| LB-1525  | 12 1/2x15 1/2x5"    | 35.25    |
| *LB-1494 | 9 1/2x14 1/2x4 1/4" | 21.50    |
| LB-1383A | 8 1/2x13 1/2x4"     | 23.25    |


\*No lock &amp; LB-Sheet Metal 0.8mm

### Camera Housing

|           |                 |         |
|-----------|-----------------|---------|
| *LD-1244  | 2 1/2x10 1/2x4" | \$55.00 |
| **LD-1516 | 3 1/2x13 1/2x4" | 29.50   |
| **LD-1565 | 4x13 1/2x5 1/4" | 31.75   |

\*LD-Stainless Steel 0.7mm  
\*\*LD-Sheet Metal 1mm

Camera Housing

 

### TRANSFORMERS

Toroidal Transformers

|      |             |          |
|------|-------------|----------|
| #001 | 28/30Vx2 6A | \$ 30.00 |
| #002 | 36Vx2 3A    | 25.00    |
| #003 | 40Vx2 6A    | 32.00    |
| #004 | 24Vx2 6A    | 25.00    |
| #005 | 26Vx2 3A    | 19.00    |
| #006 | 18Vx2 5A    | 19.00    |
| #007 | 53Vx2 8A    | 47.00    |
| #008 | 28/30Vx2 6A | 40.00    |
| #009 | 48/53Vx2 8A | 66.00    |
| #012 | 33/42Vx2 6A | 48.00    |

### Modular Desktop Consoles

|        |            |         |
|--------|------------|---------|
| LE-453 | 4x4 1/2x3" | \$ 7.50 |
| LE-653 | 6x4 1/2x3" | 9.75    |
| LE-853 | 8x4 1/2x3" | 11.75   |

LE-Black finished aluminum 1mm



\*Toroidal Transformer



Transformer


Minimum order: \$ 20.00. We accept Visa, MasterCard & Money Orders. Checks allow 2 weeks for clearance. We ship by UPS ground inside US (min \$5.00) and ship by US mail outside US. Please call for orders shipping & handling or fax (foreign) orders. Purchase Orders are welcome from schools. Shipping within 24 hours. Foreign orders from Mexico, South America or European countries are welcome. In business since 1985.

CIRCLE 326 ON FREE INFORMATION CARD


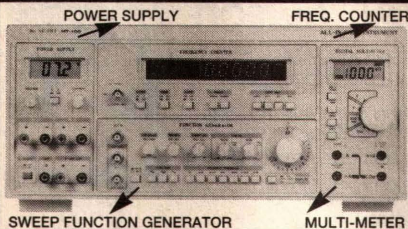
# Unbeatable Discount Prices

1 YEAR WARRANTY  
15 DAY MONEY BACK GUARANTEE



## MT-100

Reg. \$599.

**\$419.00**

### Four Instruments in One Instrument

#### 1 Function Generator

- Sine, Square, Triangle, Pulse, Skewed Sine, Ramp, TTL
- 0.2 Hz ~ 2MHz

#### 2 Frequency Counter

- 8 Digit LED
- 1 Hz ~ 100MHz
- $\pm (1 \text{ Hz} + 1 \text{ dgt.} + \text{Time Base Error})$

#### 3 Power Supply


- 3-1/2 Digit LCD
- Triple output: #1. 0-50V, 0.5A MAX
- #2, 15V, 1A #3. 5V, 2A

#### 4 Digital Multimeter

- 3-1/2 Digit LCD
- DCV, ACV,  $\Omega$ , DCA, ACA
- $\pm (0.5\% + 2 \text{ dgt.})$

### FG-140 2MHz Function Generator


Reg. \$249. **\$149.00**

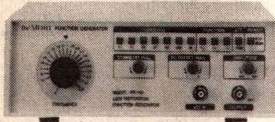

- 0.2 Hz ~ 2.0 MHz, 7 Decades
- Sine, Square, Triangle, Pulse, Ramp, Skewed Sine
- VCF, Symmetry
- Variable DC Offset Control

### 2MHz Sweep Function Gen. w/Freq. Counter


FG-150  
Reg. \$399. **\$229.00**

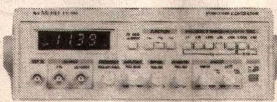

- 4 Digit LED Display
- Sine, Square, Triangle, TTL, Pulse, Ramp, Skewed Sine
- Linear/Logarithmic Sweep
- 10 MHz Freq. Counter

### 1.0GHz Frequency Counter, High Resolution

FC-200  
Reg. \$399. **\$219.00**

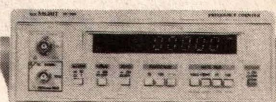


- 1.0 Hz ~ 1.0 GHz
- 8 Digit LED Display
- Auto & Manual Range
- 4 Selectable Gate Times
- 1M $\Omega$  & 50 $\Omega$  Input Impedance
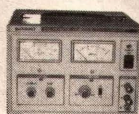
### Oscilloscope Probe Set

Switch Selectable X1/X10



- HP-9060, 60MHz Reg. \$29. **\$17.00**
- HP-9150, 150MHz Reg. \$49. **\$27.00**
- HP-9250, 250MHz Reg. \$59. **\$37.00**



### PS-500 DC Power Supply

Reg. \$249. **\$159.00**

- 0-30 VDC
- 0.1 ~ 3A
- Short & Overload Protection



### PS-540 DC Power Supply

Reg. \$399. **\$249.00**


- 0-16 VDC
- 0.1 ~ 10A
- Short & Overload Protection

### Deluxe O'scopes w/Phillips CRT.

### "BEST BUY!"


#### OS-3304

Reg. \$499. **\$349.00**

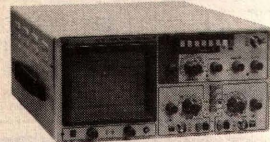

#### OS-3324

Reg. \$599. **\$429.00**

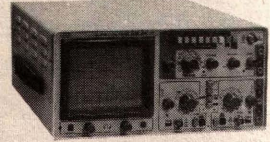

#### OS-3344

Reg. \$899. **\$649.00**



#### OS-3304 25MHz, Dual Trace

- 1 DC to 25 MHz. Dual Channel
- 6" Rectangular CRT with Internal Graticule 10x8cm (Phillips P31)
- Uncalibration LED.
- High Sensitivity 1 mV/div to 2mV/div X-Y modes, Z Axis (intensity modulation)
- Rise time 14n Sec. or less.
- Full TV Trigger for TV-V & TV-H
- Acceleration Potential 2kV
- 60MHz (X1.X10) Probe Kit: 2 sets
- Power: 115/230V AC

#### OS-3324, 3 Function


- 1 OS-3304
- 2 Dual Component Tester/Comparator
- 3 Triple DC Power Supply 5VDC, +12 VDC, -12VDC

#### OS-3344, 5 Function

- 1 + 2 + 3 • OS-3324
- 4 Frequency Counter 100MHz, 7 Digit LED Display
- 5 Function Generator 0.02 Hz to 2.0 MHz

#### OS-3315 40MHz, Dual Trace Sweep Delayed

Reg. \$799. **\$549.00**

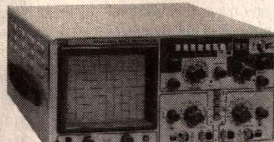


- DC to 40 MHz. Dual Channel
- Delayed Sweep 100ns to 1.0S 7 decade
- 6" Rectangular CRT with Internal Graticule 10x8cm (Phillips P31)
- Uncalibration LED.
- High Sensitivity 1 mV/div to 2mV/div X-Y modes, Z Axis (intensity modulation)
- Rise time 8.5ns or less.
- Full TV Trigger for TV-V & TV-H
- Acceleration Potential 12kV
- Variable Hold Off
- 16ns ~ 1.0s Time Base
- 60MHz (X1.X10) Probe Kit: 2 sets
- Power: 115/230V AC

### Bel MERIT

#### DM5050C DM5100

Reg. \$149. **\$89.00**

Including Deluxe Holster

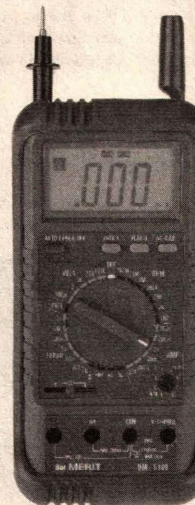

#### Features (DM5050C/DM5100)

- Basic DCV Accuracy:  $\pm 0.25\%$
- AC/DC Volt & Amp, Ohm
- Diode, Continuity Beeper
- Alligator Clip Test-Leads
- Lead Holders/Yelcro Strap Holster

#### DM5050C, DMM + Capacitance

- 9 Function / 42 Range
- Multimeter
  - Ohm: Up to 2000M $\Omega$
  - Amp: AC/DC 2 Amp
- Extended Capacitance Meter (9 Range) 0.1pF - 20,000 $\mu$ F
- Zero Adjust Knob
- Trig Lamp

#### DM5100, Wide Range w/Logic

- 11 Function / 45 Range
- Auto Power Off
- Data Hold & Peak Hold
- Freq: Up to 20MHz
- Amp: Up to 20A AC/DC
- Ohm: Up to 200M $\Omega$
- Capacitance: 1p - 200 $\mu$ F
- Logic: TTL, TR hFE

### Digital Engine Analyzer

Reg. \$119. **\$69.00**



- DM230
- 3 1/2 Digit LCD
- Engine Analyzer
- Taco, Dwell, Duty Cycle
- DMM
- DCV, DCA,  $\Omega$
- Temperature 0 ~ 1,999°F
- Diode
- Continuity
- Holster, Temp. Probe, Clip Leads

### Capacitance Meter

Reg. \$79. **\$49.00**



- CM210
- 3 1/2 Digit LCD
- 0.1p-20,000 $\mu$ F
- 9 Ranges
- 0.5% basic Accu.
- Zero Adjust Knob
- Test Leads & Built in Socket

### Pen-Type DMM w/Logic

Reg. \$79. **\$59.00**



- DM150
- 3 1/2 Digit
- Dual Display
- Auto & Manual
- DCV, ACV, ACA, DCA,  $\Omega$
- Logic CMOS/TTL
- Data Hold
- Diode
- Continuity

### Multifunction DMM

Reg. \$99. **\$64.00**



- DM4050
- 3 1/2 Digit
- Basic Accuracy: 0.25%
- Heavy Duty, 20A AC/DC
- Resistance 20M $\Omega$
- Capacitance
- Freq. up to 20MHz
- TR-hFE
- Diode
- Continuity
- Deluxe Holster

**BMC** Your Best Source for  
High Standard Electronics

P.O. Box 744, Lake Forest, CA 92630-0744

Order & Free Catalog

**800-532-3221**

(714) 586-2310 Fax (714) 586-3399




November 1996, Electronics Now


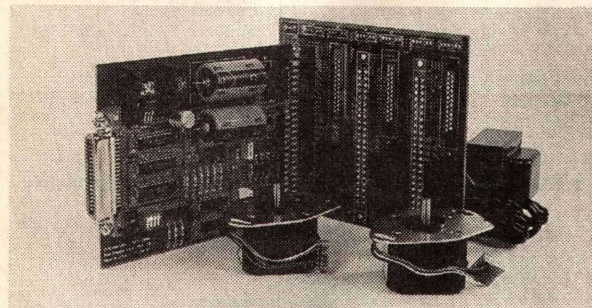
## Motion Control System

\$299.95

**INCLUDES NEW!** (3) Slot Motherboard, Dual Stepper Controller Card, 12VCT 3 Amp Transformer, (2) Stepper Motors, Easy to use I.B.M Software!



### Complete System "Nothing more to Buy!"

Unit# SKC-2000

- \* Design Robots, Plotters, Laser Systems, CNC Machines!
- \* Drives (2), 100 step, 3.6 degree, 4 Phase Stepping Motors!
- \* Unipolar 12v motors full step control. Torque is 8oz inches!
- \* Bi-Directional 8 Bit Read and Write Port!
- \* Board Addressable, 16 Possible Choices!
- \* Fits in Standard 19" inch Card Rack!
- \* Connects to any compatible I.B.M. LPT Port (1,2,3).
- \* With Additional Cards Control 32 Motors on 1 LPT Printer Port!
- \* Features Include: Variable Speed, Step, Range, Direction, and On/Off Control!
- \* System is expandable, Add I/O cards, Slave cards, and Amplifier cards.
- \* Free QBasic & Gwbasic Source Code \$ 59.95 value! \*

Send Check or M.O. to:

**CYBERMATION**

"Intelligent Controllers"

1943 Sunny Crest Dr., Suite 288,  
Fullerton, CA 92635

Call Us Today!

Tel (714) 879-2000

Fax (714) 992-2082

Visa/Master/Amex Charge Accepted

Units are in stock and ready to be shipped!

\* Add \$12.00 S&H: CA residents please add sales tax \*

## Satellite TV 'BIBLE'

### 4th 'DIGITAL' edition

The acclaimed 'bible' of satellite TV  
- ALL the TECHNICAL DETAILS -

- Operation, installation & troubleshooting of analog and digital satellite systems
- The transition from analog to digital TVRO

**1-800-483-2423**

TO ORDER

or for a FREE books/software/video CATALOG


BAYLIN

publications

1905 Mariposa, Boulder, Colorado 80302, USA  
Telephone: 303-449-4551

FAX: 303-939-8720

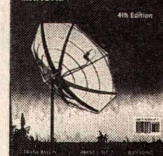HOME SATELLITE TV  
INSTALLATION  
AND TROUBLESHOOTING  
MANUAL



324 pages  
8-1/2" x 11"  
\$30 plus \$4 s/h



### Robotic Arm Kit \$180.00

Build your own Robotic Arm.  
The kit comes complete with all hardware, base enclosure, structural components, servos, servo controller kit, software and an illustrated assembly manual. Makes an excellent addition to a small mobile robot base. Great for teaching motion control.



S&H charges; USA \$7.50, international \$15.00 (surface) or \$25.00 (air mail). 10% off for 10 or more. IL residents add 6.25% to total.


Send check or money order to:  
Technical Service & Solutions  
104 Partridge Road  
Pekin, IL 61554-1403 USA

We accept  
Mastercard  
and Visa

Tel: 309-382-1816  
Fax: 309-382-1254  
www.lynxmotion.com  
jfrye@mtco.com

## "6-WAY COPY CAT \$1495.00\*"

**ASK  
ABOUT  
EE3!**

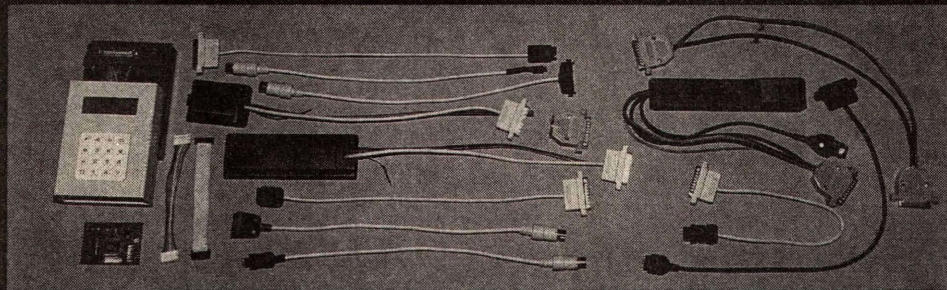

| MENU# | PROGRAMS THE FOLLOWING PHONES                       | PRICE  |
|-------|-----------------------------------------------------|--------|
| 1     | <u>MOTOROLA</u> ONLY w/elite & 951C !!!             | \$1495 |
| 2     | Above PLUS <u>NEC</u> P100-200-300-400-600-700      | FREE   |
| 3     | All of above PLUS <u>SONY</u>                       | FREE   |
| 4     | All of above PLUS <u>GE /Ericsson</u> (newest mode) | FREE   |
| 5     | All of above PLUS <u>AUDIOVOX</u> (does new 800!)   | FREE   |
| 6     | All of above PLUS <u>MITSUBISHI/DiamondTel</u>      | FREE   |

**Not a  
Kit!**

**Full 5 year  
warranty!**

\*Cables optional

All units are sold for **EXPERIMENTAL AND EDUCATIONAL PURPOSES ONLY!**

**CALL US TODAY AT 770.973.8474** ..web page @ [www.celltec.com](http://www.celltec.com)



# ATTENTION DEALERS

**BUY DIRECT FROM THE WHOLESALE**

**GET THE BEST PRICES AND SERVICE**

**ALL UNITS ARE IN STOCK FOR IMMEDIATE SHIPMENT**

## ADD-ONS

|                | QTY<br>5 | QTY<br>10 | QTY<br>20 | QTY<br>50+ |
|----------------|----------|-----------|-----------|------------|
| STEALTH-1000-P | \$55     | \$48      | \$45      | CALL       |
| TVT-3 GOLD     | \$48     | \$41      | \$38      | CALL       |
| TNT-3          | \$52     | \$45      | \$42      | CALL       |
| STEALTH 80 - P | \$61     | \$54      | \$49      | CALL       |
| M-80           | \$70     | \$64      | \$58      | CALL       |
| PIO+           | \$75     | \$68      | \$58      | CALL       |

## NEW CONVERTERS

|                 |      |      |      |      |
|-----------------|------|------|------|------|
| CENTURY CT-3000 | \$68 | \$64 | \$60 | CALL |
| SA - 8511       | \$75 | \$70 | \$65 | CALL |

## NOVAVISIONS

|         |       |       |       |      |
|---------|-------|-------|-------|------|
| NV-5600 | \$205 | \$195 | \$185 | CALL |
| NV-5700 | \$195 | \$185 | \$175 | CALL |
| NV-5800 | \$195 | \$185 | \$175 | CALL |
| NV-5750 | \$305 | \$295 | \$285 | CALL |

## BOSS COMBOS

|        |       |       |       |      |
|--------|-------|-------|-------|------|
| BOSS 1 | \$210 | \$195 | \$185 | CALL |
| BOSS 2 | \$210 | \$195 | \$185 | CALL |
| BOSS 3 | \$210 | \$195 | \$185 | CALL |

## ZENITHS

|         |       |       |       |      |
|---------|-------|-------|-------|------|
| ST-1600 | \$210 | \$195 | \$185 | CALL |
|---------|-------|-------|-------|------|

## REFURBISHED CONVERTERS

REGAL • SA • PANASONIC      CALL FOR THIS MONTH'S SPECIALS

# 1-800-800-0766

## KIMTRONICS INC

30 day money back guarantee. All shipping and handling at customers expense.  
Anyone implying theft of cable service will be denied sale. NO FLORIDA SALES.

**WE WILL MEET OR BEAT ALL COMPETITOR'S PRICES IN THIS MAGAZINE**

KIM-3

CIRCLE 328 ON FREE INFORMATION CARD







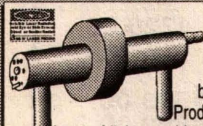
# AMAZING ELECTRONIC & SCIENTIFIC DEVICES

Lasers, Tesla, Ions, Anti-Gravity, Magnetics & More!

Plans • Ready-to-Use • Easy-to-Build Kits




**Laser Ray Gun**  
Handheld, battery operated. Produces an intense burst of light capable of burning holes.  
LAGUN2 Plans ..... \$20.00  
LAGUN2K Kit / Plans ..... Price on Req



**250KV Tesla Coil**  
10-14" of Explosive Bolts of Lightning!  
• Transmit Wireless Energy  
• Ion Motors  
• Anti-Gravity  
• Strange and bizarre pyrotechnical effects  
• Many other experiments shown in detail  
• Award winning science project!  
BTC3 Plans ..... \$15.00  
BTC3K Kit/Plans with coil ..... \$299.50  
BTC30 Assbld Ready to Use ..... \$399.50  
BTC4 Plans, 500KV unit ..... \$20.00

**ATTENTION: Experimenters & Researchers!**  
Anti-Gravity, Rail & Coil Guns, Mass Warping, Levitation Research, Exploding Water, Propulsion Drivers, Lattice Snapping, EMP etc. Loss-less Energy Charger with triggered spark switch. • Adjustable 500 to 3KV out  
• Charges up to 25KJ • Programmable Output  
HEP1 Plans ..... \$15.00  
HEP1K Kit/Plans with 500J ..... \$399.50  
HEP10 Lab Assembled - to your spec's.  
Write, call or fax for price & delivery

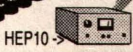

HEP10  
...shown connected to potential rail gun system

**Visible Beam Gas Lasers**  
Millions degree temp equiv. Illuminates low level clouds  
• Light Shows  
• Window Listener  
• Optical Projects  
• 12/115V  
• Science Project  
LAS1KM 1 mw, low cost Kit ..... \$69.50  
LGU6K 2-3mw Kit ..... \$119.50  
HNE70 5-7mw, ready to use ..... \$299.50



**Gravity Generator**  
Levitate an object!  
Great science fair project!  
GRA1 Plans ..... \$15.00  
GRA1K Power Supply Kit/Plans ..... \$99.50  
GRA10 Assbld Kit/Plans ..... \$149.50  
Includes text book on Anti-Gravity theory!



**Solid State Tesla Coil**  
• Generate fiery electrical plasma discharge  
• Powers light and objects without contact  
• Experiment with electrical and mechanical fields. TCL5 Plans ..... \$8.00  
TCL5K Kit/Plans 12VDC ..... \$49.50



**Pioneer a Futuristic Weapon!**  
Electric Gun - prototype designed in our lab - Join the research!  
• Ballistic Velocities  
• Handheld • Battery Operated  
• Labelled as DANGEROUS Product  
Experiment now before it is classified as a firearm! EGUN1 Plans ..... \$20.00  
(Must be 21 for purchase of hardware)



**Ion Ray Gun**  
Project Energy!  
Star Wars technology demonstrates weapons potential. IOG7K Kit/Plans \$99.50



**4000 Volts 10ma High Voltage Module** - Ready to use - for many projects from hoverboards to pyrotechnics.  
MINMAX4 While they last! ..... \$19.50

**"Talking" Plasma Globe**  
Spectacular color. Pulsates to music, sounds! 8-9", with intensity and sound controls. PLASMA1 Ready to Use ..... \$79.50



**Electronic Hypnotizer** *Caution Required*  
Control their minds! Programmable audible and visual stimuli induces hypnotic trances. HYP2K Kit with Book ..... \$39.95  
EH2 Hypnosis Book & Plans ..... \$14.95



**We can design and build high voltage systems - to your specs!**  
Call or fax us with your requirements!

## TACTICAL ELECTRONICS

**Cybernetic Ear!**  
Enhances normal hearing 3-4 times!  
Adjustable volume control, fits easily into either ear. Many, many uses.  
Ready to Use!  
CYBEREAR ..... \$19.95



**Telephone Line Grabber**  
**Infinity Transmitter**  
Use any Tone phone to monitor a premises, access other calls or control up to 8 devices! TELCON3K Plans/Kit \$99.50  
TELCON30 Ready to Use ..... \$149.50



**Long Range Microphone**  
24" dish focuses signals to an ultra-high gain amplifier.  
PM5K Kit/Plans ..... \$149.50  
• Optional wireless module transmits captured sounds to an FM radio.  
WM5K Kit for Wireless Option ..... \$29.50



**Phasor Sonic Blast Pistol**  
Rids areas of unwanted pests. Trains and conditions wild and domestic animals. Great for barns, attics, cellars, gardens.  
PPP1K Kit/Plans ..... \$39.50



**3 Mi Telephone Xmitter**  
• Tune-able 80-130 Mhz • Undetectable  
• Only transmits when phone is used  
VWPM7K Kit/Plans ..... \$39.50

**3 Mi Voice Transmitter**  
• Ultra-Sensitive Mike  
• Crystal Clear  
• Tunes 80-130 MHz.  
FMV1K Kit/Plans ..... \$39.50



**FireBall Gun**  
Shoots flaming ball - two shot capacity. Great for special effects and remote fire starting. CAUTION REQUIRED!  
FIREBALL Plans (dangerous product) ..... \$10.00




**Shocker Force Field/Vehicle Electrifier**  
Make hand and shock balls, shock wands and electrify objects. Great payback for those wiseguys!  
SHK1K Easy to Assemble Kit ..... \$19.50



**Extended Play Telephone Taping System**  
• Tapes Phone Conversation • Extends Tape X4 • Check Local Laws before using!  
TAP30X Ready to Use ..... \$84.50



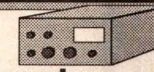**Invisible Pain Field Intruder Deterrent**  
System detects intrusions and turns on a sonic field of pain, causing disorientation, acute paranoia, nausea and more. The perpetrator - man or animal - soon vacates! Protects 4 individual areas up to 5000 sq ft. Non hazardous when used as instructed.  
PPG4K Kit/Plans ..... \$129.50  
PPG40 Ready to Use ..... \$199.50



**See In Total DARKNESS!**  
• High Quality IR Night Vision  
Scope with IR illuminator.  
SD10 Ready to Use ..... \$199.50



**Electric Charge Gun**  
Life is Precious - PROTECT IT!  
Stuns & immobilizes attackers 15 feet away! Check your state laws for legality. More knockdown power than most handguns. No permanent injury. ID coded.  
ECG1 Data (Creditable to purch) ..... \$10.00  
ECG10 Charge Gun, Ready to Use, includes FREE Stun Gun! ..... \$249.50  
STUN GUNS - sold separately:  
STUN100 100,000 Volts ..... \$34.50  
STUN200 200,000 Volts ..... \$49.50



**3 Mi Tracker Transmitter**  
• Tunable Output  
• Uses FM Radio  
• Excellent Signal Beacon  
HOD1K Kit/Plans ..... \$39.50



**MIND CONTROL!**  
Places subjects under your control. Programmable audible & visual stimuli with biofeedback. Induces strange & bizarre hallucinations without drugs. Caution - not FDA approved.  
MIND2 Plans ..... \$15.00  
MIND2K Kit and Plans ..... \$49.50  
MIND20 Assembled Unit ..... \$69.50



**FANTASTIC BRIGHTNESS!**  
High Quality Laser Pointer  
LAPN64 15mw equiv, 2000' ..... \$39.50  
LAPN61 50mw equiv, 4000' ..... \$84.50



**1000' Potato Cannon**  
Not a Toy! Uses electronic or piezo ignition. CAUTION REQUIRED!  
POT1 Plans (dangerous product) ..... \$10.00



**Window Bounce Laser Listener**  
Aim at window and listen to sounds from reflected light. CAUTION - Not for illegal use. LWB3 Plans ..... \$10.00  
LWB3K Kit/Plans (req's vid tripod) ..... \$149.50



**VISIT US ON THE WEB!**  
<http://www.amazing1.com>

**INFORMATION UNLIMITED**

Dept ENS-6, Box 716, Amherst, NH 03031  
Phone: 603-673-4730 FAX: 603-672-5406  
MC, VISA, COD, Checks accepted Please add \$5.00 S & H


**CATALOG!**  
FREE with Order or send \$1 P&H

24 Hour Phone  
**800-221-1705**  
Orders Only Please!



# New and Pre-Owned Test Equipment

## Goldstar

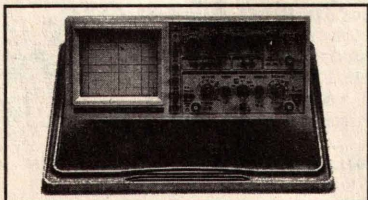

Model OS-9100P → **\$899.00**  
**Full 100 MHz Bandwidth!**

- Dual-Channel, High Sensitivity
- TV Synchronization Trigger
- Calibrated Delayed Sweep
- Includes Two Probes, 2 Year Warranty

**FREE SHIPPING!**

ON GOLDSTAR EQUIPMENT  
 ANYWHERE IN THE U.S.  
 Excluding AK & HI



**BK PRECISION**

MAXTEC INTERNATIONAL CORP.

Model 4040 \$499.00  
**20 MHz Sweep/Function Generator**

- 0.2 Hz to 20 MHz, 5 digit LED Display
- AM & FM Internal or External Modulation
- Sine, Square, Triangle, TTL, CMOS Outputs
- Burst Operation
- External 30 MHz Frequency Counter

**NEW!**



**TOLL FREE 1-800-99-METER**

1-800-996-3837

## Test Equipment Depot

A FOTRONIC CORPORATION COMPANY

P.O. BOX 708 Medford, MA 02155

(617) 665-1400 • FAX (617) 665-0780

## Pre-Owned Oscilloscope Specials

B + K Precision 1476 10 MHz \$229.00  
*Great Starter Scope!*

|                |         |          |
|----------------|---------|----------|
| Tektronix 465  | 100 MHz | \$599.00 |
| Tektronix 465B | 100 MHz | \$699.00 |
| Tektronix 475  | 200 MHz | \$799.00 |
| Tektronix 475A | 250 MHz | \$899.00 |

- The Industry Standard of Oscilloscopes
- Dual Channel, Calibrated Delayed Sweep
- Professionally Refurbished
- Aligned & Calibrated to Original Specifications
- 6 Month Warranty - The Longest Available!

## LOWEST PRICES EVER!

NEW FLUKE MULTIMETERS & TEKTRONIX OSCILLOSCOPES

The Industry Standard in Multimeters

NEW!

Model 79 II ..\$172.00 Model 87 ..\$285.00


TEKTRONIX TDS SERIES  
 ON SALE!

CIRCLE 318 ON FREE INFORMATION CARD

## CADPAK for Windows

### PROFESSIONAL SCHEMATIC CAPTURE AND PCB SOFTWARE

*NEW PRICE FOR  
 WINDOWS!! \$199*

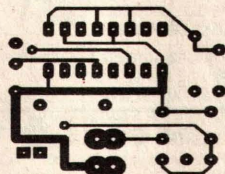

ISIS is an Easy To Use  
 Schematic Drawing Tool.

- Automatic wire routing & dot placement.
- Exports diagrams to other applications.
- Full control of drawing appearance.
- Libraries with thousands of components.

Powerfull CAD Software  
 for PCB Generation

- Advanced routing
- Libraries, including SMT
- Includes Gerber Viewing
- Fast & Easy to use.
- Exports diagrams to DTP.
- 30" x 30" board

**LOW PRICES!**

**STARTS AS LOW AS \$199 FOR WINDOWS, \$159 FOR DOS**

PRICES IS IN US FUNDS - PLEASE INCLUDE \$15 S/H

**R4 SYSTEMS INC.**

1100 GORHAM ST. SUITE 118-332  
 NEWMARKET ONTARIO  
 CANADA L3Y 7V1

905 898-0665 FAX 905 898-0683 BBS 905 898-0508

Internet r4system@astral.magic.ca

**FREE DEMO  
 WRITE OR CALL  
 TODAY**

## MICRO TV CAMERA WITH TRANSMITTER

As small as a package of cigarettes! Complete TV camera with transmitter. Available on UHF channels 14 or 24. Operates on 9V battery or may be used with a wall adapter for permanent installation. Range up to 1 mile. Perfect for any surveillance application!

**CAMERA WITH TRANSMITTER**

UPX402.....\$459.00

PLUS S&H

Please call for custom configurations.

**NEW!**

## XTAL CONTROLLED MICRO VIDEO TRANSMITTER

Circuit board area smaller than a credit card! A perfect companion to your Camcorder, but will also work with any video source. Xtal controlled. Available on UHF channel 14 or 24. Audio and other frequencies available as a custom option. Uses 9V battery or wall adapter. Range up to 1 mile with suitable antenna.

SEMI-KIT UPX51.....\$199.00

PLUS S&H with audio.....\$249.00

**5% DISCOUNT FOR MONEY ORDERS**



**B.H.S. ELECTRONICS  
 ELECTRONIC KITS**

41 EAGLERIDGE DR.  
 BRAMPTON, ONT  
 CANADA  
 L6R 1G1

TEL: 1-800-771-8656

FAX: (705) 466-3268



# ALL ELECTRONICS

C O R P O R A T I O N

QUALITY  
PARTS


FAST  
SHIPPING

DISCOUNT  
PRICING

CALL, WRITE, FAX  
or E-MAIL For A  
**Free 64 Page**  
CATALOG.  
Outside the U.S.A.  
send \$2.00 postage.
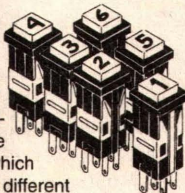
## SET OF 12, SPDT NUMBERED LIGHTED SWITCHES

Twelve push-on/push-off switches (only 6 pictured). Each switch has a 0.6" square yellow lens with a 0.25" high black numeral 1 through 12. They are lighted by a 28 volt, #85 wedge base incandescent lamp which can be easily replaced if a different voltage is desired.



CAT #PBL-12 **\$15.00** per set of 12

## SPECIAL! REDUCED PRICE 12 POSITION BARRIER STRIP



20 amp, single row, pc mount barrier strip with screw-clamp terminals. Just slip wire under clamp and tighten it down. 12 terminals on 0.375" centers. Black thermoplastic strip is 4.56" X 0.61". Barriers between screws are 0.63" high. Large quantities available.


CAT #TER-124

**65¢** each

100 for \$50.00  
1000 for \$300.00
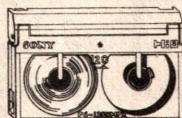
## "HI-8" VIDEO CASSETTE (USED)

SONY Hi-8  
Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box. Satisfaction Guaranteed.



**\$3.00** each

CAT #VCU-8


10 for \$28.00 • 100 for \$250.00

## 2 WAY CROSSOVER

JBL # 70561

No specs available on this two way crossover made for JBL speakers.

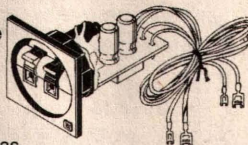2.38" square black plastic backplate has color-coded spring lever terminals and fits a 1.95" diameter hole. Crossover is attached to backplate and extends 3.17" behind mounting plate. Color coded wire leads.




CAT # LX-70561

**\$3.50** each
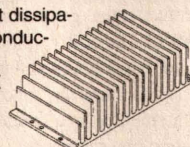
## LARGE HEATSINK

Extruded aluminum heatsink for high heat dissipation. Ideal for semiconductor or thermoelectric coolers. 6.75" X 5" X 2.27" high. Flat on one side with some small predrilled holes. 18 cooling fins.



**\$10.00** each

CAT # HS-19

## ULTRA-BRIGHT LED


Rohm # SLA-580MT-E49 T-1 3/4  
GREEN, water clear in off state. 500+ mcd @ 2.1 v, 16ma.

CAT# LED-33 **2 for \$1.00**

100 for \$40.00 • 1000 for \$300.00
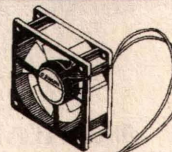
## SPECIAL PRICING! 12 VDC MINI-FAN

Sunon # KD1206PTS1  
12Vdc, 2.2 W fan. 60mm X 60mm X 25mm. Black plastic housing. Five blade impeller. 18" pigtail leads. While Supply Lasts!



**\$4.00** each

CAT# CF-35

10 for \$35.00

## THERMOELECTRIC COOLER PELTIER JUNCTIONS



NEW  
LOWER  
PRICING

These incredible miniature solid state heat pumps raise or lower temperature in a small area almost instantly. Utilizing the Peltier effect these modules perform the same cooling or heating functions as freon based refrigerators but they do it with no moving parts, and are very reliable. Current applied to the device will produce heat on one side and cold on the other side, up to 68° C difference between the two sides. Modules can be mounted in parallel to increase the heat transfer effect or can be stacked to achieve high differential temperatures. 127 thermocouples per device. Operates on 3-12 Vdc. Requires a heatsink to prevent overheating.

1.18" (30 mm) square  
X 0.15" (3.8 mm) thick.

**\$17.00** each

CAT# PJT-1  
5 for \$75.00


1.57" (40 mm) square  
X 0.15" (3.8 mm) thick.

**\$26.00** each

CAT# PJT-2  
5 for \$110.00

Quantity Pricing Available!

## 12 Vdc 1 AMP WALL TRANSFORMER

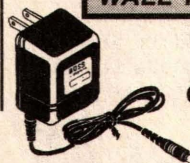

2.1 mm co-ax plug  
center positive.

CAT# DCTX-1212

**\$6.00** each

ORDER TOLL FREE

**1-800-826-5432**

MAIL ORDERS TO:  
**ALL ELECTRONICS CORP.**  
P.O. BOX 567  
VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524  
INTERNET <http://www.allcorp.com/>  
E-MAIL [allcorp@allcorp.com](mailto:allcorp@allcorp.com)

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

**MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.**



# Toronto Surplus & Scientific Inc


608 Gordon Baker Rd. Willowdale,  
Ontario Canada zip: M2H-3B4  
TEL: (416) 490-8865

VISA



OFFICE: (905) 887-0007 FAX: (905) 887-0006

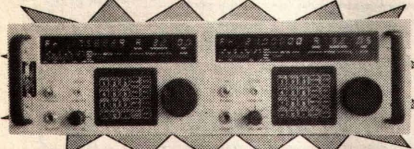
**\*\*\*SHIPPING IS NOT INCLUDED IN THESE PRICES, PLEASE CALL FOR RATES\*\*\***



## CUBIC COMMUNICATIONS DUAL VLF/HF RECEIVER


This High-Tech surveillance receiver features two fully independent high performance radios in one rack cabinet. Covers 5kHz-30MHz with a full compliment of filters incl. USB/LSB plus RS-232 remote control. The units we have in stock are in very nice condition.

Price: \$2395.00 ea.

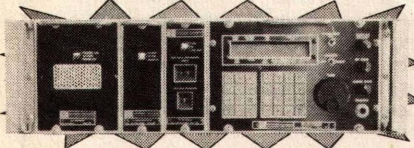
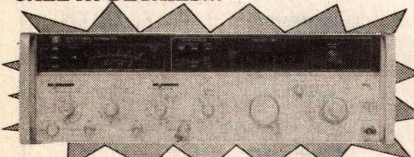
## WATKINS JOHNSON WJ-9040 SERIES RECEIVER

This awesome radio covers 200Hz-1400MHz in 13 bandwidths of AM, AM Slideback, FM, CW and SSB demodulation modes. Contains lots of features and you can bet this is a super-rare find in the used market. Price: \$5450.00 **CALL for DETAILS!!!**



## HEWLETT PACKARD 8640B SIGNAL GENERATOR


Industry Standard sig-gen 500KHz-512Mhz features internal phase lock/synchronizer and digital freq. readout. +19 to -145 dBm output. AM, FM, Ext and Pulse modulation.

Price: \$1695.00 OPT 001 add \$100.00  
OPT 003 add \$150.00


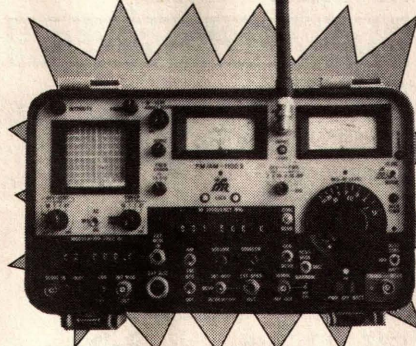
## HEWLETT PACKARD HP3312 SWEEP/FUNCTION GENERATOR

Well designed and easy to use, this function generator combines economy and quality in one compact unit. Freq range is 0.1Hz-13MHz output is 10.0VP-P into 50 ohms. Sweep, CW, AM, FM, or tone burst. This unit features-sync. out, trig. phase, symmetry, offset and more. Price: \$935.00 ea. Fully checked.



## IFR 1100S

### COMMUNICATIONS MONITOR

FM/AM-1100S is a synthesized AM/FM/SSB receiver/signal generator. Frequency range is 300KHz-1Ghz, it contains a 60 watt RF power meter, deviation/modulation meter, oscilloscope, spectrum analyzer, tone generator and internal high stability freq.-standard. It's a radio repair shop in one cabinet.

Price: \$4250.00 Fully Checked.

IFR 1000SA as above except without spectrum analyzer. Price: \$2750.00 Fully Checked.

-NEW IFR 1000 Instrument covers with sinad meter and scope probe (new unused). \$275.00




## PRC 25 - MILITARY

### TACTICAL TRANSCEIVER

Fabulous quality and design are standard in this 30Mhz-75.95 Mhz tactical transceiver. Output power level from 1.1-2 watts 150Hz squelch. The units we just received are reconditioned (newly painted) ready for issue and include the battery box. Price: \$245.00

**All Prices in U.S. \$**  
**Please include telephone/fax # with mail-in orders. Orders must be prepaid by guaranteed instrument.**  
**Prices do not include shipping.**  
**Please call us if you have any questions**

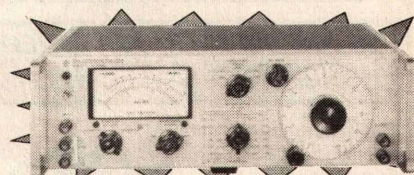
**Manuals available at extra cost**  
CIRCLE 317 ON FREE INFORMATION CARD



## HEWLETT PACKARD
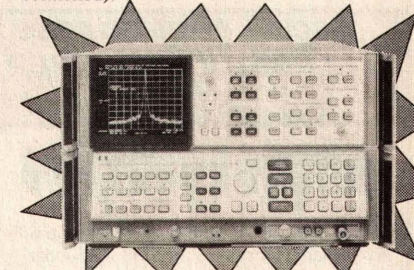
### HP 331A DISTORTION ANALYZER


Industry Standard unit covers 5Hz-600KHz & measures total harmonic distortion down to .1% full scale. We are blowing these out as-is, untested but, most we've shipped in the past have worked. Price: \$99.00 (units are scratched).



## HEWLETT PACKARD
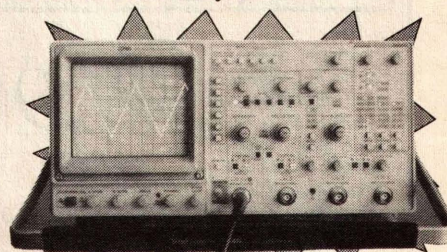
### 8568B SPECTRUM ANALYZER OPT-E96

This High Performance instrument features 3 Hz video bandwidth over the 1kHz - 1.5Ghz frequency range. Automatic zoom, signal track, multiple store/recall are only a few of the very powerful functions you will find coupled with a high performance synthesized LO and built in freq counter. Price: \$16995.00 Fully Checked




## TEK 2246 OSCILLOSCOPE

This user friendly oscilloscope features, 100MHz bandwidth on four channels, on screen scale factors, versatile triggering, 2mV/Div vert sensitivity, delayed sweep, hands-off voltmeter and smart cursors.

Looks very clean. Price: \$1950.00


(No catalog available yet!)



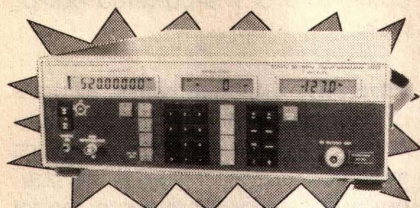
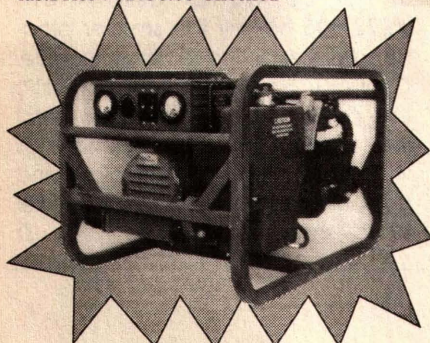
### MARCONI SYNTHESIZED SIGNAL GENERATOR Model 2018

Freq range 80KHz-520Mhz with calibrated output levels from -127 dBm to +13dBm. Resolution 10Hz. It can be freq, phase or amplitude modulated from ext or int modulation sources. RF output resolution is 0.1dB, reversepower protection of up to 50W is possible without damage to the instrument. This instrument is microprocessor controlled and very easy to use, a must for any serious repair or development lab. Price : \$1750.00 Checked



### MILITARY STANDARD D.C. GENERATOR


Superior QUALITY plus rugged design are features of this deluxe 2 cylinder 4 stroke gasoline generator. The control panel contains meters for voltage & current indication, main circuit breaker and voltage adjustment. Shielded wires and plugs comprise the RFI suppression ignition system eliminating most radio noise. These units are "new" in the original carton complete with operators manual and only require fuel and oil for operation; output voltage is adjustable approx. 10-32v (28v nom) @ 53.3A (1.5Kw) continuous duty load.

Price: \$379.00 New in Orig. Carton.

You will be impressed!!!
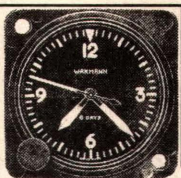
### COLLECTOR ALERT - \$39.00 8-DAY AIRCRAFT CLOCK 1-7/8" dial


Great collectors item for the ham shack, fifties vintage funct/chkd.


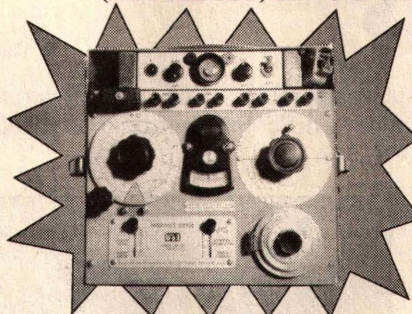
## "CAL" ASTRONAUTICS MOBILE SATELLITE COMMUNICATIONS STATION

This is a box chock full of "current" high-end communications technology. These units were designed so that mobile land based vehicles could keep in touch (via Geostationary Inmarsat satellite network) with home base using an intelligent data terminal. The terminal features a back-lit 4 line LCD display and illuminated keys; one of the transceiver's most impressive features is an "L" Band 1.2-1.55GHz 60 watt amplifier. The fabulous helix antenna (with LNA built-in) is an amazing design with all kinds of active and passive devices surface-mounted on to the antenna reflector. We consider this the "ultimate" gadgeteers goodie pack" with all kinds of up-to-date RF satellite ground technology. These systems come complete in their original shipping container with all cables and mounting bracket. Best of all they operate on 12 VDC. Operators manual supplied (but, there isn't any subscriber data).

(NOT TESTED) IN GOOD CONDITION.....\$345.00



### ESI MODEL 250 DA IMPEDANCE BRIDGE

Resistance range- 0.1 milliohms - 11 megohms, capacitance 0.1pf-1100mf, inductance 0.1  $\mu$ H to 1100 Hy. Dissipation factor (R/X or D) 0.001 to 1000. Internal oscillator 1 KHz.

Used, not functionally checked.....\$95.00  
Functionally checked.....\$165.00



### PDR-63 PORTABLE RADIAC METER

This portable radiac set is loaded with all kinds of extras featuring six ranges of sensitivity for both Gamma or Beta radiation measurements.

The 1st scale 0-1 rad/hr up to 0-5000 rad/hr. The unit comes supplied with headset & bat/charger.

Req's only 4 AA Batteries. Price: \$149.95

|                                                   |            |
|---------------------------------------------------|------------|
| -CROWN MODEL 7560 1KW PWR AMP. DC- 40KHz          | \$1,800.00 |
| -DATRON 4000A DC & OHMS CALIBRATOR                | \$4,500.00 |
| -EATON NM-17/27A EMI FIELD INT. METER             | \$1,500.00 |
| -ENI MOD 310L 250KHz-110MHz @ 50db GAIN           | \$ 365.00  |
| -ENI MOD 406L 150 KHz-250MHz @ 40db GAIN          | \$ 350.00  |
| -FLUKE 5100A CALIBRATOR                           | \$3,800.00 |
| -FLUKE 7261A FREQ. COUNTER 520mHz                 | \$ 475.00  |
| -GOULD 220 CHART RECORDER                         | \$ 450.00  |
| -GOULD RS 3800 PROGRAMABLE CHART RECORDER/w       |            |
| MOD 5900 SIG CONDITIONER & DC AMPS (NEW)          | \$3,500.00 |
| -HI- ENERGY CORP. DISCHARGE CAP. 1 $\mu$ F @ 20KV | \$ 300.00  |
| 140 $\mu$ F @ 6KV                                 | \$1,000.00 |
| -HP 204D LOW DIST. OSCILLATOR                     | \$ 350.00  |
| -HP 3551A TRANSMISSION TEST SET                   | \$ 950.00  |
| -HP 3581A WAVE ANALYZER                           | \$ 850.00  |
| -HP 4260A LCR BRIDGE                              | \$ 385.00  |


|                                            |            |
|--------------------------------------------|------------|
| -HP 4948A IN-SERVICE TMS (brand new)       | \$2,995.00 |
| -HP 5006A SIGNATURE ANALYZER               | \$ 650.00  |
| -HP 5315A UNIVERSAL COUNTER (1 GHz)        | \$ 875.00  |
| -HP 6472C POWER SUPPLY 0-64V @ 0-150A      | \$1,800.00 |
| -HP 8505 NETWORK ANALYZER SYSTEM           | \$4,980.00 |
| -HP 8558B SPECTRUM ANALYZER .01-1.5GHz     | \$2,350.00 |
| -HP 8559A SPEC-ANALYZER .01-22GHz          | \$3,995.00 |
| -MARCONI 2018 SYNTHESIZED SIGNAL GENERATOR |            |
| 80KHz - 520MHz                             | \$1,750.00 |
| -ROHDE & SCHWARZ SIG GENERATOR 4-484MHz    | \$ 750.00  |
| -TEK FG504 FUNCTION GENERATOR (40MHz)      | \$ 875.00  |
| -TEK 1502 TDR w/CHART REC                  | \$2,200.00 |
| -TEK 465 OPT 5 TV-TRIG                     | \$ 849.00  |
| -TEK 465B 100mHz OSCILLOSCOPE              | \$ 895.00  |
| -TEK 465M 100mHz OSCILLOSCOPE              | \$ 695.00  |
| -TEK 485 350 MHz OSCILLOSCOPE              | \$1195.00  |

|                                                                 |            |
|-----------------------------------------------------------------|------------|
| -TEK 1750 WAVEFORM/VECTOR MONITOR                               | \$1,850.00 |
| -SENCORE VA62 VIDEO TEST SYSTEM                                 | \$1,995.00 |
| -BOONTON 82AD AM/FM MOD-METER                                   | \$1,275.00 |
| -COLLINS 651S-1 RECEIVER                                        | \$1,250.00 |
| -GRT-22 UHF POWER AMPLIFIER                                     | \$ 200.00  |
| -R392 RECEIVER 5-30MHz                                          | \$ 165.00  |
| -T195 100w COMPANION XMTR TO 392                                | \$ 85.00   |
| -WATKINS JOHNSON 8626A-4 with WJ8626-1 & SPN 108                |            |
| 5KHz-30 MHz MIL-SPEC communications receiver                    | \$3,950.00 |
| -WAVETEK 3002 RF SIG. GENERATOR                                 | \$ 795.00  |
| *****ATTENTION DIVERS-GAS DRIVEN COMPRESSORS*****               |            |
| -BAUER 11CFM 3500 PSI COMPRESSOR SYSTEM combines a              |            |
| four stage compressor and 4 cyl wisconsin engine on a cart with |            |
| storage tanks and controls or electric version avail            | \$3,500.00 |
| -BAUER K14 3500 PSI COMPRESSOR SYSTEM same as above             |            |
| except uses briggs & stratton 8hp motor                         | \$2,750.00 |




## SPECTRUM ANALYZER

(Continued from page 52)

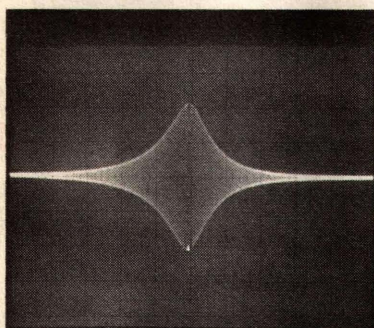

THE OSCILLOSCOPE'S VIEW of the bubble sampled from the preamplifier assembly's test point after the 145-MHz IF filter alignment. The oscilloscope's 10 × time-base magnifier is switched on. You should be able to see the zero beat at the center of the bubble.

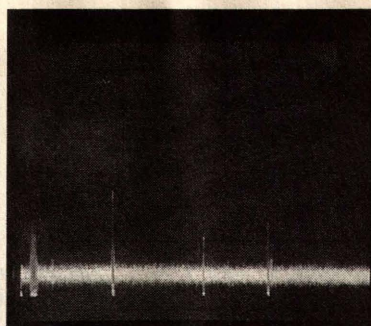For example, EMI on cables might be best observed by passing the cable through a toroid ferrite. Wrap a few turns of finer wire as a secondary and



THE OSCILLOSCOPE'S DISPLAY of the HSA output when a short-wire antenna is connected to the BNC connector. The extreme left burst is an unknown signal. Local radio-control signals from left to right are at 27.995 MHz, 53.4 MHz, and 72.280 MHz.

connect to the HSA. This allows examination of what is on a suspect cable but avoids electrostatic pickup.

It is also possible to extend the reach of the HSA with a length of coax cable with a one or two turn sniffer loop on the pickup end. In all cases, be careful when working around

power lines or line-powered equipment.

**Parts and Supplies Hints.** All parts and supplies for the Hobby Spectrum Analyzer came from electronics parts mail-order suppliers listed in the sidebar and from local hardware, model hobby, craft, and RadioShack stores. No single parts source can supply everything needed. A very few parts such as slide switches and beads came only from Digi-Key. The NE602 IC came from Ocean State Electronics and DC Electronics. The MV209 varactor comes from DC Electronics or Hosfelt. Many catalogs list ceramic disc capacitors; however, the RadioShack capacitor assortment #272-806 has all the smaller picofarad values on the RF circuit module. Consider using cut-to-length plastic ball pen handles for spacers. Metal and plastic tubing of many sizes as well as brass, aluminum, tin plate, and copper sheet is available at model hobby shops. Ω

# Robot Kits

You do ALL electronic & mechanical assembly using well-illustrated Instruction Books with assembly, experiments and testing. Each model applies different electronic & robotic principles.

## 606A "Scrambler" All Terrain Robot


This 6-legged Robot walks over rough terrain. High-tech infrared beam senses and avoids objects in its path. 32 page Book.

~~\$37.95~~  
\$35.95

## 602A "Blinky" Pathfinder Robot

Follows path made with a marker pen or tape. Red/green LEDs react to steering changes, adding fun and interest. 28 page Book. Infrared emitter/detectors.

\$36.95

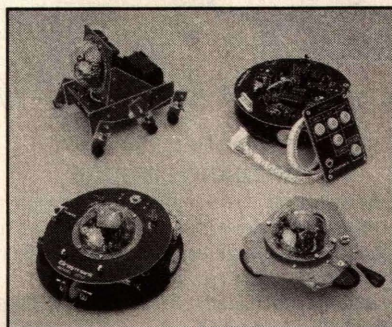

## 603A "Copycat" Programmable Robot

Program direction, light and sound using detachable keypad (included) or optional PC. Learn digital logic basics. 44 page Book.

\$57.35

## 601A "Scooter" Sound Controlled Robot

Backs up, changes direction, goes forward when it hears loud noise or hits an object. Florescent red. 24 page Book. Fast-paced excitement!

~~\$18.95~~  
\$16.95

**Technical Books** - Graymark carries a selection of technical books, including Robot Books. **Dependable Products** - Since 1963, Graymark's ONLY business has been educational electronic kits. We do one thing and we do it right.

**ORDER TODAY!** Phone: VISA/MasterCard/Discover/AMEX  
Mail: Check/Money Order, Credit Cards  
Add: \$4.00 Shipping

CALL FOR FREE  
44 PAGE CATALOG

**Graymark®**

Box 2015 • Tustin, CA 92781

<http://www.labvolt.com>

CIRCLE 309 ON FREE INFORMATION CARD

**800-854-7393**



BREAST CANCER BEGINS  
EVEN SMALLER THAN THIS.  
THAT'S WHY YOU  
NEED A YEARLY  
MAMMOGRAM.  
ESPECIALLY AS  
YOU GET OLDER.  
MAMMOGRAMS  
CAN DETECT  
LUMPS TOO  
SMALL FOR  
YOU TO FEEL  
AND EARLY  
DETECTION  
MAY SAVE  
YOUR LIFE,  
SO CALL  
1-800-  
ACS  
2345.


GET A MAMMOGRAM.  
EARLY DETECTION IS THE BEST PROTECTION.



**Free Catalog**

If you are not getting this catalog you are missing out on some of the best deals in electronics today! We have thousands of items ranging from unique, hard-to-find parts to standard production components. Call, write, or fax today to start your free subscription to the most unique catalog in the industry, filled with super values on surplus electronic and hobbyist type items. If you have a friend who would like to receive our catalog, send us their name and address and we will gladly forward them a complementary 100 page catalog.

Why pay more? Call today.

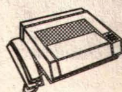

340 East First Street Fax Order Line  
Dayton, Ohio 45402 1-800-344-6324

Order Toll-Free  
1-800-344-4465


CIRCLE 251 ON FREE INFORMATION CARD

Don't waste another minute, send today for the latest free Catalog and a free sample booklet. Send your name and address to:

**Consumer Information Center  
Department TH  
Pueblo, Colorado 81009**

## ACTIVE MICRO We Want Your Excess Inventory

- \* INTEGRATED CIRCUITS
- \* MEMORY (NEW OR USED)
- \* EPROMS (NEW OR USED)
- \* CIRCUIT BOARDS
- \* DIODES
- \* TRANSISTORS
- \* LED'S

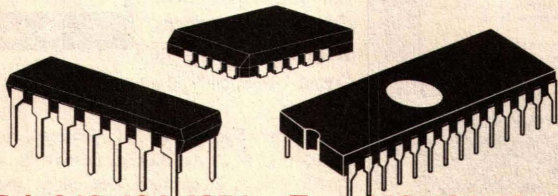

**Tel 310-494-4851 Fax 310-494-4913**  
1891 Obispo Ave Signal Hill, CA 90804


# HOME AUTOMATION

## World's Largest Selection!

### Widest Selection of X-10 Devices Available

Hundreds of hard-to-find automation, X-10 and wireless control products. Computer interfaces, software, development tools, lighting control, telephone systems, security systems, surveillance cameras, infra-red audio/video control, HVAC, pet care automation, wiring supplies, books and videos and much more!

Packed with Pictures  
& Diagrams

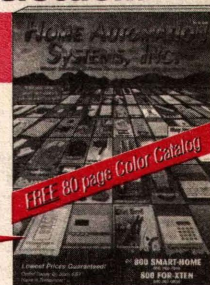

**HOME AUTOMATION SYSTEMS, INC.**

Questions: 714-708-0610 Fax: 714-708-0614


e-mail: catalog@smarthome.com

http://www.smarthome.com/smarthome

**Lowest Prices  
Guaranteed!**

24 Hours **Call 800-SMART-HOME** 800-762-7846

## AUDIO DISTORTION ANALYZER

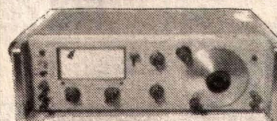



**HEWLETT-PACKARD 331A ANALYZER** measures total distortion 0.1% to 100% of full scale in 7 ranges over 5 Hz to 600 KHz. Fundamental rejection >80 DB. Voltmeter indicates 300 uv to 300 V rms in 13 ranges, 10 DB per range. Requires 115/230 VAC; 16.8x5x15.3, 24 lbs sh.

USED-CHECKED with manual ..... \$350 \$215

## H-P AUDIO OSCILLATOR

**HEWLETT-PACKARD 200CD OSCILLATOR**, popular tube-type audio generator covers 5 Hz to 600 KHz in five bands; output 10 volts into 600 ohms or 20 V open circuit. Requires 115/230 VAC 50-400 Hz. 7"Wx10.8"Hx12.5"D, 20 lbs sh.

USED-CHECKED w/book ..... \$125.00

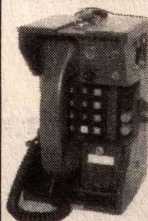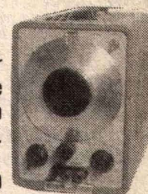

## TA-838/PT FIELD PHONE

**MILITARY TELEPHONE** has push-button numeric tone pad and is designed for 2- or 4-wire communications; replaces old EE-8 and TA-43/312 field phones. Ringing signal possible only in 4-wire hook-up. TA-838 can also be operated over standard telephone lines. Rugged thermoplastic construction; requires four C-cell batteries. 6.9x5, 8 lbs. sh.

USED-CHECKED ..... \$85.00  
Operators Manual ..... \$10.00

## JAN-BOXED ELECTRON TUBES

|                                              |                                           |
|----------------------------------------------|-------------------------------------------|
| 2A3 Penta-USA (but looks Chinese-made) ..... | \$14.00                                   |
| 2K25 Raytheon blue ...                       | \$40.00                                   |
| 4D32 Raytheon .....                          | \$35.00                                   |
| 1625 National-Union ...                      | \$4.50                                    |
| 5751 ECG .....                               | \$3.50                                    |
| 5998A Sylvania .....                         | \$9.95                                    |
| 6146W GE .....                               | \$19.95 ea; 10 for \$175.00               |
| 6922 ECG = 6DJ8 .....                        | \$3.50 ea; 10 for \$28.00; 100 / \$200.00 |
| 7360 ECG .....                               | \$15.00                                   |
| 8552 ECG, 12V Version 6146 .....             | \$12.00                                   |
| 7581A ECG, 35 W version of 6L6GC .....       | \$17.50 ea; 10/\$150.00                   |
| 4CX300A/8167 Eimac .....                     | \$65.00                                   |
| 6B4GA Sylvania .....                         | \$17.50                                   |
| 5691 Richardson .....                        | \$6.50                                    |
| 5814A ECG = 12AU7 .....                      | \$3.25                                    |
| 7025 GE = 12AX7A .....                       | \$7.50                                    |

Prices F.O.B. Lima, O. • VISA, MASTERCARD Accepted.

Allow for Shipping • Write for latest Catalog

Address Dept. ES • Phone 419/227-6573 • Fax 419/227-1313

## FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802



## Printed Circuits in Minutes Direct From LaserPrint!

- 8 1/2" x 11"  
\* Or Photocopy  
\*\* Use standard household iron or P-n-P Press.
1. LaserPrint\*
  2. Press On\*\*
  3. Peel Off
  4. Etch



Use Standard Copper Clad Board  
20 Shts \$30/ 40 Shts \$50/ 100 Shts \$100  
Visa/MC/PO/Ck/MO \$4 S&H

Techniks Inc.  
P.O. Box 463  
Ringoes NJ 08551  
ph. 908.788.8249 fax 908.788.8837  
http://chelsea.ios.com/~techniks  
Retail Dealer Inquires Invited

## "WE PURCHASE" \$\$ TOP PRICES \$\$ PAID

**JERROLD™**  
DPV7  
FPBB7  
CFT

**TOCOM™**  
5503 VIP  
5507

**PIONEER™**  
5135  
6110  
6300

**ATLANTIC  
SCIENTIFIC™**  
8570  
8580  
8590  
8600

**Midwest's Largest Brokers**  
We Buy Quantities of Ten To A Thousand Units  
**NATIONAL CABLE BROKERS**  
**(219) 935-4128**


## UPGRADE YOUR COMPUTER!

**TECHNOLOGY ASSOCIATES**  
959 W. 5th St. • Reno, NV 89503  
(702) 322-6875 • Fax (702) 324-3900  
www.techass.com • sales@hoopware.com

| Memory                                        | Hard Drives                                  | Modems                                         |
|-----------------------------------------------|----------------------------------------------|------------------------------------------------|
| 1Mb (1x8-70 ns) \$9                           | WD 540 Mb IDE \$180                          | 14.4 Int Fax/Modem \$38                        |
| 4Mb (4x8-70 ns) \$27                          | WD 850 Mb IDE \$175                          | 28.8 Int Fax/Modem \$97                        |
| 4Mb (1x32-60 ns) \$25                         | WD 1.2Gb IDE \$250                           | 28.8 Int Supra PNP Fax/Modem \$102             |
| 8Mb (2x32-60 ns) \$52                         | WD 1.6Gb IDE \$250                           | 28.8 Int Supra PNP Fax/Modem for Windows \$115 |
| 16Mb (4x32-60 ns) \$98                        | WD 2.1Gb IDE \$340                           | 33.6 Int Fax/Modem \$89                        |
| 32Mb (8x32-60 ns) \$188                       |                                              |                                                |
| CPU's                                         | Video Cards                                  | Sound Cards                                    |
| AMD 486DX4-100 \$33                           | 256K ISA VGA \$23                            | 16-bit Sound Blaster Pro compatible \$40       |
| AMD 5x86-133 \$42                             | Trident 9500 1Mb ISA SVGA \$38               | 16-bit SB Pro PnP \$80                         |
| Cyrix 5x86-120 \$65                           | Trident 9440 1Mb VLB SVGA \$38               | Sound Blaster 32 PnP \$141                     |
| Cyrix 686-110 \$140                           | SIS 1Mb PCI SVGA \$38                        |                                                |
| Intel Pentium 100 \$142                       | Trident 9680 1Mb PCI SVGA w/MPEG \$45        |                                                |
| Cyrix 686-120 \$178                           |                                              |                                                |
| Intel Pentium 133 \$250                       |                                              |                                                |
| Cyrix 686-133 \$209                           |                                              |                                                |
| Intel Pentium 150 \$425                       |                                              |                                                |
| Intel Pentium 166 \$499                       |                                              |                                                |
| Motherboards                                  | Miscellaneous                                |                                                |
| 486sx VLB, 256K \$72                          | 1.44Mb FDD \$29                              |                                                |
| 486sx PCI, 256K \$99                          | 1.2Mb FDD \$60                               |                                                |
| Pentium Intel Triton2 VX, 256K pipeline \$128 | 6X CD-ROM IDE \$80                           |                                                |
| Pentium Intel Triton2 VX, 512K pipeline \$162 | 8X CD-ROM IDE \$95                           |                                                |
| Pentium Pro \$310                             | Colorado Traven T1000 850mb tape drive \$195 |                                                |
|                                               | 3-button serial mouse \$9                    |                                                |
|                                               | Spill-resistant 101-key \$20                 |                                                |

Prices and availability subject to change without notice.  
**CALL FOR DAILY LOW PRICES!**

## Smart Battery Charger

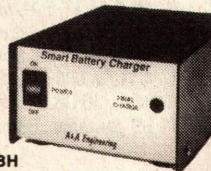

JUN 87 QST  
BY WARREN DION N1BBH

**FOR GEL-CELLS or LEAD ACID BATTERIES.**  
**Features:** Precision temperature tracking voltage reference & three mode charging sequence. Standard kit is for 12V @ 1/2 or 1 Amp, user selectable. Can be connected to the battery indefinitely, will not overcharge. Weighs 2 pounds and measures 4"W x 5 1/2"D x 2 1/2"H. Finished enclosure included in kit.

**Complete Kit Only . . . . . \$59.95**  
**Assembled & Tested . . . . . \$79.95**

CA Residents add 7.75% sales tax. S&H: \$5.00 (insured). Foreign orders add 20%. For more info or price list; send legal size SASE (52¢) to:

**A&A Engineering**  
2521 W. La Palma #K • Anaheim, CA 92801  
(714) 952-2114 • FAX: (714) 952-3280

## NEW EASY PC

BRITISH  
DESIGN  
AWARD

**SCHEMATIC and PCB C.A.D.**

ONLY **\$135**

Includes

- MGA, CGA, EGA & VGA compatible.
- Design large multi layer boards.

- One level pull down menu and quick keys for fast layout.

- Dot matrix, laser, plotter, Gerber & N.C. drill output.

- 6 Month Free update
- Free Demo



7840 ANGEL RIDGE ROAD  
ATHENS, OHIO 45701  
(614) 592-1810

Visa & MasterCard Accepted

## Timid about getting on the . . World Wide Web?

You've heard about the *Information Superhighway* and all the hype that goes with it! Sort of makes you feel timid about getting on the Web. Put your fears aside! A new book, *The Internet and World Wide Web Explained*, eliminates all the mystery and presents clear, concise information to build your confidence. The jargon used is explained in simple English. Once the tech-talk is understood, and with an hour or two of Web time under your belt, your friends will believe you are an Internet guru!

To order Book #403 send \$6.95 plus \$3.00 for shipping in the U.S. and Canada only to Electronics Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240. Payment in U.S. funds by U.S. bank check or International Money Order. Please allow 6-8 weeks for delivery.

## GIANT! SPY ELECTRONICS CATALOG

**Just Like In The Movies!**  
Fiber-optics • IR Detectors • UV Powder  
Covert TV Cameras • Phone Transmitters  
Laser/Parabolic Mic's • Nightvision • Wrist Watch  
Cameras • Time Lapse VCR's, Surveillance-Counter  
Surveillance • Homing Xmitter's • Fiberscopes • Police  
Electronics • Micro-TV's • Phone Bug's • TV Xmitters  
Transmitters • Books/Videos's and Much, Much More!

**SECRET EVIDENCE LOCATOR**  
Just whistle your secret  
code and it whistles back  
**\$7.77+2.00 S&H**


**MODULAR JACK  
PHONE XMITTER**  
**\$25.95 + 2.00 S&H**

**Subscription! \$5.00 to CIA ASSOCIATES**  
4101-267EN11 Green Oaks,  
Arlington, TX 76016
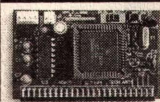
## ADAPT-11 68HC11 Module for Solderless Breadboards

- miniature 2.0" by 2.8" module
- plugs vertically into solderless breadboard
- reset circuit, button, & mode select switch
- RS-232 int., 5V reg. & ext. pwr. conn.
- all I/O lines on dual row connector
- programs 68HC811E2 & 7111E9 chips

Starter Package comes with ADAPT-11 module, 68HC811 microcontroller with 2K EEPROM on-chip (re-programmable in circuit 1000s of times; no EPROM programmer or eraser required), PC serial cable for downloading code, Motorola Programming Reference Guide, ADAPT-11 User Manual, freely distributable 68HC11 software, and demo program. #AD11-SP \$74.95 + \$5 shipping & handling.



Use PLCC's in your Solderless Breadboard!  
• Solderless breadboard socket adapters for all popular PLCC sizes.  
• Vertical design saves space on breadboard.

Also available:  
Solderless breadboard adapters for DB9 & DB25, and IDC (ribbon cable) connectors, from \$5.


Visa, MasterCard, AmEx, Discover

**TECHNOLOGICAL ARTS**  
309 Aragona Blvd., Suite 102, Box 418, Va. Beach, VA 23462  
1644 Bayview Avenue, Box 1704, Toronto, ON M4G 3C2  
voice/fax: (416) 963-8996 www.io.org/~techart
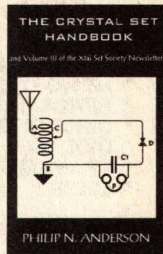
## INSIDE CRYSTAL SETS

An easy-to-read book on crystal set theory and construction opens vistas for novices and pros alike. Build radios like Grandpa did, do it better, and know what you are doing. *The Crystal Set Handbook*, published by The Crystal Set Society, is an authentic guide on the topic.

To order *The Crystal Set Handbook*, send \$10.95 plus \$4.00 for shipping in the U.S. and Canada only to Electronics Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240. Payment in U.S. funds by U.S. bank check or International Money Order. Please allow 6-8 weeks for delivery.





# Books that work the way you work...


**SPECIAL OFFER**  
No obligation

**SAVE  
OVER 10%**

**NEW  
FROM  
JOHN LENK**



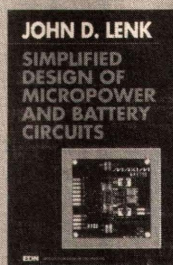
1996, paperback  
~~\$29.95~~ \$26.95  
0-7506-9821-7



1996, paperback  
~~\$29.95~~ \$26.95  
0-7506-9510-2




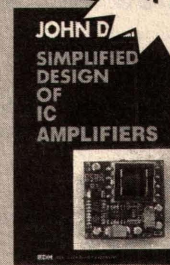1996, paperback  
~~\$29.95~~ \$26.95  
0-7506-9820-9




June 1996, paperback  
~~\$29.95~~ \$26.95  
0-7506-9508-0

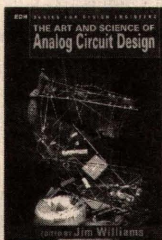Butterworth-Heinemann brings you something for everyone from John Lenk's Simplified Design Series. These books are all-inclusive, one-stop guides. Each has step-by-step instructions and diagrams that make it easy-to-use for the student, experimenter, and professional. All are available in paperback.



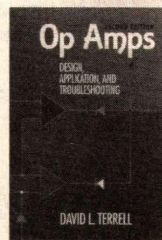
1995, hardcover  
~~\$49.95~~ \$44.95  
0-7506-9505-6



1996, hardcover  
~~\$49.95~~ \$44.95  
0-7506-9702-4



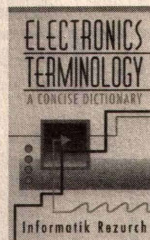1995, paperback  
~~\$29.95~~ \$26.95  
0-7506-9694-X




1996, paperback  
~~\$12.95~~ \$10.95  
0-7506-9751-2




1996, paperback  
includes disk  
~~\$39.95~~ \$35.95  
0-7506-9700-8



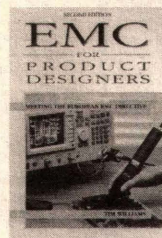July 1996, hardcover  
~~\$49.95~~ \$44.95  
0-7506-9747-4



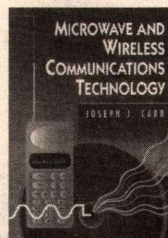1996, paperback  
~~\$47.95~~ \$42.95  
0-7506-2466-3



1996, paperback  
~~\$44.95~~ \$39.95  
0-7506-9707-5



1995, paperback  
~~\$47.95~~ \$42.95  
0-7506-2281-4



1996, paperback  
~~\$37.95~~ \$33.95  
0-7506-2591-0

☐ Please send me the book(s) listed below at 10% off! **Phone: 1-800-366-BOOK FAX: 1-800-446-6520**

Please add \$4.00 for handling for the first item ordered and \$1.50 for each additional item ordered to all check and credit card orders. Billed orders will be charged additional shipping based on weight and destination. All US orders must include your state sales tax. Prepayment or company purchase order is required for all orders. Canadian customers please pay by credit card or in US funds and include 7% GST on books and handling. Prices subject to change without notice.

Write book number(s) here

|  |  |  |  |
|--|--|--|--|
|  |  |  |  |
|--|--|--|--|

Charge my: ☐ VISA ☐ AMEX ☐ MC Card # \_\_\_\_\_ EXP Date \_\_\_\_\_

Name \_\_\_\_\_ Signature \_\_\_\_\_

Address \_\_\_\_\_ City/ State/ ZIP \_\_\_\_\_

Tel \_\_\_\_\_ E-mail \_\_\_\_\_

Visit us on the Internet @ <http://www.bh.com/bh/el>

☐ Send me a FREE catalog (item 642)

**B**UTTERWORTH  
**H**EINEMANN

313 Washington Street, Newton, MA 02158  
from outside US and Canada, call 617-928-2500

TS123

CIRCLE 333 ON FREE INFORMATION CARD



**CALL TOLL FREE**  
(800) 292-7711 orders only  
Se Habla Español

# C&S SALES

EXCELLENCE IN SERVICE

**CALL OR WRITE FOR  
A FREE 60 PAGE  
CATALOG!**  
(800) 445-3201


## XK-550 Digital / Analog Trainer

Elenco's advanced designed Digital / Analog Trainer is specially designed for school projects. It is built on a single PC board for maximum reliability. It includes 5 built-in power supplies, a function generator with continuously sine, triangular and square wave forms. 1560 tie point breadboard area.

**XK-550**  
Assembled and Tested  
**\$169.<sup>95</sup>**

**XK-550K - Kit**  
**\$139.<sup>95</sup>**


Tools and meter shown optional

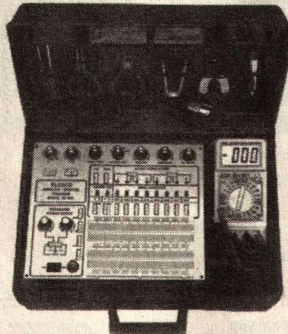

**TK-3000**  
**\$89.<sup>95</sup>**
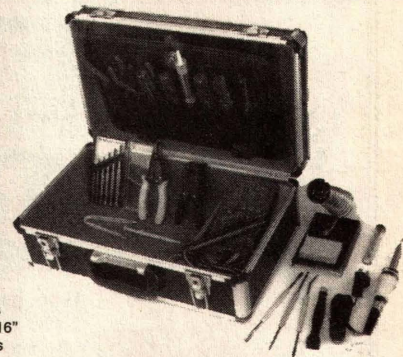
### Tools Included:

- SR-2 - Deluxe Soldering Iron
- SH-1 - Soldering Iron Stand
- ST-1 - Diagonal Pliers
- ST-2 - Long Nose Pliers
- ST-30 - Deluxe Wire Stripper
- SE-1 - Solder Ease Kit
- ND-3 - 3 pc. Nut Driver Set
- TL-8 - Precision Screw Drivers
- ST-5 - Screw Driver Slotted 3/16"
- ST-6 - Screw Driver #1 Phillips
- ET-10 - IC Puller
- SP-2 - Solder Pump
- ST-20 - Safety Goggles
- ST-9 - Pocket Screw Driver
- ST-4 - Solder Tube
- SW-3 - Solder Wick



A professional technician service tool kit in a metal reinforced tool case with heavy-duty handle and locks. A removable pallet handles most of the tools listed with more room for tools and parts in the lower half.

## GF-8026 w/ Frequency


- Linear and Log Sweep
- .02Hz to 2MHz
- Counter Range 1Hz to 10MHz
- 4 Digit Display

**\$225**


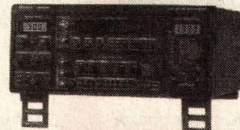
## MX-9300 Four Functions in One

• One instrument with four test and measuring systems:  
1.3GHz Frequency Counter • 2MHz Sweep Function Generator  
Digital Multimeter • Digital Triple Power Supply  
(0-30V @ 3A, 15V @ 1A, 5V @ 2A)




**\$479.<sup>95</sup>**

## Model XP-581

**4 Fully Regulated DC Power Supplies in One Unit**

4 DC voltages: 3 fixed - +5V @ 3A, +12V @ 1A, -12V @ 1A  
1 Variable - 2.5 - 20V @ 2A

**\$85**

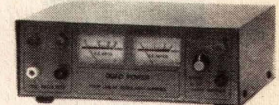

**Auto Ranging Hand-Held  
DMM w/ Bar Graph  
Model EDM-163**

**\$99.<sup>95</sup>**

7 Functions with data hold  
Compares to Fluke Model 77II

## Digital Multimeter Model M-1700

**\$39.<sup>95</sup>**

11 functions including freq to 20MHz,  
cap to 20µF. Meets UL-1244 safety  
specs.



## Fluke Multimeters

### 70 Series

Model 70II .....\$69.95  
Model 73II .....\$97.50  
Model 75II .....\$135.00  
Model 77II .....\$154.95  
Model 79II .....\$175.00

### 80 Series

Model 83 .....\$235.00  
Model 85 .....\$269.00  
Model 87 .....\$289.00

## B&K Precision Multimeters

Model 391 .....\$159.00  
Model 390 .....\$139.00  
Model 389 .....\$109.00  
Model 388A .....\$99.00  
Model 2707 .....\$79.00  
Model 2860A .....\$85.00

## Kit Corner

over 100 kits available

### PT-223K


**\$15.<sup>95</sup>**

Phone kit  
with  
train-  
ing  
course.



**Fiber Optics  
Technology  
with training course  
Model FO-30K**


**\$19.<sup>95</sup>**

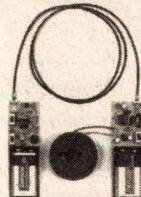

### Model AM/FM-108K Transistor Radio Kit

with training course

**\$29.<sup>95</sup>**

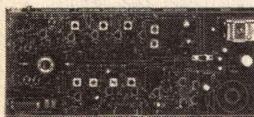

### M-1005K Compact Multimeter Kit

**\$19.<sup>95</sup>**

6 Functions &  
Transistor  
Test




## Model M-6100

### Programmable DMM

Includes **FREE** Computer Interface  
and **FREE** Software

- Analog Bar Graph
- Large 3 3/4" LCD Display
- Menu Driven
- Triple Display
- RS-232 Interface
- True RMS
- 9 Basic Functions including cap. & freq.
- Auto Power Off
- Easy-to-use

**\$125**

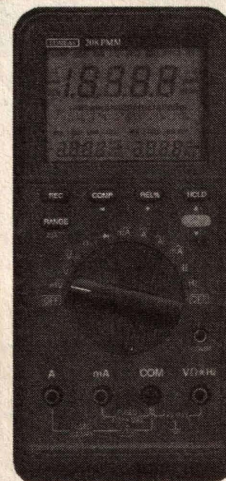

**WE WILL NOT BE UNDERSOLD**

UPS SHIPPING: 48 STATES 5%  
OTHERS CALL FOR DETAILS  
IL Residents add 8% Sales Tax

**C&S SALES, INC.**

150 W. CARPENTER AVENUE  
WHEELING, IL 60090  
FAX: (847) 520-9904 (847) 541-0710  
[http://www.elenco.com/cs\\_sales/](http://www.elenco.com/cs_sales/)



**15 DAY MONEY BACK  
GUARANTEE  
FULL FACTORY WARRANTY**

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

CIRCLE 308 ON FREE INFORMATION CARD



**FREE PROBES  
WITH ALL  
SCOPES**

# OSCILLOSCOPES


**Lowest Prices of the Year!**

**CALL OR WRITE FOR  
A FREE 60 PAGE  
CATALOG!  
(800) 445-3201**

## B&K Precision Scopes

### 60MHz ANALOG WITH DIGITAL STORAGE

Model 2560

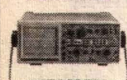

- Cursors and readouts
- RS-232 port
- 20MS/s real time sampling
- 1GHz equivalent time sampling (at 0.1µs/div.)
- Prints via RS-232 port to any HP-GL plotter

**\$1995**

### 20MHz ANALOG WITH DIGITAL STORAGE

Model 2522A



- 20MHz analog bandwidth
- 20MS/s sampling rate
- 2K memory per channel
- 300MHz equivalent time sampling
- Pre-trigger capture

**\$869.95**

### 100MHz THREE-TRACE

Model 2190A



- 1mV/division sensitivity
- Sweeps to 5ns/division
- Dual time base
- Signal delay line
- 15KV accelerating voltage

**\$1379.95**

### 60MHz DUAL-TRACE

Model 2160A



- 1mV/division sensitivity
- Sweeps to 5ns/division
- Dual time base
- Signal delay line
- V mode-displays two signals unrelated in frequency
- Component tester

**\$949.95**

### 40MHz DUAL-TRACE

Model 1541C



- 1mV/division sensitivity
- Video sync separators
- Z-axis input
- Single Sweep
- V mode displays two signals unrelated in frequency
- Component tester

**\$695**

### 60MHz, CURSORS & READOUTS, DUAL TIME BASE

Model 2260



- Cursors and readouts
- 1mV/div sensitivity
- 23 calibrated ranges - main time base
- 19 calibrated ranges - delayed time base
- Signal delay time
- V-mode - displays 2 signals unrelated in frequency
- Component tester
- Z-axis input
- Single sweep

**\$1225**

### 20MHz DUAL-TRACE

Model 2120 - 2 Year Warranty

**Special \$389.95**


Model 2125 with delayed sweep

**\$539.95**



- 1mV/division sensitivity
- AUTO/NORM triggered sweep operation
- AC, TVH, TVV and line coupling
- Calibrated 19 step time-base with x10 magnifier
- Compact low-profile design

## Quality Scopes by Elenco

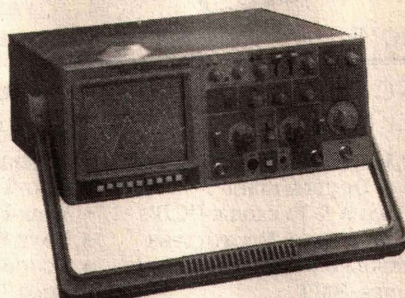


**60MHz**

**DS-603 \$1350**

- Analog / Digital Storage
- 20MS/s Sampling Rate

**S-1360 \$749**

- Analog with Delayed Sweep

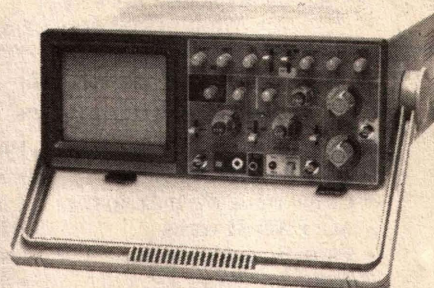

**40MHz**

**S-1345 \$569**

- Analog with Delayed Sweep

**S-1340 \$475**

- Analog

**25/30MHz**

**DS-303 \$1095**

- Analog / Digital Storage

**S-1330 \$439**

- 25MHz Analog
- Delayed Sweep

**S-1325 \$325**

- 25MHz Analog

**2 Year  
Warranty**

### OSCILLOSCOPE SELECTION CHART

#### ANALOG

| Model  | Bandwidth MHz | Sensitivity (max) | No. of Channels | Sweep Rate Max ns/div | Delayed Sweep | Video Sync | Component Tester | Beam Find | Time Base |
|--------|---------------|-------------------|-----------------|-----------------------|---------------|------------|------------------|-----------|-----------|
| S-1360 | 60            | 1mV/div           | 2               | 10ns/div              | Yes           | Yes        | Yes              | Yes       | 2         |
| S-1345 | 40            | 1mV/div           | 2               | 10ns/div              | Yes           | Yes        | Yes              | Yes       | 2         |
| S-1340 | 40            | 1mV/div           | 2               | 10ns/div              | No            | Yes        | No               | No        | 1         |
| S-1330 | 25            | 1mV/div           | 2               | 10ns/div              | Yes           | Yes        | Yes              | Yes       | 2         |
| S-1325 | 25            | 1mV/div           | 2               | 10ns/div              | No            | Yes        | No               | No        | 1         |

#### DIGITAL STORAGE

| Model  | Bandwidth MHz | Analog Sen (max) | No. of Channels | Sampling Rate | Memory Channel | Internally Backed Up | Pretrigger %  | Output |
|--------|---------------|------------------|-----------------|---------------|----------------|----------------------|---------------|--------|
| DS-303 | 30            | 1mV/div          | 2               | 20MS/S        | 2K             | Yes                  | 0, 25, 50, 75 | RS232  |
| DS-603 | 60            | 1mV/div          | 2               | 20MS/S        | 2K             | Yes                  | 0, 25, 50, 75 | RS232  |

## Affordable Spectrum Analyzers by B&K

### 500MHz Series

Model 2615 - \$1595  
Model 2620 w/ tracking generator - \$1895

### 1.05GHz Series

Model 2625 - \$2395  
Model 2630 w/ tracking generator - \$2995



**HITACHI SCOPES**  
Inventory Reduction Sale  
Lowest Prices of the Decade!

|                                                                     |                                                                  |
|---------------------------------------------------------------------|------------------------------------------------------------------|
| V-209 - 20MHz Battery Operated<br>Was \$1505, NOW \$1095 Save \$410 | V-695 - 60MHz w/ Cursors<br>Was \$1815, NOW \$1395 Save \$420    |
| V-422 - 40MHz Was \$965,<br>NOW \$765 Save \$200                    | V-1065A - 100MHz w/ Cursors<br>Was \$2139, NOW \$1565 Save \$574 |
| V-525 - 10MHz w/ Cursors<br>Was \$1355, NOW \$955 Save \$400        | V-1560 - 100MHz Was \$1790,<br>NOW \$1490 Save \$300             |
| V-552 - 50MHz Was \$1195,<br>NOW \$850 Save \$345                   | V-1565 - 100MHz w/ Cursors<br>Was \$1960, NOW \$1595 Save \$365  |
| V-555 - 50MHz w/ Cursors<br>Was \$1375, NOW \$975 Save \$400        | V-252 - 20MHz <b>\$419</b>                                       |

## Fluke Scopemeters



|     |        |
|-----|--------|
| 91  | \$1225 |
| 92B | \$1445 |
| 96B | \$1695 |
| 97  | \$1795 |
| 97A | \$2945 |
| 99B | \$2095 |

Call or write for  
complete specs.

**WE WILL NOT BE UNDERSOLD**

**C&S SALES, INC.**

150 W. CARPENTER AVENUE  
WHEELING, IL 60090  
FAX: (847) 520-9904 (847) 541-0710  
[http://www.elenco.com/cs\\_sales/](http://www.elenco.com/cs_sales/)



**15 DAY MONEY BACK  
GUARANTEE**

**FULL FACTORY WARRANTY**  
PRICES SUBJECT TO CHANGE WITHOUT NOTICE

November 1996, Electronics Now





- PRODUCT ENGINEERING
- FIRMWARE DEVELOPMENT

- MICRO CONTROLLER & EPROM HARDWARE & SOFTWARE DEVELOPMENT

**"QUALITY  
IS OUR  
CAPITAL  
CONCERN."**

**Complete On Site  
Electrical Engineering Lab**

- REVERSE ENGINEERING
- RF CIRCUIT DESIGN & MANUFACTURING

From Auto-Routing to CNC Routing to Electronic Assemblies...  
**Capital Electronics** is Your Best Route For Printed Circuit Boards.

#### DESIGN/LAYOUT

- CAD LAYOUT SERVICES
- COMPATIBLE WITH ALMOST ALL CAD SYSTEMS
- FROM SCHEMATICS OR SAMPLE PCB'S
- PHOTOPLOTTING SERVICES
- 28,800 BAUDE MODEM

#### PRINTED CIRCUIT BOARDS

- SINGLE & DOUBLE SIDED
- MULTI-LAYER & FLEXIBLE PCB'S
- FROM QUICK TURN PROTOTYPES TO SCHEDULED PRODUCTION RUNS
- FINE LINES, SMT
- ELECTRICAL TESTING
- PRECIOUS METAL PLATING

#### ASSEMBLY SERVICES

- FAST TURN BOARD STUFFING
- WIRE HARNESSSES
- WAVE SOLDERING
- ACQUISITION OF PARTS
- FINAL TESTING
- TURNKEY SERVICES
- CUSTOM ENCLOSURES

*For Quick & Competitive Pricing or More Information,  
Please Call Us Today!*

852 Foster Avenue • Bensenville, IL 60106

**(708) 350-9510**

Fax (708) 350-9760 • Modem (708) 350-9761

#### Internet Access:

For Automated Info Response:  
INFO@capital-elec.com

E-Mail: Quote@capital-elec.com

Web Access: <http://www.capital-elec.com>

CIRCLE 332 ON FREE INFORMATION CARD

Radiotelephone - Radiotelegraph

**FCC** Commercial  
License

### Why Take Chances?

Discover how easy it is to pass the exams. Study with the most current materials available. Our **Homestudy** Guides, Audio, Video or PC "Q&A" disks make it so fast, easy and inexpensive. No college or experience needed. The new commercial FCC exams have been revised, covering updated Aviation, Marine, Radar, Microwave, New Rules & Regs, Digital Circuitry & more. We feature the Popular "Complete Electronic Career Guide". 1000's of satisfied customers **Guarantee** to pass or money back. Newest Q&A pools.

Send for **FREE DETAILS** or call

**1-800-800-7588**

**WPT Publications**  
4701 N.E. 47th St.  
Vancouver, WA 98661

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ St. \_\_\_\_\_ Zip \_\_\_\_\_


**1-800-800-7588**

Electronics Now, November 1996

124


## CONTROL RELAYS • LIGHTS • MOTORS MEASURE TEMPERATURE • PRESSURE • LIGHT LEVELS • HUMIDITY INPUT SWITCH POSITIONS • THERMOSTATS • LIQUID LEVELS

### MODEL 30 ..... \$79

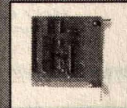

- PLUGS INTO PC BUS
- 24 LINES DIGITAL I/O
- 8 CHANNEL
- 8 BIT A/D IN
- 12 BIT COUNTER
- UP TO 14K SMP/SEC

### MODEL 45 ..... \$189

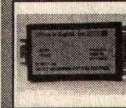


- RS-232 INTERFACE
- 8 DIGITAL I/O
- 8 ANALOG INPUTS
- 2 ANALOG OUTPUTS
- 2 COUNTERS-24 BIT

### MODEL 100 ..... \$279



- 12 BIT 100 KHZ A/D
- 4 ANALOG OUTPUTS
- 3 TIMER COUNTERS
- 24 DIGITAL I/O

### MODEL 60 ..... \$179

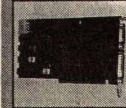

- 32-AMP RELAY
- 16 DIGITAL I/O
- 1 8-BIT ANALOG INPUT

### MODEL 40 ..... \$99



- RS-232 INTERFACE
- 28 LINES DIGITAL I/O
- 8 ANALOG INPUTS
- PWM OUTPUT
- OPTIONAL 12 BIT A/D

### MODEL 70 ..... \$239



- RS-232 INTERFACE
- 18 BIT A/D
- 5.5 DIGIT
- UP TO 60 SMP/SEC

**NEED A CUSTOM PCB? TRY US.**

**PRAIRIE DIGITAL, INC.**

PHONE 608-643-8599 • FAX 608-643-6754

846 SEVENTEENTH STREET • PRAIRIE DU SAC, WISCONSIN 53578

CIRCLE 321 ON FREE INFORMATION CARD




## Synthesized FM Stereo Transmitter



Microprocessor controlled for easy freq programming using DIP switches, no drift, your signal is rock solid all the time - just like the commercial stations. Audio quality is excellent, connect to the line output of any CD player, tape deck or mike mixer and you're on-the-air. Foreign buyers will appreciate the high power output capability of the FM-25; many Caribbean folks use a single FM-25 to cover the whole island! New, improved, clean and hum-free runs on either 12 VDC or 120 VAC. Kit comes complete with case set, whip antenna, 120 VAC power adapter - easy one evening assembly.

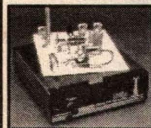**FM-25, Synthesized FM Stereo Transmitter Kit ..... \$129.95**



## Tunable FM Stereo Transmitter

A lower cost alternative to our high performance transmitters. Offers great value, tunable over the 88-108 MHz FM broadcast band, plenty of power and our manual goes into great detail outlining aspects of antennas, transmitting range and the FCC rules and regulations. Connects to any cassette deck, CD player or mixer and you're on-the-air, you'll be amazed at the exceptional audio quality! Runs on internal 9V battery or external power from 5 to 15 VDC, or optional 120 VAC adapter. Add our matching case and whip antenna set for a nice finished look.

**FM-10A, Tunable FM Stereo Transmitter Kit ..... \$34.95**

**CFM, Matching Case and Antenna Set. .... \$14.95**

## RF Power Booster Amplifier



Add some serious muscle to your signal, boost power up to 1 watt over a frequency range of 100 KHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM Stereo transmitters, providing radio service through an entire town. Power required: 12 to 15 volts DC at 250mA, gain of 38dB at 10 MHz, 10 dB at 1000 MHz. For a neat, professionally finished look, add the optional matching case set.

**LPA-1, Power Booster Amplifier Kit ..... \$39.95**

**CLPA, Matching Case Set for LPA-1 Kit ..... \$14.95**

**LPA-1WT, Fully Wired LPA-1 with Case ..... \$99.95**



## Micro FM Wireless Mike

World's smallest FM transmitter. Size of a sugar cube! Uses SMT (Surface Mount Technology) devices and mini electret condenser microphone, even the battery is included. We give you two complete sets of SMT parts to allow for any errors or mishaps-build it carefully and you've got extra SMT parts to build another! Audio quality and pick-up is unbelievable, transmission range up to 300 feet, tunable to anywhere in standard FM band 88 to 108 MHz. 7/8" w x 3/8" h x 3/4" h.

**FM-5 Micro FM Wireless Mike Kit ..... \$19.95**

## Crystal Controlled Wireless Mike



Super stable, drift free, not affected by temperature, metal or your body! Frequency is set by a crystal in the 2 meter Ham band of 146.535 MHz, easily picked up on any scanner radio or 2 meter rig. Changing the crystal to put frequency anywhere in the 140 to 160 MHz range-crystals cost only five or six dollars. Sensitive electret condenser mike picks up whispers anywhere in a room and transmit up to 1/4 mile. Powered by 3 volt Lithium or pair of watch batteries which are included. Uses the latest in SMT surface mount parts and we even include a few extras in case you sneeze and lose a part!


**FM-6, Crystal Controlled FM Wireless Mike Kit ..... \$39.95**

**FM-6WT Fully Wired FM-6 ..... \$69.95**

**Call for our Free Catalog !**

# RAMSEY

## Super Pro FM Stereo Radio Transmitter

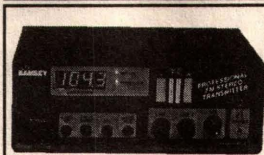

A truly professional frequency synthesized FM Stereo transmitter station in one easy to use, handsome cabinet. Most radio stations require a whole equipment rack to hold all the features


we've packed into the FM-100. Set frequency easily with the Up/Down freq buttons and the big LED digital display. Plus there's input low pass filtering that gives great sound no matter what the source (no more squeals or swishing sounds from cheap CD player inputs!) Peak limiters for maximum 'punch' in your audio - without over modulation, LED bargraph meters for easy setting of audio levels and a built-in mixer with mike and line level inputs. Churches, drive-ins, schools and colleges find the FM-100 to be the answer to their transmitting needs, you will too. No one offers all these features at this price! Kit includes sharp looking metal cabinet, whip antenna and 120 volt AC adapter. Also runs on 12 volts DC.

We also offer a high power export version of the FM-100 that's fully assembled with one watt of RF power, for miles of program coverage. The export version can only be shipped outside the USA, or within the US if accompanied by a signed statement that the unit will be exported.

**FM-100, Professional FM Stereo Transmitter Kit ..... \$299.95**

**FM-100WT, Fully Wired High Power FM-100 ..... \$429.95**

## Speech Descrambler Scrambler

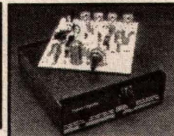

Decode all that gibberish! This is the popular descrambler / scrambler that you've read about in all the Scanner and Electronic magazines. The technology used is known as speech inversion which is compatible with most cordless phones and many police department systems, hook it up to scanner speaker terminals and you're in business. Easily configured for any use: mike, line level and speaker output/inputs are provided. Also communicate in total privacy over telephone or radio, full duplex operation - scramble and unscramble at the same time. Easy to build, all complex circuitry contained in new custom ASIC chip for clear, clean audio. Runs on 9 to 15VDC, RCA phono type jacks. Our matching case set adds a super nice professional look to your kit.

**SS-70A, Speech Descrambler/Scrambler Kit ..... \$39.95**

**CSS, Custom Matching Case and Knob Set ..... \$14.95**

**SS-70AWT, Fully Wired SS-70A with Case ..... \$79.95**

**AC12-5, 12 Volt DC Wall Plug Adapter ..... \$9.95**

## Tone-Grabber Touch Tone Decoder / Reader



Dialed phone numbers, repeater codes, control codes, anywhere touch-

tones are used, your TG-1 will decode and store any number it hears. A simple hook-up to any radio speaker or phone line is all that is required, and since the TG-1 uses a central office quality decoder and microprocessor, it will decode digits at virtually any speed! A 256 digit non-volatile memory stores numbers for 100 years - even with the power turned off, and an 8 digit LED display allows you to scroll through anywhere in memory. To make it easy to pick out numbers and codes, a dash is inserted between any group or set of numbers that were decoded more than 2 seconds apart. The TG-1 runs from any 7 to 15 volt DC power source and is both voltage regulated and crystal controlled for the ultimate in stability. For stand-alone use add our matching case set for a clean, professionally finished project. We have a TG-1 connected up here at the Ramsey factory on the FM radio. It's fun to see the phone numbers that are dialed on the morning radio show! Although the TG-1 requires less than an evening to assemble (and is fun to build, too), we offer the TG-1 fully wired and tested in matching case for a special price.

**TG-1, Tone Grabber Kit ..... \$99.95**

**CTG, Matching Case Set for TG-1 Kit ..... \$14.95**

**TG-1WT, Fully Wired Tone Grabber with Case ..... \$149.95**

**AC12-5, 12 Volt DC Wall Plug Adapter ..... \$9.95**




## Mini-Peeper Micro Video Camera

Super small, high quality fully assembled 8 & W CCD TV camera the size of an ice cube! Provides excellent pictures in low light (2 lux), or use our IR-1 Infra-Red light source to invisibly illuminate an entire room on a pitch black night! Imagine the possibilities... build it into a smoke detector, wall clock, lamp, book, radio. Exact same camera that's in big buck detective catalogues and stores. Kit includes: fully assembled CCD camera module, connectors, interface PC board kit with proper voltage regulation and filtering, hook-up details, even a mini microphone for sensitive sound! Two models available: Wide Angle Lens 3.6mm/12, adjustable focus lens, 92 degree view; Pinhole Lens 5.5mm/14.5, 60 degree view. The Pinhole Lens is physically much flatter and provides even greater depth of focus. The camera itself is 1.2" square. The Wide Angle Lens is about 1" long, Pinhole Lens about 1/2", interface PC board is 1" x 2" and uses RCA jacks for easy hook-up to VCRs, TVs or cable runs. Power required is 9 to 14 VDC @ 150 mA. Resolution: 380 x 350 lines. Instruction manual contains ideas on mounting and disguising the Mini-Peeper along with info on adding one of our TV Transmitter kits (such as the MTV-7 unit below) for wireless transmission!

**MP-1, Wide Angle Lens CCD TV Camera Outfit ..... \$169.95**

**MP-1PH, Pin-Hole Lens CCD TV Camera Outfit ..... \$189.95**
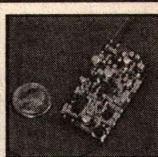
## MicroStation Synthesized UHF TV Transmitter



Now you can be in the same league as James Bond. This transmitter is so small that it can fit into a pack of cigarettes - even including a CCD TV camera and battery! Model airplane enthusiasts put the MTV-7A into airplanes for a dynamite view from the cockpit, and the MTV-7A is the transmitter of choice for balloon launches. Transmitter features synthesized, crystal controlled operation for drift-free transmission of both audio and video on your choice of frequencies: Standard UHF TV Channel 52 (which should only be used outside of the USA to avoid violating FCC rules), and 439.25 MHz or 911.25 MHz which are in the amateur ham bands. The 439.25 MHz unit has the nifty advantage of being able to be received on a regular 'cable-ready' TV set tuned to Cable channel 68, or use our ATV-74 converter and receive it on regular TV channel 3. The 911.25 MHz unit is suited for applications where reception on a regular TV is not desired, an ATV-79 must be used for operation. The MTV-7A's output power is almost 100 mW, so transmitting range is pretty much 'line-of-sight' which can mean many miles! The MTV-7A accepts standard black and white or color video and has its own, on-board, sensitive electret microphone. The MTV-7A is available in kit form or fully wired and tested. Since the latest in SMT (Surface Mount Technology) is used to provide for the smallest possible size, the kit version is recommended for experienced builders only. Runs on 12 VDC @ 150 mA and includes a regulated power source for a CCD camera.

**MTV-7A, UHF TV Channel 52 Transmitter Kit ..... \$159.95**

**MTV-7AWT, Fully Wired Channel 52 Transmitter ..... \$249.95**

**MTV-7A4, 439.25 MHz TV Transmitter Kit ..... \$159.95**

**MTV-7A4WT, Fully Wired 439.25 MHz Transmitter ..... \$249.95**

**MTV-7A9, 911.25 MHz TV Transmitter Kit ..... \$179.95**

**MTV-7A9WT, Fully Wired 911.25 MHz Transmitter ..... \$269.95**

**ATV-74, 439.25 MHz Converter Kit ..... \$159.95**

**ATV-74WT, Fully Wired 439.25 MHz Converter ..... \$249.95**

**ATV-79, 911.25 MHz Converter Kit ..... \$179.95**

**ATV-79WT, Fully Wired 911.25 MHz Converter ..... \$269.95**

## RAMSEY ELECTRONICS, INC.

793 Canning Parkway  
Victor, NY 14564


**Order Toll-free: 1-800-446-2295**  
Sorry, no tech info or order status at this number

**Technical Info, Order Status**  
**Call Factory direct: (716) 924-4560**



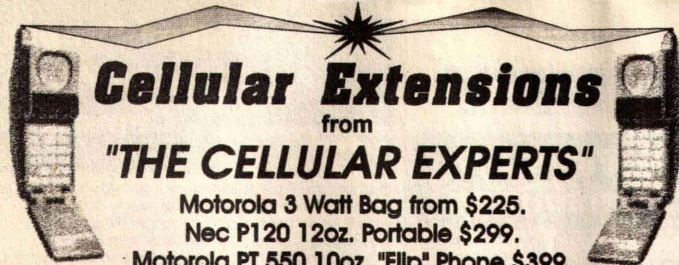**ORDERING INFO:** Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$4.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.





Others available, buy new from us, or send us your phone.  
Get a second or third phone with no additional monthly charges!  
Motorola, NEC, Panasonic, Audiovox and many others!

Fax Back Hotline, For 24hr. info. call from your FAX (714) 581-7460 or call  
**(800) 457-4556**  
Nationwide paging available. C.G.C. Dealer inquires welcome.

## Move Up to the Ultimate in Robotic Kits.



OWI's "Next Generation" of affordable, rugged Robot Kits challenge the enthusiast to solder circuit boards and mechanically assemble.

Visit our homepage @  
<http://www.owirobot.com>

Each OWIKIT also incorporates the basic principles of robotic experiments, sensing and locomotion, guaranteeing an exciting, hands-on adventure of knowledge and fun!

But remember! OWI is the recognized founder and leader in Educational Robot Kits. ACCEPT NO IMITATIONS.

|                                |                                 |              |       |  |
|--------------------------------|---------------------------------|--------------|-------|--|
| <b>NEW</b>                     |                                 |              |       |  |
| <b>ROBOT.TECH.CURR. MV-RTC</b> | Teacher's Manual                | 158 Pg. Book | 74.95 |  |
| <b>ELECTRO-MAGNETIC TRAIN</b>  |                                 |              | 14.95 |  |
| <b>S-CARGO</b>                 | OWI-936K Sound Sensor           | 47 Pg. Book  | 29.95 |  |
| <b>WAO II</b>                  | OWI-961K Programmable - Graphic | 59 Pg. Book  | 69.95 |  |
| <b>SPIDER</b>                  | OWI-962K Infrared Sensor        | 49 Pg. Book  | 49.95 |  |
| <b>LINE TRACKER</b>            | OWI-963K Infrared Sensor        | 48 Pg. Book  | 49.95 |  |
| <b>MANTA</b>                   | OWI-966K Sound / Touch Sensor   | 44 Pg. Book  | 29.95 |  |
| <b>MOON WALKER</b>             | OWI-989K Solar Sensor           | 10 Pg. Book  | 34.95 |  |



**EK**  
ELEKIT


1160 Mahalo Place, Suite B  
Rancho Dominguez, CA  
90220-5443  
(310) 638-7970  
Fax: (310) 638-8347



## —LASERS— & ACCESSORIES

WE SPECIALIZE IN  
**Laser and Laser  
Related Surplus  
Inventory**

### HENE LASERS

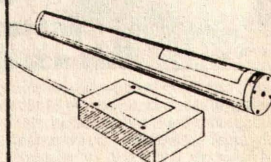


- Complete Systems
- Plasma Tubes
- Power Supplies

### DIODE LASERS



- Visible I/R
- Complete Modules
- Collimating Optics
- Drive Circuits

### ACCESSORIES

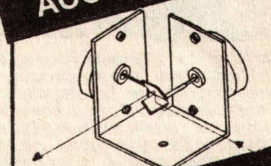

- Books
- Optics
- Electro-Optics

**CALL  
FOR A  
FREE  
CATALOG!**

We want your Laser related surplus items. Call or Fax us today for a quote!

**MEREDITH**  
**INSTRUMENTS**

P O Box 1724  
5035 N. 55th Ave. #5  
Glendale, AZ 85301

Phone: 602-934-9387  
Fax: 602-934-9482


[HTTP://WWW.MI-LASERS.COM](http://www.MI-LASERS.COM)


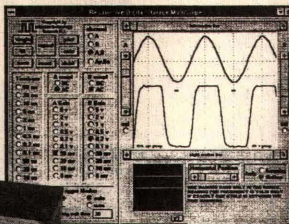
## TURN YOUR PC INTO A DIGITAL STORAGE OSCILLOSCOPE!

The PC-  
MultiScope  
by mission  
technology

Featured  
in May '96  
Electronics  
Now!



above: actual scope screen on PC  
**\$399+** S/H. Visa/MC/Check.

Dual channel; up to 20Ms/sec sampling; 2Mhz analog bandwidth; install thru PC parallel port; easy Windows interface; strip chart recd/spectrum analyzer modes; ext. trig. +\$40; VB source code +\$99

### AMAZE ELECTRONICS CO.

Tel: 800-996-2008 Fax: 408-996-0366

<http://www.hooked.net/users/amaze>  
or email: [amaze@hooked.net](mailto:amaze@hooked.net)



### Restores Horizontal and Vertical Sync Lines from Distorted Analogue Video Formats

For Free Information Package on Completed Units and Pricing

• Call Toll Free •  
**1-800-236-5778**

R.C. Distributing • PO Box 552 • South Bend, IN 46624

### CELLULAR PROGRAMMERS!

**COPYCAT MOTOROLA CELLULAR PROGRAMMER:**  
program any Motorola Phone up to 951C. Complete  
Assembly: **\$999**

**COPYCAT KIT ONLY** (unassembled complete with  
instructions): **\$750**

**ERICSON CLIP** (program through the keypad): **\$350**

**OKI 900** modified (up to 5 numbers programmed  
in): **\$400**

**OKI CHIP** only: **\$75**

Also different programs available for all brands!  
FOR DEALERS ONLY MASTER FILES AVAILABLE  
DISCOUNT FOR QUANTITIES.

PH: 718-575-1474 718-768-4963


Fax: 718-369-3989

E MAIL: [104170.3043@COMPUSERVE.COM](mailto:104170.3043@COMPUSERVE.COM)
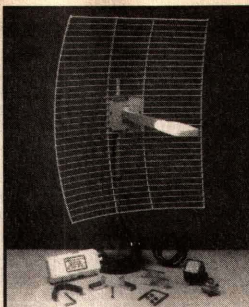
### CABLE TV CONVERTERS

Equipment & Accessories  
Wholesalers Welcome

Call C&D ELECTRONICS  
1-800-310-1153 M-F 10a-8p



**CHALLENGER SYSTEM**  
33-Channel 52dB+ Gain  
Complete Grid \$265  
Five Year Warranty  
**FREE SHIPPING**

## Quality Microwave TV Systems

**WIRELESS CABLE - ITFS - MMDS  
ATV - INTERNATIONAL - S-BAND**  
Amplifiers • Antennas • Books • Components  
Filters • Systems • Video Products

- RF Frequency 1990 - 2700 MHz
- Cable Ready - VHF - UHF Outputs
- SASE For "FREE" Catalog or Send \$1

## PHILLIPS-TECH ELECTRONICS

PO Box 8533 • Scottsdale, AZ 85252

**ORDER LINE 800-880-MMDS**

**CATALOG / INFO 602-947-7700**

**FAX LINE 602-947-7799**

Visa • M/C • Amx • Disc • COD's • Qty Pricing


CIRCLE 310 ON FREE INFORMATION CARD

# IN STOCK

quality \ 'kwäl - et - ē \ noun

- An inherent and essential feature or element:  
exhibiting a degree of excellence and superiority.  
syn. see Mouser Electronics

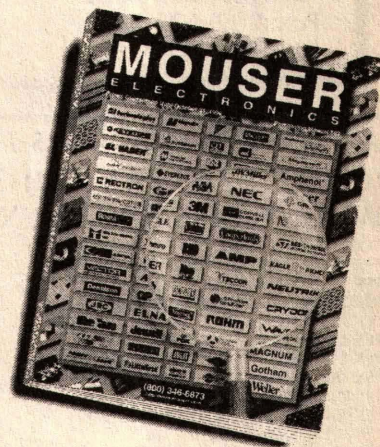Call for your  
**FREE 332**  
page catalog  
**TODAY!**



67,092 Products

126 Manufacturers

All Orders Ship Same Day

- Passive Components ■ Semiconductors
- Electromechanical ■ Connectors/Cable
- Surface Mount and Through Hole

## MOUSER<sup>®</sup> ELECTRONICS

**800-346-6873**

FAX: 817-483-0931

<http://www.mouser.com>  
[sales@mouser.com](mailto:sales@mouser.com)

958 North Main St., Mansfield, TX 76063

CIRCLE 324 ON FREE INFORMATION CARD



## PC-Based 6MHz Sweep/Function Generator \$549

- Wide frequency range from 0.2Hz to 6 MHz
- Sine, square, triangular output waveforms plus sweep function
- 3 operating modes: sweep, gated burst and voltage control frequency
- Designed and made in USA

Turn your PC into a test station with :

|                                |       |
|--------------------------------|-------|
| Dual 100 MHz Universal Counter | \$399 |
| 60 MHz Digital Storage Scope   | \$749 |
| 100 MHz Digital Storage Scope  | \$999 |

**TC INSTRUMENTS INC.®**

Tel: (909) 622-2006  
Fax: (909) 622-7778  
<http://www.tcinst.com>

We  
do OEM  
Distributors wanted

## ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401 (612)332-2378 FAX (612)332-8481 30 DAY WARRANTY WE BUY TEST EQUIPMENT AND COMPONENTS.

|                                         |           |                                        |           |
|-----------------------------------------|-----------|----------------------------------------|-----------|
| TEK 7A13 DIFFERENTIAL COMPARATOR        | \$150.00  | TEK 7B15 1 GHZ DELAYING TIME BASE      | \$250.00  |
| TEK 7A16P PROG.200MHZ VERT.AMPLIFIER    | \$75.00   | TEK 7B50A 150 MHZ TIME BASE            | \$75.00   |
| TEK 7A17 150 MHZ SINGLE TRACE AMPLIFIER | \$50.00   | TEK 7B52 DUAL TIME BASE                | \$75.00   |
| TEK 7A18 75 MHZ DUAL TRACE AMPLIFIER    | \$50.00   | TEK 7B53 100 MHZ DUAL TIME BASE        | \$75.00   |
| TEK 7A19 600 MHZ SINGLE TRACE AMPLIFIER | \$150.00  | TEK 7B70 200 MHZ TIME BASE             | \$75.00   |
| TEK 7A22 DIFFERENTIAL AMPLIFIER         | \$200.00  | TEK 7B71 DELAYING TIME BASE            | \$75.00   |
| TEK 7A24 400 MHZ DUAL TRACE AMPLIFIER   | \$200.00  | TEK 7B80 400 MHZ DELAYED TIME BASE     | \$100.00  |
| TEK 7A26 200 MHZ DUAL TRACE AMPLIFIER   | \$75.00   | TEK 7B85 400 MHZ DELAYING TIME BASE    | \$125.00  |
| TEK 7D11 DIGITAL DELAY UNIT             | \$50.00   | TEK 7B90P PROGRAMABLE TIME BASE        | \$200.00  |
| TEK 7D12 A/D CONVERTER MAINFRAME        | \$50.00   | TEK 7B92A 500 MHZ DELAYING TIME BASE   | \$125.00  |
| TEK 7D13 DIGITAL MULTIMETER             | \$50.00   | TEK AM502 DIFFERENTIAL AMPLIFIER       | \$75.00   |
| TEK 7M11 DUAL 50 OHM DELAY LINE         | \$100.00  | TEK MX5010 MULTIFUNC.INTERFACE EXTEN.  | \$200.00  |
| TEK 7M13                                | \$50.00   | TEK 7834 400 MHZ STORAGE MAIN FRAME    | \$400.00  |
| TEK 7S11 SAMPLING PLUG IN               | \$200.00  | TEK 7844 400 MHZ MAIN FRAME            | \$400.00  |
| TEK 7S12 GENERAL PURPOSE SAMPLER        | \$350.00  | TEK 7854 400 MHZ DIGITAL STORAGE FRAME | \$500.00  |
| TEK 7S14 1 GHZ SAMPLING PLUG IN         | \$350.00  | TEK 7904 500 MHZ MAIN FRAME            | \$250.00  |
| TEK PS5010 PROG.TRIPLE POWER SUPPLY     | \$250.00  | TEK 7104 1GHZ FRAME WITH-              | \$2750.00 |
| TEK 485 350 MHZ PORTABLE SCOPE          | \$600.00  | (7A29,7A29,7B10,7B15)                  |           |
| KEITHLEY 480 PICOAMMETER                | \$300.00  | TEK 2235 100MHZ OSCILLOSCOPE           | \$650.00  |
| LEADER LBO516 100MHZ OSCILLOSCOPE       | \$300.00  | TEK 2246 100MHZ OSCILLOSCOPE           | \$1200.00 |
| GENRAD 1657 RLC BRIDGE                  | \$750.00  | GENRAD 1658 RLC BRIDGE                 | \$900.00  |
| SENCOR LC53 CAP-IND. METER              | \$400.00  | TEK 608 MONITOR                        | \$650.00  |
| FLUKE 8505A 6.5 DIGIT DMM               | \$250.00  | TEK 577 D1/177 CURVE TRACER            | \$1500.00 |
| TEK DAS9100 WITH PROBES                 | \$750.00  | HP 1651 LOGIC ANALYZER                 | \$1200.00 |
| TEK 7D20 PROGRAMABLE DIGITIZER          | \$500.00  | HP 8012A PULSE GENERATOR               | \$400.00  |
| FLUKE 343A DC VOLTAGE CALIBRATOR        | \$750.00  | BRADLEY 192 O-SCOPE CALIBRATOR         | \$750.00  |
| TEK 453 50 MHZ OSCILLOSCOPE             | \$200.00  | TEK 475 200 MHZ OSCILLOSCOPE           | \$500.00  |
| AYCOM PSA-35A SPECTRUM ANALYZER         | \$1000.00 | LEADER LBO516 100 MHZ OSCILLOSCOPE     | \$300.00  |
| SENCOR LC53 CAP-IND. METER              | \$400.00  | RACAL-DANA 1991 160 MHZ COUNTER        | \$300.00  |
| EMI SCR300-3 POWER SUPPLY               | \$300.00  | TEK 608 MONITOR                        | \$650.00  |
| HP 141T/8553B/8552B SPECTRUM ANALYZER   | \$1500.00 | HP 8601 110 MHZ SWEEP/SIGNAL GEN.      | \$350.00  |

## Invest a stamp...Save a bundle

For the price of a stamp, you can get the latest edition of the federal government's free Consumer Information Catalog. It lists more than 200 free or low-cost publications on federal benefits, jobs, health, housing, education, cars, and more.  
So stamp out ignorance with our free Catalog. Send your name and address to:  
Consumer Information Center, Department SB, Pueblo, Colorado 81009

## Cable TV Descramblers

Converters \* Filters \* Accessories

30 day Free Trial - NO RISK!  
Unbeatable wholesale prices!  
Affordable extended warranty  
1 Year Warranty on all products

Free  
Catalog

Call the cable professionals!

Credit Cards Welcome!

**1-800-379-3976**

Prices starting  
as low as \$99!

## New Surveillance Devices!

Smoke Alarm and Table Clock Video Cameras Ultra miniature video cameras hidden in smoke alarm or alarm clock - your choice. Wide field of view and super 1 lux low light sensitivity! Undetectable!

SC-800 TC-70 High quality B/W with 420 lines of resolution for ultra sharp images. Direct output of video and audio. \$219.95 ea.

Best price on surveillance cameras anywhere!

Telephone Transmitter Kit hidden in dual modular adaptor Transmits both sides of conversation to any FM radio up to 1/4 mile. "SnapKit" technology. Uses phone line for power and antenna! Goes completely unnoticed. MA-100 \$25.95

High quality cassette deck plugs directly into telephone jack! Records up to 12 hours of conversations on a single cassette. Recording starts and stops automatically when phone is used! \$99.95

Free shipping! Check/Money orders also accepted

Seymour-Radix Inc. Box 166055-N Irving, TX 75016

Now you can visit us on the internet at: <http://www.why.net/home/sr/>



## MULTI FREQUENCY CUBES!

WIRELESS CABLE BOX TESTER

EXTERNAL AND INTERNAL MULTI-FREQUENCY

WORKS ON ALL MODELS: J\*\*\*\* SA, PIONEER, ALSO FOR CFT 2200!

WORKS EVERYWHERE.

AUTOMATIC FREQUENCY FINDER!

60 DAYS WARRANTY

QUANTITY DISCOUNT AVAILABLE

DEALERS WELCOME!

PH: 718-575-1474 718-768-4963

Fax: 718-369-3989

E MAIL: 104170.3043@COMPUSERVE.COM

AMEX MO & COD

Pocket cube is a test generator only

## CABLE TV CONVERTERS

Equipment & Accessories  
Wholesalers Welcome

Call C&D ELECTRONICS

1-800-310-1153 M-F 10a-8p

## SURVEILLANCE

The Latest High Tech  
Professional Electronic Devices

Our latest catalog offers a HUGE selection of surveillance, privacy devices including: hidden video equipment, electronic kits, telephone recording systems, touch tone decoders, scanners, telephone tap detectors, bug detectors, voice disguisers, telephone scramblers, locksmithing tools, and more. Catalog \$5.00.

SPY OUTLET

P.O. Box 337, Buffalo, NY 14226  
(716) 691-3476/(716) 695-8660



## WE HAVE IT ALL! Surveillance

Infinity Transmitters  
FM Wireless Transmitter Kits  
Vehicle Tracking Systems  
Bug Detectors  
Caller I.D.  
Wired Mikes  
Telephone Register with Printer  
Long-play Recorders  
Shotgun Mikes  
Telephone Recording Adapters  
Alcohol Testers  
Telephone Scramblers  
Hidden Video Cameras  
Telephone Tap Detectors  
Drug Testers  
**MUCH, MUCH, MUCH MORE.**

*Our 27th Year!*

Small catalog FREE.  
Larger catalog send \$5.

Mail Order only.

Visa, MasterCard and C.O.D. accepted.

*Inquire for dealers' prices.*

**A.M.C. SALES, INC.**

193 Vaquero Dr. • Boulder, CO 80303  
Mon.-Fri. 8 a.m.-5 p.m. Mtn. Time

**800-926-2488**

(303) 499-5405 • Fax (303) 494-4924

## PHONE LINE MANAGER

**Better than Caller ID!**

This device detects an incoming call. If you subscribe to caller ID, the unit will automatically receive and display the caller's telephone number. If not, the unit will ask the caller to enter their telephone or personal ID number. The device will then display and compare this telephone or personal ID number to a memory bank of numbers that you've installed. If the system finds a match your phone will ring. If the system does NOT find a match, the caller will be directed to leave a message. All messages are digitally recorded. No tape or answering machine necessary. New, in factory cartons, with documentation.

**96U001 \$59.95 each**

## UHF LINEAR AMPLIFIER

890 to 940 MHz. Gain: 17dB. Bias: 18V @ 100mA. Used in cellular communications equipment.

**96V001 \$14.95 each**

**Send \$2.00 for our Latest Catalog!**

\$4.00 Foreign. Refundable on First Order.

## ALLTRONICS

2300-D Zanker Road • San Jose, CA 95131

Voice (408) 943-9773 • Fax (408) 943-9776


World Wide Web: <http://www.alltronics.com>

On-Line Ordering: (408) 943-0622

14400-N-8-1-24 Hrs

Shipping Additional on All Orders..

031196

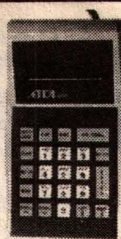

## CABLE TV DESCRAMBLERS



We Carry A Full Line Of Premium Converters And Descramblers Compatible With:

- Scientific Atlanta™ Systems
- Jerrold™ Systems
- Tocom™ Systems
- Zenith™ Systems
- Pioneer™ Systems

**SATISFACTION GUARANTEED  
OR YOUR MONEY BACK!  
BEST PRICES FREE CATALOG**

Please have the MAKE & MODEL # of your full premium service cable box ready when you call!

**ALLSTAR ELECTRONICS**

**800-782-7214**

**HOURS: 9-6 M-F 10-3 Sat EST**

It is not the intent of Allstar Electronics to defraud any pay TV operator. Anyone implying theft of service will be denied assistance. All brand names are registered trademarks of their respective owners & are used for reference only. 110-64 Queens Blvd., #465, Forest Hills, NY 11375. NO NYS SALES!

Many Electronics inc  
RFT,FTG,PIO-Supers,  
Filters,FTG KIT's  
**800-716-3561 9-7est**

## BUGGED??

**SAVEDROPPING** is unbelievably widespread! Electronic Devices with amazing capabilities can be monitoring your telephone and room conversations RIGHT NOW! Are you sure you're safe? **FREE CATALOG** tells you fast! Includes Free Bonus details on fantastic opportunities now open in Counter-Surveillance field. Exciting, immensely interesting and EXTREMELY profitable (up to \$250 hr) full/part-time income. Call Now! **1-800-732-5000**


**Cable Aids Test**  
Orders Only Information  
**1-800-615-9221 407-998-7883**

Test Chips that fully activate Jerrold, Tocom, Zenith, SA, Pioneer and more. Quick-Board installation!  
Prices from \$5 to \$49.95 ea. **MC SPECIALTIES**  
1 Year Warranty!


No FL Sales. Not for use in cable co. owned equip. For test or repair only.
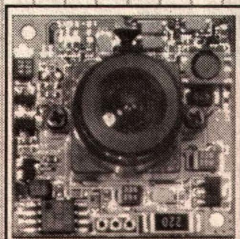
## MICRO SIZE CCD VIDEO CAMERAS

- Wireless Models Available.
- Color Board Cameras
- "V" / "C" SVHS signal.
- Models to 600 Line Res.
- 9V Battery Operation.
- Monitor in Darkness with IR Option.
- Can be plugged into any VCR or Monitor.
- Stealth/Covert Cameras.
- Low LUX/Low Noise.
- Low Power Consumption.
- Standard NTSC Output.
- Options: Lenses/Wireless/Fiber Optics & More.




**MB-750U (1.25" sq.)**

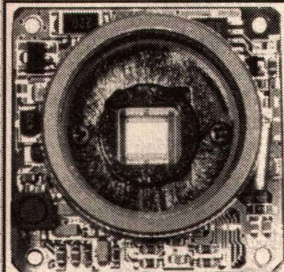

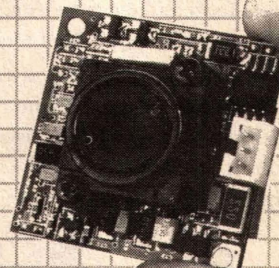**MB-750UX (1.5" sq.)**

Visit Polaris Ind. Web Site at:  
<http://www.polarisusa.com>



**MB-750P (1.25" sq.)**

**Polaris Industries**  
**1-800-752-3571**

New Literature  
Available for  
All Models

Same Day  
Shipping  
from Stock!



141 West Wieuca Road • Suite 300 • Atlanta GA • 30342-3251 • Tech Info: 404-252-3340 • FAX 404-252-8929



## New! Surveillance, & PIC microcontroller, project kits.

Most kits use surface mount technology. Among the kits are an ultra small wireless FM mic, and our new phone transmitter SLeach™. All kits include our exclusive surface mount soldering guide. Many kits under \$20, call!

**Pager Decoder Interface for your PC,**  
Only \$19.<sup>95</sup> + S&H  
includes shareware software.

We carry the TDA2005  
20W Power Amplifier IC.  
Great for auto alarm projects!

**Order 1-800-417-6689**

Mon. - Fri. 9AM-5PM ET.  
Visa, MC, Money Orders  
IEC, P O Box 52347, Knoxville, TN  
37950-2347

Sorry, no refund for used kits.  
Do not use these devices without authorization  
from your local officials.

Prices subject to change. No TN sales  
This ad quotes cash discount pricing.  
Returns are subject to a restocking fee.

©1996 IEC

# TRIDENT



**\$699<sup>00</sup>**  
SV150

**1000KHz to 1.00GHz  
Spectrum Analyzer System  
Up to 500MHz Span. Two bands.**

All the advantages of a Spectrum Analyzer at a very affordable price. Great for interference and signal hunting. RS232 connect for logging signals to disk. Real time display sweep outputs on any X,Y scope. Variable span and sweep rate. Marker function and selectable bandwidth. Demods in AM/NFM/WFM plus BFO for CW/SSB modes. For instant information use our fax back service at 317 849 8683, #405. Or, email Scanns@www.acecomms.com. http://www.acecomms.com/Scanns.



**Order Line: 1 888 445 7717**

10707 E. 106th, Fishers, IN 46038 International: 317 842 7115

Fax 317 849 8794 Email: Scanns@www.acecomms.com

CIRCLE 289 ON FREE INFORMATION CARD

## CABLE CONVERTERS/DESCRAMBLERS

★★★★ **SUPER BUYS** ★★★★★  
★ **FULLY REFURBISHED UNITS** ★

TOCOM™ ★ JERROLD™ ★ SCIENTIFIC ATLANTA™ ★ PIONEER™  
"WE SERVICE MOST PRIVATELY OWNED CABLE CONVERTERS"

Phone **(219) 935-4128**



**SORRY, NO INDIANA SALES**

## NATIONAL CABLE BROKERS


1801 W. JEFFERSON ST., PLYMOUTH, IN 46563

**OUR POLICY:** All products carry a two year warranty. Warranty covers parts and labor and return shipping.  
**WARNING:** Theft of cable services is a crime. National Cable will not knowingly defraud any pay TV operator and we will not assist any individual or company in doing the same.

# LASERS

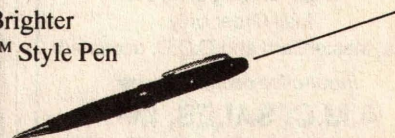**Pen & Pointer in One**

- Four Times Brighter
- Mont Blanc™ Style Pen



This laser pointer functions as a fine writing instrument and laser pointer all in one. The 650nm laser appears four times brighter than standard laser pointers. Output power: 3.5 to 4.5 milliwatts. Includes batteries and gift box. One year warranty.

Cat. #: LPEN

**\$57.00**

## FREE CATALOG

- Helium-Neon
- Argon
- Semiconductor
- Ruby
- Scanners
- Lightshow Equipment

30 Day Satisfaction Guarantee.



**Midwest Laser Products**

P.O. Box 262, Frankfort, IL 60423

Phone: (815) 464-0085 FAX: (815) 464-0767

Please include \$7.50 S&H within US. IL res. add 7.75% sales tax.

Email: mlp@nlx.com  
VISA / MC Accepted

## CONVERTERS & DESCRAMBLERS



**TARGET ELECTRONICS**

(800) 995-1749

**We sell Test Chips!**  
MC, VISA, AE, C.O.D

**DEALERS WELCOME!**

## The Electronic Experimenter's Journal

It's part catalog, part magazine and part data book with kits, parts, plans, articles, and application notes.


Call for your **FREE** copy today

Decco Electronics  
4025 Edwards Rd.  
Cincinnati, OH 45209

**1 800 423-4499**



One tree can make  
3,000,000 matches.

 

One match can burn  
3,000,000 trees.



A Public Service of This Magazine  
& The Advertising Council







## Electronic Training Videos From UCANDO

Now you can learn from the same training videos that are being used by technical schools, the Army, Navy, Air Force, Coast Guard, CET's and industries all across the United States and around the world. Advancing your troubleshooting skills has never been easier, thanks to UCANDO's extraordinary video training library. These unique training videos will teach you more in less time as you watch theory come to life. Each video is approximately one hour long and comes complete with a student workbook.



### Basic Series

| MODEL | DESCRIPTION                                                                                         | REGULAR | SALE  |
|-------|-----------------------------------------------------------------------------------------------------|---------|-------|
| VT201 | Direct Current: Series circuits, Parallel Circuits, Ohm's law, how to use the DMM. 55 Minutes       | 44.95   | 39.95 |
| VT202 | Alternating Current: The sine wave, coils, capacitors, transformers. 62 minutes                     | 44.95   | 39.95 |
| VT203 | Semiconductors: Semiconductor theory, common diodes, transistors, switching devices. 57 Minutes     | 44.95   | 39.95 |
| VT204 | Power Supplies: Rectifier circuits, filter circuits, regular circuits, troubleshooting. 56 Minutes. | 44.95   | 39.95 |
| VT205 | Amplifier: Amplifier basics, class A, class B, class C, operational amplifiers. 57 Minutes          | 44.95   | 39.95 |
| VT206 | Oscillators: LC and RC oscillators, crystal oscillators, crystal ovens. 56 Minutes                  | 44.95   | 39.95 |

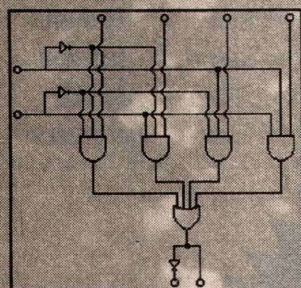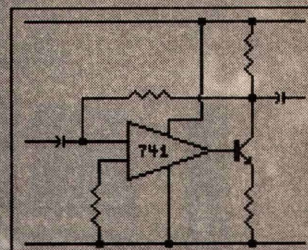


### Digital Series

| MODEL | DESCRIPTION                                                                                           | REGULAR | SALE  |
|-------|-------------------------------------------------------------------------------------------------------|---------|-------|
| VT301 | Digital 1: Digital basics, basic gates, binary notation, binary math, decimal notation. 54 Minutes    | 44.95   | 39.95 |
| VT302 | Digital 2: Octal notation, hexadecimal notation, flip-flops, counter circuits. 55 Minutes             | 44.95   | 39.95 |
| VT303 | Digital 3: Complement numbers, multiplexers, registers, decoder drivers, displays. 56 Minutes         | 44.95   | 39.95 |
| VT304 | Digital 4: R-2R DAC circuits, binary weighted no.s, slope circuits, S/A & flash circuits. 57 Minutes. | 44.95   | 39.95 |
| VT305 | Digital 5: Memory devices. ROM, PROM, EPROM, EEPROM, SRAM, DRAM, MBM. 56 Minutes                      | 44.95   | 39.95 |
| VT306 | Digital 6: The central processing unit, input devices, output devices. 56 Minutes                     | 44.95   | 39.95 |

### Other Popular Videos

| MODEL | DESCRIPTION                                                                                                                 | REGULAR | SALE  |
|-------|-----------------------------------------------------------------------------------------------------------------------------|---------|-------|
| VT401 | AM Radio: Major stages of AM, signal conversion, signal detection, audio reproduction, AM stereo. 61 Minutes                | 44.95   | 39.95 |
| VT402 | FM Radio Part 1: Bandwidths, RF amplifier, mixer-oscillator, IF amplifier, limiter FM detector. 58 Minutes                  | 44.95   | 39.95 |
| VT403 | FM Radio Part 2: Frequency doubler, stereo demultiplexer, audio amp stages, digital data encoding/decoding. 58 Minutes      | 44.95   | 39.95 |
| VT404 | TV Part 1, Intro to TV: Gain an overview of the television system and how the stages work together. 56 Minutes              | 44.95   | 39.95 |
| VT405 | TV Part 2, The Front End: UHF-VHF tuning stages, automatic fine tuning, remote control. 58 Minutes                          | 44.95   | 39.95 |
| VT406 | TV Part 3, Audio: The sound strip, stereo TV, secondary audio programming, professional channels. 57 Minutes                | 44.95   | 39.95 |
| VT501 | Understanding Fiber Optics: Basic fundamentals, cable design, connectors, couplers, splicing. 58 Minutes                    | 44.95   | 39.95 |
| VT502 | Laser Technology: Laser theory, types of lasers, applications, safety precautions. 57 Minutes                               | 44.95   | 39.95 |
| VT102 | Intro to VCR Repair: This video is designed for the serious technician. (workbook not available). 84 Minutes                | 44.95   | 39.95 |
| VT103 | Learn How To Clean Your Own VCR: This video is not technical, but will save you money. (workbook not available). 32 Minutes | 29.95   | 25.95 |

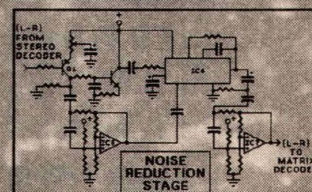

### SAVE EVEN MORE!

Buy any six videos for only \$216.00. Order your UCANDO videos today!



Call for your free 84 page test instrument catalog today!!!  
8931 Brookville Road \* Silver Spring, Maryland \* 20910

\* Phone 800-638-2020 \* Fax 800-545-0058 \* email SMPRODINTL@AOL.com



# Fix It Yourself!



**It's easy, fast, and rewarding to repair it yourself with the Electronics Repair Manual!**

- Hands-on, detailed, troubleshooting instructions
- "How to" primer for test equipment: oscilloscopes, frequency counters, video analyzers, etc.
- Schematic diagrams
- Trouble analysis flowcharts
- Preventive maintenance techniques
- Safety precaution checklists
- Comprehensive replacement parts list
- Directory of manufacturers

## Leading Manufacturers Represented...

- |           |             |         |             |
|-----------|-------------|---------|-------------|
| • Emerson | • Nintendo  | • RCA   | • Technics  |
| • Hitachi | • Panasonic | • Sanyo | • Toshiba   |
| • IBM     | • Pioneer   | • Sharp | • Zenith    |
| • NEC     | • Quasar    | • Sony  | and others! |

## ✓ Dozens of Fix-It-Yourself Projects for...

- |                                             |                                          |
|---------------------------------------------|------------------------------------------|
| <input type="checkbox"/> CD Players         | <input type="checkbox"/> Amplifiers      |
| <input type="checkbox"/> VCRs               | <input type="checkbox"/> Car Radios      |
| <input type="checkbox"/> Televisions        | <input type="checkbox"/> Home Appliances |
| <input type="checkbox"/> Camcorders         | <input type="checkbox"/> AM/FM Tuners    |
| <input type="checkbox"/> Computer Equipment | <input type="checkbox"/> Thermostats     |
| <input type="checkbox"/> Fax Machines       | <b>...and more!</b>                      |
| <input type="checkbox"/> Telephones         |                                          |

**30-Day Free Trial!**




## Keep Your Skills Up-to-Date!

The Electronics Repair Manual and the Modern Manual Electronics Manual will be a valuable reference for years to come. Supplements, each containing over 125 pages, add new repair projects, valuable insights into new technologies, diagnostic and repair techniques, electronics projects, and more schematic diagrams into your manual. Just \$35 each for Electronics Repair and \$49.50 each for Modern Electronics plus shipping and handling. Supplements are sent 4-5 times a year and are fully guaranteed. Return any supplements you don't want within 30-days and owe nothing. Cancel anytime.

CIRCLE 311 ON FREE INFORMATION CARD



# Build It Yourself!

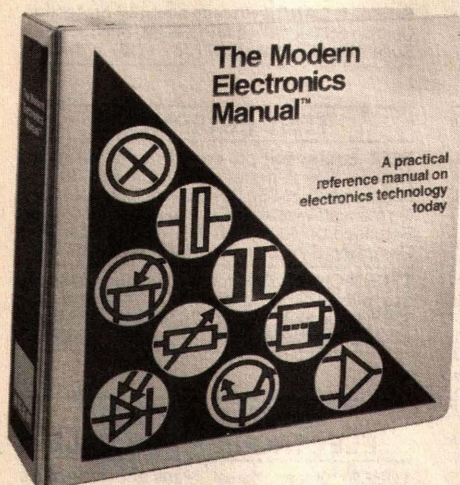

**Expand your  
knowledge while  
sharpening your  
skills!**

- **A lifetime of exciting electronics projects**
- **Complete project plans**
- **Step-by-step instructions, flow charts, schematics, and photos**
- **Troubleshoot and repair**
- **Make your own printed circuit board (acetate board layouts provided)**
- **Component suppliers' addresses**
- **Handy 3-ring workbench binder**

## Electronics Fundamentals...

- Electronic Components and their Characteristics
  - The Op-Amp Explained
  - General Diagnostic Techniques
- ...plus much more!**

## 30 Day Free Trial Order Form

- |                                                                     |       |
|---------------------------------------------------------------------|-------|
| <input type="checkbox"/> Yes! Please rush me my copy of:            |       |
| <input type="checkbox"/> Electronics Repair Manual for only \$59.95 | 32856 |
| <input type="checkbox"/> Modern Electronics Manual for only \$59.95 | 32857 |
| <input type="checkbox"/> Both Manuals for just \$99.95.             | 32858 |

*I may take \$10 off the total price when I enclose my check or credit card authorization by 12/31/96. Plus, I get free shipping and handling! I understand that if I am not satisfied, I may return the book(s) within 30 days for a full 100% refund of the purchase price.*

- ☐ My payment is enclosed. I've deducted \$10 if I am ordering by 12/31/96.

- ☐  ☐  No.           Exp.

- ☐
- Check Enclosed.**

- ☐
- Optional express delivery (available in U.S. only).

Enclose an additional \$10 and we'll guarantee delivery within 5 business days from receipt of your order (prepaid orders only; no P.O. Boxes).

- ☐ Bill me later including \$6.50 shipping and handling per book, subject to credit approval. *Signature and phone number required to process your order. P.O. Box addresses must be prepaid.*

**Signature (required)**

Daytime phone ( )

Mr./Mrs./Ms.

Company \_\_\_\_\_

Street Address

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Shipping and handling to Canada, \$10 (U.S. Currency); Overseas, \$15 (foreign orders must be prepaid); CT residents add 6% sales tax. Supplements will be sent 4-5 times a year on a fully guaranteed, 30-day trial basis. They may be cancelled at any time.

MAIL TO: WEKA Publishing, Inc.

1077 Bridgeport Avenue, P.O. Box 886, Shelton, CT 06484

Call 1-800-222-WEKA or fax to 1-800-256-5915 for fast service!

## Dozens of Exciting Projects such as...

- ☐ Simple Logic Probe
  - ☐ Multi-Purpose Gas Detector
  - ☐ Digital Combination Lock
  - ☐ Radiation Detector
  - ☐ Portable Frequency Counter
- ...and many other projects!



MONDO • TRONICS

# ROBOT STORE

\* KITS \*

Your

\* BOOKS \*

Mailorder

\* PARTS \*

Source

\* VIDEOS \*

For

\* MODELS \*

Robots!

\* MORE! \*

(REQUEST OUR FREE CATALOG)

www.robotstore.com

800-374-5764

Or write to us:

524 San Anselmo Ave #107-120  
San Anselmo CA 94960

Phone 415-455-9330

Fax 415-455-9333

Email info@mondo.com

# CLASSIFIED

## SATELLITE EQUIPMENT

**FREE catalog** of big dish systems, upgrades, and accessories. Warranties, satisfaction guaranteed. **SKYVISION**, 800-334-6455, 1012 Frontier Drive, Fergus Falls, MN 56537. www.skyvision.com. See full page ad in the Shopper Section.

**THE best television comes on a DISH™.** Digital 18" satellite systems, mobile satellite systems, home entertainment accessories, and more. **SKYVISION** 800-500-9264; 1018 Frontier Drive, Fergus Falls, MN 56537. www.skyvision.com. See our full page ad in the Shopper Section.

**VIDEOCYPHER II** descrambling manual. Schematics, video and audio. Explains DES, EPROM, CloneMaster, Pay-per-view (HBO, Cinemax, Showtime, Adult, etc.) \$16.95, \$2.00 postage. Schematics for Videocypher II Plus, \$20.00. Schematics for Videocypher II 032, \$15.00. Software to copy and alter EPROM codes, \$25.00. VCII Plus EPROM, binary and source code, \$30.00. **CABLETRONICS**, Box 30502R, Bethesda, MD 20824.

**OBTAINING sound** for your VCII and VCII Plus is easy. No codes needed. **Details 1 (800) 211-5635.**

**DSS reverse engineering package.** Software, schematics, chip programmer plans, reviews & more! \$49.95. **VISA/MC. TELECODE**, 1 (520) 726-2833.

**SOUND** for Videocypher-11 and plus without codes. Free details. **SASE. NASSIRIAN**, Box 382-E, Rio Linda, CA 95673.

## PLANS-KITS-SCHEMATICS

**CRYSTAL set Handbook** — Visit antiquity by building the radios your grandfather built. Assemble a "Quaker Oats" rig, wind coils that work and make it look like the 1920s! Only \$10.95 plus \$4.00 for shipping and handling. **CLAGGK INC.**, PO Box 4099, Farmingdale, NY 11735. US funds only! USA and Canada — no foreign orders.

**FREE Catalog.** 100 Leading-Edge kits. K1, PIC. Full instructions, source code. 1 (800) 875-3214. **SCIENCE FIRST**, 95 Botsford Place, Buffalo, NY 14216.

**BUILD** your own DC motor control. 1 to 480 amps w/surplus parts. **BEYOND ELECTRONICS**, 1 (800) 747-2861. Free catalog.

**AWESOME kits:** Voice changer, levitator, laser, gas sensor and more! Catalog \$1.00. **LNS TECHNOLOGIES**, 20993 Foothill Blvd., Suite 307R, Hayward, CA 94541.

**ELECTRONIC Project Kits.** www.qkits.com 1-888-GO-4-KITS. 292 Queen St., Kingston, ON, K7K 1B8. **QUALITY KITS.**

**HACKERS Catalog.** Hard-to-find kits and assembled equipment (Red box, spy, cable, etc.) Low prices. \$1.00. **SMITH-04**, Box 371, Cedar Grove, NJ 07009.

## EDUCATION & INSTRUCTION

**ELECTRONIC engineering.** 8 volumes complete. \$109.95. No prior knowledge required. Free brochure. **BANNER TECHNICAL BOOKS**, 1203 Grant Avenue, Rockford, IL 61103.

**LEARN VCR repair.** Great profits. Home study. **P.C.D.I.**, Atlanta, Georgia. Free literature. (800) 362-7070 Dept. VRM342.

**LEARN PC repair-troubleshooting, servicing.** Home study. Free literature. **P.C.D.I.**, Atlanta, Georgia. (800) 362-7070 Dept. JJM342.

**BASIC mechanics for electronic technicians.** Send S.A.S.E. to **RM COMPANY**, PO Box 2124, Pomona, CA 91768.

## SECURITY

**SURVEILLANCE** Privacy security protection. Catalog \$5.00. **SPY EMPORIUM**, 6065 Hillcroft, Suite 413, Houston, TX 77081. (713) 774-1000.

## TEST EQUIPMENT

**TEST Equipment** pre-owned now at affordable prices. Signal generators from \$50.00, oscilloscopes from \$50.00. Other equipment including manuals available. Send \$2.00 US for catalog. Refunded on first order. **J.B. Electronics**, 3446 Dempster, Skokie, IL 60076. (847) 982-1973.

**TECHNICIANS:** Electronic component tester for use with oscilloscope. Satisfaction guaranteed. \$29.95 plus S&H. Info: **ELECTROHM**, 529 Brentwood, Lawrence, KS, 66049. Fax: (913) 832-2481.

## MISCELLANEOUS ELECTRONICS FOR SALE

**TUBES:** "oldest", "latest". Parts and schematics. **SASE** for lists. **STEINMETZ**, 7519 Maplewood Ave., EN, Hammond, IN 46324.

**FIBER-Optic Projects** — Swing into the new technology by assembling tried and true projects recently published. "Practical Fiber-Optic Projects" - BP374 is only \$9.95. (price includes shipping) **ELECTRONIC TECHNOLOGY TODAY INC.**, PO Box 240, Massapequa Park, NY 11762-0240.

**GREEN Thumb Alert** — Electronics enters the Garden! New exciting book points out how gardeners can build simple gadgets to promote success where the elements work against you. Some of the projects are: over/under temperature monitoring, dusk/dawn switching, automatic plant watering, warming cables, etc. "Electronic Projects for the Garden" only \$9.95 (price includes shipping) **ELECTRONIC TECHNOLOGY TODAY INC.**, PO Box 240 Massapequa Park, NY 11762-0240.

**CBers** Order new CB Trick III CB book. Shows CB tune ups, amplifiers, and expert CB info! Send \$19.95 to **MEDICINE MAN CB**, PO Box 37, Clarksville, AR 72830.

**RESISTORS** 20 for \$1.00. LEDs 4 for \$1.00. Catalog \$1.00. **ZIPFAST**, Box 12238, Lexington, KY 40581-2238.

**POOR** reception on your A.M. radio? Our Signal Booster will help. Guaranteed! Send \$2.00 for details (refundable with order). **FALA ELECTRONICS**, PO Box 1376, Dept. 4, Milwaukee, WI 53201.

**POWERIZE yourself!** New "easy use", low cost, personal computer peripheral for non-computer experts. Connects serial port. Measure/log physical conditions. Control machines, mechanical-electrical devices, processes. Can send data/control/alerts via modem. Time interval controller, too. Convenience, productivity, profit! Includes detailed training manual; tells how! lots of free software! Information: **CYBER BOX**, Box 53743, Lubbock, TX 79453, 1 (800) 299-6971.

**CONVERTER-** descramblers: Examples, Zenith Ztac \$225.00, Scientific Atlanta 85XX \$185.00, 8580 compatible \$215.00, 8600 \$335.00, DPV-7212 compatible \$215.00, Jerold 400 \$115.00. All Pioneer test generator \$150.00. Most makes in stock, COD ok. **MOUNT HOOD ELECTRONICS**, (503) 543-7239.

# BUY BONDS



# CLASSIFIED

## INVENTORS

**REGISTERED Patent Attorney.** Free handbook/advice. Patent/trademark protection for your ideas. 1 (800) 876-6670. J.P. HALVONIK.

## CABLE TV TURN-ON CHIPS

**SUPER Cable TV "Test Chips".** Provides full service activation. Excellent; Instructions & illustrations. **Jerrold Starcom:** DP(V)5..DP(V)7..DPBB7..CFT-2000..CFT-2200 Series. **Pioneer:** BA-5000 thru BA-6700. **Pioneer: Custom Programmer** (Clears E2 & rewrites new I.D. codes). **Scientific Atlanta:** 8500 thru 8600. **Tocom:** 5503-VIP. 5507. **Zenith:** ST-1000 thru ST-5612. **Call Now!! MASTER COMPONENTS.** 1 (800) 233-0570.

## THE CABLE TV SUPER CUBE

**THE Mobilizer!!** External "Test Cube" activator. Easy plug-n-play operation. Excellent instructions & illustrations. Supports all DP(V)7..DPBB7..CFT-2000..CFT-2200 series converters. **New enhanced performance features:** Locked box revitalizer! Restore command! Plus much more! **Dealers wanted! Call Now!! MASTER COMPONENTS** 1 (800) 233-0570.

## CABLE TV

**ATTN, cable box owners.** Order your ID signal and bullet stopper before it's too late. Send \$23.00 to **R.R. ENTERPRISE**, Box 3532, Easton, PA 18043.

**CABLE Descrambling New secret manual.** Build your own descramblers for cable and subscription TV. Instructions, schematics for **SSAVI**, Gated Sync, Sinewave, (HBO, Cinemax, Showtime, UHF, Adult) \$12.95, \$2 postage. **CABLE-TRONICS**, Box 30502R, Bethesda, MD 20824.

**CABLE TV Equipment & Accessories** Wholesalers welcome! 30 day moneyback guarantee! Free catalog! **PERFORMANCE ELECTRONICS INC.**, 1 (800) 815-1512.

**CABLE TV Test Chips** for Jerrold, Tocom, Pioneer, Scientific Atlanta, etc... **Quick installation!** New Multi-Mode modules available. Prices from \$5.00 each. 1 (800) 786-9025.

**CABLE-safe.** Guarantee cable privacy. The one-way valve for your cable TV signal. Cable signals come in, but they don't go out! \$29.95 + \$3.00 S&H. **VISA/MC/AMEX. ELECTROMAN**, Box 24474, New Orleans, LA 70184. (504) 482-3017.

**"CABLE Unscrambled.** Everything you want to know about cable, but are afraid to ask. \$10.00. **"Descrambler Schematics Revealed."** A powerful guide to descrambling schemes. \$10.00. **"Baseband Video Explained."** Discover what a Baseband Signal is and how it's constructed. \$10.00. Special offer. Get all three for only \$25.00! **VISA/MC/AMEX. ELECTROMAN**, Box 24474, New Orleans, LA 70184. (504) 482-3017.

**UNIVERSAL Descrambler.** Unscramble signals using your VCR as the tuner. Works with virtually any system, this is the only one you need. Declare cable box independence! Fully assembled. \$129.95 + \$5.00 S&H. **VISA/MC/AMEX. ELECTROMAN**, Box 24474, New Orleans, LA 70184. (504) 482-3017.

**"BULLET Buster".** Protect your cable box against the infamous cable "bullet". The "Bullet" Buster acts as an electronic shield. Installs in-line in seconds. Don't wait until it's too late! \$19.95 + \$3.00 S&H. **VISA/MC/AMEX. ELECTROMAN**, Box 24474, New Orleans, LA 70184. (504) 482-3017.

**CABLE Descrambler!** Anyone can build in seven steps with **Radio Shack** parts. **Plans/Kit** from \$5.00 plus free bonus!! 1 (800) 818-9103.

**DESCRAMBLER Cable** using simple circuit. E-Z to follow instructions \$10.00. Complete kit with free "Bullet Stopper". \$20.00. 1 (800) 522-8053.

**CABLE Bullet "Terminator/I.D. Blocker."** Electronically shields yourself and your box. Factory direct. **Lifetime Guarantee \$14.95.** 1 (800) 820-9024.

**CABLE TV notch filters.** Request our free brochure by calling our voicemail at 1 (800) 433-6319 or write to **STAR CIRCUITS** PO Box 94917, Las Vegas, NV 89193. Visit our web site at <http://our-world.compuserve.com/homepages/starcircuits>

**CABLE test modules/cubes.** Pioneers, S/A, Tocom, Jerrold. Latest technology. Quantity discounts. Voice/Fax (718) 426-8515.

**CABLE TV testers/descramblers.** All makes/models. Best prices guaranteed! 1 Yr. warr. <http://www.concentric.net/rmvideo1> or call (602) 581-1496.

**CABLE TV, descramblers, converters.** Quantity discounts. 30 day free trial. Competitive prices. Call now! 1 (800) 322-0921 **REGAL SALES, INC.**

**DESCRAMBLE** cable with simple circuit added to Radio Shack RF modulator and using VCR as tuner. Instructions \$10.00. **TELCOM**, Box 832 E11, Brusly, LA 70719.

**25+ Master test chip files.** Jerrold, Scientific Atlanta, Tocom, Pioneer, Zenith. Software & book. \$79.95. **TELECODE** 1 (520) 726-2833.

**CARL'S Electronics-** The Cable Hacker's Guide, stopping power meters, and electronic plans now available on-line. <http://www.ultra-net.com/~carlton>. Call for a free catalog (508) 534-3228.

**WIRELESS** cubes for any box \$150.00. Instruction, plans, parts list - \$7.00. Call (718) 545-5146. 1 Year warranty.

**JERROLD - RFT's, FTG's.** Lowest prices. Minimum order 5. 4pm to 8pm Eastern 1 (607) 734-2262.

**R.F.T.'s \$58.00!** Diagnostic cubes, F.T.G.'s with filter \$58.00! (JER.-PIO.-S.A.). 1 (800) 688-0097. Testers for educational only.

## COMPUTER SOFTWARE

**JOYSTICK-To-Mouse.** Now run Windows with any joystick! "Fly" the internet! 3.x/95 compatible. Only \$29.95! "www.IMG Presents.com" 1 (818) 346-3581, 1 (800) 889-0987.

## COMPONENTS

**RARE blue LEDs** 12 for \$18.00, includes \$4.00 S&H. CA residents add \$1.44 tax. Hurry, quantities limited. **DIGITON**, 18620 Hatteras Street, #254, Tarzana, CA 91356-1827.

**TRANSFORMERS - TOROIDAL:** 37&52VA, 120V- 30VCT & 7.5V RMS. Simple, compact and cost effective solution to supplying +5V and ±15V for digital/analog projects. Dealers welcome. **OMEGATRON**, (418) 831-1749.


## EXERCISE.

**American Heart Association**



## VIRTUAL REALITY

# VR InfoSource

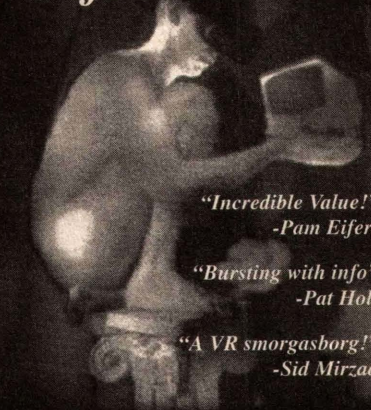

"Incredible Value!"  
-Pam Eifert

"Bursting with info!"  
-Pat Holt

"A VR smorgasborg!"  
-Sid Mirzad

## FIVE GREAT PUBLICATIONS! ONE LOW PRICE!

**Virtual Reality an Exploding Technology** is an exclusive report on the explosion of VR in medical, amusement, consumer and other arenas. Plus news blurbs on market entry by heavyweights & Fortune 500's.

**VR Resource Directory** is your guide to hundreds of companies involved in VR products, books, software, professional trade organizations, clubs, more!

**VRML Primer** explains VRML, building virtual worlds on the internet, great VR worlds to visit on the internet. ABCs of setting up your own internet home page, more!

**Desktop VR** contains a complete primer on using VR on your PC, plus, where to get low cost HMDs (head mounted displays) & other equipment, the famous Mattel Powerglove hack (converting a \$69 Powerglove for use with VR), Powerglove sources, listing of virtual world building software, comprehensive listing of HMD compatibility with popular games & software, more!

**VR InfoMania** contains great listings of internet websites devoted to VR, VR books, VR magazine articles & research papers, internet FTP download sites & VR-related newsgroups, article listings from back issues of VR magazines, where to go to experience real VR, reviews of popular VR books, glossary of VR terms, great VR applications, the future of virtual sex, more!

## FREE BONUS!

The first 1,000 orders will receive the publication **VR Cartoons** featuring dozens of funny cartoons about VR! Yours absolutely FREE! Limited printing, don't miss out! Order today!

**FIVE PUBLICATION SET!**  
Plus FREE BONUS: VR Cartoons

\$99 Value! **ONLY \$49.95\*\***

Special Introductory Price!  
**ONLY \$39.95\*\***  
Limited time!

Plus \$3.00 S&H  
Calif. residents  
add sales tax

2-3 Day Delivery \$7.95  
Fedex Overnight Air \$14.95

30-Day 100% Satisfaction  
Money-Back Guarantee!

24 HOUR  
TOLL FREE  
ORDER LINE

**1-800-951-7100**  
FAX ORDERS 619-485-8968

Send Check or Money Order to: Virtual Reality Publishing  
16486 Bernardo Center Drive, Suite 378, San Diego CA 92128

\*Same day shipping on orders received before 4pm EST. Personal check orders held 2 weeks for check to clear. No COD orders. Int'l orders must be paid in US funds. Call for Int'l S&H charges. We participate in the BBB Care Program through the Better Business Bureau of San Diego.

**ORDER TODAY... HAVE IT TOMORROW!\***

November 1996, Electronics Now



## ADVERTISING INDEX

Electronics Now does not assume any responsibility for errors that may appear in the index below.

| Free Information Number                 | Page | Free Information Number                | Page  |
|-----------------------------------------|------|----------------------------------------|-------|
| — ABC Electronics .....                 | 130  | — Lindsay Publications .....           | 86    |
| — AES .....                             | 94   | — M <sup>2</sup> L Electronics .....   | 86    |
| 289 Ace Communications .....            | 130  | 326 Mark V Electronics .....           | 108   |
| — Active Micro .....                    | 119  | 327 MCM Electronics .....              | 87    |
| — Aegis Research, Canada .....          | 104  | 251 Mendelson Electronics Surplus ..   | 119   |
| 213 Alfa Electronics .....              | 88   | — Mental Automation .....              | 96    |
| 214 All Electronics .....               | 115  | — Meredith Instruments .....           | 126   |
| — Allison Technology .....              | 84   | — Merrimack Valley Systems .....       | 94    |
| — Allstar Electronics .....             | 129  | 325 Micro 2000 .....                   | 93    |
| — Alltronics .....                      | 129  | 128 MicroCode Engineering .....        | 17    |
| — AlphaLab .....                        | 90   | — Micro Engineering Labs .....         | 92    |
| — Amaze Electronics .....               | 127  | — Midwest Laser Products .....         | 130   |
| — AMC Sales .....                       | 129  | — Milestone Products .....             | 85    |
| 315 American Eagle Publications .....   | 106  | — Modern Electronics .....             | 86    |
| — Andromeda .....                       | 96   | — Mondo-tronics Inc. ....              | 134   |
| 77 B&K Precision .....                  | 27   | 324 Mouser Electronics .....           | 127   |
| 334 Basic Electrical Supply .....       | 103  | — MWK Industries .....                 | 104   |
| — Baylin Publications .....             | 110  | — National Cable Brokers .....         | 130   |
| 335 Bel-Merit .....                     | 109  | 257 Needham Electronics .....          | 108   |
| — BHS Electronics .....                 | 114  | — NRI Schools .....                    | 9     |
| 336 Brigar Electronics .....            | 102  | 322 OWI .....                          | 126   |
| — Bsoft Software, Inc. ....             | 94   | 262 Parts Express Inc. ....            | 83    |
| 333 Butterworth Heinemann .....         | 121  | 310 Phillips Tech Electronics .....    | 127   |
| 337 C&S Sales, Inc. ....                | 122  | — Polaris Industries .....             | 129   |
| — CGC .....                             | 126  | 321 Prairie Digital .....              | 124   |
| 332 Capital Electronics .....           | 124  | 264 Print (Pace) .....                 | 131   |
| 312 Circuit Specialists .....           | 100  | — R-4 Systems Inc. ....                | 114   |
| — Cleveland Institute of Electronics .. | 21   | 78 Radio Shack .....                   | 5     |
| — Command Productions .....             | 98   | 266 Ramsey Electronics .....           | 125   |
| 331 Computer Monitor Maintenance ..     | 86   | — RC Distributing Co. ....             | 127   |
| 226 Consumertronics .....               | 84   | — RF Parts .....                       | 85    |
| 320 Conway Engineering Inc. ....        | 97   | — Sil Walker .....                     | 112   |
| 58 Cook's Institute of Elec. Eng. ....  | 4    | — Sirius Micro Systems .....           | 96    |
| 228 Cool Amp Conducto Lube .....        | 98   | 270 Skyvision Inc. ....                | 15    |
| 305 CTG .....                           | 110  | — Street Smart Security .....          | 103   |
| — Cybermation .....                     | 110  | 319 Sun Equipment .....                | 13    |
| 234 Dalbani Electronics .....           | 105  | — Tab Books .....                      | 1, 46 |
| 235 Danbar Sales .....                  | 99   | — TC Instruments .....                 | 130   |
| — Emac Inc. ....                        | 90   | 273 Tech Systems .....                 | 80    |
| — Electronic Technology Today .....     | 73   | — Technical Serv. & Solutions .....    | 110   |
| — Fair Radio .....                      | 119  | 92 Tektronix, Inc. ....                | CV3   |
| 121 Fluke Corp. ....                    | CV2  | 290 Telulex .....                      | 103   |
| 307 Foley-Belsaw Co. ....               | 95   | — Test Equipment Sales .....           | 81    |
| 318 Fotronic .....                      | 114  | 275 Timeline .....                     | 82    |
| 330 Gateway Products .....              | 106  | 317 Toronto Surplus & Scientific ..... | 116   |
| — General Device Instruments .....      | 96   | — U.S. Cyberlab .....                  | 91    |
| — Geo-Ban Engineering .....             | 106  | — Virtual Reality Publishing .....     | 135   |
| — Grantham Col. of Engineering .....    | 73   | — Vision & Motion Surplus .....        | 112   |
| 309 Graymark International .....        | 118  | 316 Visitec Inc. ....                  | 104   |
| — Home Automation .....                 | 119  | — Visual Communications .....          | 45    |
| 323 Howard Electronics .....            | 107  | 98 Wavetek Corp. ....                  | 7     |
| — IEC .....                             | 130  | — Weeder Technologies .....            | 81    |
| — Information Unlimited .....           | 113  | 311 Weka Publishing .....              | 132   |
| 126 Interactive Image Technologies ..   | CV4  | 314 White Star Electronics .....       | 85    |
| — Intronics, Inc. ....                  | 92   | — Windjammer Barefoot Cruises .....    | 4     |
| 329 IVEX Design International .....     | 91   | — World College (Div. of C.I.E.) ..... | 31    |
| — J&M Microtek, Inc. ....               | 92   | — WPT Publications .....               | 124   |
| 328 Kimtronics .....                    | 111  | 281 Xandi Electronics .....            | 90    |

## ADVERTISING SALES OFFICES

**Gernsback Publications, Inc.**  
500 Bi-County Blvd.  
Farmingdale, NY 11735-3931  
1-(516) 293-3000  
Fax 1-(516) 293-3115

**Larry Steckler**  
publisher (ext. 201)

**Christina Estrada**  
assistant to the publisher (ext. 209)

**Arline Fishman**  
advertising director (ext. 206)

**Michele Torrillo**  
advertising assistant (ext. 211)

**Adria Coren**  
credit manager (ext. 208)

### For Advertising ONLY

#### EAST/SOUTHEAST

**Stanley Levitan**  
Eastern Advertising  
1 Overlook Ave.  
Great Neck, NY 11021-3750  
1-516-487-9357  
Fax 1-516-487-8402

#### MIDWEST/Texas/Arkansas/Okla.

**Ralph Bergen**  
Midwest Advertising  
One Northfield Plaza, Suite 300  
Northfield, IL 60093-1214  
1-847-559-0555  
Fax 1-847-559-0562  
bergenrj@aol.com

#### PACIFIC COAST

**Janice Woods**  
Pacific Advertising  
Hutch Looney & Associates, Inc.  
6310 San Vicente Blvd.  
Suite 360  
Los Angeles, CA 90048-5426  
1-213-931-3444 (ext. 228)  
Fax 1-213-931-7309

#### Electronic Shopper

**Joe Shere**  
National Representative  
P.O. Box 169  
Idyllwild, CA 92549-0169  
1-909-659-9743  
Fax 1-909-659-2469

**Megan Mitchell**  
National Representative  
1201 N. Rainbow Blvd., #50  
Las Vegas, NV 89108-6819  
1-702-259-7043  
Fax 1-702-259-7043

#### Customer Service

1-800-999-7139  
7:00 AM - 6:00 PM M-F MST



# The scope can be held with one hand. The awards can't.



The TekScope® Handheld Digital Oscilloscope has won virtually every major award a handheld scope or DMM can. Because it allows you to sample at 500 MS/s on both of its channels simultaneously. Because it comes with Isolated Channel™ Architecture. Because it has a True RMS DMM. All surrounded by an intuitive, rugged package that will rest comfortably in the palm of your hand. For these reasons and more, TekScope has repeatedly been voted number one by customers like yourself.

Awards can be a handful, sure. But we're not complaining. For more information, call 1-800-479-4490, Action Code 722, or visit us at [www.tek.com](http://www.tek.com).

**Tektronix**





# Better Designs —Faster

## Guaranteed with Electronics Workbench!

Just click and drag to create and edit schematics. Mix analog and digital devices in any combination with full control over values, models and behavior. Try 'what if' scenarios and fine tune effortlessly. And on-screen waveforms always match actual circuit response. You'll create better designs faster—*Guaranteed!*
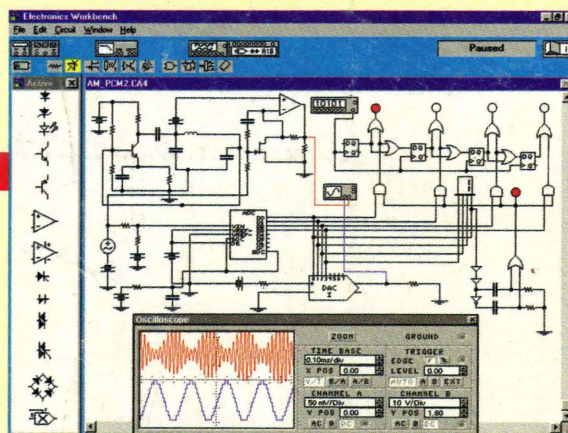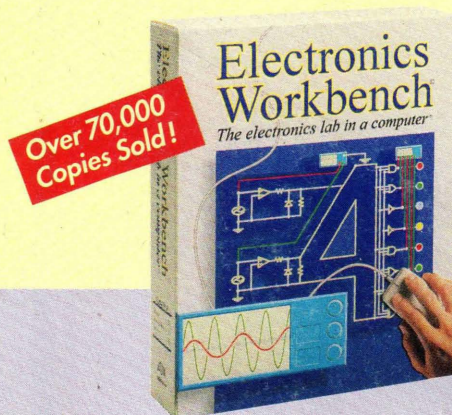
### Guaranteed Satisfaction

Join over 70,000 customers and experience the power, flexibility and value that only Electronics Workbench offers. Receive unequalled service and free, unlimited technical support by phone, fax, e-mail, WWW, CompuServe and BBS. You'll be delighted. We guarantee it.\*



### True Mixed-Mode Power

Connect any analog or digital device to any other device without limit. Only Electronics Workbench offers this professional power for under \$2,000.

### Real-World Digital

Real-world TTL and CMOS, complete with propagation delays and fanout. Unique at this price.

### 32-Bit Speed

Integrated SPICE analog and native-mode digital simulation in full 32-bit. Unique at this price.

### Real-World Results

Unlimited supply of over 200 components and ICs and 350 real-world models—all perform as real devices.

## Electronics Workbench®

**\$299**

### \*30-DAY MONEY-BACK GUARANTEE

VERSION 4.1 FOR WINDOWS 95/NT/3.1, DOS AND MACINTOSH.

Ask about our Engineer's Pack with thousands of additional models and more. Version 4.0 users call for your free upgrade.

**800-263-5552**



Fax: 416-977-1818 Internet: <http://www.interactiv.com>  
CompuServe: 71333,3435/BBS: 416-977-3540/E-mail: [ewb@interactiv.com](mailto:ewb@interactiv.com)

INTERACTIVE IMAGE TECHNOLOGIES LTD., 908 Niagara Falls Boulevard, #068, North Tonawanda, New York 14120-2060/Telephone 416-977-5555  
TRADEMARKS ARE PROPERTY OF THEIR RESPECTIVE HOLDERS. OFFER IS IN U.S. DOLLARS AND VALID ONLY IN THE UNITED STATES AND CANADA. ALL ORDERS SUBJECT TO \$15 SHIPPING AND HANDLING CHARGE.

Australia: 2-519-3933 • Belgium: 2-384-73-09 • Brazil: 11-453-5588 • Canada: 416-977-5550 • Chile: 2-236-0300 • Cyprus: 9-641-801 • Czech Republic: 4-823-454 • Denmark: 33-25-0109 • Finland: 0-297-503  
France: 1-49-08-90-00 • Germany: 711-62-7740 • Greece: 1-524-9981 • Hungary: 1-215-0082 • India: 11-578-7055 • Indonesia: 21-470-0815 • Israel: 3-647-5613 • Italy: 11-437-5549 • Japan: 3-5395-21  
Malaysia: 3-774-2189 • Mexico: 5-593-5260 • Netherlands: 10-450-4949 • New Zealand: 9-267-1756 • Norway: 22-16-70-45 • Philippines: 973-27-0118 • Portugal: 1-814-6609 • Singapore: 777-2303 • Slovenia: 61-317-8  
South Africa: 331-6-8309 • South Korea: 2-3452-9757 • Spain: 1-383-8335 • Sweden: 8-740-5500 • Taiwan: 2-366-0080 • Thailand: 2-398-6952 • UAE: 4-453505 • UK: 203-23-3216 • USA: 416-977-5555

CIRCLE 126 ON FREE INFORMATION CARD